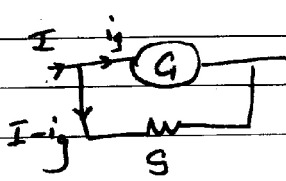
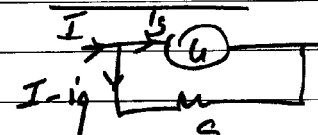
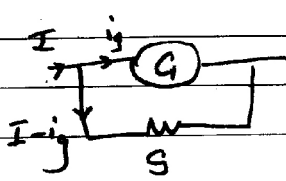
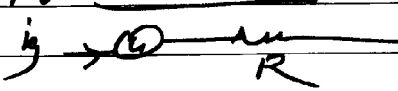


<p>(1) <u>Data:</u>  <math>n = 50</math>  <math>l = 5\text{cm} = 0.05\text{m}</math>  <math>b = 3\text{cm} = 0.03\text{m}</math>  <math>B = 0.050\text{T}</math>  <math>c = 1.5 \times 10^{-9}\text{ Nm/degree}</math>  <math>\theta = 30^\circ</math></p> <p><u>Solution:</u>  <math>A = lb</math>  <math>= 0.05 \times 0.03</math>  <math>= 0.0015\text{m}^2</math></p> <p><math>\tau_d = \tau_r</math>  <math>\therefore BIA \times A = c\theta</math>  <math>0.050 \times I \times 50 \times 0.0015 = 1.5 \times 10^{-9} \times 30</math>  <math>\therefore I = \frac{1.5 \times 10^{-9} \times 30}{0.050 \times 50 \times 0.0015}</math>  <math>\therefore I = 1.2 \times 10^{-5}\text{A}</math></p> <p><u>Data:</u></p>	<p><math>i_g \cdot G = (I - i_g) \cdot S</math>  <math>5 \times 10^{-3} \times 40 = (5 - 5 \times 10^{-3}) \cdot S</math>  <math>\therefore S = 0.04\ \Omega</math></p> <p><math>\therefore</math> Connect a <math>0.04\ \Omega</math> Resistance in parallel to the galvanometer.</p>
<p>(2) <u>Data:</u>  <math>G = 40\ \Omega</math>  <math>i_g = 5 \times 10^{-3}\text{A}</math>  <math>S = ?</math>  <math>I = 5\text{A}</math></p> 	<p>(3) <u>Data:</u>  <math>G = 60\ \Omega</math>  <math>I = 5\text{A}</math>  <math>i_g = 50 \times 10^{-3}\text{A}</math>  <math>V = 50\text{V}</math></p> <p><u>For Ammeter:</u></p>  <p><math>i_g \cdot G = (I - i_g) \cdot S</math>  <math>60 \times 50 \times 10^{-3} = (5 - 50 \times 10^{-3}) \cdot S</math>  <math>\therefore S = 0.6061\ \Omega</math></p> <p>Connect <math>0.6061\ \Omega</math> in parallel</p>
<p><u>Data:</u></p> <p>(2) <u>Data:</u>  <math>G = 40\ \Omega</math>  <math>i_g = 5 \times 10^{-3}\text{A}</math>  <math>S = ?</math>  <math>I = 5\text{A}</math></p> 	<p><u>For Voltmeter:</u></p>  <p><math>V = i_g G + i_g R</math>  <math>50 = 50 \times 10^{-3} (60 + R)</math>  <math>\therefore R = 940\ \Omega</math> in series</p>

(4) Data :

$$G = 16 \Omega$$


$$i_g = 20 \times 10^{-3} \text{ A}$$

$$S = 0.04 \Omega$$

$$R = ?$$

$$I = 10 \text{ A}$$

Solution:

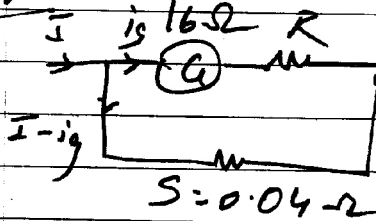

$$i_g (G + R) = (I - i_g) S$$

$$20 \times 10^{-3} (16 + R) = (10 - 20 \times 10^{-3}) \times 0.04$$

$$16 + R = \frac{0.3992}{20 \times 10^{-3}}$$

$$\therefore R = 3.96 \Omega$$


(5) Data :

$$G = 297 \Omega$$

$$S = 3 \Omega$$

$$\frac{i_g}{I} = ?$$

Solution:

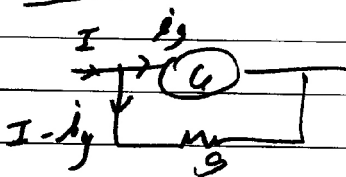

$$i_g G = (I - i_g) S$$

Divide by I

$$\frac{i_g}{I} \cdot G = \left(1 - \frac{i_g}{I}\right) \cdot S$$

$$\therefore \frac{i_g}{I} (G + S) = S$$

$$\frac{i_g}{I} = \frac{S}{G + S}$$

$$= \frac{3}{297 + 3}$$

$$= \frac{3}{300}$$

$$= \frac{1}{100}$$

ie. 1%

(6)  $G = 1000 \Omega$

$$G \parallel S = 25 \Omega$$

$$S = ?$$

Solution:

$$G \parallel S = \frac{GS}{G + S}$$

$$25 = \frac{1000S}{1000 + S}$$

$$25 \cdot 1000 + 25S = 1000S$$

$$25000 = 975S$$

$$\therefore S = 25.64 \Omega$$

$$(7) \mu = 50$$

$$A = 12 \times 10^{-4} \text{ m}^2$$

$$B = 0.025 \text{ T}$$

$$C = 15 \times 10^{-10} \text{ Nm/degree}$$

$$S = \frac{dQ}{dI} = \frac{\eta BA}{C}$$

$$\therefore S = \frac{50 \times 0.025 \times 12 \times 10^{-4}}{15 \times 10^{-10}}$$

$$= 10^6 \text{ dir/A}$$