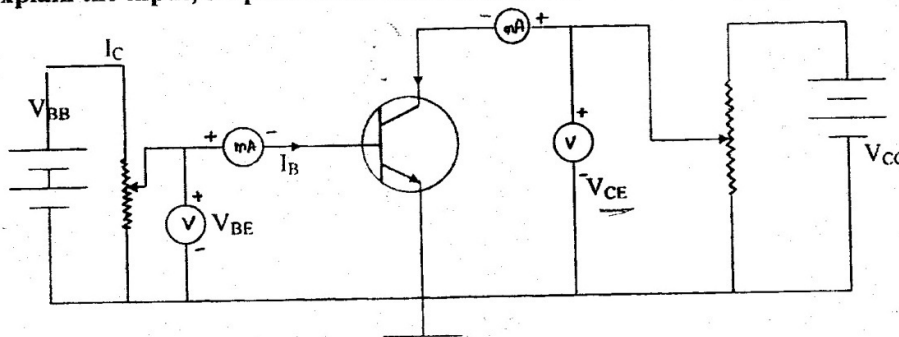


Q.15 Explain the input, output and current transfer characteristics of CE mode.


Ans.



**Input characteristics :** It is a set of graphs of input current v/s input voltage for constant value of output voltage. In CE mode it is a graph of  $I_B$  v/s  $V_{BE}$  for constant value of  $V_{CE}$ . As we increase the  $V_{BE}$  by adjusting value rheostat  $R_{B1}$ , the increase in base current is negligible. However, as  $V_{BE}$  increases above the turn on voltage of base-emitter junction diode, the base current increases.

If we keep  $V_{BE}$  constant and increase  $V_{CE}$  then the  $I_B$  decreases. This is because as we increase  $V_{CE}$ , the collector-base junction is more reverse biased due to which **depletion region widens more in the base region than in the collector region** (This is because of the fact that base is lightly doped as compared to collector region). This reduces the effective width of the base region. Hence, the recombination in the base region reduces. This reduces the base current. **This effect is called Early effect.**

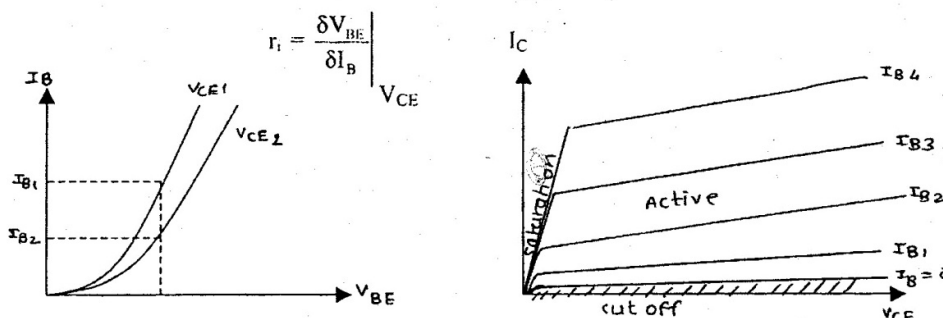The ratio of change in  $V_{BE}$  to that of  $I_B$  is called input resistance of transistor.



**Output characteristics :** The output characteristics is set of graph of output current v/s output voltage for constant value of input current. In CE mode output characteristics is graph of  $I_C$  v/s  $V_{CE}$  for constant value of  $I_B$ . This graph is divided into three regions as follows :

- Active region :** In this region collector-base junction is reverse biased and emitter-base junction is forward biased. Therefore,  $I_C$  is almost independent of  $V_{CE}$  (slight dependence of  $I_C$  on  $V_{CE}$  is due to early effect). However,  $I_C$  increases with the increase in  $I_B$  and **this results in the amplification action of transistor.** In this region a small change in  $I_B$  causes large change in  $I_C$ .
- Saturation region :** In this region, **both the junctions i.e. base-collector and base-emitter are forward biased.** The collector current in this region is maximum and does not change with the change in base current.
- Cutoff region :** In this region, **both the junctions i.e. base-collector and base-emitter are reverse biased.** The collector current in this region is minimum (almost zero) and does not change with the change in base current.

**To use transistor as an amplifier, it is used in active region and to use it as a switch in computers it is operated in the saturation and cutoff regions.**

Be With The Best

# Navlakhhi

	CE	CC	CB
Voltage gain, $A_v$	High $R_C/r'_e$	Low $\cong 1$	High $R_C/r'_e$
Current gain, $A_{i(max)}$	High $\beta_{ac}$	High $\beta_{ac}$	Low $\cong 1$
Power gain, $A_p$	Very high $A_i A_v$	High $\cong A_i$	High $\cong A_v$
Input resistance, $R_{i(max)}$	Low $\beta_{ac} r'_e$	High $\beta_{ac} R_E$	Very low $r'_e$
Output resistance, $R_{out}$	High $R_C$	Very low $(R_C/\beta_{ac}) \parallel R_E$	High $R_C$

9820246760 / 9769479368

Be With The Best

navlakhhi.com | navlakhhi.mobi