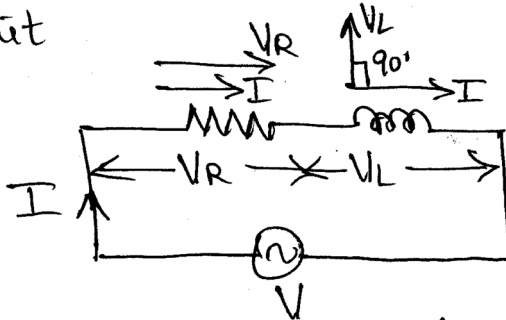


SERIES A.C. CIRCUITS

TYPE I: - A.C. THROUGH RESISTANCE AND INDUCTANCE

(R-L CIRCUITS):-
Consider a resistance (R) connected in series with an inductor (L) across a.c. supply as shown in following circuit



If V = r.m.s. value of applied voltage (In volts)

I = r.m.s. value of supply current (In Amperes)

R = resistance of circuit (In Ohms)

L = inductance of circuit (In Henry)

$X_L = 2\pi fL = \omega L$ (In Ohms)

= inductive reactance of circuit


$\omega = 2\pi f$ = Supply frequency (In rad/sec)

f = supply frequency (In Hertz)


$V_R = I \cdot R$ = voltage across resistor (In volts)

$V_L = I \cdot X_L$ = voltage across inductor (In volts)


Power Triangle is

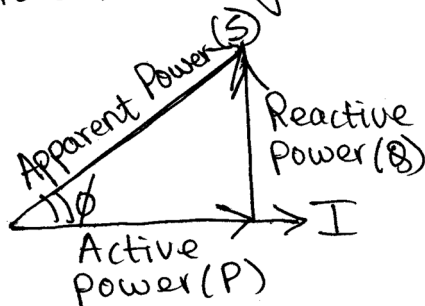

Voltage Triangle is

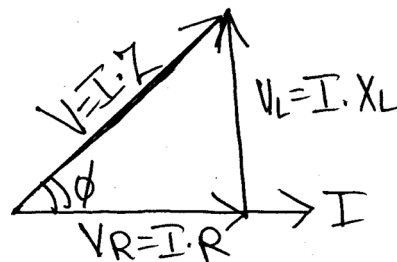

Impedance triangle is

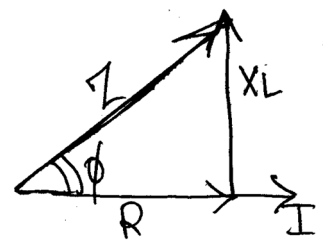

$V = IZ$ = voltage of supply (In volts)
 From voltage triangle

$$V = \sqrt{(VR)^2 + (VL)^2}$$

$$\therefore IZ = \sqrt{(IR)^2 + (IX_L)^2}$$

$$\therefore IZ = I\sqrt{R^2 + X_L^2}$$

$$\therefore Z = \sqrt{R^2 + X_L^2}$$

Where Z = impedance of circuit (In Ohms)

$$\text{Power factor (pf)} = \cos\phi = \frac{R}{Z} \quad (\text{Lagging})$$

$$\text{Quality factor (Q-factor)} = \frac{1}{\text{p.f.}} = \frac{1}{\cos\phi}$$

$$\text{Active power (P or } W) = V \cdot I \cdot \cos\phi$$

$$= I^2 R$$

(Units is Watts)

$$\text{Reactive power (Q)} = V \cdot I \cdot \sin\phi$$

$$= I^2 X_L$$

(Units is VAR - volts ampere reactive)

$$\text{Apparent power (S)} = V \cdot I$$

$$= I^2 Z$$

(Units is VA - volts ampere)

Ans 1) $i(t) = 5 \sin(314t + 2\pi/3)$

Comparing with

$$i(t) = I_m \sin(\omega t + \theta_1)$$


$$\therefore I_m = 5A, \omega = 314 \text{ rad/sec}, \theta_1 = \frac{2\pi}{3} = 120^\circ$$

$$V(t) = 15 \sin(314t + 5\pi/6)$$

Comparing with

$$V(t) = V_m \sin(\omega t + \theta_2)$$
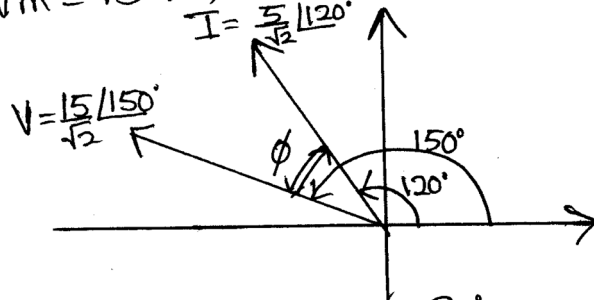
$$\therefore V_m = 15V, \omega = 314 \text{ rad/sec}, \theta_2 = \frac{5\pi}{6} = 150^\circ$$



$$\therefore \phi = \theta_2 - \theta_1 = 150 - 120 = 30^\circ$$

$$I = \frac{I_m}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.54A$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{15}{\sqrt{2}} = 10.61V$$

$$(a) Z = \frac{V}{I} = \frac{10.61}{3.54} = 3\Omega$$

$$(b) \therefore \cos \phi = \frac{R}{Z}$$

$$\therefore \cos 30^\circ = \frac{R}{3} \therefore R = 2.6\Omega$$

$$(c) Z = \sqrt{R^2 + X_L^2}$$

$$\therefore 3 = \sqrt{(2.6)^2 + X_L^2}$$

$$\therefore X_L = 1.5\Omega$$

$$\therefore X_L = 2\pi fL = \omega L$$

$$\therefore 1.5 = 314 \times L$$

$$\therefore L = 4.78 \times 10^{-3} H$$

$$\begin{aligned}
 \text{(d) Average Power} &= \text{Active Power} \\
 &= V \cdot I \cos \phi \\
 &= 10.61 \times 3.54 \times \cos 30^\circ \\
 &= 32.53 \text{ W}
 \end{aligned}$$

$$\begin{aligned}
 \text{(e) P.f.} &= \cos \phi = \cos 30^\circ \\
 &= 0.866 \text{ (lag)}
 \end{aligned}$$

$$\begin{aligned}
 \text{Ans 2) } R &= 3.5 \Omega \\
 L &= 0.1 \text{ H} \\
 f &= 50 \text{ Hz} \\
 V &= 220 \angle 30^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{(i) } X_L &= 2\pi fL \\
 &= 2\pi \times 50 \times 0.1 \\
 &= 31.42 \Omega
 \end{aligned}$$


$$\begin{aligned}
 Z &= \sqrt{R^2 + X_L^2} \\
 &= \sqrt{(3.5)^2 + (31.42)^2}
 \end{aligned}$$

$$Z = 31.61 \Omega$$

$$I = \frac{V}{Z} = \frac{220}{31.61} = 6.96 \text{ A}$$

$$\cos \phi = \frac{R}{Z} = \frac{3.5}{31.61} = 0.111 \text{ (lag)}$$

$$\therefore \phi = 83.64^\circ$$

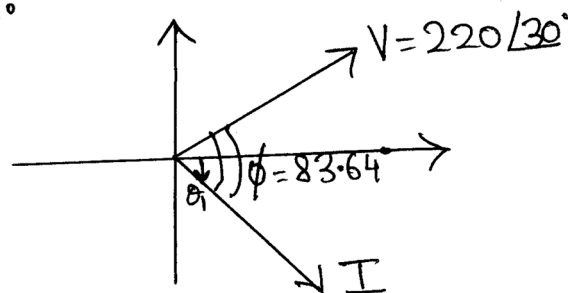

$$\begin{aligned}
 \theta_1 &= 83.64 - 30 \\
 &= 53.64^\circ
 \end{aligned}$$


$$\therefore I = 6.96 \angle -53.64^\circ$$

$$\begin{aligned}
 \text{(ii) P.f.} &= \cos \phi = \cos(83.64^\circ) \\
 &= 0.111 \text{ (lag)}
 \end{aligned}$$

$$\text{Q3) } V = 80 + j60 = 100 \angle 36.87^\circ$$

$$i = -4 + j10 = 10.77 \angle 111.8^\circ$$
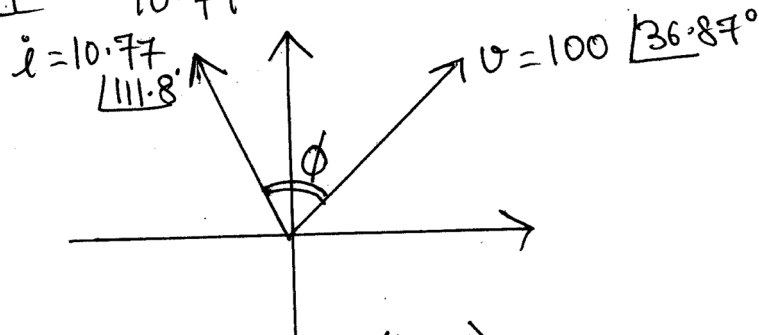
$$(i) \quad Z = \frac{V}{I} = \frac{100}{10.77} = 9.29 \Omega$$



$$\phi = 111.8^\circ - 36.87^\circ = 74.93^\circ \text{ (lead)}$$

$$Z = \frac{V}{i} = \frac{80 + j60}{-4 + j10} = 2.41 - j8.97 = 9.29 \angle -74.93^\circ$$

(ii) Comparing with $Z = |Z| \angle \phi$
 $\therefore \phi = 74.93^\circ \text{ (lead)}$

$$P = VI \cos \phi$$

$$= 100 \times 10.77 \cos(74.93^\circ)$$

$$= 280.02 \text{ W}$$

(iii) Phase angle = ϕ
 $= 74.93^\circ \text{ (lead)}$

$$\text{Q4) } V = 100 \text{ V}$$

$$I = 10 \text{ A}$$

$$\phi = 30^\circ \text{ (lead)}$$

(i) p.f. is leading

$$(ii) \text{ p.f.} = \cos \phi = \cos 30^\circ = 0.866 \text{ (lead)}$$

(iii) Circuit is capacitive


$$(iv) \text{ Active power} = VI \cos \phi$$

$$= 100 \times 10 \times \cos 30^\circ = 866.03 \text{ W}$$

$$\text{Reactive power} = VI \sin \phi$$

$$= 100 \times 10 \times \sin 30^\circ = 500 \text{ VAR}$$
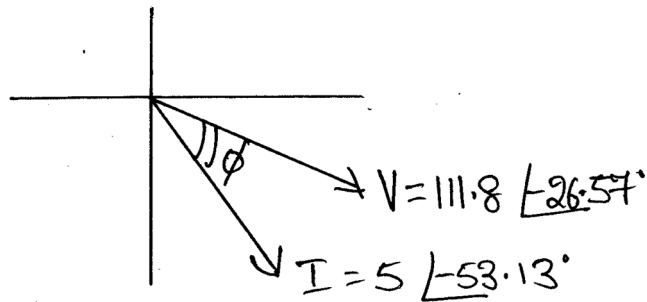
$$\begin{aligned} Q5) \quad V &= 100 - j50 = 111.8 \angle -26.57^\circ \\ i &= 3 - j4 = 5 \angle -53.13^\circ \end{aligned}$$




$$\phi = 53.13 - 26.57 = 26.56^\circ \text{ (lag)}$$

$$\begin{aligned} \text{Real power} &= \text{Active power} \\ &= V \cdot I \cos \phi \\ &= 111.8 \times 5 \times \cos(26.56^\circ) \\ &= 500 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= V \cdot I \sin \phi \\ &= 111.8 \times 5 \times \sin(26.56^\circ) \\ &= 249.95 \text{ VAR} \end{aligned}$$
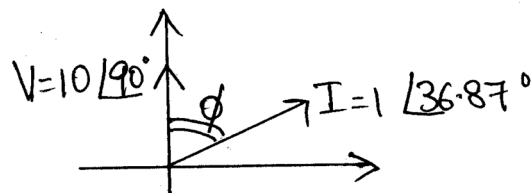
$$\begin{aligned} Q6) \quad V &= 0 + j10 = 10 \angle 90^\circ \\ i &= 0.8 + j0.6 = 1 \angle 36.87^\circ \end{aligned}$$



$\phi = 90 - 36.87 = 53.13^\circ$ (lag)
 Since current is lagging the voltage $\therefore$ pf. is lagging
 $\therefore$ Circuit is inductive

$$\begin{aligned} Z &= \frac{V}{i} = \frac{0 + j10}{0.8 + j0.6} \\ &= 6 + j8 \end{aligned}$$

Comparing with $Z = R + jX_L$
 $\therefore R = 6 \Omega$ and $X_L = 8 \Omega$

$$Q7) e = v = 200\sqrt{2} \sin(\omega t + 20^\circ)$$

Comparing with

$$v = V_m \sin(\omega t + \theta_1)$$

$$\therefore V_m = 200\sqrt{2} \text{ V}$$

$$\theta_1 = 20^\circ$$

Comparing with

$$i = 10\sqrt{2} \cos(314t - 25^\circ) = 10\sqrt{2} \sin(314t - 25 + 90)$$

$$\therefore i = 10\sqrt{2} \sin(314t + 65^\circ)$$

$$\because \sin(90 + \theta) = \cos \theta$$


$$i = I_m \sin(\omega t + \theta_2)$$

$$\therefore I_m = 10\sqrt{2} \text{ A}$$

$$\theta_2 = 65^\circ$$

$$\omega = 314 \text{ rad/s}$$
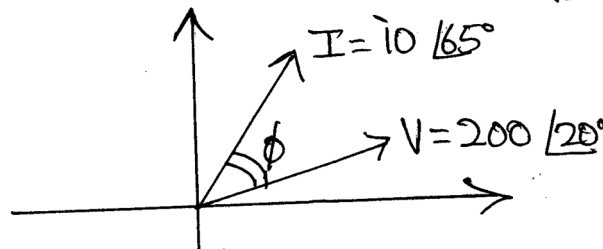
$$V = \frac{V_m}{\sqrt{2}} = \frac{200\sqrt{2}}{\sqrt{2}} = 200 \text{ V} \text{ and } I = \frac{I_m}{\sqrt{2}} = \frac{10\sqrt{2}}{\sqrt{2}} = 10 \text{ A}$$



$$\phi = 65 - 20 = 45^\circ \text{ (lead)}$$

$$Z = \frac{V}{I} = \frac{200}{10} = 20 \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$\therefore \cos 45^\circ = \frac{R}{20}$$

$$\therefore R = 14.14 \Omega$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\therefore 20 = \sqrt{(14.14)^2 + X_C^2}$$

$$\therefore X_C = 14.14 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$

$$\therefore 14.14 = \frac{1}{314 \times C} \therefore C = 2.25 \times 10^{-4} \text{ F}$$

Q8) $I = 10\text{A}$
 Active power $= 1\text{kW} = 1000\text{W}$
 $V = 200\text{V}$
 $f = 50\text{Hz}$

Active power $= VI \cos\phi$
 $\therefore 1000 = 200 \times 10 \times \cos\phi$
 $\therefore \phi = 60^\circ (\text{lag})$

$Z = \frac{V}{I} = \frac{200}{10} = 20\Omega$

$\cos\phi = \frac{R}{Z}$

$\therefore \cos 60^\circ = \frac{R}{20} \quad \therefore R = 10\Omega$

$Z = \sqrt{R^2 + X_L^2}$

$\therefore 20 = \sqrt{(10)^2 + X_L^2}$

$\therefore X_L = 17.32\Omega$

(i) $Z = R + jX_L$
 $= (10 + j17.32)\Omega$

(ii) $Z = 20 \angle 60^\circ \Omega$

(iii) p.f. $= \cos\phi$
 $= \cos 60^\circ$
 $= 0.5 (\text{lag})$

(iv) Reactive power $= VI \sin\phi$
 $= 200 \times 10 \times \sin 60^\circ$
 $= 1,732.05 \text{ VAR}$

(v) Apparent power $= V \cdot I$
 $= 200 \times 10$
 $= 2000 \text{ VA}$

89) Coil A

$$V_1 = 100V$$

$$f_1 = 50Hz$$

$$I_1 = 8A$$

$$P_1 = 120W$$

$$Z_1 = \frac{V_1}{I_1} = \frac{100}{8} = 12.5\Omega$$

$$P_1 = V_1 I_1 \cos \phi_1$$

$$\therefore 120 = 100 \times 8 \times \cos \phi_1$$

$$\therefore \phi_1 = 81.37^\circ (\text{lag})$$

$$\cos \phi_1 = \frac{R_1}{Z_1}$$

$$\therefore \cos 81.37^\circ = \frac{R_1}{12.5}$$

$$\therefore R_1 = 1.88\Omega$$

$$Z_1 = \sqrt{R_1^2 + X_{L1}^2}$$

$$\therefore 12.5 = \sqrt{(1.88)^2 + X_{L1}^2}$$

$$\therefore X_{L1} = 12.36\Omega$$

Coil B

$$V_2 = 100V$$

$$f_2 = 50Hz$$

$$I_2 = 10A$$

$$P_2 = 500W$$

$$Z_2 = \frac{V_2}{I_2} = \frac{100}{10} = 10\Omega$$

$$P_2 = V_2 I_2 \cos \phi_2$$

$$\therefore 500 = 100 \times 10 \times \cos \phi_2$$

$$\therefore \phi_2 = 60^\circ (\text{lag})$$

$$\cos \phi_2 = \frac{R_2}{Z_2}$$

$$\therefore \cos 60^\circ = \frac{R_2}{10}$$

$$\therefore R_2 = 5\Omega$$

$$Z_2 = \sqrt{R_2^2 + X_{L2}^2}$$

$$\therefore 10 = \sqrt{(5)^2 + X_{L2}^2}$$

$$\therefore X_{L2} = 8.66\Omega$$

When coil A and coil B are connected in series

$$\text{Total } R = R_1 + R_2$$

$$= 1.88 + 5 = 5.88\Omega$$

$$\text{Total } X_L = X_{L1} + X_{L2}$$

$$= 12.36 + 8.66 = 21.02\Omega$$

$$\text{Total } Z = \sqrt{R^2 + X_L^2} = \sqrt{(5.88)^2 + (21.02)^2} = 21.83\Omega$$

$$V = 100V$$

$$I = \frac{V}{Z} = \frac{100}{21.83} = 4.58A$$

$$\cos \phi = \frac{R}{Z} = \frac{5.88}{21.83} = 0.27 (\text{lag})$$

$$\text{Power} = VI \cos \phi = 100 \times 4.58 \times 0.27 = 123.36W$$

$$Q10) I_{dc} = 6A$$

$$V_{dc} = 24V$$

$$V_{dc} = I_{dc} \times R$$

$$\therefore 24 = 6 \times R$$

$$\therefore R = 4\Omega$$

For a.c. supply,

$$I = 6A$$

$$V = 30V$$

$$f = 50Hz$$

$$Z = \frac{V}{I} = \frac{30}{6} = 5\Omega$$

$$pf = \cos \phi = \frac{R}{Z} = \frac{4}{5} = 0.8 (\text{lag})$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\therefore 5 = \sqrt{(4)^2 + X_L^2}$$


$$\therefore X_L = 3\Omega$$

$$X_L = 2\pi fL$$

$$\therefore 3 = 2\pi \times 50 \times L$$

$$\therefore L = 9.55 \times 10^{-3} H$$

Q11) Assuming lamp to be resistive

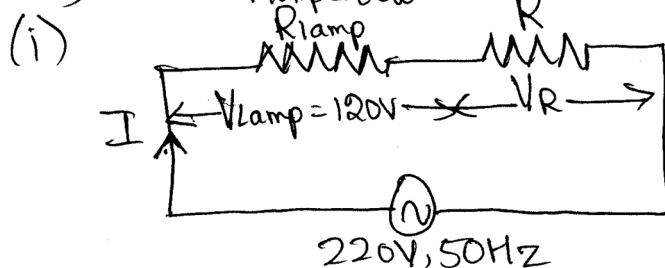

When resistor is connected in series

$$P_{\text{lamp}} = V_{\text{lamp}} \times I$$

$$\therefore 60 = 120 \times I$$

$$\therefore I = 0.5A$$

$$V_{\text{lamp}} = I \times R_{\text{lamp}}$$

$$\therefore 120 = 0.5 \times R_{\text{lamp}}$$

$$\therefore R_{\text{lamp}} = 240\Omega$$


$$V = I(R_{\text{lamp}} + R)$$

$$\therefore 220 = 0.5(240 + R)$$

$$\therefore R = 200 \Omega$$

$$\begin{aligned} \text{Total power} &= I^2(R_{\text{lamp}} + R) \\ &= 0.5^2(240 + 200) \\ &= 110 \text{ W} \end{aligned}$$

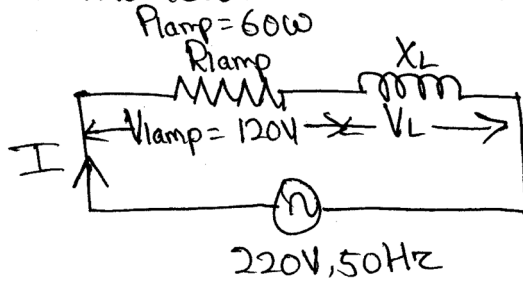(ii) When inductor is connected in series



$$P_{\text{lamp}} = V_{\text{lamp}} \times I$$

$$\therefore 60 = 120 \times I$$

$$\therefore I = 0.5 \text{ A}$$

$$V_{\text{lamp}} = I \times R_{\text{lamp}}$$

$$\therefore 120 = 0.5 \times R_{\text{lamp}}$$

$$\therefore R_{\text{lamp}} = 240 \Omega$$

$$V = IZ$$

$$\therefore 220 = 0.5 \times Z$$

$$\therefore Z = 440 \Omega$$

$$Z = \sqrt{R_{\text{lamp}}^2 + X_L^2}$$

$$\therefore 440 = \sqrt{(240)^2 + X_L^2}$$

$$\therefore X_L = 368.78$$

$$X_L = 2\pi fL$$

$$\therefore 368.78 = 2\pi \times 50 \times L$$

$$\therefore L = 1.17 \text{ H}$$

$$\cos \phi = \frac{R_{\text{lamp}}}{Z} = \frac{240}{440} = \cancel{1.09(\text{lag})} 0.546(\text{lag})$$

$$\text{Total power} = VI \cos \phi = 220 \times 0.5 \times 0.546 = 60.06 \text{ W}$$

Method (ii) is preferred since power consumed is less.

Q12) $I = 8A$

$V_R = 100V$

$V_R = I \cdot R$

$\therefore 100 = 8 \times R$

$\therefore R = 12.5 \Omega$

$V = 220V$

$I = 8A$

$Z = \frac{V}{I} = \frac{220}{8} = 27.5 \Omega$

$Z = \sqrt{R^2 + X_L^2}$

$\therefore 27.5 = \sqrt{(12.5)^2 + X_L^2}$

$\therefore X_L = 24.5 \Omega$


$X_L = 2\pi fL$

$24.5 = 2\pi \times 50 \times L$

$\therefore L = 0.078H$

$\cos \phi = \frac{R}{Z} = \frac{12.5}{27.5}$

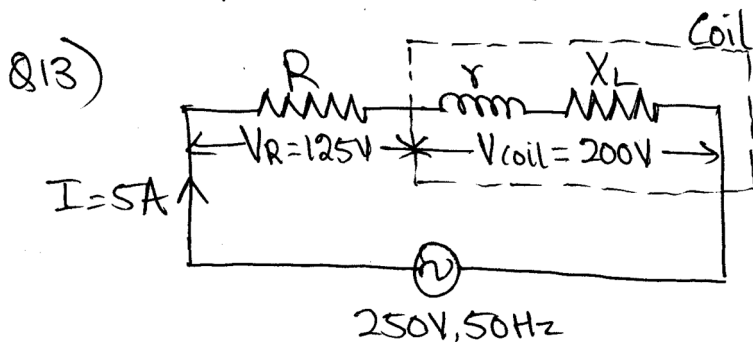$\therefore \phi = 62.96^\circ (\text{lag})$



$V_R = I \cdot R$

$\therefore 125 = 5 \times R$

$\therefore R = 25 \Omega$

$V_{\text{coil}} = I \cdot Z_{\text{coil}}$

$\therefore 200 = 5 \times Z_{\text{coil}}$

$\therefore Z_{\text{coil}} = 40 \Omega$

$$V = I \cdot Z$$

$$\therefore 250 = 5 \times Z$$

$$\therefore Z = 50 \Omega$$

$$Z_{\text{coil}} = \sqrt{r^2 + X_L^2}$$

$$\therefore 40 = \sqrt{r^2 + X_L^2}$$

$$\therefore r^2 + X_L^2 = 1600 \quad \text{--- (I)}$$

$$Z = \sqrt{(R+r)^2 + X_L^2}$$

$$\therefore 50 = \sqrt{(25+r)^2 + X_L^2}$$

$$\therefore 2500 = 625 + 50r + r^2 + X_L^2$$

Substituting from eqn (I)

$$\therefore 2500 = 625 + 50r + 1600$$

$$\therefore r = 5.5 \Omega$$

Substituting in eqn (I)

$$(5.5)^2 + X_L^2 = 1600$$

$$\therefore X_L = 39.62 \Omega$$

$$(ii) \cos \phi_{\text{coil}} = \frac{r}{Z_{\text{coil}}} = \frac{5.5}{40} = 0.1375 \text{ (lag)}$$

$$\begin{aligned} P_{\text{coil}} &= V_{\text{coil}} \cdot I \cdot \cos \phi_{\text{coil}} \\ &= 200 \times 5 \times 0.1375 \\ &= 137.5 \text{ W} \end{aligned}$$

$$(iii) \cos \phi = \frac{R+r}{Z} = \frac{25+5.5}{50} = 0.61 \text{ (lag)}$$


$$\begin{aligned} P &= VI \cos \phi \\ &= 250 \times 5 \times 0.61 \\ &= 762.5 \text{ W} \end{aligned}$$

$$V_r = I \cdot r = 5 \times 5.5 = 27.5 \text{ V}$$

$$V_L = I \cdot X_L = 5 \times 39.62 =$$

$$\phi_{\text{coil}} = 82.1^\circ \text{ (lag)}$$

$$\phi = 52.41^\circ \text{ (lag)}$$

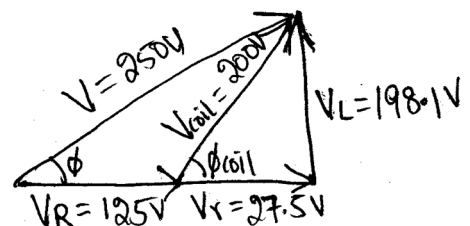

$$\text{Q14)} \quad V = 240V$$

$$f = 50\text{Hz}$$

$$R_A = 5\Omega$$

$$L_B = 0.015\text{H}$$

$$\text{Active power} = 3\text{kW} = 3000\text{W}$$

$$\text{Reactive power} = 2\text{VAR} = 2000\text{VAR}$$

$$\text{Active power} = VI \cos \phi$$

$$\therefore 3000 = 240 \times I \times \cos \phi \quad \text{--- (I)}$$

$$\text{Reactive power} = VI \sin \phi$$

$$\therefore 2000 = 240 \times I \times \sin \phi \quad \text{--- (II)}$$

Dividing eqn. (II) by (I)

$$\therefore \tan \phi = \frac{2}{3} \quad \therefore \phi = 33.69^\circ (\text{lag})$$

Substituting in eqn (I)

$$\therefore 3000 = 240 \times I \times \cos 33.69^\circ$$

$$\therefore I = 15.02\text{A}$$

$$Z = \frac{V}{I} = \frac{240}{15.02} = 15.98\Omega$$

$$\cos \phi = \frac{R_A + R_B}{Z}$$

$$\therefore \cos 33.69^\circ = \frac{5 + R_B}{15.98}$$

$$\therefore R_B = 8.3\Omega$$

$$Z = \sqrt{(R_A + R_B)^2 + (X_{L_A} + X_{L_B})^2}$$

$$\therefore X_{L_B} = 2\pi f \cdot L_B = 4.71\Omega$$

$$\therefore 15.98 = \sqrt{(5 + 8.3)^2 + (X_{L_A} + 4.71)^2}$$

$$X_{L_A} = 4.15$$

$$X_{L_A} = 2\pi f \cdot L_A$$

$$\therefore 4.15 = 2\pi \times 50 \times L_A$$

$$\therefore L_A = 0.013\text{H}$$

$$\begin{aligned}
 Z_{\text{coil A}} &= \sqrt{R_A^2 + X_{L_A}^2} \\
 &= \sqrt{5^2 + 4.15^2} \\
 &= 6.5 \Omega
 \end{aligned}$$

$$\begin{aligned}
 V_{\text{coil A}} &= I \cdot Z_{\text{coil A}} \\
 &= 15.02 \times 6.5 \\
 &= 97.63 \text{ W}
 \end{aligned}$$

$$\begin{aligned}
 Z_{\text{coil B}} &= \sqrt{R_B^2 + X_{L_B}^2} \\
 &= \sqrt{8.3^2 + 4.71^2} \\
 &= 9.54 \Omega
 \end{aligned}$$

$$\begin{aligned}
 V_{\text{coil B}} &= I \cdot Z_{\text{coil B}} \\
 &= 15.02 \times 9.54 \\
 &= 143.34
 \end{aligned}$$

Q15) $e = 141.4 \sin(377t + 30^\circ)$

$$R = 4 \Omega$$

$$X_L = 1.25 \Omega \text{ at } f_1 = 25 \text{ Hz}$$

$$X_L = 2\pi f_1 L$$

$$\begin{aligned}
 \therefore 1.25 &= 2\pi \times 25 \times L \\
 \therefore L &= 7.96 \times 10^{-3} \text{ H}
 \end{aligned}$$

Comparing with

$$e = V_m \sin(\omega t + \theta_1)$$

$$\therefore V_m = 141.4 \text{ V}$$

$$\omega = 377 \text{ rad/sec}$$

$$\theta_1 = 30^\circ$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 99.99 \text{ V}$$

$$X_L = \omega L = 377 \times 7.96 \times 10^{-3}$$

$$\therefore X_L = 3 \Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{4^2 + 3^2}$$

$$\therefore Z = 5 \Omega$$

$$I = \frac{V}{Z} = \frac{99.99}{5} = 20 \text{ A}$$

$$\cos \phi = \frac{R}{Z} = \frac{4}{5} = 0.8$$

$$\therefore \phi = 36.87^\circ$$

$$I_m = I \times \sqrt{2} = 20 \times \sqrt{2} = 28.28 \text{ A}$$

$\therefore$ Expression for current is

$$i = I_m \sin(\omega t + \theta_1 - \phi)$$

$$= 28.28 \sin(377t + 30 - 36.87)$$

$$= 28.28 \sin(377t - 6.87^\circ)$$

$$V_R = I \cdot R$$

$$= 20 \times 4 = 80 \text{ V}$$

$$V_{Rm} = V_R \times \sqrt{2} = 80 \times \sqrt{2} = 113.14 \text{ V}$$

Expression for voltage across resistor is:-

$$v_R = V_{Rm} \sin(\omega t + \theta_1 - \phi)$$

$$= 113.14 \sin(377t - 6.87^\circ)$$

$$V_L = I \cdot X_L = 20 \times 3 = 60 \text{ V}$$

$$V_{Lm} = V_L \times \sqrt{2} = 60 \times \sqrt{2} = 84.85 \text{ V}$$

Expression for voltage across inductor is:-

$$v_L = V_{Lm} \sin(\omega t + \theta_1 - \phi + 90^\circ)$$

$$= 84.85 \sin(377t - 6.87 + 90^\circ)$$

$$= 84.85 \sin(377t + 83.13^\circ)$$

$$Q16) \text{ Output Power} = 7.46 \text{ kW} = 7460 \text{ W}$$

$$V = 400 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\eta = 85\%$$

$$\text{p.f.} = \cos \phi = 0.8 \text{ (lag)}$$

$$\eta = \frac{\text{Output power}}{\text{Input power}} \times 100$$

$$\therefore 85 = \frac{7460}{\text{Input power}} \times 100$$

$$\therefore \text{Input power} = 8776.47 \text{ W}$$

$$\therefore \text{Input power} = VI \cos \phi$$

$$\therefore 8776.47 = 400 \times I \times 0.8$$

$$\therefore I = 27.43 \text{ A}$$

$$\begin{aligned} \text{(a) Apparent power} &= V \cdot I \\ &= 400 \times 27.43 \\ &= 10972 \text{ VA} \\ &= 10.972 \text{ kVA} \end{aligned}$$


$$\begin{aligned} \text{(b) Reactive component of input current} &= I \sin \phi \\ &= 27.43 \times \cancel{0.4359} 0.6 \\ &= 16.46 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{(c) Reactive power} &= VI \sin \phi \\ &= 10.972 \times 0.6 \\ &= 6.5832 \text{ VAR} \\ &= 6.5832 \text{ kVAR} \end{aligned}$$

TYPE II :- R-C CIRCUITS

A.C. THROUGH RESISTANCE AND CAPACITANCE :-

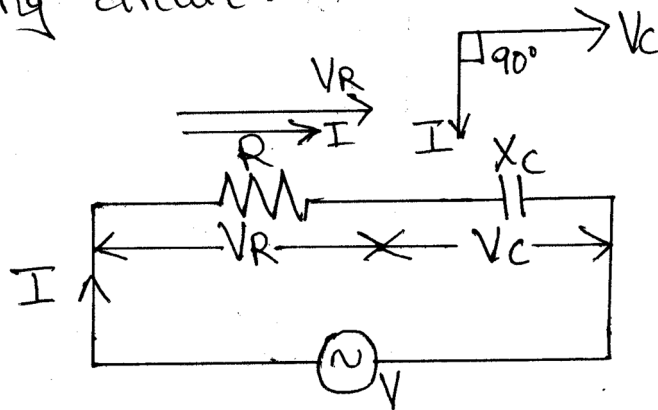Consider a resistance (R) connected in series with an capacitor (C) across a.c. supply as shown in following circuit :-



If V = r.m.s. value of applied voltage (In volts)

I = r.m.s. value of supply current (In Amperes)

R = resistance of circuit (In Ohms)

C = capacitance of circuit (In Farads)

$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C} \quad (\text{In Ohms})$$

= inductive capacitive reactance of circuit.


$\omega = 2\pi f$ = supply frequency (In rad/sec)

f = supply frequency (In Hertz)


$V_R = I \cdot R$ = voltage across resistor (In volts)

$V_C = I \cdot X_C$ = voltage across capacitor (In volts)

Voltage Triangle is

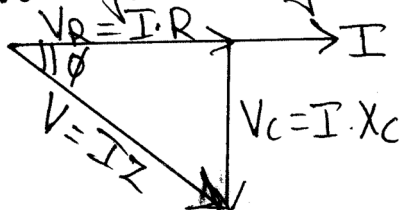

Impedance triangle is

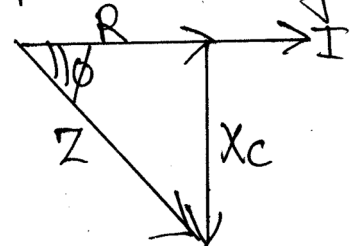

$V = IZ$ = voltage of supply (In volts)
From voltage triangle

$$V = \sqrt{(V_R)^2 + (V_C)^2}$$

$$\therefore IZ = \sqrt{(IR)^2 + (IX_C)^2}$$

$$\therefore IZ = I \sqrt{R^2 + X_C^2}$$

$$\therefore Z = \sqrt{R^2 + X_C^2}$$

where Z = impedance of circuit (In Ohms)

$$\text{Power factor (p.f.)} = \cos \phi = \frac{R}{Z} \text{ (leading)}$$

$$\text{Quality factor (Q-factor)} = \frac{1}{\text{p.f.}} = \frac{1}{\cos \phi}$$

$$\text{Active power (P or W)} = V \cdot I \cdot \cos \phi$$

$$= I^2 R$$

(Units is Watts)

$$\text{Reactive power (Q)} = V \cdot I \cdot \sin \phi$$

$$= I^2 X_C$$


(Units is VAR - volts ampere reactive)

$$\text{Apparent power (S)} = V \cdot I$$

$$= I^2 Z$$

(Units is VA - volts ampere)

Q1). Assuming the bulb to be resistive

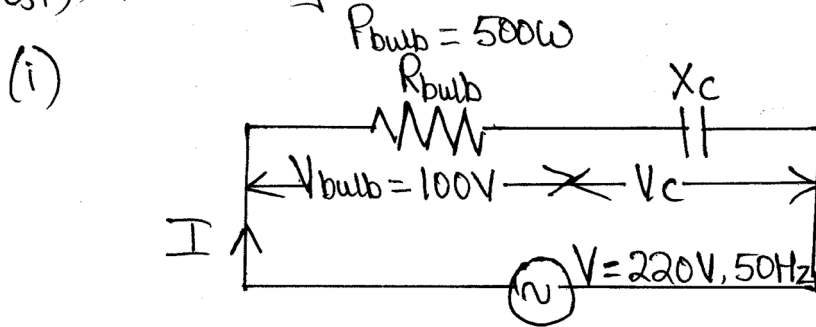

$$P_{bulb} = V_{bulb} \times I$$

$$\therefore 500 = 100 \times I$$

$$\therefore I = 5A$$

$$V_{bulb} = I \times R_{bulb}$$

$$\therefore 100 = 5 \times R_{bulb}$$

$$\therefore R_{bulb} = 20\Omega$$

$$V = I \cdot Z$$

$$\therefore 220 = 5 \times Z$$

$$\therefore Z = 44\Omega$$

$$Z = \sqrt{R_{bulb}^2 + X_c^2}$$

$$\therefore 44 = \sqrt{20^2 + X_c^2}$$

$$\therefore X_c = 39.19\Omega$$

$$X_c = \frac{1}{2\pi fC}$$

$$\therefore 39.19 = \frac{1}{2\pi \times 50 \times C}$$


$$\therefore C = 81.26 \times 10^{-6} F$$

$$(ii) P.f. = \cos \phi = \frac{R_{bulb}}{Z} = \frac{20}{44} = 0.4545 \text{ (lead)}$$

(iii) Vector diagram is:-

$$V_c = I \cdot X_c = 5 \times 39.19 = 195.95V$$

$$\phi = 62.96^\circ \text{ (lead)}$$

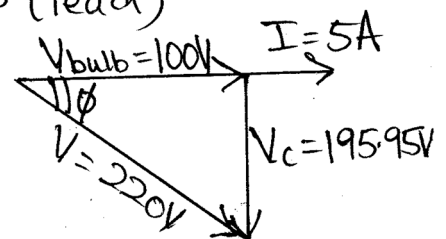

$$\begin{aligned} Q2) \quad R &= 50 \Omega \\ C &= 100 \times 10^{-6} \text{ F} \\ V &= 100 \text{ V} \\ f &= 50 \text{ Hz} \end{aligned}$$

$$(i) \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.85 \Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(50)^2 + (31.85)^2}$$

$$\therefore Z = 59.28 \Omega$$

$$(ii) \quad I = \frac{V}{Z} = \frac{100}{59.28} = 1.69 \text{ A}$$


$$(iii) \quad pf = \cos \phi = \frac{R}{Z} = \frac{50}{59.28} = 0.8435 \text{ (lead)}$$

$$(iv) \quad \phi = 32.49^\circ \text{ (lead)}$$

$$\begin{aligned} (v) \quad V_R &= I \cdot R \\ &= 1.69 \times 50 = 84.5 \text{ V} \end{aligned}$$

$$\begin{aligned} (vi) \quad V_C &= I \cdot X_C \\ &= 1.69 \times 31.85 = 53.83 \text{ V} \end{aligned}$$

Vector or Phasor diagram is :-

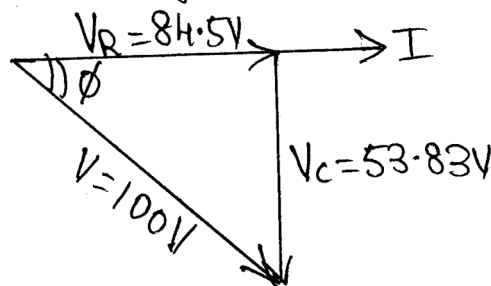

$$\therefore \phi = 32.49^\circ \text{ (lead)}$$

$$\begin{aligned} Q3) \quad V &= 240V \\ f &= 50\text{Hz} \\ I &= 20A \end{aligned}$$

Current leads voltage by $1/900$ secs.

$$T = \frac{1}{f} = \frac{1}{50} \text{ sec.}$$

$$\therefore \frac{1}{50} \text{ sec.} \text{ --- } 360^\circ$$

$$\therefore \frac{1}{900} \text{ sec.} \text{ --- } ? = \frac{1}{900} \times 50 \times 360^\circ = 20^\circ$$

$$\therefore \phi = 20^\circ (\text{lead})$$

$$(i) \text{ Pf} = \cos \phi = \cos 20^\circ = 0.9397 (\text{lead})$$

$$\begin{aligned} (ii) \text{ Average power} &= \text{Active power} \\ &= V \cdot I \cdot \cos \phi \\ &= 240 \times 20 \times \cos 20^\circ \\ &= 4,510.53 \text{ W} \end{aligned}$$

$$(iii) Z = \frac{V}{I} = \frac{240}{20} = 12 \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$\therefore \cos 20^\circ = \frac{R}{12}$$

$$\therefore R = 11.28 \Omega$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\therefore 12 = \sqrt{(11.28)^2 + X_C^2}$$

$$\therefore X_C = 4.09 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$\therefore 4.09 = \frac{1}{2\pi \times 50 \times C} \quad \therefore C = 778.66 \times 10^{-6} \text{ F}$$

$$Q4) v = 100 \sin 314t$$

$$R = 25 \Omega$$

$$C = 80 \times 10^{-6} F$$

(i) Comparing with

$$v = V_m \sin \omega t$$

$$\therefore V_m = 100 V, \omega = 314 \text{ rad/sec}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314 \times 80 \times 10^{-6}} = 39.81 \Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(25)^2 + (39.81)^2} = 47.01 \Omega$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71 V$$

$$I = \frac{V}{Z} = \frac{70.71}{47.01} = 1.5 A$$

$$I_m = I \times \sqrt{2} = 1.5 \times \sqrt{2} = 2.12 A$$

$$\cos \phi = \frac{R}{Z} = \frac{25}{47.01} = 0.5318 (\text{lead})$$

$$\therefore \phi = 57.87^\circ (\text{lead})$$

Expression for current is:-

$$i = I_m \sin(\omega t + \phi)$$

$$= 2.12 \sin(314t + 57.87^\circ) \text{ --- (I)}$$

$$(ii) \text{ Power} = V \cdot I \cdot \cos \phi$$

$$= 70.71 \times 1.5 \times \cos 57.87^\circ$$

$$= 56.41 W$$

$$(iii) i = \frac{1}{2} \cdot I_m = \frac{2.12}{2} = 1.06 A$$

Subs. in eqn (I)

$$\therefore 1.06 = 2.12 \sin(314t + 57.87^\circ)$$

$$\therefore \sin^{-1}\left(\frac{1}{2}\right) = 314t + 57.87^\circ$$

$$\therefore 30^\circ = 314t + 57.87^\circ$$

$$\therefore t = -0.089 \text{ sec.}$$

$$V_c = I \cdot X_c$$

$$= 1.5 \times 39.81 = 59.72V$$

$$V_{cm} = V_c \times \sqrt{2} = 59.72 \times \sqrt{2}$$


$$V_{cm} = 84.44V$$

Expression for voltage across capacitor is:-

$$V_c = V_{cm} \sin(\omega t + \phi - 90^\circ)$$

$$= 84.44 \sin(314 \times (-0.089) + 57.87 - 90)$$

$$V_c = -73.18V$$

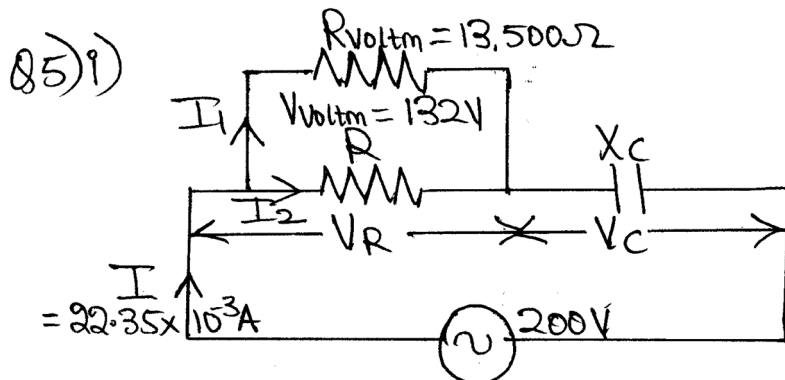

$$V_R = V_{\text{voltm}} = 132V$$

$$I_1 = \frac{V_{\text{voltm}}}{R_{\text{voltm}}} = \frac{132}{13500} = 9.78 \times 10^{-3} A$$

$$I_2 = I - I_1 = 12.57 \times 10^{-3} A$$

$$R = \frac{V_R}{I_2} = \frac{132}{12.57 \times 10^{-3}} = 10,501.19 \Omega$$

$$\frac{1}{R_{\text{Total}}} = \frac{1}{R_{\text{voltm}}} + \frac{1}{R}$$

$$= \frac{1}{13,500} + \frac{1}{10,501.19}$$

$$\therefore R_{\text{Total}} = 5,906.63 \Omega$$


$$Z = \frac{V}{I} = \frac{200}{22.35 \times 10^{-3}} = 8,948.55 \Omega$$

$$Z = \sqrt{(R_{\text{Total}})^2 + X_c^2} \quad \therefore 8948.55 = \sqrt{5906.63^2 + X_c^2}$$

$$\therefore X_c = 6722.22 \Omega$$


$$\begin{aligned}
 V_C &= I \cdot X_C \\
 &= 22.35 \times 10^{-3} \times 6722.22 \\
 &= 150.24 \text{ V}
 \end{aligned}$$

Phasor or vector diagram is :-

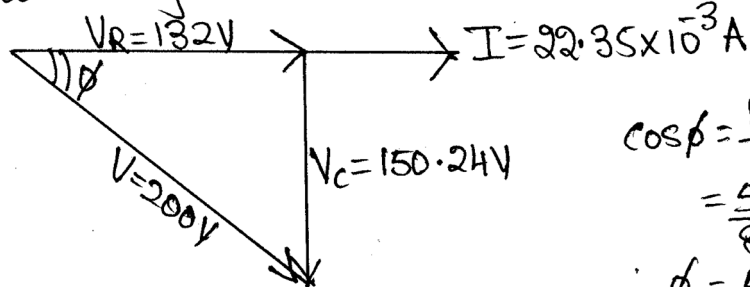

$$\begin{aligned}
 \cos \phi &= \frac{R_{\text{total}}}{Z} \\
 &= \frac{5906.63}{8948.55} \\
 \therefore \phi &= 48.7^\circ (\text{lag})
 \end{aligned}$$

(ii) When voltmeter is disconnected :-

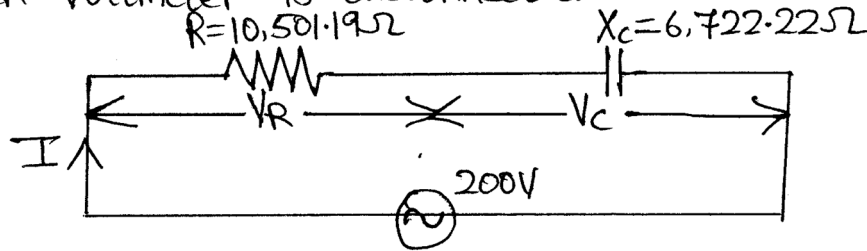

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(10,501.19)^2 + (6,722.22)^2}$$


$$\therefore Z = 12,468.49 \Omega$$

$$I = \frac{V}{Z} = \frac{200}{12,468.49} = 16.04 \times 10^{-3} \text{ A}$$

$$\begin{aligned}
 V_R &= I \cdot R = 16.04 \times 10^{-3} \times 10,501.19 \\
 V_R &= 168.44 \text{ V}
 \end{aligned}$$


$$\begin{aligned}
 V_C &= I \cdot X_C = 16.04 \times 10^{-3} \times 6,722.22 \\
 &= 107.83 \text{ V}
 \end{aligned}$$

Phasor or vector diagram is :-

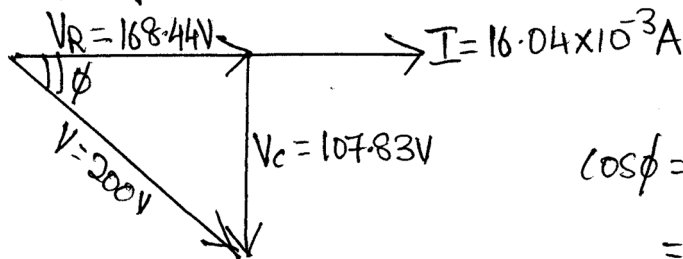

$$\begin{aligned}
 \cos \phi &= \frac{R}{Z} \\
 &= \frac{10,501.19}{12,468.49} \\
 \therefore \phi &= 32.63^\circ (\text{lag})
 \end{aligned}$$

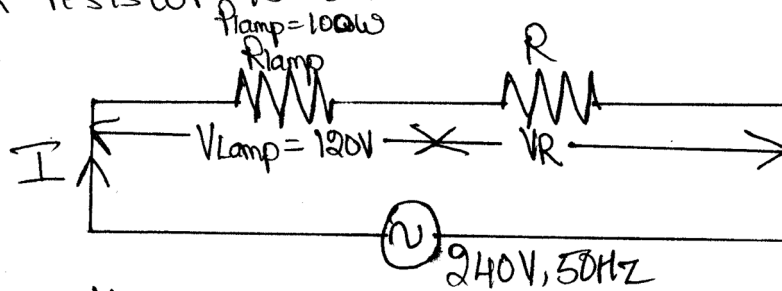Q6) Assuming lamp to be resistive:
 (a) When resistor is connected in series with the lamp



$$P_{lamp} = V_{lamp} \cdot I$$

$$\therefore 100 = 120 \times I$$

$$\therefore I = 0.83A$$

$$V_{lamp} = I \cdot R_{lamp}$$

$$\therefore 120 = 0.83 \times R_{lamp}$$

$$\therefore R_{lamp} = 144.58 \Omega$$

$$V = I (R_{lamp} + R)$$

$$\therefore 240 = 0.83 (144.58 + R)$$

$$\therefore R = 144.58 \Omega$$

$$V_R = I \cdot R$$

$$= 0.83 \times 144.58$$

$$V_R = 120V$$


$$P.f. = \cos \phi = 1 \quad (\because \text{Circuit is totally resistive})$$

$$P = I^2 (R_{lamp} + R)$$

$$= (0.83)^2 [144.58 + 144.58]$$

$$P = 199.2 W$$

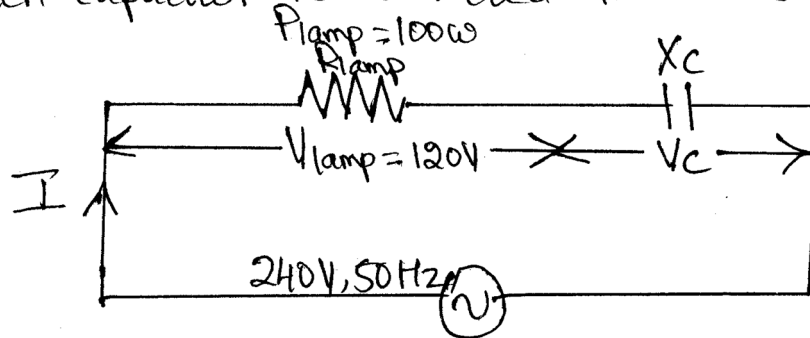(b) When capacitor is connected in series with the lamp



$$P_{lamp} = V_{lamp} \cdot I$$

$$\therefore 100 = 120 \times I$$

$$\therefore I = 0.83A$$

$$V_{lamp} = I \cdot R_{lamp}$$

$$\therefore 120 = 0.83 \times R_{lamp}$$

$$\therefore R_{lamp} = 144.58 \Omega$$

$$Z = \frac{V}{I} = \frac{240}{0.83} = 289.16 \Omega$$

$$Z = \sqrt{(R_{lamp})^2 + (X_c)^2}$$

$$\therefore 289.16 = \sqrt{(144.58)^2 + X_c^2}$$


$$\therefore X_c = 250.42 \Omega$$

$$X_c = \frac{1}{2\pi f \cdot C} \quad \therefore 250.42 = \frac{1}{2\pi \times 50 \times C} \quad \therefore C = 1.27 \times 10^{-5} F$$

$$\cos \phi = \frac{R_{lamp}}{Z} = \frac{144.58}{289.16} = 0.5 (\text{lead})$$

$$\begin{aligned} P &= VI \cos \phi \\ &= 240 \times 0.83 \times 0.5 \\ &= 99.6 W \end{aligned}$$

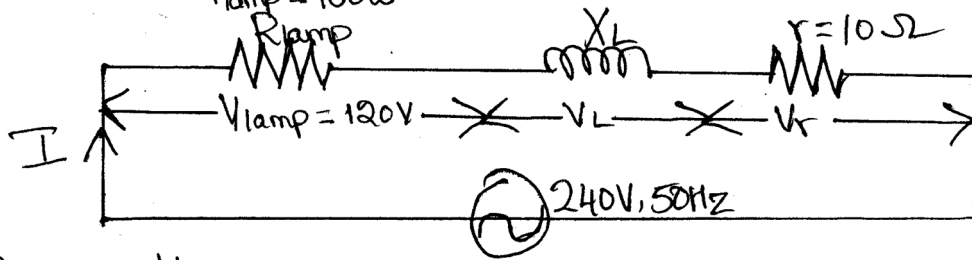(c) When inductor with 10Ω resistor is connected in series with the lamp



$$P_{lamp} = V_{lamp} \cdot I$$

$$\therefore 100 = 120 \times I$$

$$\therefore I = 0.83A$$

$$V_{lamp} = I \cdot R_{lamp}$$

$$\therefore 120 = 0.83 \times R_{lamp}$$

$$\therefore R_{lamp} = 144.58\Omega$$

$$Z = \frac{V}{I} = \frac{240}{0.83} = 289.16\Omega$$

$$Z = \sqrt{(R_{lamp} + r)^2 + X_L^2}$$

$$\therefore 289.16 = \sqrt{(144.58 + 10)^2 + X_L^2}$$

$$\therefore X_L = 244.37\Omega$$

$$X_L = 2\pi f \cdot L$$

$$\therefore 244.37 = 2\pi \times 50 \times L$$

$$\therefore L = 0.778H$$

$$\cos \phi = \frac{R_{lamp} + r}{Z} = \frac{144.58 + 10}{289.16} = 0.535 (\text{lag})$$

$$P = VI \cos \phi$$

$$= 240 \times 0.83 \times 0.535$$

$$= 106.49W$$

Method (b) is preferred since power consumed is the least.

$$\begin{aligned} \text{Q7) } P &= 700 \text{ W} \\ \text{pf} &= 0.707 \text{ (lead)} \\ v &= 141.4 \sin(314t + 30^\circ) \end{aligned}$$

Comparing with

$$v = V_m \sin(\omega t + \theta_1)$$

$$\therefore V_m = 141.4 \text{ V}, \quad \omega = 314 \text{ rad/sec}, \quad \theta_1 = 30^\circ$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 99.99 \text{ V}$$

$$P = VI \cos \phi$$

$$\therefore 700 = 99.99 \times I \times 0.707$$

$$\therefore I = 9.9 \text{ A}$$

$$Z = \frac{V}{I} = \frac{99.99}{9.9} = 10.1 \Omega$$

$$\cos \phi = \frac{R}{Z}$$

$$\therefore 0.707 = \frac{R}{10.1} \quad \therefore R = 7.14 \Omega$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\therefore 10.1 = \sqrt{(7.14)^2 + X_C^2}$$

$$\therefore X_C = 7.14 \Omega$$


$$X_C = \frac{1}{\omega C}$$

$$\therefore 7.14 = \frac{1}{314 \times C}$$


$$\therefore C = 4.46 \times 10^{-4} \text{ F}$$

TYPE III :- AC THROUGH RESISTANCE, INDUCTANCE AND CAPACITANCE (R-L-C CIRCUIT):-

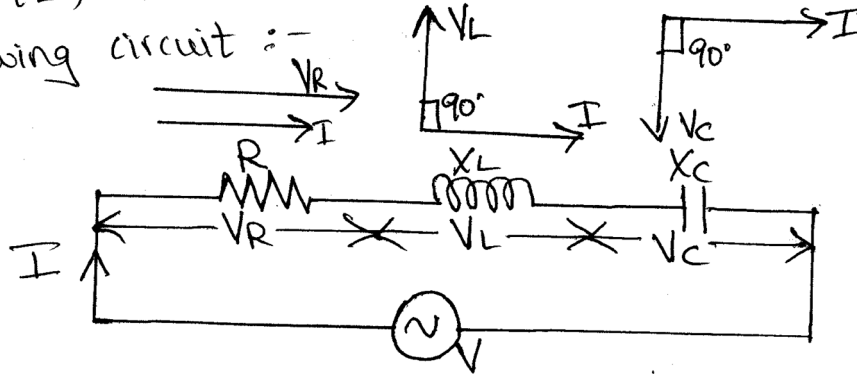
Consider a resistance (R) connected in series with an inductor (L) and capacitor (C) across a.c. supply as shown in following circuit :-



Voltage triangle is

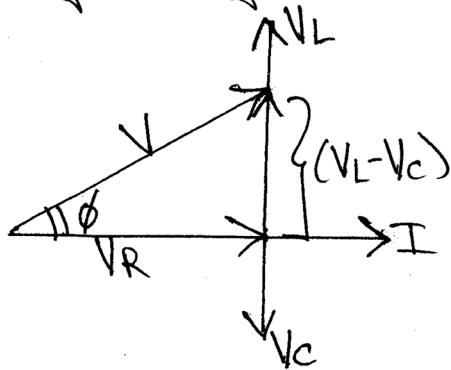

Impedance triangle is

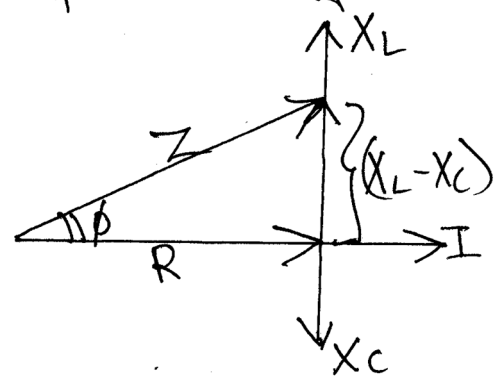

{ We assume $V_L > V_C$ }

From voltage triangle

$$V = \sqrt{(V_R)^2 + (V_L - V_C)^2}$$

$$\therefore IZ = \sqrt{(IR)^2 + (I X_L - I X_C)^2}$$

$$\therefore IZ = I \cdot \sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$P.f. = \cos \phi = \frac{R}{Z} \quad \begin{matrix} \text{(lag or lead)} \\ \text{if } X_L > X_C \quad \text{if } X_C > X_L \end{matrix}$$

$$Z = R + j[X_L - X_C] \text{ if } X_L > X_C$$

$$Z = R - j[X_C - X_L] \text{ if } X_C > X_L$$

TYPE OF IMPEDANCE	VALUE OF IMPEDANCE	PHASE ANGLE OF CURRENT	POWER FACTOR
Resistance only	R	0°	1
Inductance only	$X_L = 2\pi f \cdot L$	90° (lag)	0
Capacitance only	$X_C = \frac{1}{2\pi f \cdot C}$	90° (lead)	0
R-L circuit	$Z = \sqrt{R^2 + X_L^2}$	$0^\circ < \phi < 90^\circ$ (lag)	$0 < \text{Pf} < 1$ (lag)
R-C circuit	$Z = \sqrt{R^2 + X_C^2}$	$0^\circ < \phi < 90^\circ$ (lead)	$0 < \text{Pf} < 1$ (lead)
R-L-C circuit	$Z = \sqrt{R^2 + (X_L - X_C)^2}$	$0^\circ < \phi < 90^\circ$ (lag or lead)	$0 < \text{Pf} < 1$ (lag or lead)

Q1) $V = 5V$

$V_R = 3V$

$V_L = 1V$

$$V = \sqrt{V_R^2 + |V_L - V_C|^2}$$

$$\therefore 5 = \sqrt{(3)^2 + |1 - V_C|^2}$$

$$\therefore 16 = |1 - V_C|^2$$


$$\therefore 1 - V_C = \pm 4$$

$$\therefore V_C = -5V \text{ or } V_C = 3V$$

Since voltage across capacitor is vectorly negative

$$\therefore V_C = -5V$$

Phasor Diagram is:-

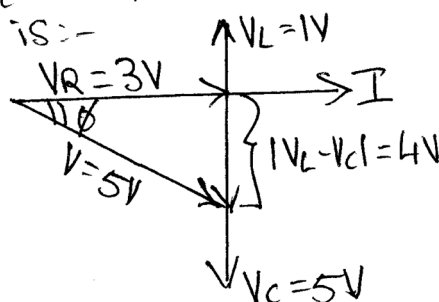

$$\cos \phi = \frac{R}{Z} = \frac{I R}{I Z} = \frac{V_R}{V}$$

$$\therefore \cos \phi = \frac{3}{5} = 0.6 \text{ (lead)}$$

$$\therefore \phi = 53.13^\circ \text{ (lead)}$$

$$\begin{aligned}
 Q2) \quad R &= 10 \Omega \\
 L &= 0.1 \text{ H} \\
 C &= 150 \times 10^{-6} \text{ F} \\
 V &= 200 \text{ V} \\
 f &= 50 \text{ Hz}
 \end{aligned}$$

$$\begin{aligned}
 (i) \quad X_L &= 2\pi fL \\
 &= 2\pi \times 50 \times 0.1 = 31.42 \Omega
 \end{aligned}$$

$$(ii) \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 150 \times 10^{-6}} = 21.22 \Omega$$

$$\begin{aligned}
 (iii) \quad Z &= \sqrt{R^2 + (X_L - X_C)^2} \\
 &= \sqrt{(10)^2 + (31.42 - 21.22)^2} \\
 Z &= 14.28 \Omega
 \end{aligned}$$

$$(iv) \quad I = \frac{V}{Z} = \frac{200}{14.28} = 14 \text{ A}$$

$$(v) \quad \text{Pf} = \cos \phi = \frac{R}{Z} = \frac{10}{14.28} = 0.7 \text{ (lag)}$$

$$\begin{aligned}
 (vi) \quad Z_{\text{coil}} &= \sqrt{R^2 + X_L^2} = 32.97 \Omega \\
 V_{\text{coil}} &= I \cdot Z_{\text{coil}} = 14 \times 32.97 \\
 &= 461.58 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_C &= I \cdot X_C = 14 \times 21.22 \\
 &= 297.08 \text{ V}
 \end{aligned}$$

$$\begin{aligned} Q3) \quad V &= 100 \sin 314t \\ R &= 10 \Omega \\ L &= 0.0318 \text{ H} \\ C &= 63.6 \times 10^{-6} \text{ F} \end{aligned}$$

Comparing with

$$v = V_m \sin \omega t$$

$$\therefore V_m = 100 \text{ V}, \quad \omega = 314 \text{ rad/sec}$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.71 \text{ V}$$

$$X_L = \omega L = 314 \times 0.0318 = 9.99 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314 \times 63.6 \times 10^{-6}} = 50.07 \Omega$$

$$Z = \sqrt{R^2 + (X_C + X_L)^2} = \sqrt{10^2 + (50.07 + 9.99)^2}$$

$$\therefore Z = 41.31 \Omega$$

$$I = \frac{V}{Z} = \frac{70.71}{41.31} = 1.71 \text{ A}$$

$$I_m = I \times \sqrt{2} = 2.42 \text{ A}$$

$$(i) \text{ P.f.} = \cos \phi = \frac{R}{Z} = \frac{10}{41.31} = 0.242 \text{ (lead)}$$

$$(ii) \therefore \phi = 75.99^\circ \text{ (lead)}$$

$$(i) i(t) = I_m \sin(\omega t + \phi) = 2.42 \sin(314t + 75.99^\circ)$$

$$\begin{aligned} (iv) \text{ Active power} &= VI \cos \phi \\ &= 70.71 \times 1.71 \cos 75.99^\circ \\ &= 29.27 \text{ W} \end{aligned}$$

$$\begin{aligned} (v) \text{ Peak value of pulsating energy} &= VI + VI \cos \phi \\ &= 70.71 \times 1.71 + 29.27 \\ &= 150.18 \text{ W} \end{aligned}$$

Q4) Coil Z_1
 $V_1 = 230V$
 $f_1 = 50Hz$
 $P_1 = 100W$
 $\cos \phi_1 = 0.5 \text{ (lag)}$
 $P_1 = V_1 I_1 \cos \phi_1$
 $\therefore 100 = 230 \times I_1 \times 0.5$
 $\therefore I_1 = 0.87A$

$$Z_1 = \frac{V_1}{I_1} = \frac{230}{0.87} = 264.37 \Omega$$

$$\cos \phi_1 = \frac{R_1}{Z_1}$$

$$\therefore 0.5 = \frac{R_1}{264.37}$$

$$\therefore R_1 = 132.19 \Omega$$

$$Z_1 = \sqrt{R_1^2 + X_{L1}^2}$$

$$\therefore 264.37 = \sqrt{(132.19)^2 + X_{L1}^2}$$

$$\therefore X_{L1} = 228.95 \Omega$$

Coil Z_2
 $V_2 = 230V$
 $f_2 = 50Hz$
 $P_2 = 60W$
 $\cos \phi_2 = 0.6 \text{ (lead)}$
 $P_2 = V_2 I_2 \cos \phi_2$
 $60 = 230 \times I_2 \times 0.6$
 $I_2 = 0.44A$

$$Z_2 = \frac{V_2}{I_2} = \frac{230}{0.44} = 522.73 \Omega$$

$$\cos \phi_2 = \frac{R_2}{Z_2}$$

$$\therefore 0.6 = \frac{R_2}{522.73}$$

$$\therefore R_2 = 313.64 \Omega$$

$$Z_2 = \sqrt{R_2^2 + X_{C2}^2}$$

$$\therefore 522.73 = \sqrt{(313.64)^2 + X_{C2}^2}$$

$$\therefore X_{C2} = 418.18 \Omega$$

When coil Z_1 and Z_2 are connected in series

$$Z = \sqrt{(R_1 + R_2)^2 + (X_{C2} + X_{L1})^2}$$

$$= \sqrt{(132.19 + 313.64)^2 + (228.95 - 418.18)^2}$$

$$Z = 484.33 \Omega$$

$$I = \frac{V}{Z} = \frac{230}{484.33} = 0.48A$$

$$P_f = \cos \phi = \frac{R_1 + R_2}{Z} = \frac{132.19 + 313.64}{484.33} = 0.921 \text{ (lead)}$$

$$P = VI \cos \phi = 230 \times 0.48 \times 0.921 = 101.68W$$

(ii) In rectangular form:-

$$\begin{aligned} Z &= (R_1 + R_2) + j(X_L - X_C) \\ &= (132.19 + 313.64) + j(228.95 - 418.18) \\ &= 445.83 - j189.23 \end{aligned}$$

For overall p.f. to be unity, circuit should be in resonance. $\therefore$ It should be a purely resistive circuit.

Hence we include

$$X_{L3} = +j189.23$$

$$\begin{aligned} \therefore \text{Total } Z &= Z + X_{L3} \\ &= 445.83 - j189.23 + j189.23 \\ &= 445.83 \text{ (purely resistive)} \end{aligned}$$

$$\therefore X_{L3} = 2\pi f \cdot L_3$$

$$\therefore 189.23 = 2\pi \times 50 \times L_3$$

$$\therefore L_3 = 0.6 \text{ H.}$$

$$Q5) L = 0.01H$$

$$\begin{aligned} v &= 400 \cos(3000t - 10^\circ) \\ &= 400 \sin(3000t - 10^\circ + 90^\circ) \\ &= 400 \sin(3000t + 80^\circ) \\ i &= 10\sqrt{2} \cos(3000t - 55^\circ) \\ &= 10\sqrt{2} \sin(3000t - 55^\circ + 90^\circ) \\ &= 10\sqrt{2} \sin(3000t + 35^\circ) \end{aligned}$$

Comparing with

$$v = V_m \sin(\omega t + \theta_1)$$

$$\therefore V_m = 400V, \quad \omega = 3000 \text{ rad/sec}, \quad \theta_1 = 80^\circ$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{400}{\sqrt{2}} = 282.84V$$

Comparing with

$$i = I_m \sin(\omega t + \theta_2)$$

$$\therefore I_m = 10\sqrt{2}A, \quad \omega = 3000 \text{ rad/sec}, \quad \theta_2 = 35^\circ$$

$$I = \frac{I_m}{\sqrt{2}} = \frac{10\sqrt{2}}{\sqrt{2}} = 10A$$

$$Z = \frac{V}{I} = \frac{282.84}{10} = 28.28\Omega$$

$$\cos\phi = \frac{R}{Z}$$

$$\therefore \cos 45^\circ = \frac{R}{28.28}$$

$$\therefore R = 20\Omega$$


$$X_L = \omega L = 3000 \times 0.01 = 30\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \therefore 28.28 = \sqrt{20^2 + (30 - X_C)^2}$$

$$X_C = 10\Omega$$

$$X_C = \frac{1}{\omega C} \quad \therefore 10 = \frac{1}{3000 \times C}$$

$$\therefore C = 3.33 \times 10^{-5} F$$

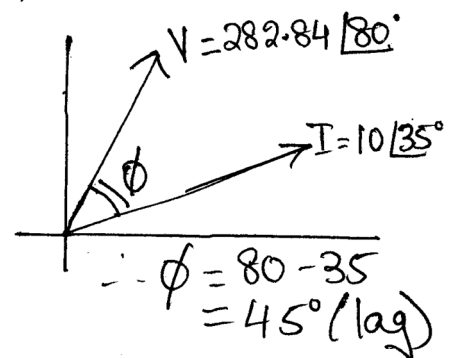

$$\begin{aligned} Q6) R &= 8 \Omega \\ X_L &= 16 \Omega \\ V &= 100V \\ f &= 50 \text{ Hz} \\ I &= 12.5 \text{ A} \end{aligned}$$

$$(i) Z = \frac{V}{I} = \frac{100}{12.5} = 8 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore 8 = \sqrt{(8)^2 + (16 - X_C)^2}$$

$$\therefore 16 - X_C = 0$$

$$\therefore X_C = 16 \Omega$$

$$X_C = \frac{1}{2\pi f \cdot C}$$

$$\therefore 16 = \frac{1}{2\pi \times 50 \times C}$$

$$\therefore C = 1.99 \times 10^{-4} \text{ F}$$

$$\begin{aligned} (ii) V_C &= I \cdot X_C \\ &= 12.5 \times 16 = 200 \text{ V} \end{aligned}$$

$$(iii) \text{ pf } = \cos \phi = \frac{R}{Z} = \frac{8}{8} = 1$$

$$88) \quad i = 4.5 + j12 = 12.82 \angle 69.44^\circ$$

$$V = 100 + j150 = 180.28 \angle 56.31^\circ$$

$$a) \quad Z = \frac{V}{i} = \frac{100 + j150}{4.5 + j12} = 13.7 - j3.2$$

Comparing with $Z = R - jX_c$

$$\therefore R = 13.7 \Omega, \quad X_c = 3.2 \Omega$$

Circuit is capacitive $\therefore Z = 14.06 \angle 13.13^\circ$
 $\therefore \phi = 13.13^\circ (\text{lead})$

$$b) \quad P = V \cdot I \cos \phi$$

$$= 180.28 \times 12.82 \times \cos(13.13^\circ)$$

$$P = 2250.77 \text{ W}$$

$$c) \quad \phi = 13.13^\circ (\text{lead})$$

$$89) i) \quad Z_1 = 4 + j3 = 5 \angle 36.87^\circ$$

$$Z_2 = 6 - j8 = 10 \angle -53.13^\circ$$

$$Z_3 = 4 = 4 \angle 0^\circ$$

$$V = 100 \angle 0^\circ = 100 + j0$$

Total $Z = Z_1 + Z_2 + Z_3$ (only in rectangular form)

$$\therefore Z = 4 + j3 + 6 - j8 + 4$$

$$\therefore Z = 14 - j5 = 14.87 \angle -19.65^\circ$$

$$I = \frac{V}{Z} = \frac{100 + j0}{14 - j5} = 6.33 + j2.26 = 6.73 \angle 19.65^\circ$$

$$ii) \quad V_1 = I \cdot Z_1 = (6.33 + j2.26)(4 + j3)$$

$$= 18.54 + j28.03 = 33.61 \angle 56.52^\circ$$

$$V_2 = I Z_2 = (6.33 + j2.26)(6 - j8)$$

$$= 56.06 - j37.08 = 67.21 \angle -33.48^\circ$$

$$V_3 = I Z_3 = (6.33 + j2.26)(4) = 25.32 + j9.04 = 26.89 \angle 19.65^\circ$$

$$\begin{aligned}
 10) \quad R_1 &= 10 \Omega \\
 L_1 &= 0.05 \text{ H} \\
 R_2 &= 20 \Omega \\
 L_2 &= 0.1 \text{ H} \\
 C_2 &= 50 \times 10^{-6} \text{ F}
 \end{aligned}$$

$$V = 200 \text{ V}, f = 50 \text{ Hz}$$

$$X_{L1} = 2\pi f L_1 = 2\pi \times 50 \times 0.05 = 15.71 \Omega$$

$$X_{L2} = 2\pi f L_2 = 2\pi \times 50 \times 0.1 = 31.42 \Omega$$

$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = 63.66 \Omega$$

$$Z_1 = R_1 + jX_{L1} = 10 + j15.71$$

$$\begin{aligned}
 Z_2 &= R_2 + j(X_{L2} - X_{C2}) = 20 + j(31.42 - 63.66) \\
 &= 20 - j32.24
 \end{aligned}$$

$$\begin{aligned}
 \text{Total } Z &= Z_1 + Z_2 \quad (\text{Only in rectangular or cartesian form}) \\
 \therefore Z &= 30 - j16.53 = 34.25 \angle -28.86^\circ
 \end{aligned}$$

$$i) I = \frac{V}{Z} = \frac{200}{30 - j16.53} = 5.11 + j2.82 = 5.84 \angle 28.86^\circ$$

$$ii) V_1 = I Z_1 = (5.11 + j2.82)(10 + j15.71) = 6.87 + j108.52 = 108.74 \angle 86.38^\circ$$


$$V_2 = I Z_2 = (5.11 + j2.82)(20 - j32.24) = 193.12 - j108.35 = 221.43 \angle -29.29^\circ$$

$$\cancel{V_3 = I Z_3 = (5.11 + j2.82)(\quad)}$$

$$iii) \text{ Comparing with } Z = |Z| \angle \phi$$

$$\therefore \phi = 28.86^\circ (\text{lead})$$
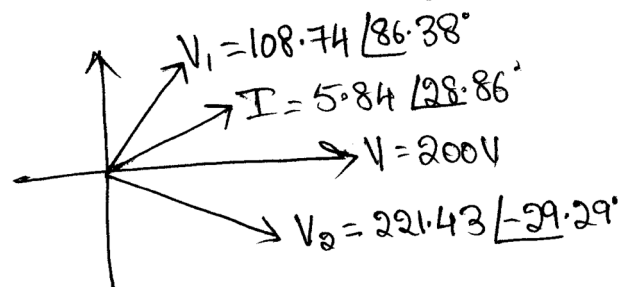
$$\begin{aligned}
 \therefore \text{pf} &= \cos \phi = \cos 28.86^\circ \\
 &= 0.8758 (\text{lead})
 \end{aligned}$$



1) $\therefore$ Voltage lags current by 30°
 $\therefore$ Current leads voltage by 30°
 $\therefore \phi = 30^\circ$ (lead)

a) $\therefore$ p.f. is leading

b) p.f. = $\cos \phi = \cos 30^\circ = 0.866$ (lead)

c) Circuit is capacitive

d) $Z_1 = 3 + j4$
 $Z_2 = 2 + j3.46$
 $Z_3 = 1 - j7.46$
 $V_1 = 10$

i) $I = \frac{V_1}{Z_1} = \frac{10}{3 + j4} = 1.2 - j1.6 = 2 \angle -53.13^\circ$

ii) $V_2 = IZ_2 = (1.2 - j1.6)(2 + j3.46) = 7.94 + j0.95 = 7.99 \angle 6.84^\circ$
 $V_3 = IZ_3 = (1.2 - j1.6)(1 - j7.46) = -10.74 - j10.55 = 15.05 \angle -135.5^\circ$

iii) $V = V_1 + V_2 + V_3$
 $= 10 + 7.94 + j0.95 - 10.74 - j10.55$
 $= 7.2 - j9.6 = 12 \angle -53.12^\circ$

RESONANCE IN SERIES R-L-C CIRCUIT:-

A Series R-L-C circuit is said to resonate if:-

- i) $X_L = X_C$
- ii) $V_L = V_C$
- iii) $Z = R$ i.e. impedance is only resistive.
- iv) Current is maximum i.e. $I = \frac{V}{Z} = \frac{V}{R}$
- v) $\text{P.f.} = \cos\phi = 1$ (Unity)
- vi) Resonance frequency is $f_0 = \frac{1}{2\pi\sqrt{LC}}$
- vii) Quality factor (Q-factor) $= \frac{X_L}{R} = \frac{2\pi f_0 L}{R}$
- viii) Half power points are at frequencies
 $f_1 = f_0 - \frac{R}{4\pi L}$ and $f_2 = f_0 + \frac{R}{4\pi L}$

81) $R = 10 \Omega$
 $L = 0.2 \text{ H}$
 $C = 40 \times 10^{-6} \text{ F}$
 $V = 100 \text{ V}$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \times 40 \times 10^{-6}}} = 56.27 \text{ Hz}$$

At resonance

$$I = \frac{V}{R} = \frac{100}{10} = 10 \text{ A}$$

$$\text{P.f.} = \cos\phi = 1$$


$$P = VI \cos\phi = 100 \times 10 \times 1 = 1000 \text{ W}$$

$$V_R = IR = 10 \times 10 = 100 \text{ V}$$

$$V_L = IX_L = 10 \times 2\pi f_0 L = 10 \times 2 \times \pi \times 56.27 \times 0.2 = 707.14$$

$$V_C = V_L = 707.14$$

Phasor Diagram is:-

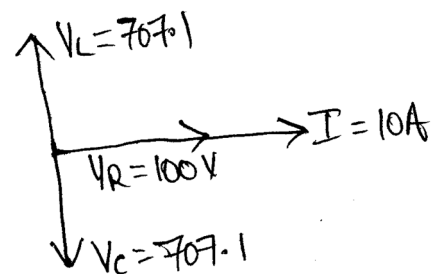

$$\begin{aligned} Q2) \quad R &= 1000 \, \Omega \\ L &= 100 \times 10^{-3} \, H \\ C &= 10 \times 10^{-12} \, F \\ V &= 100 \, V \end{aligned}$$

$$i) \quad f_0 = \frac{1}{2\pi\sqrt{LC}} =$$

$$ii) \quad Q_{\text{factor}} = \frac{X_L}{R} = \frac{2\pi f_0 L}{R} =$$

$$iii) \quad \text{Frequency at half power points is at}$$

$$f_1 = f_0 - \frac{R}{4\pi L} =$$

$$f_2 = f_0 + \frac{R}{4\pi L} =$$

$$Q3) \quad \text{Since current becomes maximum}$$

$$\therefore \text{Resonance frequency is } f_0 = \frac{600}{2\pi} \, \text{Hz.}$$

$$f' = \frac{400}{2\pi} \, \text{Hz at } I' = \frac{1}{2} I_{\text{max}}$$

$$R = 3 \, \Omega$$

$$\therefore f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore \frac{600}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore \sqrt{LC} = \frac{1}{600} \quad \therefore LC = \frac{1}{360000} \quad \text{--- (I)}$$

$$\therefore I' = \frac{1}{2} I_{\text{max}}$$

$$\therefore \frac{V}{Z} = \frac{1}{2} \frac{V}{R} \quad \therefore Z = 2R$$

$$\therefore \sqrt{R^2 + (X_L - X_C)^2} = 2R$$

$$\therefore \sqrt{9 + \left(2\pi f' L - \frac{1}{2\pi f' C}\right)^2} = 2(3)$$

$$\therefore 9 + \left(\frac{4\pi^2 f'^2 LC - 1}{2\pi f' C}\right)^2 = 36$$

$$\therefore \frac{4\pi^2 f^2 C - 1}{2\pi f^2 C} = \pm \sqrt{27}$$

Subs. from eqn (I)

$$\therefore \frac{4\pi^2 \times \left(\frac{400}{2\pi}\right)^2 \times \frac{1}{360000} - 1}{2\pi f^2 C} = \pm \sqrt{27}$$

$$\therefore \frac{16\pi^2}{360000\pi^2} - 1 = -5.196$$

$$\therefore \frac{0.4444}{2\pi \left(\frac{400}{2\pi}\right)^2 C} = -5.196$$

$$\therefore C = 2.14 \times 10^{-4} \text{ F}$$

Subs. in eqn (I)

$$\therefore L = 0.013 \text{ H}$$

PARALLEL A.C. CIRCUITS.

For R-L Circuits in Series

$$Z = R + jX_L$$

For Parallel R-L Circuits

$$Y = G - jB$$

$$\text{where Admittance (Y)} = \frac{1}{\text{Impedance (Z)}}$$

$$\text{Conductance (G)} = \frac{1}{\text{Resistance (R)}}$$

$$\text{Susceptance (B)} = \frac{1}{\text{Reactance (X}_L)}$$

For R-C circuits in Series

$$Z = R - jX_C$$

For parallel R-C Circuits

$$Y = G + jB$$

$$81) Z_1 = 6 + j8 = 10 \angle 53.13^\circ$$

$$Z_2 = 8 - j6 = 10 \angle -36.87^\circ$$

$$V = 100V$$

$$i) I_1 = \frac{V}{Z_1} = \frac{100}{6 + j8} = 6 - j8 = 10 \angle -53.13^\circ$$

$$I_2 = \frac{V}{Z_2} = \frac{100}{8 - j6} = 8 + j6 = 10 \angle 36.87^\circ$$

Comparing with $Z_1 = |Z_1| \angle \phi_1 \therefore \phi_1 = 53.13^\circ (\text{lag})$
 & $Z_2 = |Z_2| \angle \phi_2 \therefore \phi_2 = 36.87^\circ (\text{lead})$

$$\therefore \text{Pf}_1 = \cos \phi_1 = \cos 53.13^\circ = 0.6$$

$$\text{Pf}_2 = \cos \phi_2 = \cos 36.87^\circ = 0.8$$

ii) Since Z_1 & Z_2 are connected in parallel

$$\therefore \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\therefore \frac{1}{Z} = \frac{1}{6 + j8} + \frac{1}{8 - j6}$$

$$\therefore Z = 7 + j = 7.07 \angle 8.13^\circ$$

$$I = \frac{V}{Z} = \frac{100}{7 + j} = 14 - j2 = 14.14 \angle -8.13^\circ$$


Comparing with $Z = |Z| \angle \phi \therefore \phi = 8.13^\circ (\text{lag})$

$$\therefore \text{Pf} = \cos \phi = \cos 8.13^\circ = 0.99 (\text{lag})$$

$$iii) P_1 = VI_1 \cos \phi_1 = 600W$$

$$P_2 = VI_2 \cos \phi_2 = 800W$$

Phasor Diagram is :-

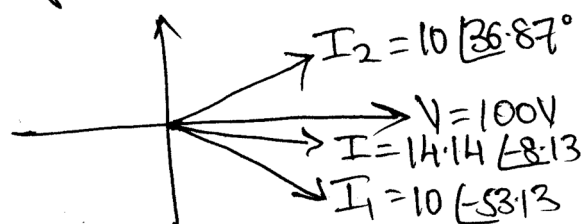

$$\begin{aligned} Q2) \quad i_a &= 7.07 \sin(314t - \pi/4) \\ i_b &= 21.2 \sin(314t + \pi/3) \\ V &= 354 \sin 314t \end{aligned}$$

Comparing with

$$i_a = I_{am} \sin(\omega t + \theta_1)$$

$$\therefore I_{am} = 7.07 \text{ A}, \quad \omega = 314 \text{ rad/sec}, \quad \theta_1 = -\pi/4^\circ = -45^\circ$$

$$I_a = \frac{I_{am}}{\sqrt{2}} = 5 \text{ A}$$

$$\therefore I_a = 5 \angle -45^\circ = 3.53 - j3.53$$

Comparing with

$$i_b = I_{bm} \sin(\omega t + \theta_2)$$

$$\therefore I_{bm} = 21.2 \text{ A}, \quad \omega = 314 \text{ rad/sec}, \quad \theta_2 = \frac{\pi}{3}^\circ = 60^\circ$$

$$I_b = \frac{I_{bm}}{\sqrt{2}} = 14.99 \text{ A}$$

$$\therefore I_b = 14.99 \angle 60^\circ = 7.5 + j12.98$$

Comparing with

$$V = V_m \sin \omega t$$

$$\therefore V_m = 354 \text{ V}, \quad \omega = 314 \text{ rad/sec}$$

$$V = \frac{V_m}{\sqrt{2}} = 250.32 \text{ V}$$

$$\therefore V = 250.32 \angle 0^\circ = 250.32 + j0$$

$$Z_a = \frac{V}{I_a} = \frac{250.32}{3.53 - j3.53} = 35.46 + j35.46$$

$$\therefore Z_a = R_a + jX_{La} \quad \therefore R_a = 35.46 \Omega, \quad X_{La} = 35.46 \Omega$$

$$Z_b = \frac{V}{I_b} = \frac{250.32}{7.5 + j12.98} =$$

$$I = I_a + I_b \quad (\text{Only in rectangular or cartesian form})$$

=