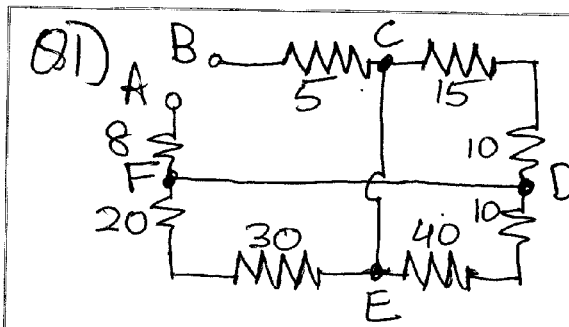


Navlakhi's



Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**




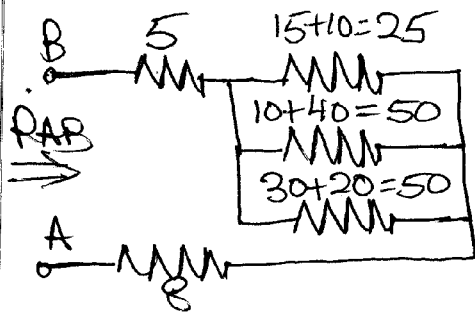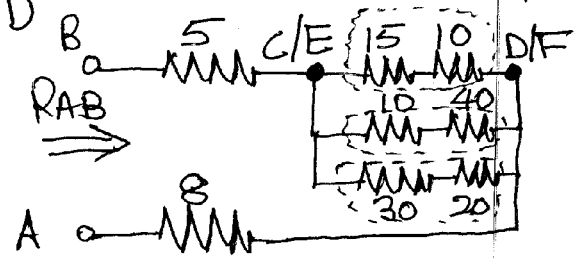Points F and D, C and E are shorted hence they can be considered as one points



$$25\Omega // 50\Omega // 50\Omega$$
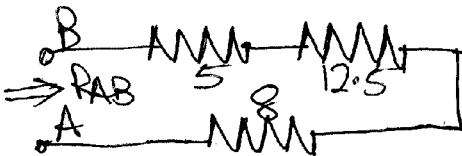
$$\therefore \frac{1}{R} = \frac{1}{25} + \frac{1}{50} + \frac{1}{50} \therefore R = 12.5\Omega$$



$$\therefore R_{AB} = 5 + 12.5 + 8 = 25.5\Omega$$

Q2) $R_{40} = 25\Omega$, $R_{100} = 40\Omega$, $R_0 = ?$, $\alpha_0 = ?$

$$\therefore R_t = R_0(1 + \alpha_0 t)$$

Put $t = 40^\circ\text{C}$ $\therefore R_{40} = R_0(1 + 40\alpha_0) \dots (I)$

Put $t = 100^\circ\text{C}$ $\therefore R_{100} = R_0(1 + 100\alpha_0) \dots (II)$

$$\therefore \frac{R_{40}}{R_{100}} = \frac{R_0(1 + 40\alpha_0)}{R_0(1 + 100\alpha_0)} \quad \left\{ \text{Dividing eqn (I) \& (II)} \right\}$$

Tel: 9820246760 / 23886023 / 23868356

Tel: 9820246760 / 9769479368

navlakhi.com: Home of Education

navlakhi.com

Best One Can Get

Navlakhhi's

Navlakhhi's




Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368


Tel: 9820246760 / 23886023 / 23868356


$\therefore \frac{25}{40} = \frac{1 + 40\alpha_0}{1 + 100\alpha_0}$; $\therefore 25 + 2500\alpha_0 = 40 + 4000\alpha_0$
 $\therefore \alpha_0 = 0.0167/^\circ\text{C}$ Subs. in eqn (I)
 $\therefore 25 = R_0(1 + 40 \times 0.0167)$
 $\therefore R_0 = 15\Omega$

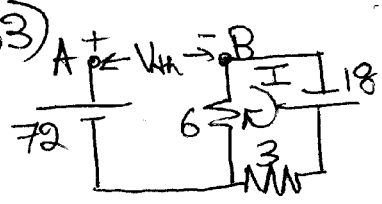
Q3) 

KVL to loop II :-
 $\therefore 9I = 18$
 $\therefore I = 2\text{A}$

KVL to loop I :-
 $\therefore -6I = 72 - V_{th} \therefore V_{th} = 84\text{V}$

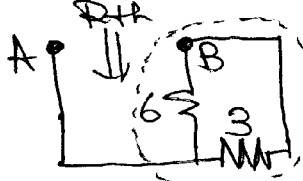For R_{th} , short 18V & 72V Batteries

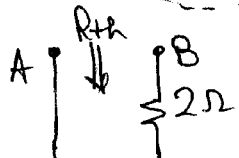 $6\Omega // 3\Omega = 2\Omega$

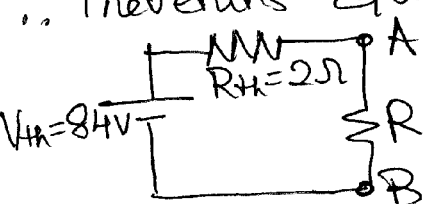
 $\therefore R_{th} = 2\Omega$

\therefore Thevenin's Equivalent circuit is:-


navlakhhi.com

navlakhhi.com: Home of Education

Best One Can Get


Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Q4) For V_{th} :-

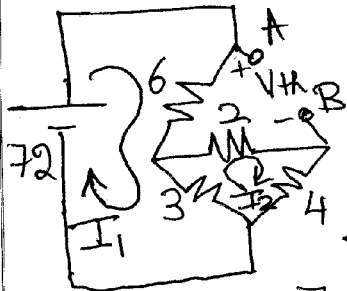

KVL to loop I :-
 $9I_1 - 3I_2 = 72 \dots (I)$

KVL to loop II :-
 $-3I_1 + 9I_2 = 0 \dots (II)$

matrix form :-

$$\begin{bmatrix} 9 & -3 \\ -3 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 72 \\ 0 \end{bmatrix}$$


$\therefore I_1 = 9A, I_2 = 3A$

KVL to loop III :-

$-6I_1 - 2I_2 = -V_{th}$

$\therefore V_{th} = 60V$

For R_{th} , short 72V Battery


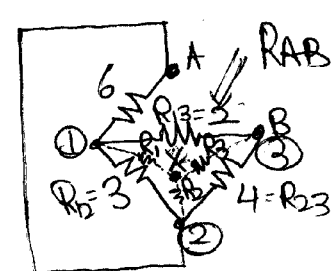


Converting Delta to Star

$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{23} + R_{13}} = \frac{3 \times 2}{3 + 4 + 2} = 0.67\Omega$

$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{23} + R_{13}} = 1.33\Omega$

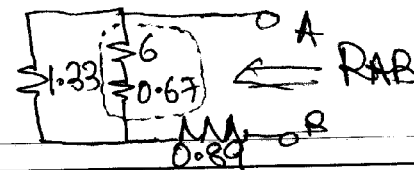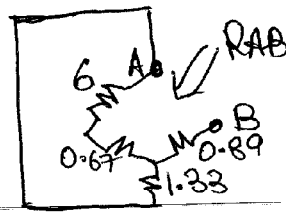$R_3 = \frac{R_{23} \cdot R_{13}}{R_{12} + R_{23} + R_{13}} = 0.89\Omega$



Tel: 9820246760 / 23886023 / 23868356

Tel: 9820246760 / 9769479368

navlakhhi.com

navlakhhi.com: Home of Education

www.navlakhhi.com

Kunal Navlakhhi

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

$1.33\Omega \parallel 6.67\Omega$
 $\therefore \frac{1}{R} = \frac{1}{1.33} + \frac{1}{6.67} \therefore R = 1.11\Omega$

$\therefore R_{AB} = 0.89 + 1.11 = 2\Omega$

For maximum power transfer
 $R_L = R_{th} = R_{AB} \therefore R_L = 2\Omega \therefore R = 2\Omega$

Thevenin's Eq. ckt. is:-

By KVL,
 $4I = 60 \therefore I = 15A$

Maximum power = $I^2 \cdot R_L = 450W$

Q5)

KCL at node A:-
 $I_1 + I_2 + I_3 = 0$
 $\frac{V_1 - 10}{2} + \frac{V_1}{10} + \frac{V_1 - V_2}{5} = 0 \therefore V_1 \left(\frac{1}{2} + \frac{1}{10} + \frac{1}{5} \right) + V_2 \left(-\frac{1}{5} \right) = 5$ --- (I)

navlakhhi.com

navlakhhi.com: Home of Education

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

KCL at node B:-
 $I_3 = I_4 + \frac{1}{3} + I_5$
 $\therefore \frac{V_1 - V_2}{5} = \frac{V_2}{15} + \frac{1}{3} + \frac{V_2 - 18}{3} \therefore V_1 \left(\frac{1}{5}\right) + V_2 \left(\frac{1}{5} - \frac{1}{15} - \frac{1}{3}\right) = 1 - 6$ --- (I)
 $V_1 = 9.39V, V_2 = 12.58V$
 Current through 2Ω is $I_1 = \frac{V_1 - 10}{2} = -0.305A$
 Current through 3Ω is $I_5 = \frac{V_2 - 18}{3} = -1.81A$

NOTE: For verification we use source conversion and mesh analysis

$\therefore I_1 = 0.303, I_2 = -0.64, I_3 = -1.81A$
 $I_{2\Omega} = I_1 = 0.303, I_{3\Omega} = I_3 = -1.81A$

86) KVL to loop I:-
 $3I_1 - 2I_2 = 100$ --- (I)
 KVL to loop II:-
 $-2I_1 + 4I_2 = 0$ --- (II)

In matrix form
 $\begin{bmatrix} 3 & -2 \\ -2 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix} \therefore I_1 = 50A, I_2 = 25A$

\therefore Reading of ammeter = $I_2 = 25A$

navlakhhi.com

navlakhhi.com: Home of Education

www.navlakhhi.com

Kunal Navlakhhi

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

Q7) For V_{th} :-

Eqn. of supermesh is:-
 $I_2 - I_1 = 13$
 $\therefore -I_1 + I_2 = 13 \dots (I)$
 KVL to loop I & loop II:-
 $15I_1 + 100I_2 = 150 \dots (II)$

In matrix form:-

$$\begin{bmatrix} -1 & 1 \\ 15 & 100 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 13 \\ 150 \end{bmatrix} \therefore I_1 = -10A, I_2 = 3A$$

KVL to loop III:-
 $-40I_2 = -V_{th} - 50 \therefore V_{th} = 70V$

For R_{th} , short 150V, 50V Batteries & open 13A current source

$75\Omega \parallel 40\Omega \therefore \frac{1}{R_{th}} = \frac{1}{75} + \frac{1}{40} \therefore R_{th} = 26.09\Omega$

Thevenin's Eq. ckt. is:-

By KVL,
 $I = 1.25A$

NOTE: For verification we use mesh & supermesh:-
 Eqn. of supermesh is:-
 $I_2 - I_1 = 13 \therefore -I_1 + I_2 + 0I_3 = 13$
 KVL to loop I & II:-
 $15I_1 + 100I_2 - 40I_3 = 150$
 KVL to loop III:-
 $0I_1 - 40I_2 + 70I_3 = -50$

navlakhi.com

navlakhi.com: Home of Education

www.navlakhi.com

$I_1 = -9.57A$
 $I_2 = 3.43A$
 $I_3 = 1.25A$

Kunal Navlakhi

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhhi.com: Home of Education

navlakhhi.com

Q8) For V_{th} , open R_L

KVL to loop I: $12I_1 - 6I_2 + 0I_3 = 18 \dots (I)$
 KVL to loop II: $-6I_1 + 15I_2 - 6I_3 = 0 \dots (II)$
 KVL to loop III: $0I_1 - 6I_2 + 12I_3 = 0 \dots (III)$

In matrix form: $\begin{bmatrix} 12 & -6 & 0 \\ -6 & 15 & -6 \\ 0 & -6 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 18 \\ 0 \\ 0 \end{bmatrix}$ $\therefore I_1 = 2A, I_2 = 1A, I_3 = 0.5A$

KVL to loop IV: $-3I_3 = -V_{th} \therefore V_{th} = 1.5V$

For R_{th} , short 18V Battery:

$6\Omega // 6\Omega = 3\Omega$

$6\Omega // 6\Omega = 3\Omega$

$6\Omega // 3\Omega \therefore \frac{1}{R_{th}} = \frac{1}{6} + \frac{1}{3} \therefore R_{th} = 2\Omega$

Thevening eq.ckt is:

For max power $R_L = R_{th} = 2\Omega$
 By KVL, $I = 0.375 A$
 Max power = $I^2 R_L = (0.375)^2 \times 2 = 0.28125 W$

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

Q9) $R'_{30} = 400\Omega$, $R''_{30} = 200\Omega$, $\alpha'_{30} = 0.001$, $\alpha''_{30} = 0.004$

$$\alpha_t = \frac{\alpha_0}{1 + \alpha_0 t} \therefore \alpha'_{30} = \frac{\alpha'_0}{1 + 60\alpha'_0} \therefore 0.001 = \frac{\alpha'_0}{1 + 30\alpha'_0} \therefore \alpha'_0 = 1.031 \times 10^{-3}/^\circ\text{C}$$

$$\alpha''_{30} = \frac{\alpha''_0}{1 + 30\alpha''_0} \therefore 0.004 = \frac{\alpha''_0}{1 + 30\alpha''_0} \therefore \alpha''_0 = 4.55 \times 10^{-3}/^\circ\text{C}$$

$$\therefore R_t = R_0(1 + \alpha_0 t) \therefore R'_{60} = R'_0(1 + 60\alpha'_0) \text{--- (I)}; R''_{30} = R''_0(1 + 30\alpha''_0) \text{--- (II)}$$

Dividing (I) by (II) $\therefore \frac{R'_{60}}{R''_{30}} = \frac{1 + 60\alpha'_0}{1 + 30\alpha''_0} \therefore R'_{60} = 412\Omega$

$$R'_{60} = R'_0(1 + 60\alpha'_0) \text{--- (III)}; R''_{30} = R''_0(1 + 30\alpha''_0) \text{--- (IV)}$$

Dividing (III) by (IV) $\therefore \frac{R'_{60}}{R''_{30}} = \frac{1 + 60\alpha'_0}{1 + 30\alpha''_0} \therefore R'_{60} = 224.02\Omega$

$$\therefore \text{At } 60^\circ\text{C}, R_{60} = R'_{60} + R''_{60} = 636.02\Omega$$

$$\therefore \text{From eq. (I) \& (III), } R'_0 = 388\Omega, R''_0 = 175.98\Omega$$

$$\text{At } 0^\circ\text{C}, R_0 = R'_0 + R''_0 = 563.98\Omega$$


$$\therefore R_t = R_0(1 + \alpha_0 t) \therefore R_{60} = R_0(1 + 60\alpha_0)$$

$$\therefore 636.02 = 563.98(1 + 60\alpha_0) \therefore \alpha_0 = 2.13 \times 10^{-3}/^\circ\text{C}$$

Q10) Since current is zero in branch CA
 \therefore circuit is balanced wheatstone's bridge

$$\therefore \frac{1}{4} = \frac{1.5}{R} \therefore R = 6\Omega$$

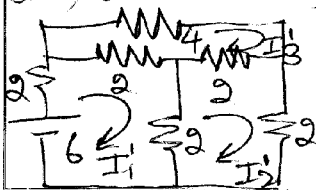Q11) Considering 6V Battery & shorting 10V & opening SA



KVL to loop I: -

$$6I_1 - 2I_2 - 2I_3 = 6 \text{--- (I)}$$

KVL to loop II: -

$$-2I_1 + 6I_2 - 2I_3 = 0 \text{--- (II)}$$

KVL to loop III: -

$$-2I_1 - 2I_2 + 8I_3 = 0 \text{--- (III)}$$

www.navlakhi.com

Kunal Navlakhi

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

In matrix form

$$\begin{bmatrix} 6 & -2 & -2 \\ -2 & 6 & -2 \\ -2 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1' \\ I_2' \\ I_3' \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix} \therefore I_1' = 1.375A \\ I_2' = 0.625A \\ I_3' = 0.5A, I_4' = 0A$$

Considering 10V Battery & shorting 6V & opening 5A

KVL to loop I: $6I_1'' - 2I_2'' - 2I_3'' = 0$
 KVL to loop II: $-2I_1'' + 6I_2'' - 2I_3'' = 0$
 KVL to loop III: $-2I_1'' - 2I_2'' + 8I_3'' = 10$

In matrix form:

$$\begin{bmatrix} 6 & -2 & -2 \\ -2 & 6 & -2 \\ -2 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1'' \\ I_2'' \\ I_3'' \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10 \end{bmatrix} \therefore I_1'' = 0.833A \\ I_2'' = 0.833A \\ I_3'' = -1.67A, I_4'' = 0A$$

Considering 5A current source & shorting 6V & 10V

KVL to loop I: $6I_1''' - 2I_2''' - 2I_3''' = 0$
 KVL to loop II: $-2I_1''' + 6I_2''' - 2I_3''' - 2I_4''' = 0$
 $\therefore I_4''' = -5A \therefore -2I_1''' + 6I_2''' - 2I_3''' = -10$
 KVL to loop III: $-2I_1''' - 2I_2''' + 8I_3''' = 0$

In matrix form:

$$\begin{bmatrix} 6 & -2 & -2 \\ -2 & 6 & -2 \\ -2 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1''' \\ I_2''' \\ I_3''' \end{bmatrix} = \begin{bmatrix} 0 \\ -10 \\ 0 \end{bmatrix} \therefore I_1''' = -1.042A \\ I_2''' = -2.29A \\ I_3''' = -0.833A, I_4''' = -5$$

By Superposition theorem,

$$I_1 = I_1' + I_1'' + I_1''' = 1.166A, I_2 = I_2' + I_2'' + I_2''' = -0.833A \\ I_3 = I_3' + I_3'' + I_3''' = 1.337A, I_4 = -5A$$

NOTE: For verification we use mesh analysis

KVL to loop I: $6I_1 - 2I_2 - 2I_3 = 6$
 KVL to loop II: $-2I_1 + 6I_2 - 2I_3 - 2I_4 = 0$
 $\therefore I_4 = -5A \therefore -2I_1 + 6I_2 - 2I_3 = -10$
 KVL to loop III: $-2I_1 - 2I_2 + 8I_3 = 10$
 $\therefore I_1 = 1.167A, I_2 = -0.833A, I_3 = 1.333A$

www.navlakhhi.com

Kunal Navlakhhi

navlakhhi.com

navlakhhi.com: Home of Education

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 **POWER**

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com: Home of Education

navlakhi.com

Q12) i) Using mesh analysis :-

KVL to loop I :- $6I_1 - 2I_2 - 4I_3 = 10$
 KVL to loop II :- $-2I_1 + 11I_2 - 4I_3 = 12$
 KVL to loop III :- $-4I_1 - 4I_2 + 23I_3 = 10$

In matrix form :-

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 11 & -4 \\ -4 & -4 & 23 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 12 \\ 10 \end{bmatrix}$$

$\therefore I_1 = 3.33A$
 $I_2 = 2.21A$
 $I_3 = 1.4A$

\therefore Current through 15Ω resistor $= I_3 = 1.4A$

ii) Using Thevenin's theorem :-

KVL to loop I :- $6I_1 - 2I_2 = 10$
 KVL to loop II :- $-2I_1 + 11I_2 = 12$

In matrix form :-

$$\begin{bmatrix} 6 & -2 \\ -2 & 11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 12 \end{bmatrix}$$

$\therefore I_1 = 2.16A$
 $I_2 = 1.48A$

KVL to loop III :- $-4I_1 - 4I_2 = V_{th} + 10 \therefore V_{th} = 24.56V$

For R_{th} , short $10V, 12V, 10V$ Batteries

$25\Omega // 4\Omega = 1.33\Omega$
 $5\Omega // 1.33\Omega = 1.07\Omega$
 $1.07\Omega // 5\Omega = 0.83\Omega$
 $\therefore R_{th} = 2.58\Omega$

Thevening Eq. ckt is

By KVL, $I_L = -1.4A$


Best One Can Get

Navlakhhi's

Navlakhhi's



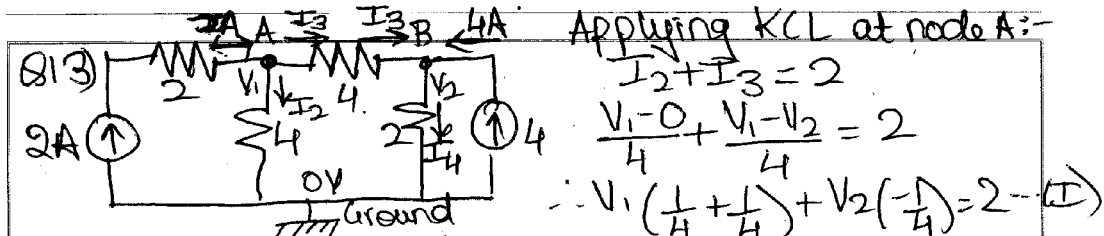Tel: 23868356 / 23886023 / 9820246760 **POWER**



Applying KCL at node A:-

$$I_2 + I_3 = 2$$

$$\frac{V_1 - 0}{4} + \frac{V_1 - V_2}{4} = 2$$


$$\therefore V_1 \left(\frac{1}{4} + \frac{1}{4} \right) + V_2 \left(-\frac{1}{4} \right) = 2 \quad \text{--- (I)}$$

KCL at node B:- $I_3 + 4 = I_4 \therefore \frac{V_1 - V_2}{4} + 4 = \frac{V_2 - 0}{4}$

$$\therefore V_1 \left(\frac{1}{4} \right) + V_2 \left(-\frac{1}{4} - \frac{1}{4} \right) = -4 \quad \text{--- (II)}$$

$$\therefore V_1 = 8V, V_2 = 8V$$

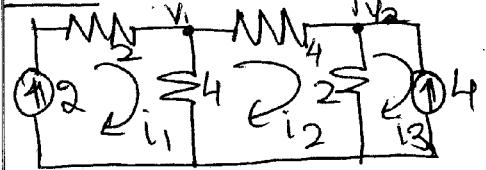NOTE:- For verification we use mesh analysis




$$i_1 = 2A; i_2 = -4A$$

KVL to loop II:-

$$-4i_1 + 10i_2 - 2i_3 = 0$$

$$\therefore i_2 = 0A$$
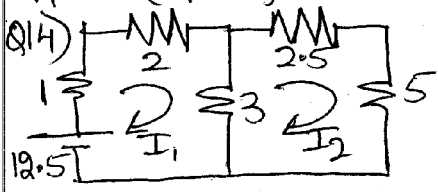
$$V_1 = 4(i_1 - i_2) = 4(2 - 0) = 8V \quad \& \quad V_2 = 2(i_2 - i_3) = 2(0 + 4) = 8V$$




KVL to loop I:- $6I_1 - 3I_2 = 12.5$

KVL to loop II:- $-3I_1 + 10.5I_2 = 0$

$$\begin{bmatrix} 6 & -3 \\ -3 & 10.5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12.5 \\ 0 \end{bmatrix} \therefore I_1 = 2.43A$$

\therefore Current through 1Ω resistor is $2.43A$ in clockwise direction

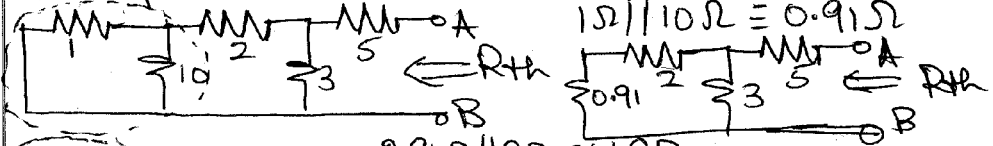Q15) For max. power $R_L = R_{th}$. We short 5V battery and open 1A current source.



$$1\Omega // 10\Omega = 0.91\Omega$$

$$0.91\Omega // 2\Omega = 0.64\Omega$$

$$2.91\Omega // 3\Omega = 1.48\Omega$$

$$R_{th} = 5 + 1.48 = 6.48\Omega$$

$$\therefore R_L = R_{th} = 6.48\Omega$$

Tel: 9820246760 / 23886023 / 23868356

Tel: 9820246760 / 9769479368

navlakhhi.com: Home of Education

navlakhhi.com

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

Q16)

$V_{15\Omega} = 30V \because V_{15\Omega} = I \times 15$
 $\therefore 30 = I \times 15 \therefore I = 2A$
 Applying KVL to loop:-
 $+15I + 5(5+I) + I \times R = 100$
 $\therefore 30 + 35 + 2R = 100 \therefore R = 17.5\Omega$

Q17)

By KVL:- $4I = 8 \therefore I = 2A$
 $V_{AB} = 2I + 4I = 12V$
 $P_{2\Omega} = I^2 \times 2 = 8W$

Q18)

KVL to loop I:-
 $10I_1 - 10I_2 = 10 \dots (i)$
 Eqn. of supermesh is
 $I_3 - I_2 = 4 \dots (ii)$
 KVL to loop II & III:-
 $-10I_1 + 10I_2 + 7I_3 = -20$
 $\begin{bmatrix} 10 & -10 & 0 \\ 0 & -1 & 1 \\ -10 & 10 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 4 \\ -20 \end{bmatrix}$
 $\therefore I_1 = -4.43A$
 $I_2 = -5.43A, I_3 = -1.43A$

KVL to loop IV:- $-5I_3 + 2(0) = 8 + 6 - V_{th} \therefore V_{th} = 6.85V$
 For R_{th} , short 10V, 12V, 8V, 6V Batteries & open 4A current source
 $10\Omega // \text{short} = \text{short}, 4\Omega \text{ series open} = \text{open}$
 $2\Omega // 5\Omega = 1.43\Omega$
 $\therefore R_{th} = 1.43 + 2 = 3.43\Omega$

Thevenin's Eq. ckt. is

 By KVL,
 $5.43I = 6.85$
 $\therefore I = 1.26A$

NOTE: For verification use mesh

KVL to loop I:- $10I_1 - 10I_2 = 10$
 Eqn. of supermesh:- $I_3 - I_2 = 4$
 KVL to loop IV:- $-5I_3 + 2I_4 = 14$
 $\therefore I_4 = (14 + 5I_3) \dots (iii)$
 KVL to loop II & III:- $-10I_1 + 10I_2 + 7I_3 - 5I_4 = -20$
 From eq (i):- $-10I_1 + 10I_2 + 7I_3 = -20$
 $I_1 = -3.53, I_2 = -4.53, I_3 = -0.53, I_4 = 1.26$
 Kunal Navlakhhi

www.navlakhhi.com

navlakhhi.com

navlakhhi.com: Home of Education

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 **POWER**

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

Q19) **Converting delta to star**

$$R_1 = \frac{R_2 \cdot R_3}{R_2 + R_3 + R_1} = \frac{2R \times 2R}{2R + 2R + 2R} = \frac{4R}{5}$$

$$R_2 = \frac{R_1 \cdot R_3}{R_2 + R_3 + R_1} = \frac{2R \times R}{2R + 2R + 2R} = \frac{2R}{5}$$

$$R_3 = \frac{R_2 \cdot R_1}{R_2 + R_3 + R_1} = \frac{2R \times R}{2R + 2R + 2R} = \frac{2R}{5}$$

$7R/5 \parallel 14R/5 = \frac{14R}{5}$

$$R_{AB} = \left(\frac{14R}{5} + \frac{2R}{5} \right) \parallel R = \frac{4R}{7}$$

NOTE: - For verification we convert inner star to delta

$$R_{12} = R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3} = 2R + 2R + \frac{2R \times 2R}{2R} = 6R$$

$$R_{23} = R_2 + R_3 + \frac{R_2 \cdot R_3}{R_1} = 6R$$

$$R_{13} = R_1 + R_3 + \frac{R_1 \cdot R_3}{R_2} = 6R$$

$R \parallel 6R = \frac{6R}{7}$

$$R_{AB} = \frac{12R}{7} \parallel 6R/7 = \frac{4R}{7}$$

20) i) One resistor burns out (open circuit)

$\therefore I = 8A$
 $I_1 = I_2 = 4A$

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 POWER


Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com: Home of Education

navlakhi.com

(ii) If one resistor gets shorted

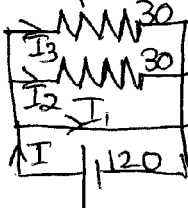

$$\begin{aligned} I_1 &= \text{Infinite} \\ I_2 &= I_3 = 0A \end{aligned}$$

Q21) $R_{15} = 50\Omega$, $R_{55} = 58\Omega$, $\alpha_0 = ?$


$$R_t = R_0(1 + \alpha_0 t)$$

$$\therefore R_{15} = R_0(1 + 15\alpha_0) \therefore 50 = R_0(1 + 15\alpha_0) \dots (I)$$

$$R_{55} = R_0(1 + 55\alpha_0) \therefore 58 = R_0(1 + 55\alpha_0) \dots (II)$$

Divide eq. (I) & (II)
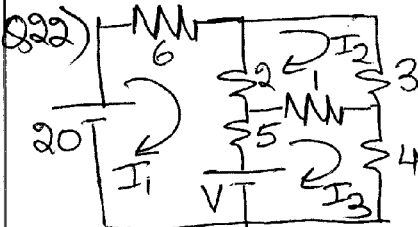
$$\therefore \frac{50}{58} = \frac{1 + 15\alpha_0}{1 + 55\alpha_0} \therefore \alpha_0 = 4.26 \times 10^{-3} / ^\circ C$$



By KVL to loop I:-

$$13I_1 - 2I_2 - 5I_3 = 20 - V \dots (I)$$

By KVL to loop II:-

$$-2I_1 + 6I_2 - I_3 = 0 \dots (II)$$

By KVL to loop III:-

$$-5I_1 - I_2 + 10I_3 = V \dots (III)$$

Put $I_1 = 0$ in eqn. (I), (II) & (III)


$$\therefore V - 2I_2 - 5I_3 = 20$$

$$6I_2 - I_3 = 0$$

$$-V - I_2 + 10I_3 = 0$$

$$\begin{bmatrix} 1 & -2 & -5 \\ 0 & 6 & -1 \\ -1 & -1 & 10 \end{bmatrix} \begin{bmatrix} V \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix} \begin{cases} V = 43.7V \\ I_2 = 0.744A \\ I_3 = 4.44A \end{cases}$$

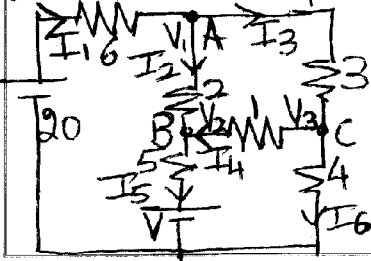NOTE: For verification we use Nodal Analysis:-



By KCL, $I_1 = 20 - V_1 \therefore I_1 = 0 \therefore V_1 = 20V$

KCL at node A:- $I_1 = I_2 + I_3 \therefore I_1 = 0$

$$\therefore I_2 + I_3 = 0 \therefore \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{5} = 0$$

$$\therefore \frac{V_2}{2} + \frac{V_3}{5} = 16.67 \dots (I)$$

By KCL at node B:-

$$I_2 + I_4 = I_5 \therefore \frac{V_1 - V_2}{2} + \frac{V_3 - V_2}{4} = \frac{V_2 - V_1}{5}$$

$$\therefore \frac{V_2(1+2)}{5} - \frac{V_3 - V_1}{5} = 10 \dots (II)$$

KCL at node C:-

$$I_3 = I_4 + I_6 \therefore \frac{V_1 - V_3}{5} = \frac{V_3 - V_2}{4} + \frac{V_3}{4}$$

$$\therefore -V_2 + V_3(1 + \frac{1}{4} + \frac{1}{4}) = 6.67 \dots (III)$$

$$\therefore V_2 = 21.49V, V_3 = 17.78V, V = 43.7V$$

www.navlakhi.com

Kunal Navlakhi


Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356/23886023/9820246760 POWER

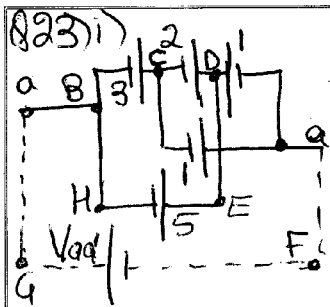


By KVL to loop F-G-a-B-C-D-a'-F

$$\therefore V_{aa'} + 3 + 2 - 1 = 0 \therefore V_{aa'} = -4V$$

By KVL to loop F-G-a-B-H-E-D-a'-F
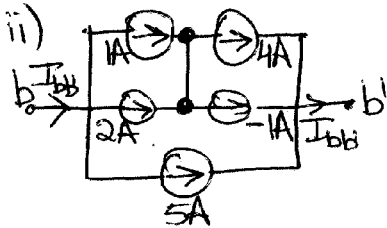
$$V_{aa'} + 5 - 1 = 0 \therefore V_{aa'} = -4V$$




By KCL at node b:-

$$I_{bb} = 1 + 2 + 5 = 8A$$

By KCL at node b':-
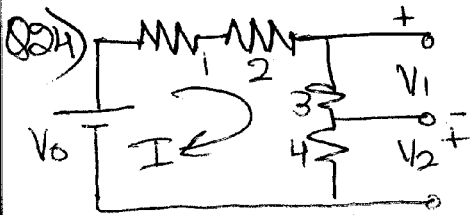
$$4 - 1 + 5 = I_{bb'} \therefore I_{bb'} = 8A$$



By KVL,

$$I + 2I + 3I + 4I = V_0$$

$$\therefore I = V_0/10$$

$$\text{Also, } V_1 = 3I = 3V_0/10$$

$$\therefore V_1/V_0 = 0.3$$

$$\text{Also, } V_2 = 4I = 4V_0/10 \therefore V_2/V_0 = 0.4$$

Q25) Short 1Ω resistor for I_{sc} :-



$$I_1 = 1A$$

KVL to loop II:-

$$-3I_1 + 5I_2 - 2I_{sc} = 1$$

$$\therefore 5I_2 - 2I_{sc} = 4 \dots (I)$$

$$\text{KVL to loop III:- } 4I_3 - 2I_{sc} = -1 \dots (II)$$

$$\text{KVL to loop IV:- } -2I_2 - 2I_3 + 4I_{sc} = 0 \dots (III)$$

$$\begin{bmatrix} 5 & 0 & -2 \\ 0 & 4 & -2 \\ -2 & -2 & 4 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_{sc} \end{bmatrix} = \begin{bmatrix} 4 \\ -1 \\ 0 \end{bmatrix} \therefore \begin{matrix} I_2 = 1A \\ I_3 = 0A \\ I_{sc} = 0.5A \end{matrix}$$

Tel: 9820246760 / 23886023 / 23868356

navlakhhi.com

navlakhhi.com: Home of Education

www.navlakhhi.com

Kunal Navlakhhi

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhhi.com: Home of Education

For R_{th} short IV Battery & open IA current source

$R_{th} = 3\Omega || 2\Omega = 1.2\Omega$
 $2\Omega || 2\Omega = 1\Omega$
 $R_{th} = \frac{1.2 \times 1}{1.2 + 1} = 0.52\Omega$

Norton's Eq.ckt is:-
 $I_{sc} = 0.5A$
 $R_{th} = 2.2\Omega$
 $R_L = 1\Omega$

By current division formula:-
 $I_L = I_{sc} \left(\frac{R_{th}}{R_{th} + R_L} \right) = 0.5 \left(\frac{2.2}{2.2 + 1} \right) = 0.344A$

NOTE: For verification we use mesh analysis:-

KVL to loop II:- $-3I_1 + 5I_2 - 2I_4 = 1$
 $5I_2 - 2I_4 = 4 \dots (I)$
 KVL to loop III:- $4I_3 - 2I_4 = -1 \dots (II)$
 KVL to loop IV:- $-2I_2 - 2I_3 + 5I_4 = 0 \dots (III)$
 $I_2 = 0.94A, I_3 = -0.078A, I_4 = 0.344A$

Applying KCL at node A:- $I_1 + I_2 + I_3 = 3$
 $\frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_1 - 36 - V_3}{4} = 3 \Rightarrow V_1 \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) + \frac{V_2}{2} + \frac{V_3}{4} = 3 \dots (IV)$

Applying KCL at node B:- $I_1 = I_4 + I_5$
 $\frac{V_1 - V_2}{2} = \frac{V_2}{100} + \frac{V_2 - V_3}{5} \Rightarrow V_1 \left(\frac{1}{2} \right) + V_2 \left(\frac{1}{2} - \frac{1}{100} - \frac{1}{5} \right) + \frac{V_3}{5} = 0 \dots (V)$

Applying KCL at node C:- $I_3 + I_5 = I_6 \Rightarrow \frac{V_1 - 36 - V_3}{4} + \frac{V_2 - V_3}{5} = \frac{V_3}{20} \dots (VI)$

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} + \frac{1}{4} & \frac{1}{2} & \frac{1}{4} \\ \frac{1}{2} & \frac{1}{2} - \frac{1}{100} - \frac{1}{5} & \frac{1}{5} \\ \frac{1}{4} & \frac{1}{5} & -\frac{1}{4} - \frac{1}{5} - \frac{1}{20} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 9 \end{bmatrix}$$

$V_1 = 13.41V, V_2 = 7.06V, V_3 = -8.47V$
 $I_5 = 3.11A$

NOTE: For verification use mesh analysis:-
 $I_1 = 3A$
 KVL to loop II:- $-4I_1 + 106I_2 - 100I_3 - 2I_4 = 0$
 $106I_2 - 100I_3 - 2I_4 = 12 \dots (I)$
 KVL to loop III:- $-100I_2 + 125I_3 - 5I_4 = 0 \dots (II)$
 KVL to loop IV:- $-2I_2 - 5I_3 + 1I_4 = -36 \dots (III)$
 $I_2 = -0.352A, I_3 = -0.424A, I_4 = -3.53A$
 $I_{50} = I_3 - I_4 = 3.11A$

www.navlakhhi.com Kunal Navlakhhi

www.navlakhhi.com

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com: Home of Education

Q27) $3\Omega \parallel \text{short} \equiv \text{short}$

KVL to loop I: $-2I_1 = -5 \Rightarrow I_1 = -2.5A$
 $I_2 = 2A$, KVL to loop B-A-D-C-B: $-2I_1 + 10(0) + 5I_2 = V_{AB} + 8$
 $\therefore V_{AB} = 7V$

Q28) $R_{20} = 15\Omega, R_{50} = 20\Omega, R_t = 25\Omega$
 $R_t = R_o(1 + \alpha t) \therefore R_{20} = R_o(1 + 20\alpha) \therefore 15 = R_o(1 + 20\alpha)$ (I)
 $R_{50} = R_o(1 + 50\alpha) \therefore 20 = R_o(1 + 50\alpha)$ (II) Divide (I) by (II)
 $\therefore \frac{15}{20} = \frac{1 + 20\alpha}{1 + 50\alpha} \therefore \alpha = 0.0143\%$ Subs. in (I) $\therefore R_o = 11.67\Omega$
 $\therefore R_t = R_o(1 + \alpha t) \therefore 25 = 11.67(1 + 0.0143t) \therefore t = 79.88\%$

Q29)

KVL to loop I: $10I_1 - 10I_2 = 10$ (I)
 Eqn. of supermesh $I_3 - I_2 = 4$ (II)
 KVL to loop II & III: $-10I_1 + 10I_2 + 7I_3 = -20$ (III)
 $\begin{bmatrix} 10 & -10 & 0 \\ 0 & -1 & 1 \\ -10 & 10 & 7 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 4 \\ -20 \end{bmatrix}$
 $\therefore I_1 = -4.43A, I_2 = -5.43A, I_3 = -1.43A$
 KVL to loop IV: $-5I_3 + 9(0) = 8 + 6 - V_{th}$
 $V_{th} = 6.85V$

For R_{th} , short 10V, 12V, 8V, 6V Batteries & open 4A current source

$10\Omega \parallel \text{short} \equiv \text{short}$
 4Ω series with open \equiv open
 $2\Omega \parallel 15\Omega = 1.43\Omega$
 $\therefore R_{th} = 1.43 + 2 = 3.43\Omega$

Thevenin's Eq.ckt is: $R_{th} = 3.43\Omega, V_{th} = 6.85V$

NOTE: For verification we can assume $R_L = 2\Omega$ & find I_L in Thevenin & verify with mesh (same as Q18)

navlakhi.com

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com: Home of Education

navlakhi.com

Q30) Consider 6V Battery, short 10V & open 5A

By KVL, $5I_1 = 6$
 $\therefore I_1 = 1.2A$
 By KVL, $-5I_1 = -V_{AB}'$
 $\therefore V_{AB}' = 6V$

Consider 10V Battery, short 6V & open 5A current source

$5A \parallel \text{short} = \text{short}$
 $V_{AB}'' = 10V$

Consider 5A current source & short 6V & 10V Batteries

$5A \parallel \text{short} = \text{short}$
 $V_{AB}''' = 0V$

By Superposition theorem, $V_{AB} = V_{AB}' + V_{AB}'' + V_{AB}''' = 16V$

NOTE: For verification

$I_2 = 5A$
 By KVL to loop I: $5I_1 = 6$
 $\therefore I_1 = 1.2A$
 By KVL to loop III: $-5I_1 = 10 - V_{AB}$ $\therefore V_{AB} = 16V$

Q31)

KVL to loop I: $-11I_1 - 9I_2 = 50$ --- (I)
 KVL to loop II: $-9I_1 + 18I_2 = 0$ --- (II)

$$\begin{bmatrix} 11 & -9 \\ -9 & 18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$
 $\therefore I_1 = 7.69A$
 $I_2 = 3.85A$
 KVL to loop B-A-C-B: $-8I_1 + 13I_2 = V_{th}$
 $\therefore V_{th} = -11.47V$

www.navlakhi.com

Kunal Navlakhi

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

For R_{th} , Short 50V Battery

Converting delta to star

$$R_1 = \frac{R_2 \times R_3}{R_2 + R_3 + R_1} = 1.82\Omega$$

$$R_2 = \frac{R_1 \times R_3}{R_2 + R_3 + R_1} = 0.73\Omega$$

$$R_3 = \frac{R_2 \times R_1}{R_2 + R_3 + R_1} = 0.91\Omega$$

Thevening eq. ckt. is

By KVL, $V_{th} = I_L(R_{th} + R_L) \therefore I_L = -1.75A$
 Max power $P_L = I_L^2 R_L = 10.06W$

Applying KVL to loop I:-
 $40I_1 - 40I_2 = 50 \dots (I)$
 KVL to loop II:- $-40I_1 + 110I_2 - 20I_{sc} = -10 \dots (II)$
 KVL to loop III:- $-20I_2 + 20I_{sc} = 10 \dots (III)$

$$\begin{bmatrix} 40 & -40 & 0 \\ -40 & 110 & -20 \\ 0 & -20 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_{sc} \end{bmatrix} = \begin{bmatrix} 50 \\ -10 \\ 10 \end{bmatrix}$$

$\therefore I_1 = 2.25A$
 $I_2 = 1A$
 $I_{sc} = 1.5A$

For R_{th} short 50V, 10V Batteries

$50\Omega \parallel 20\Omega$
 $\therefore R_{th} = 14.29\Omega$

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com: Home of Education

navlakhi.com

Norton's Eq. ckt. is:-
 By current division formula

$$I_L = I_{sc} \left(\frac{R_{th}}{R_{th} + R_L} \right) = 0.88A$$

$$I_{sc} = 1.5A$$

$$R_{th} = 14.29\Omega$$

$$R_L = 10\Omega$$

Using Nodal analysis:-
 At node A:-
 $V_1 = +50V$
 KCL at node B:-
 $I_1 + I_2 + I_3 = 0$

$$\therefore \frac{V_2 - V_1}{50} + \frac{V_2 - 10}{20} + \frac{V_2}{10} = 0 \quad \therefore V_2 = 8.82V$$

$$I_3 = \frac{V_2}{10} = 0.882A$$

Q33)
$$I_1 = \frac{V_{AB}}{600} = \frac{5}{600} = 0.00833A$$

$$I_2 = \frac{V_{AB}}{1200} = \frac{5}{1200} = 0.00417A$$

$$I = I_1 + I_2 = 0.0125A$$

By KVL, $600I_1 + RI = 35$
 $\therefore 600(0.00833) + R(0.0125) = 35 \quad \therefore R = 2400.16\Omega$

Q34) When S is closed
 $R \parallel \text{short} \equiv \text{short}$

$$I = \frac{220}{R}$$

www.navlakhi.com

Kunal Navlakhi

Best One Can Get

Navlakhi's

Navlakhi's




Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

Q35) $R_{AB} = 6\Omega$, $R_{BC} = 11\Omega$, $R_{AC} = 9\Omega$
 $\therefore R_A + R_B = 6\Omega$; $R_B + R_C = 11\Omega$, $R_A + R_C = 9\Omega$
 $\therefore R_A = 2\Omega$, $R_B = 4\Omega$, $R_C = 7\Omega$


Q36) 

KVL to loop I: $-60I_1 - 50I_2 - 10I_3 = 80$
 KVL to loop II: $-50I_1 + 120I_2 - 60I_3 = 0$
 KVL to loop III: $-10I_1 - 60I_2 + 120I_3 = 0$

$$\begin{bmatrix} 60 & -50 & -10 \\ -50 & 120 & -60 \\ -10 & -60 & 120 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 80 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{cases} I_1 = 3.13A \\ I_2 = 1.91A \\ I_3 = 1.22A \end{cases}$$

$I_{60\Omega} = I_2 - I_3 = 0.69A$

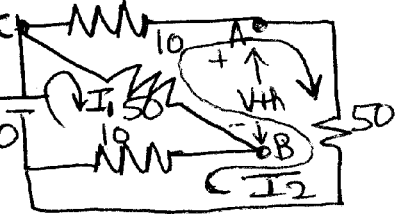


KVL to loop I: $-60I_1 - 50I_2 = 80$
 KVL to loop II: $-50I_1 + 120I_2 = 0$

$$\begin{bmatrix} 60 & -50 \\ -50 & 120 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 80 \\ 0 \end{bmatrix}$$

$$\begin{cases} I_1 = 2.04A \\ I_2 = 0.85A \end{cases}$$


By KVL to loop B-A-C-B: $-50I_1 - 60I_2 = V_{th}$ $\therefore V_{th} = 5V$

For R_{th} short 80V Battery:-

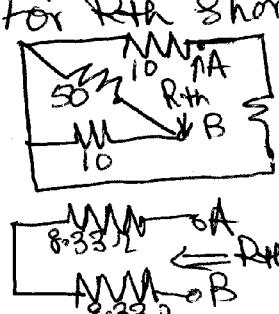

$R_{th} = 16.66\Omega$

Thevenin Eq. ckt is:-

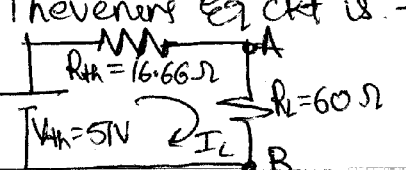

By KVL:-

$$I_L = \frac{V_{th}}{R_{th} + R_L} = 0.67A$$

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhhi.com: Home of Education

Q37) $6\Omega // 6\Omega$
 $\therefore R_{AB} = 3\Omega$

Q38) $A_1 = \pi r_1^2 = \frac{\pi d_1^2}{4} = \frac{\pi d^2}{4}$, $A_2 = \pi r_2^2 = \frac{\pi d_2^2}{4} = \frac{\pi (2d)^2}{4} = \pi d^2$
 $R_1 = \frac{\rho l}{A_1}$, $R_2 = \frac{\rho (4l)}{A_2}$ $\therefore \frac{R_2}{R_1} = \frac{\rho (4l)}{A_2} \times \frac{A_1}{\rho l}$
 $\therefore \frac{R_2}{R} = \frac{4}{\pi d^2} \times \frac{\pi d^2}{4} \therefore \boxed{R_2 = R}$

Q39) $R_1 = 10$, $R_2 = 40$, $R_3 = 20$
 Converting star to delta
 $R_2 = R_1 + R_2 + \frac{R_1 R_2}{R_3} = 77.5\Omega$
 $R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} = 155\Omega$
 $R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2} = 34.44\Omega$

 $R_{xy} = 26.57\Omega // 36.64\Omega = \boxed{15\Omega}$

Q40) Considering 25V Battery & shorting 12V Battery

 KVL to loop I: $13I_1 - 7I_2 - 4I_3 = 25$
 KVL to loop II: $-7I_1 + 12I_2 - 2I_3 = 0$
 KVL to loop III: $-4I_1 - 2I_2 + 16I_3 = 0$

$$\begin{bmatrix} 13 & -7 & -4 \\ -7 & 12 & -2 \\ -4 & -2 & 16 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 25 \\ 0 \\ 0 \end{bmatrix}$$

 $\therefore I_1 = 3.47A$
 $I_2 = 2.21A$
 $I_3 = 1.14A$

navlakhhi.com

www.navlakhhi.com

Kunal Navlakhhi

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Considering 12V Battery & shorting 25V Battery

KVL to loop I: $13I_1'' - 7I_2'' - 4I_3'' = 0$

12 KVL to loop II: $-7I_1'' + 12I_2'' - 2I_3'' = 12$

KVL to loop III: $-4I_1'' - 2I_2'' + 16I_3'' = 0$

$$\begin{bmatrix} 13 & -7 & -4 \\ -7 & 12 & -2 \\ -4 & -2 & 16 \end{bmatrix} \begin{bmatrix} I_1'' \\ I_2'' \\ I_3'' \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \end{bmatrix}$$

$I_1'' = 1.06A$
 $I_2'' = 1.7A$
 $I_3'' = 0.48A$

By superposition theorem:-
 $I_1 = I_1'' + I_1''' = 4.53A$, $I_2 = I_2'' + I_2''' = 3.91A$, $I_3 = I_3'' + I_3''' = 1.62A$
 ∴ Current through 10Ω is $I_3 = 1.62A$

(ii) By Thevenin's theorem:-

KVL to loop I: $13I_1 - 7I_2 = 25$

KVL to loop II: $-7I_1 + 12I_2 = 12$

KVL to loop III: $-4I_1 - 2I_2 = -V_{th}$ ∴ $V_{th} = 20.54V$

For R_{th} , short 25V, 12V Batteries:-

Converting delta to star:-
 $R_1 = \frac{R_2 R_3}{R_1 + R_2 + R_3} = 0.615\Omega$
 $R_2 = \frac{R_1 R_3}{R_1 + R_2 + R_3} = 1.077\Omega$
 $R_3 = \frac{R_1 R_2}{R_1 + R_2 + R_3} = 2.154\Omega$

Thevenin's eq. ckt. is:-

By KVL,
 $I_L = \frac{V_{th}}{R_{th} + R_L} = 1.62A$

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

Q41) 8A

By source-transformation:-

$I_1 = 8A$, KVL to loop II: $-8I_1 + 1I_2 = 2 \therefore I_2 = 6A$
 KVL to loop III: $-3I_2 = V_{th} - 2 \therefore V_{th} = -16V$
 For R_{th} , short 4V, 2V batteries & open 8A current source

$8\Omega \parallel 3\Omega$
 $\therefore R_{th} = 2.18\Omega$

For max. power $R_L = R_{th} = 2.18\Omega$

Thevenin's Eq. ckt is:-

$I_L = \frac{V_{th}}{R_{th} + R_L} = 3.67A$
 Max. power = $I_L^2 R_L = 29.36W$

Eq. of supermesh for loop I & II:-

$I_1 - I_2 = 5 \dots (I)$
 KVL to loop I & II:-
 $9I_1 + 8I_2 - 7I_3 - 5I_4 = 4 \dots (II)$

Eq. of supermesh for loop III & IV:-

$I_4 - I_3 = 15 \therefore I_4 = 15 + I_3 \dots (III)$
 KVL to loop III & IV:-
 $-7I_1 - 5I_2 + 16I_3 + 5I_4 = 0 \dots (IV)$

Subs. eqn. (III) in (II) & (IV):

$9I_1 + 8I_2 - 12I_3 = 79 \dots (V)$
 $-7I_1 - 5I_2 + 21I_3 = -75 \dots (VI)$

$$\begin{bmatrix} 1 & -1 & 0 \\ 9 & 8 & -12 \\ -7 & -5 & 21 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 79 \\ -75 \end{bmatrix}$$

$I_1 = 6.0A$
 $I_2 = 1.1A$
 $I_3 = -1.28A$

From eq. (III)
 $I_4 = 13.72A$

navlakhhi.com

navlakhhi.com: Home of Education

www.navlakhhi.com

Kunal Navlakhhi

Best One Can Get

Navlakhhi's

Navlakhhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 23886023 / 23868356

$V_{3\Omega} = 3 \times I_2 = 3.3V$

By Superposition theorem:-
 Considering 4V battery & opening 5A, 15A current source

By KVL to loop I: $-17i_1 - 12i_2 = 4$ --- (I)
 By KVL to loop II: $-12i_1 + 21i_2 = 0$ --- (II)

$$\begin{bmatrix} 17 & -12 \\ -12 & 21 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix} \therefore \begin{matrix} i_1 = 0.394A \\ i_2 = 0.225A \end{matrix}$$

$I_1' = I_2' = i_1 = 0.394A$ & $I_3' = I_4' = i_2 = 0.225A$

Consider 5A current source, short 4V & open 15A

Eqn. of supermesh of loop I & II is:-
 $I_1'' - I_2'' = 5$ --- (I)
 KVL to loop I & II:-
 $9I_1'' + 8I_2'' - 12i'' = 0$ --- (II)

KVL to loop III:-
 $-7I_1'' - 5I_2'' + 2i'' = 0$ --- (III)

$$\begin{bmatrix} 1 & -1 & 0 \\ 9 & 8 & -12 \\ -7 & -5 & 2 \end{bmatrix} \begin{bmatrix} I_1'' \\ I_2'' \\ i'' \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \therefore \begin{matrix} I_1'' = 2.53A \\ I_2'' = -2.465A \\ i'' = 0.258A \end{matrix}$$

$I_3'' = I_4'' = i'' = 0.258A$

Considering 15A current source, short 4V & open 5A

KVL to loop I: $-17i''' - 7I_3''' - 5I_4''' = 0$ --- (I)
 Eqn. of supermesh:- $I_4''' - I_3''' = 15$ --- (II)
 KVL to loop III & loop IV:-
 $-12i''' + 16I_3''' + 5I_4''' = 0$ --- (III)

$$\begin{bmatrix} 17 & -7 & -5 \\ 0 & -1 & 1 \\ -12 & 16 & 5 \end{bmatrix} \begin{bmatrix} i''' \\ I_3''' \\ I_4''' \end{bmatrix} = \begin{bmatrix} 0 \\ 15 \\ 0 \end{bmatrix} \therefore \begin{matrix} i''' = 3.169A \\ I_3''' = -1.761A \\ I_4''' = 13.24A \end{matrix}$$

$I_1''' = I_2''' = i''' = 3.169A$

navlakhhi.com

navlakhhi.com: Home of Education

Best One Can Get

Navlakhi's

Navlakhi's



Tel: 23868356/23886023/9820246760 **POWER**

Tel: 9820246760/9769479368

Tel: 9820246760 / 23886023 / 23868356

By Superposition theorem:-
 $I_1 = I_1' + I_1'' + I_1''' = 6.1A$, $I_2 = I_2' + I_2'' + I_2''' = 1.1A$
 $I_3 = I_3' + I_3'' + I_3''' = -1.28A$, $I_4 = I_4' + I_4'' + I_4''' = 13.72A$
 $V_{3\Omega} = 3 \times I_2 = 3.3V$

Q43) Converting outer delta to star:-
 $R_1 = \frac{R_2 \cdot R_3}{R_2 + R_3 + R_1} = 1.67\Omega$
 $R_2 = \frac{R_1 \cdot R_3}{R_2 + R_3 + R_1} = 2.14\Omega$
 $R_3 = \frac{R_1 \cdot R_2}{R_2 + R_3 + R_1} = 3\Omega$

$2.67\Omega // 5.14\Omega$
 $4.76\Omega // 2\Omega$
 $\therefore R_{AB} = 1.41\Omega$

navlakhi.com

navlakhi.com: Home of Education

Best One Can Get

Navlakhhi's

Q44)a) Since dc arc and resistor are connected in series, current I remains the same.

Voltage across resistor is $V_R = I \cdot R$.

For DC component $V_{\text{supply}} = V_{\text{arc}} + V_R$

$$\therefore 100 = \left(44 + \frac{30}{I}\right) + IR \quad \text{--- (I)}$$

Also, $V_{\text{arc}} = V_R$ (given)

$$\therefore 44 + \frac{30}{I} = I \cdot R \quad \text{--- (II)}$$

Subs. (II) in (I)

$$\therefore 100 = IR + IR$$

$$\therefore 2IR = 100$$

$$\therefore IR = 50 \quad \text{--- (III)}$$

Subs. (III) in (II)

$$\therefore 44 + \frac{30}{I} = 50$$

$$\therefore \frac{30}{I} = 50 - 44$$

$$\therefore \frac{30}{I} = 6$$

$$\therefore I = \frac{30}{6} = 5A$$

Subs. in (III)

$$\therefore 5R = 50 \quad \boxed{\therefore R = 10 \Omega}$$

b) $L_{Al} = 10m = 10000cm$, $d_{Al} = 2mm = 0.2cm$, $L_{Cu} = 6m = 6000cm$

$I = 2A$, $I_{Al} = 1.25A$, $\rho_{Cu} = 1.6 \times 10^{-6} \Omega cm$, $\rho_{Al} = 2.6 \times 10^{-6} \Omega cm$

$$A_{Al} = \pi r_{Al}^2 = \frac{\pi}{4} \times (0.1)^2 = 0.0314 cm^2$$

$$R_{Al} = \frac{\rho_{Al} L_{Al}}{A_{Al}} = 0.083 \Omega$$

$$R_{Cu} = \frac{\rho_{Cu} L_{Cu}}{A_{Cu}} = \frac{0.0096}{A_{Cu}} \Omega$$

Navlakhhi's

For parallel connection,

$$I = I_{Ae} + I_{cu}$$

$$\therefore I_{cu} = 2 - 1.25 = 0.75A$$

Since $V_{Ae} = V_{cu}$ (for parallel connection)

$$I_{Ae} \cdot R_{Ae} = I_{cu} \cdot R_{cu}$$

$$\therefore 1.25 \times 0.083 = 0.75 \times \frac{0.0096}{A_{cu}}$$

$$\therefore A_{cu} = 0.0694 \text{ cm}^2$$

$$\therefore A_{cu} = \pi r_{cu}^2$$


$$\therefore 0.0694 = 3.142 \times r_{cu}^2$$

$$\therefore r_{cu} = 0.149 \text{ cm}$$

$$d_{cu} = 0.297 \text{ cm} = 2.97 \text{ mm}$$



By source conversion,

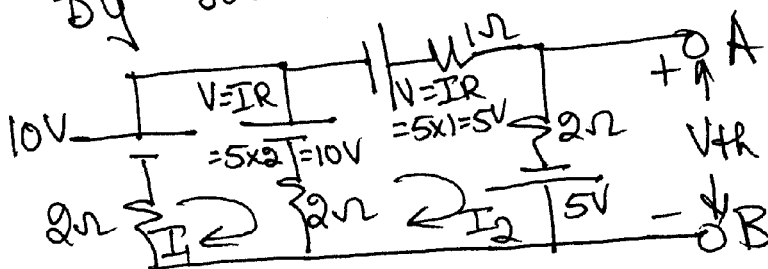

By KVL to loop I,

$$4I_1 - 2I_2 = 0 \quad \text{--- (I)}$$

By KVL to loop II,

$$-2I_1 + 5I_2 = 20 \quad \text{--- (II)}$$

$$\therefore I_1 = 2.5A$$

$$I_2 = 5A$$

Best One Can Get


Navlakhhi's

By KVL to loop III,


$$-2I_2 = -5 - V_{th}$$

$$\therefore V_{th} = 5V$$

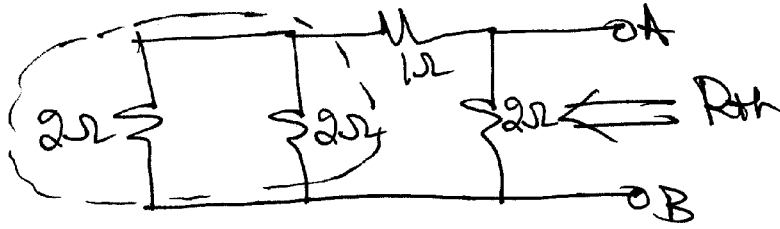For R_{th} , open 5A current sources and short 10V and 5V batteries,



$$2\Omega // 2\Omega = 1\Omega$$

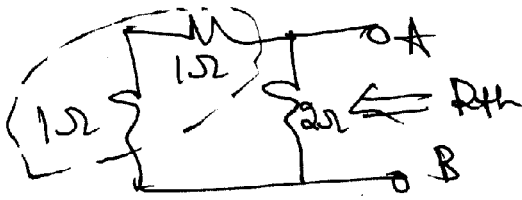


$$1\Omega + 1\Omega = 2\Omega$$



$$2\Omega // 2\Omega = 1\Omega$$

$$\therefore R_{th} = 1\Omega$$

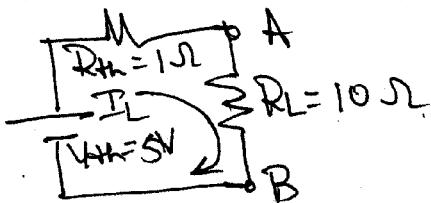\therefore Thevenin's equivalent circuit is




By KVL,

$$11I_L = 5$$

$$\therefore I_L = 0.455A$$

For Superposition theorem,

Consider circuit,

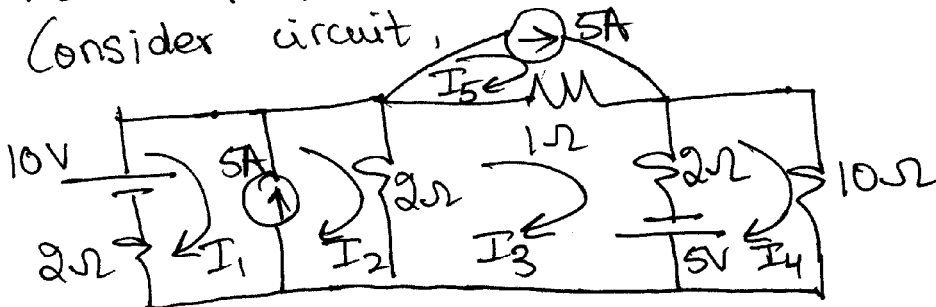


Best One Can Get

Tel:9820246760/9769479368

navlakhhi.com:Home of Education

Navlalkhi's

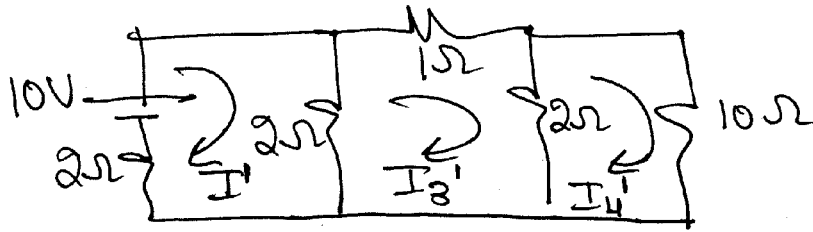Consider 10V Battery and open 5A current source and short 5V Battery



$$I_5' = 0$$

By KVL to loop I,

$$4I' - 2I_3' + 0I_4' = 10 \quad \text{--- (I)}$$

By KVL to loop II,

$$-2I' + 5I_3' - 2I_4' = 0 \quad \text{--- (II)}$$

By KVL to loop III,

$$0I' - 2I_3' + 12I_4' = 0 \quad \text{--- (III)}$$


$$\therefore I' = 3.18 \text{ A}$$

$$I_3' = 1.36 \text{ A}$$

$$I_4' = 0.23 \text{ A}$$

$$I_1' = I_3' = I' = 3.18 \text{ A}$$

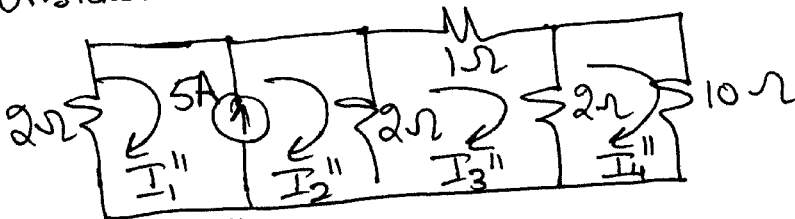Consider 5A current source, short 10V, 5V & open 5A



$$I_5'' = 0$$

Equation of supermesh for loop I & II is

$$I_3'' - I_1'' = 5$$

$$\therefore I_1'' = I_3'' - 5 \quad \text{--- (I)}$$

Navlalkhi's

By KVL to loop I & II

$$2I_1'' + 2I_2'' - 2I_3'' = 0$$

Subs. from eq (I)

$$\therefore 2I_2'' - 10 + 2I_2'' - 2I_3'' = 0$$

$$\therefore 4I_2'' - 2I_3'' + 0I_4'' = 10 \quad \text{--- (II)}$$

By KVL to loop III,

$$-2I_2'' + 5I_3'' - 2I_4'' = 0 \quad \text{--- (III)}$$

By KVL to loop IV,

$$0I_2'' - 2I_3'' + 12I_4'' = 0$$


$$\therefore I_2'' = 3.18A$$

$$I_3'' = 1.36A$$

$$I_4'' = 0.23A$$

Subs. in eq (I) $\therefore I_1'' = -1.82A$

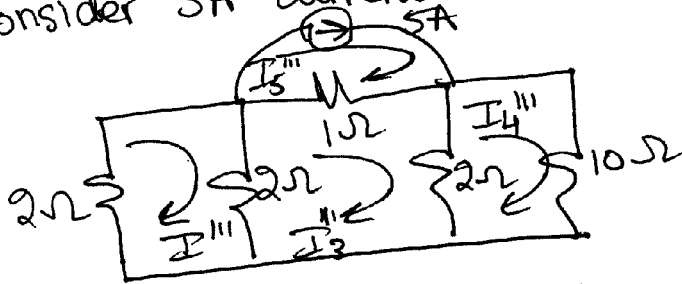Consider 5A current source, short 10V, 5V & open 5A



$$I_5''' = 5A \quad \text{--- (I)}$$

By KVL to loop I,

$$4I_1''' - 2I_3''' + 0I_4''' = 0 \quad \text{--- (II)}$$

By KVL to loop II,

$$-2I_1''' + 5I_3''' - 2I_4''' - I_5''' = 0$$

$$\therefore -2I_1''' + 5I_3''' - 2I_4''' = 5 \quad \text{--- (III)} \quad \text{Subs. from (I)}$$

By KVL to loop III,

$$0I_1''' - 2I_3''' + 12I_4''' = 0 \quad \text{--- (IV)}$$

Best One Can Get

Navlalkhi's


$$I''' = 0.68A$$

$$I_3''' = 1.36A$$

$$I_4''' = 0.23A$$

$$\therefore I_1''' = I_2''' = I''' = 0.68A$$

Consider 5V, short 10V & open 5A

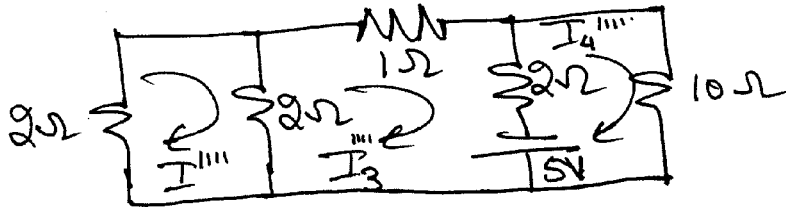

$$I_5''' = 0$$

By KVL to loop I,

$$4I''' - 2I_3''' + 0I_4''' = 0 \quad \text{--- (I)}$$

By KVL to loop II,

$$-2I''' + 5I_3''' - 2I_4''' = 5 \quad \text{--- (II)}$$

By KVL to loop III,

$$0I''' - 2I_3''' + 12I_4''' = -5 \quad \text{--- (III)}$$

$$\therefore I''' = 0.57A$$

$$I_3''' = 1.14A$$

$$I_4''' = -0.23A$$


$$I_1''' = I_2''' = I''' = 0.57A$$

By superposition theorem,




$$I_4 = I_4' + I_4'' + I_4''' + I_4'''' \\ = 0.46A$$

Navlakhhi's

Q46)

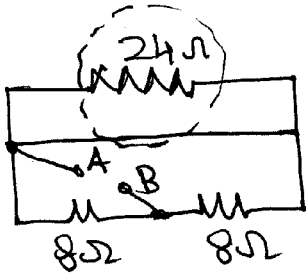

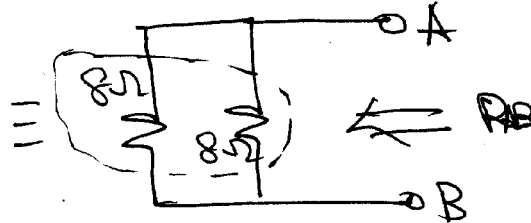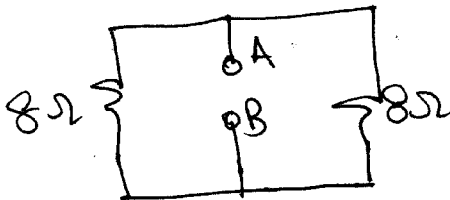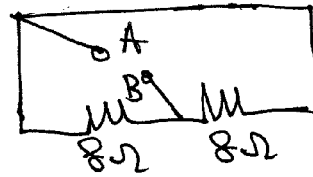
$24\Omega // \text{short} \equiv \text{short}$



$8\Omega // 8\Omega \equiv 4\Omega$

$\therefore R_{AB} = 4\Omega$

Q47)

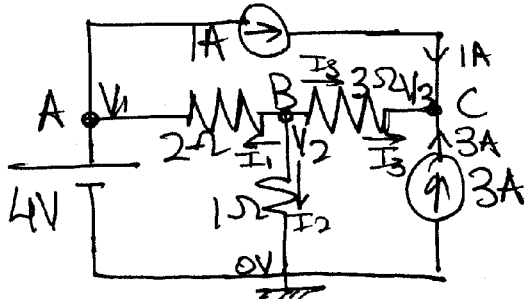

Since node A is connected to a battery and directly to ground without a series resistor

$\therefore V_1 = +4V \quad \text{--- (I)}$

KCL at node B,

$\therefore I_1 + I_2 + I_3 = 0$

$\therefore \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{1} + \frac{V_2 - V_3}{3} = 0$

$\therefore V_1(-\frac{1}{2}) + V_2(\frac{1}{2} + 1 + \frac{1}{3}) + V_3(-\frac{1}{3}) = 0 \quad \text{--- (II)}$

KCL at node C,

$I_3 + 1 + 3 = 0$

$\therefore \frac{V_2 - V_3}{3} + 4 = 0$

$\therefore V_1(0) + V_2(\frac{1}{3}) + V_3(-\frac{1}{3}) = -4 \quad \text{--- (III)}$


Best One Can Get

Navlalkhi's

$$\begin{aligned} \therefore V_1 &= 4V \\ V_2 &= 4V \\ V_3 &= 16V \end{aligned}$$

$$I_2 = \frac{V_2 - 0}{1} = 4A$$

For Thevenin's theorem,

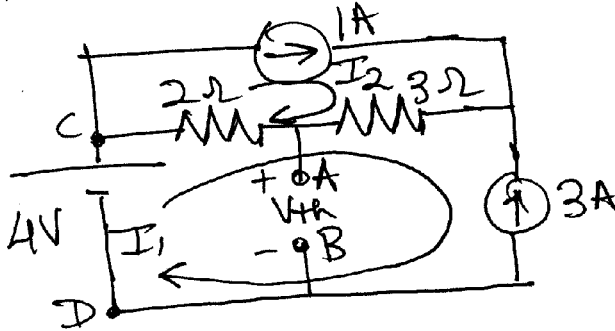

$$I_1 = -3A$$


$$I_2 = 1A$$

By KVL to loop D-C-A-B-D:-

$$2I_1 - 2I_2 = 4 - V_{th}$$


$$\therefore V_{th} = 12V$$

For R_{th} , short 4V & open 3A & 1A

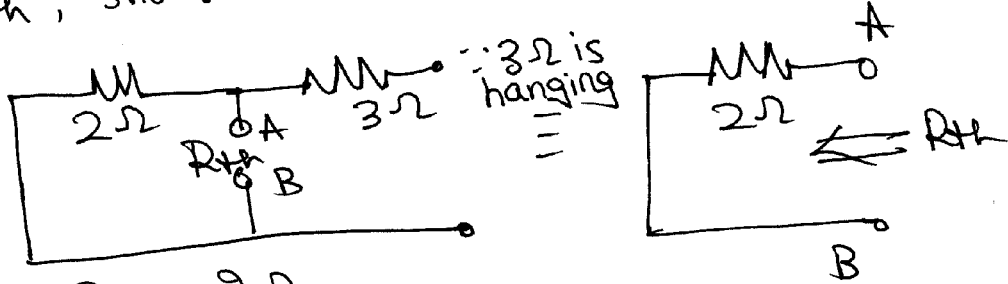

$$\therefore R_{th} = 2\Omega$$

Thevenin's eq. ckt. is

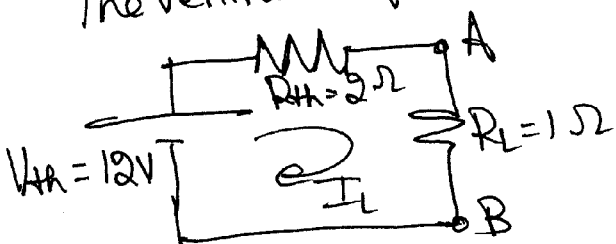


By KVL

$$3I_L = 12$$

$$\therefore I_L = 4A$$

Best One Can Get

Navlalkhi's

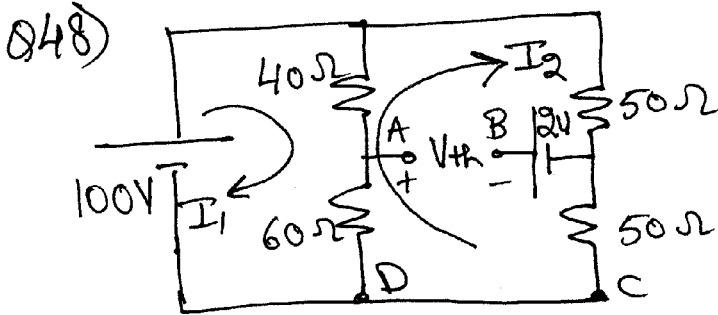

By KVL to loop I,
 $100I_1 - 100I_2 = 100 \quad \text{--- (I)}$


By KVL to loop II,
 $-100I_1 + 200I_2 = 0 \quad \text{--- (II)}$

$\therefore I_1 = 2A$




$I_2 = 1A$

By KVL to loop A-B-C-D-A,
 $-60I_1 + 110I_2 = -V_{th} - 2$
 $\therefore V_{th} = -2V$

For R_{th} , short 100V & 2V

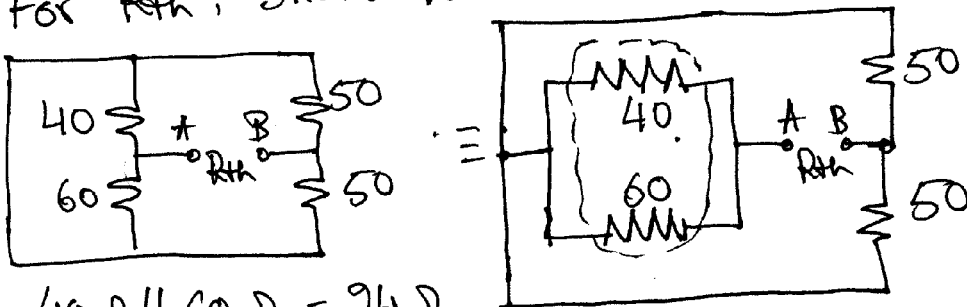

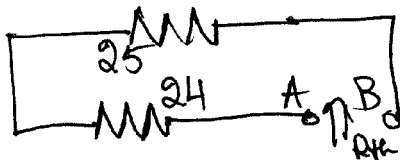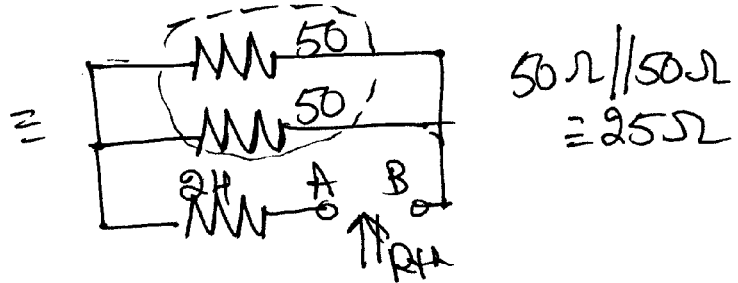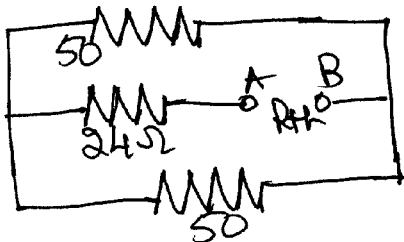$40\Omega \parallel 60\Omega \equiv 24\Omega$




$R_{th} = 25 + 24 = 49\Omega$

Best One Can Get

Navlakhhi's

Thevenin's Eq.ckt. is

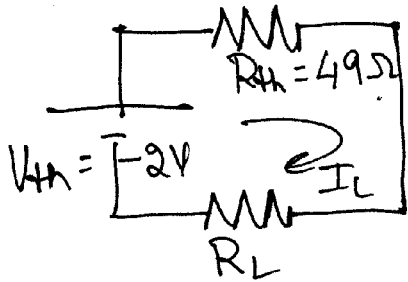


For max. power $R_L = R_{th} = 49\Omega$

$$I_L = 0.02 \text{ A}$$

$$P_L = I_L^2 \times R_L = 0.02 \text{ W}$$

Q49)

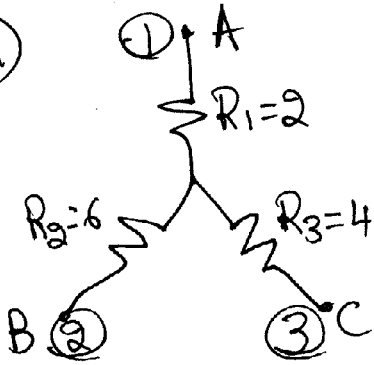

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} = 11\Omega$$


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} = \cancel{7.33} 22\Omega$$

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2} = 7.33\Omega$$

Q50)

$$\begin{aligned} \therefore E &= V + I_r \\ \therefore 12 &= 100 \times 0.10 + 100 \times r \\ \therefore 12 &= 10 + 100r \\ \therefore r &= 0.02\Omega \end{aligned}$$

Q51)

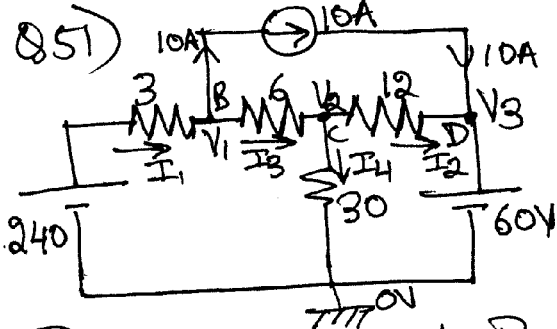

Since node D is connected to battery and ground without any resistor in series

$$\therefore V_3 = +60V$$

By KCL at node B,

$$I_1 = I_3 + 10$$

$$\therefore \frac{240 - V_1}{3} = \frac{V_1 - V_2}{6} + 10$$

$$\therefore V_1 \left(-\frac{1}{3} - \frac{1}{6} \right) + V_2 \left(\frac{1}{6} \right) = -\frac{240}{3} + 10 \quad \text{--- (I)}$$

By KCL at node C,

$$I_3 = I_4 + I_2$$

Navlakhhi's

$$\therefore \frac{V_1 - V_2}{6} = \frac{V_2 - 0}{30} + \frac{V_2 - V_3}{12}$$



$$\therefore V_1 \left(\frac{1}{6} \right) + V_2 \left(-\frac{1}{6} - \frac{1}{30} - \frac{1}{12} \right) = -\frac{60}{12} \quad \text{--- (IV)}$$

$$\therefore V_1 = 181.46 \text{ V}$$

$$V_2 = 124.39 \text{ V}$$

$$\therefore I_2 = \frac{V_2 - V_3}{12} = 5.37 \text{ A}$$

For Thevenin's theorem,

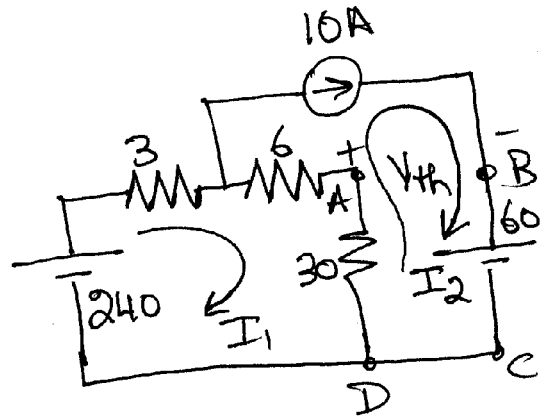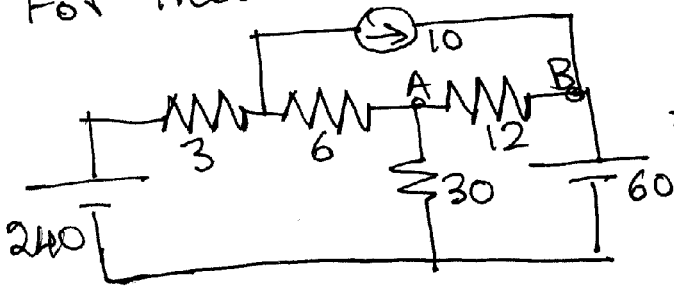

$$I_2 = 10 \text{ A}$$

By KVL to loop I,

$$39I_1 - 36I_2 = 240$$



$$\therefore I_1 = 15.385 \text{ A}$$

By KVL to loop A-B-C-D-A


$$\therefore -30I_1 + 30I_2 = -V_{th} - 60$$

$$\therefore V_{th} = 101.55 \text{ V}$$

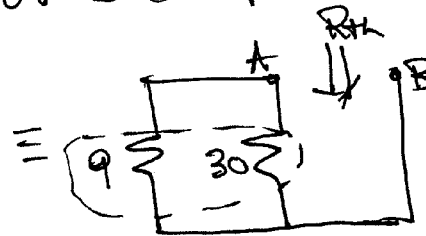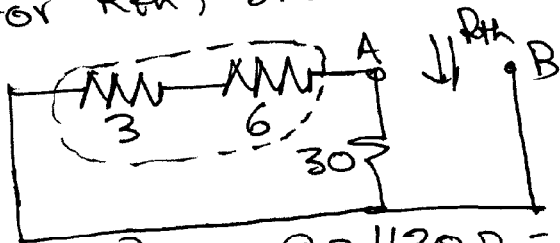For R_{th} , short 240V, 60V and open 10A


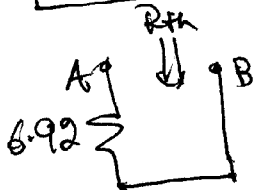
$$9\Omega \parallel 30\Omega = 6.92\Omega$$




$$\therefore R_{th} = 6.92\Omega$$


Best One Can Get

Navlakhhi's

∴ Thevenin's Eq. ckt. is

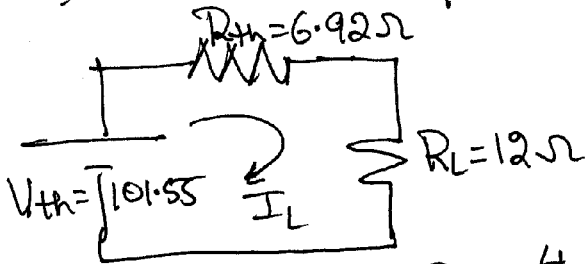


By KVL,
 $I_L = 5.37A$

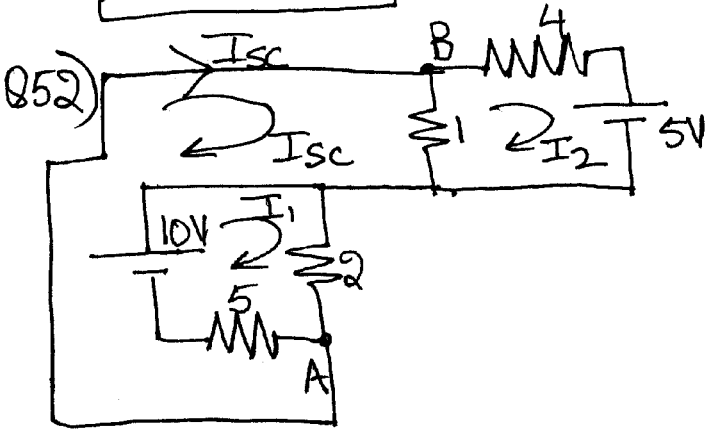


By KVL to loop I,
 $7I_1 + 0I_2 - 5I_{sc} = 10$
 By KVL to loop II,
 $0I_1 + 5I_2 - I_{sc} = -5$
 By KVL to loop III,
 $-5I_1 - I_2 + 6I_{sc} = -10$

∴ $I_1 = 0.19A$
 $I_2 = -1.35A$
 $I_{sc} = -1.73A$


For R_{th} , short 10V & 5V

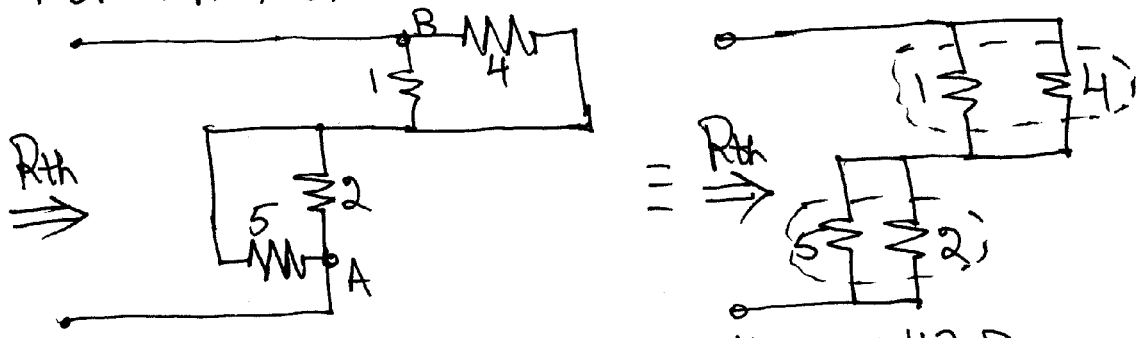

$1\Omega || 4\Omega = 0.8\Omega$, $5\Omega || 2\Omega = 1.43\Omega$

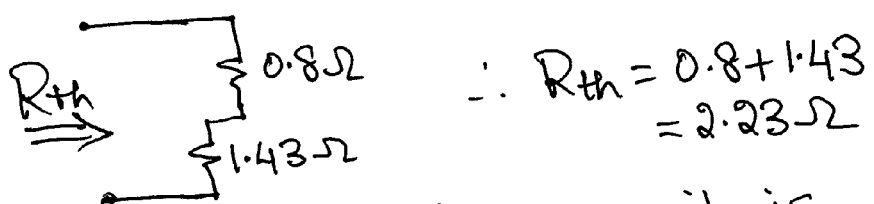

∴ $R_{th} = 0.8 + 1.43 = 2.23\Omega$

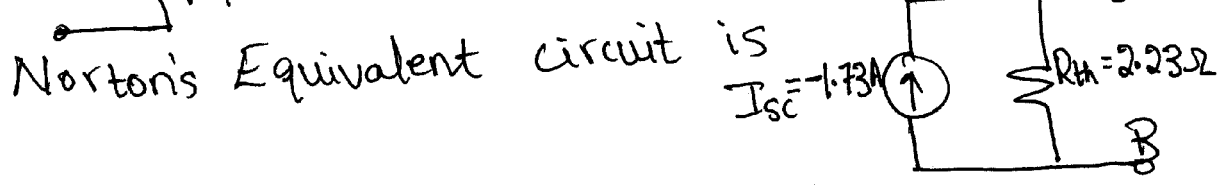


Tel:9820246760/9769479368

navlakhhi.com:Home of Education

Best One Can Get

Navlakhhi's

Q54) At node A,
 $V_1 = +5V$

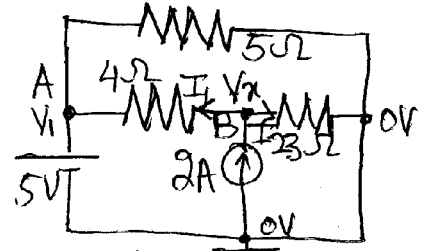

[NOTE: If a node is connected to a battery and directly to ground then nodal voltage = Battery voltage with sign as the nearest polarity to the node. KCL cannot be applied to that node.]


KCL at node B:-

$$\therefore I_1 + I_2 = 2$$

$$\therefore \frac{V_x - V_1}{4} + \frac{V_x - 0}{3} = 2$$

$$\therefore V_x = 5.57V$$

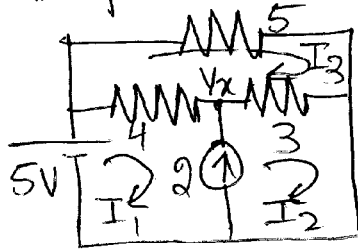NOTE: For Verification, use mesh analysis



Eq. of supermesh is

$$I_2 - I_1 = 2$$

KVL to loop I & II:-

$$4I_1 + 3I_2 - 7I_3 = 5$$

KVL to loop III:-

$$-4I_1 - 3I_2 + 12I_3 = 0$$

$$\therefore I_1 = 0.86A$$

$$I_2 = 2.86A$$

$$I_3 = 1A$$

$$I_2 - I_3 = \frac{V_x - 0}{3} \quad \therefore V_x = 5.58V$$

Q55) $R_1 = 25\Omega$

$$R_2 = 25 + \frac{10}{100} \times 25 = 27.5\Omega$$

$$T_1 = 15^\circ C, \quad T_2 = 50^\circ C$$

$$\therefore R_t = R_0 (1 + \alpha_0 t)$$

$$\therefore R_1 = R_0 (1 + \alpha_0 T_1)$$

$$\therefore 25 = R_0 (1 + 15\alpha_0) \quad \text{--- (I)}$$

$$R_2 = R_0 (1 + \alpha_0 T_2)$$

$$\therefore 27.5 = R_0 (1 + 50\alpha_0) \quad \text{--- (II)}$$

Best One Can Get

Navlakhhi's

Dividing eqn. (I) & (II)

$$\therefore \frac{25}{27.5} = \frac{1+15\alpha_0}{1+50\alpha_0}$$

$$\therefore \alpha_0 = 2.99 \times 10^{-3} / ^\circ\text{C}$$

Subs. in eq. (I)

$$\therefore R_0 = 23.93 \Omega$$

Q56) For V_{th} :-

KVL to loop I :-

$$25I_1 - 10I_2 - 10I_3 = 10 \quad \text{---(I)}$$

KVL to loop II :-

$$-10I_1 + 30I_2 - 10I_3 = 0 \quad \text{---(II)}$$

In loop III :-

$$I_3 = 10\text{A}$$

$$\therefore I_1 = 6.62\text{A}$$

$$I_2 = 5.54\text{A}$$

KVL to loop A-B-C-D-A :-

$$-10I_1 - 10I_2 + 20I_3 = -V_{th}$$

$$\therefore V_{th} = -78.4\text{V}$$




For R_{th} , short 10V Battery and open 10A current source :-

Converting Delta to Star :-

$$R_1 = \frac{R_{12} \times R_{13}}{R_{12} + R_{23} + R_{13}} = \frac{10 \times 10}{10 + 10 + 10} = 3.33 \Omega$$

$$R_2 = \frac{R_{12} \times R_{23}}{R_{12} + R_{23} + R_{13}} = \frac{10 \times 10}{10 + 10 + 10} = 3.33 \Omega$$
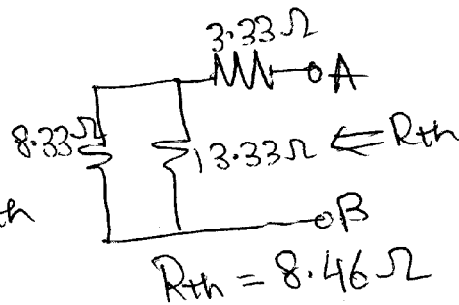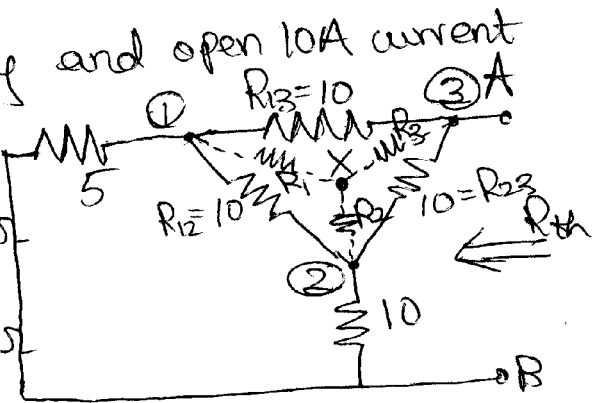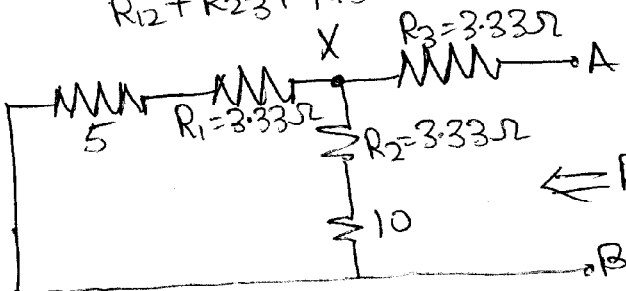
$$R_3 = \frac{R_{23} \times R_{13}}{R_{12} + R_{23} + R_{13}} = \frac{10 \times 10}{10 + 10 + 10} = 3.33 \Omega$$




Best One Can Get

Navlakhhi's

For Maximum Power,

$$R_L = R_{th} = 8.46 \Omega$$

Thevenin's Equivalent circuit is

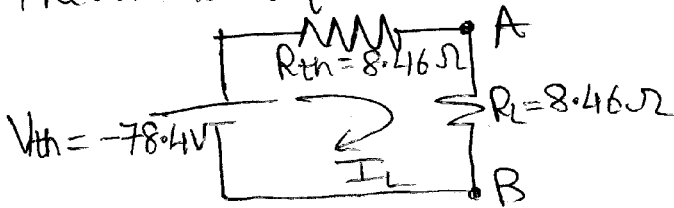


By KVL,

$$I_L = -4.63A$$

$$\text{Max Power} = 181.64W$$

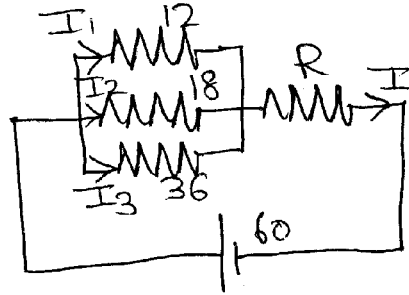Q57) $P_{12\Omega} = 36W$
 $P_{12\Omega} = I_1^2 \times 12$
 $\therefore I_1 = 1.73A$
 $V_1 = I_1 \times 12 = 20.79V$
 $V_1 = V_2 = V_3 = 20.79V$
 $I_2 = \frac{V_2}{18} = 1.16A$
 $I_3 = \frac{V_3}{36} = 0.58A$



$$I = I_1 + I_2 + I_3 = 3.47A$$

$$V = V_1 + V_R \quad \therefore V_R = 60 - 20.79 = 39.21V$$

$$V_R = I R \quad \therefore R = 11.3\Omega$$

Q58) For I_{sc} , by source conversion

By KVL to loop I:-

$$25I_1 - 10I_{sc} = 20 \quad \text{--- (I)}$$



By KVL to loop II:-

$$-10I_1 + 20I_{sc} = 24 \quad \text{--- (II)}$$

$$\therefore I_1 = 1.6A$$


$$I_{sc} = 2A$$

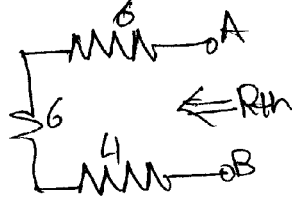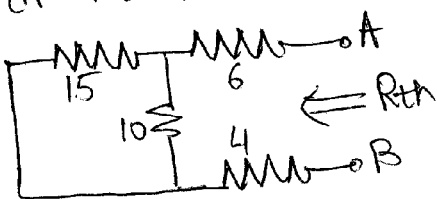For R_{th} , short 20V and open 4A current source



$$\therefore R_{th} = 16\Omega$$

Norton's Equivalent circuit is:-

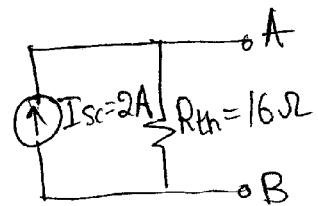

Best One Can Get

Navlakhhi's

Q59) By KVL to node A:-

$$I_1 + I_2 + I_3 + 2 = 0$$

$$\frac{V_1 - 10 - 0}{100} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{20} + 2 = 0$$

$$V_1 \left(\frac{1}{100} + \frac{1}{20} + \frac{1}{20} \right) + V_2 \left(\frac{-1}{20} \right) = \frac{10}{100} - 2 \quad \text{--- (I)}$$

By KCL at node B:-

$$I_3 = I_4 + I_5$$

$$\therefore \frac{V_1 - V_2}{20} = \frac{V_2 - 0}{20} + \frac{V_2 - 100 - 0}{30 + 10}$$

$$\therefore -V_1 \left(\frac{1}{20} \right) + V_2 \left(\frac{-1}{20} - \frac{1}{20} - \frac{1}{40} \right) = \frac{-100}{40} \quad \text{--- (II)}$$

$$V_1 = -10V$$

$$V_2 = 16V$$

$$I_1 = \frac{V_1 - 10}{100} = -0.2A$$

NOTE: For Verification, we source convert and use mesh analysis

By KVL to loop I:-

$$100i_1 - 20i_2 + 0i_3 = 50 \quad \text{--- (I)}$$

By KVL to loop II:-

$$-20i_1 + 60i_2 - 20i_3 = -40 \quad \text{--- (II)}$$

By KVL to loop III:-



$$0i_1 - 20i_2 + 60i_3 = -100 \quad \text{--- (III)}$$

$$\therefore i_1 = 0.2$$

$$i_2 = -1.3$$

$$i_3 = -2.1$$

$$\therefore I_1 = -i_1 = -0.2A$$

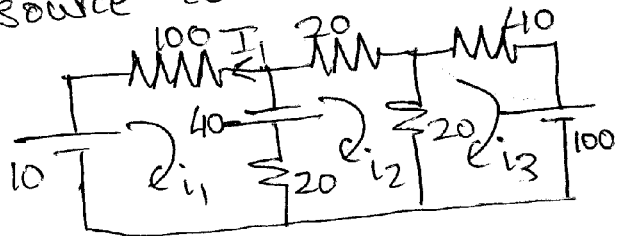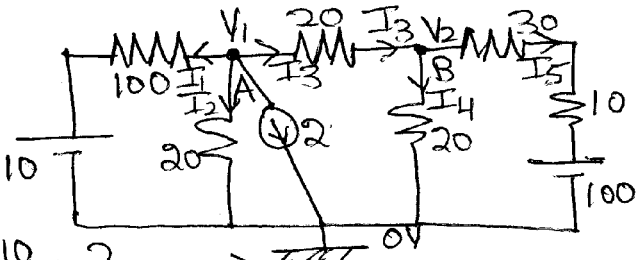

Best One Can Get

Navlakhhi's

Q60) By KCL at middle node,

$$3 + I_x = 5 + I_y + I_z \quad \text{--- (I)}$$

i) $I_y = 2, I_z = 0 \therefore I_x = 4A$

ii) $I_x = 2, I_z = 2I_y \therefore I_y = 0A$

iii) $I_x = I_y = I_z \therefore I_z = -2A$


Q61) $R_{parallel} = \frac{7.5R}{7.5+R}$

Total $R = 10 + \frac{7.5R}{7.5+R}$


By KVL,

$$20 = 1.5 \left(10 + \frac{7.5R}{7.5+R} \right)$$

$$\therefore R = 6\Omega$$

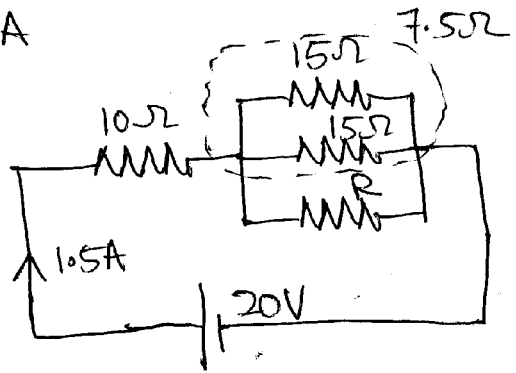

Q62) For I_{sc} , short 25Ω resistance

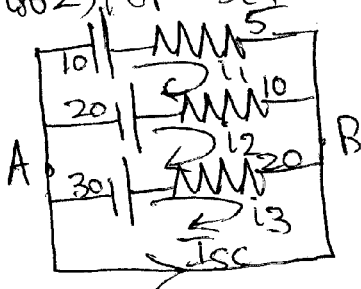

By KVL to loop I:-

$$15i_1 - 10i_2 + 0i_3 = -10$$

By KVL to loop II:-

$$-10i_1 + 30i_2 - 20i_3 = -10$$


By KVL to loop III:-

$$0i_1 - 20i_2 + 20i_3 = 30$$

$$\therefore i_1 = 2A, i_2 = 4A, i_3 = 5.5A$$

$$I_{sc} = -i_3 = -5.5A$$

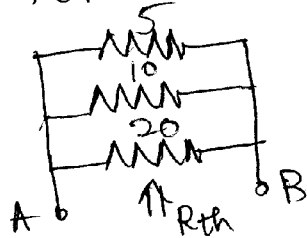
For R_{th} , short 10V, 20V, 30V Batteries



$$\therefore R_{th} = 2.86\Omega$$

Norton's Eq. ckt. is

$$\therefore I_L = 0.57A$$

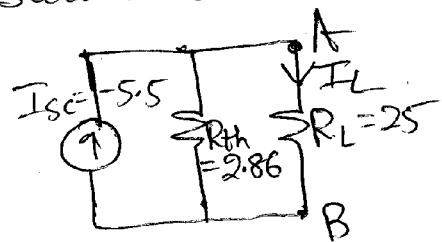

NOTE: For Verification use mesh analysis

$$15i_1 - 10i_2 + 0i_3 = -10$$

$$-10i_1 + 30i_2 - 20i_3 = -10$$

$$0i_1 - 20i_2 + 45i_3 = 30$$

$$\therefore I_L = -i_3 = -0.56A$$

Navlakhi's

Q63) By KVL to loop I:-

$$3.5i_1 - 2i_2 - 1.5i_3 = -6$$


By KVL to loop II:-

$$-2i_1 + 8i_2 - 6i_3 = 0$$

By KVL to loop III:-

$$-1.5i_1 - 6i_2 + 10.5i_3 = 0$$

$$\therefore i_1 = -4A$$

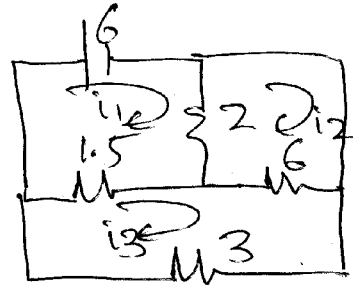

Q64) By KVL to loop I:-

$$7I_1 = 10 \therefore I_1 = 1.43A$$


By KVL to loop II:-

$$5I_2 = -5 \therefore I_2 = -1A$$

By KVL to loop A-B-C-D-A:-

$$-I_2 + 2I_1 = -V_{th}$$

$$\therefore V_{th} = -3.86V$$

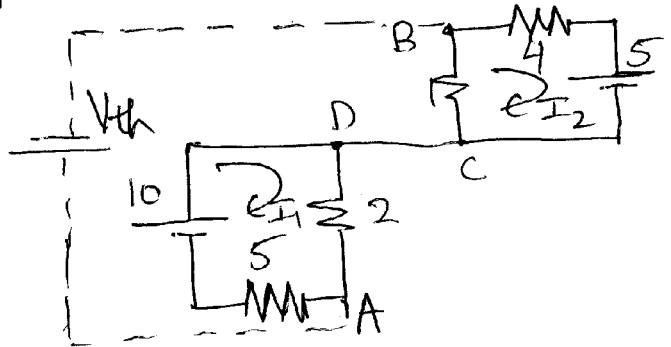

For R_{th} , short 10V & 5V Battery.


$$2\Omega // 5\Omega = 1.43\Omega$$

$$1\Omega // 4\Omega = 0.8\Omega$$


$$R_{th} = 1.43 + 0.8 = 2.23\Omega$$

$$R_{th} = 2.23\Omega$$

$$V_{th} = -3.86V$$

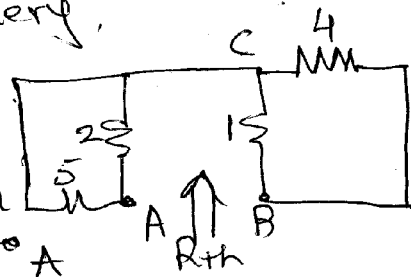

Thevenin's Eq. ckt. is

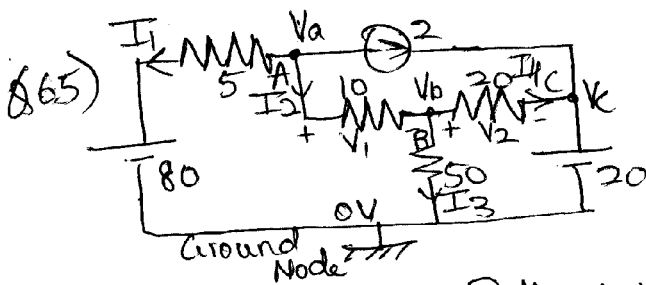

[NOTE: If a node is connected to a battery without any resistor between node and ground then KCL cannot be applied and nodal voltage = applied and nodal voltage = Battery voltage with polarity = nearest Battery nodal polarity]

\therefore At Node C:-

$$V_c = +20V$$

KCL at node A:-

$$I_1 + I_2 + 2 = 0$$

$$\therefore \frac{V_a - 80 - 0}{5} + \frac{V_a - V_b}{10} + 2 = 0$$

Navlakhhi's

$$\therefore V_a \left(\frac{1}{5} + \frac{1}{10} \right) + V_b \left(-\frac{1}{10} \right) = \frac{80}{5} - 2 \quad \text{--- (I)}$$

KCL at node B: -

$$I_2 = I_3 + I_4$$

$$\frac{V_a - V_b}{10} = \frac{V_b - 0}{50} + \frac{V_b - V_c}{20}$$

$$\therefore V_a \left(\frac{1}{10} \right) + V_b \left(-\frac{1}{10} - \frac{1}{50} - \frac{1}{20} \right) + V_c \left(\frac{1}{20} \right) = 0 \quad \text{--- (II)}$$

$$V_a = 60.49 \text{ V}$$

$$V_b = 41.46 \text{ V}$$

$$V_1 = +V_a - V_b$$

$$\therefore V_1 = 19.03 \text{ V}$$

$$V_2 = +V_b - V_c$$

$$\therefore V_2 = 21.46 \text{ V}$$

[Polarity of V_a & V_b depends on signs of V_i close to V_a & V_b]

[NOTE: Verify using Mesh Analysis: -

KVL to loop I: -

$$65I_1 - 10I_2 - 50I_3 = 80 \quad \text{--- (I)}$$

In loop II: -

$$I_2 = 2 \text{ A} \quad \text{--- (II)}$$

KVL to loop III: -

$$-50I_1 - 20I_2 + 70I_3 = -20 \quad \text{--- (III)}$$

$$\therefore I_1 = 3.9 \text{ A}$$

$$I_2 = 2 \text{ A}$$

$$I_3 = 3.07 \text{ A}$$

$$V_1 = 10(+I_1 - I_2)$$

$$\therefore V_1 = 19 \text{ V}$$

$$V_2 = 20(+I_3 - I_2)$$

$$\therefore V_2 = 21.4 \text{ V}$$

[Polarity of current depends on terminal of V_i it enters]