

A.C. CIRCUITS AND POLYPHASE

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Tel: 9820246760 / 23886023 / 23868356

Q1) Solved Eg. Type I (Q13) [R-L ckt.]


Q2) $R = 10\Omega$, $L = 0.1\text{H}$, $C = 200 \times 10^{-6}\text{F}$, $V = 230\text{V}$, $f = 50\text{Hz}$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.1 = 31.42\Omega$$

$$X_C = 1 / (2\pi fC) = 1 / (2\pi \times 50 \times 200 \times 10^{-6}) = 15.92\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 18.45\Omega$$
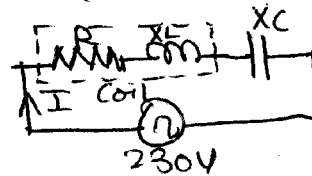
$$I = \frac{V}{Z} = \frac{230}{18.45} = 12.47\text{A}$$



$$Z_{\text{coil}} = \sqrt{R^2 + X_L^2} = 32.97\Omega$$

$$V_{\text{coil}} = I \cdot Z_{\text{coil}} = 411.17\text{V}$$

$$V_C = I \cdot X_C = 198.52\text{V}$$

At Resonance

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 200 \times 10^{-6}}} = 35.59\text{Hz}$$

$$I_0 = \frac{V}{R} = 23\text{A}$$

$$X_{L_0} = 2\pi f_0 L = 2 \times \pi \times 35.59 \times 0.1 = 22.36\Omega$$

$$X_{C_0} = 1 / (2\pi f_0 C) = 22.36\Omega$$

$$V_{C_0} = I_0 X_{C_0} = 514.27\text{V}$$

$$Z_{\text{coil}_0} = \sqrt{R^2 + X_{L_0}^2} = 24.49\Omega$$

$$V_{\text{coil}_0} = I_0 Z_{\text{coil}_0} = 563.37\text{V}$$

Q3) $R = 50\Omega$, $C = 50 \times 10^{-6}\text{F}$, $V = 440\text{V}$, $f = 50\text{Hz}$

$$X_C = 1 / (2\pi fC) = 1 / (2\pi \times 50 \times 50 \times 10^{-6}) = 63.66\Omega$$

$$Z = \sqrt{R^2 + X_C^2} = 80.95\Omega$$

navlakhi.com

For Delta Connection:-

$$V_L = V_{ph} = 440V$$

$$(a) I_{ph} = \frac{V_{ph}}{Z} = 5.44A$$

$$(b) I_L = \sqrt{3} I_{ph} = 9.42A$$

$$(c) \text{Power} = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} V_L I_L \times R/Z$$

$$= \sqrt{3} \times 440 \times 9.42 \times 50/80.95 = 4,434.22W$$

$$(d) \text{Let } V_{RY} = 440 \angle 0^\circ = 440 + j0$$

$$V_{YB} = 440 \angle 120^\circ = -220 - j381.05$$

$$V_{BR} = 440 \angle 240^\circ = -220 + j381.05$$

$$I_R = \frac{V_{RY}}{Z} = \frac{440}{50 - j63.66} = 3.36 + j4.28$$


$$I_Y = \frac{V_{YB}}{Z} = 2.02 - j5.05$$

$$I_B = \frac{V_{BR}}{Z} = -5.38 + j0.77$$

$$I_1 = I_R - I_B = 9.42 \angle 21.88^\circ$$

$$I_2 = I_Y - I_R = 9.42 \angle -98.17^\circ$$
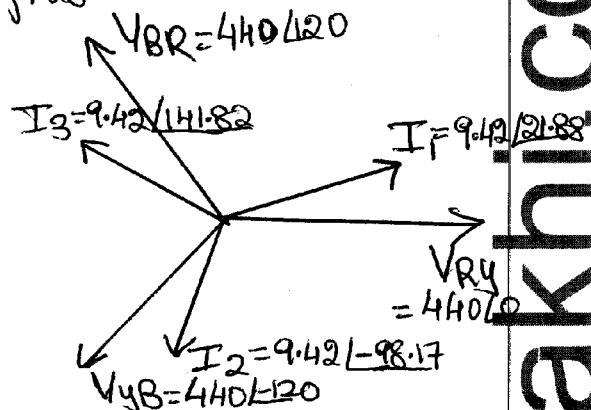
$$I_3 = I_B - I_Y = 9.42 \angle 141.82^\circ$$



$$Q4) \phi = 45^\circ (\text{lag}), V_{Lm} = 2 \times V_{cm}, v_L = 300 \sin \omega t, R = 20\Omega$$

$$f = 50\text{Hz}, \text{Comparing with } v_L = V_{Lm} \sin \omega t \therefore V_{Lm} = 300V$$

$$V_{cm} = V_{Lm}/2 = 150V$$

$$V_L = V_{cm}/\sqrt{2} = 212.13V, V_c = V_{cm}/\sqrt{2} = 106.07V$$

$$V_L = I X_L \Rightarrow 212.13 = I X_L \text{ \& } V_c = I X_c \therefore 106.07 = I X_c$$

$$\therefore \frac{I X_L}{I X_c} = \frac{212.13}{106.07} \therefore X_L = 2 X_c \dots (I)$$



$$\cos \phi = \frac{R}{Z} \quad \therefore \cos 45^\circ = \frac{20}{Z} \quad \therefore Z = 28.28 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (2X_C - X_C)^2} \text{ from eq(I)}$$

$$\therefore Z = \sqrt{R^2 + X_C^2} \quad \therefore 28.28 = \sqrt{20^2 + X_C^2} \quad \therefore X_C = 20 \Omega$$

$$X_L = 2X_C = 40 \Omega$$

$$\because X_L = 2\pi fL \quad \therefore L = 0.127 \text{ H} \quad \& \quad X_C = \frac{1}{2\pi fC} \quad \therefore C = 159.16 \mu\text{F}$$

Q5) $V = 250\text{V}, I_1 = 5\text{A}, f_1 = 50\text{Hz}, f_2 = 60\text{Hz}, I_2 = 5.8\text{A}$

$$Z_1 = \frac{V}{I_1} = \frac{250}{5} = 50 \Omega$$

$$Z_1 = \sqrt{R^2 + X_{L1}^2} \quad \therefore 50 = \sqrt{R^2 + (2\pi f_1 L)^2} \quad \therefore R^2 = 2500 - 4\pi^2 (50)^2 L^2 \quad \text{--- (I)}$$

$$Z_2 = \frac{V}{I_2} = \frac{250}{5.8} = 43.1 \Omega$$

$$Z_2 = \sqrt{R^2 + X_{L2}^2} \quad \therefore 43.1 = \sqrt{R^2 + (2\pi f_2 L)^2} \quad \therefore R^2 = (43.1)^2 - 4\pi^2 (60)^2 L^2 \quad \text{--- (II)}$$

Equating eq. (I) & (II) $\therefore 2500 - 4\pi^2 (50)^2 L^2 = (43.1)^2 - 4\pi^2 (60)^2 L^2$

$$\frac{1}{4\pi^2 (50)^2 L^2} - \frac{1}{4\pi^2 (60)^2 L^2} = 642.39 \quad \therefore C = 69.42 \mu\text{F}$$

Subs. in eq (I) $\therefore R = \sqrt{397.52} = 19.94 \Omega$

$$\cos \phi_2 = \frac{R}{Z_2} = 0.463$$

$$P_2 = VI_2 \cos \phi_2 = 250 \times 5.8 \times 0.463 = 671.35 \text{ W}$$

Q6) $V_R = 10\text{V}, V_L = 15\text{V}, V_C = 10\text{V}$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = 11.18 \text{ V}$$

Q7) $\because v = V_m \sin \theta \quad \therefore 0.5 V_m = V_m \sin \theta \quad \therefore \theta = 30^\circ$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{2\pi} (V_m \sin \theta)^2 d\theta} = \sqrt{\frac{1}{2\pi} \int_{30^\circ}^{360^\circ} V_m^2 \sin^2 \theta d\theta}$$



$$V_{rms} = \frac{V_m}{\sqrt{2\pi}} \int_{30^\circ}^{360^\circ} \sin^2 \theta d\theta = 70.77 V_m$$

Q8) $I_1 = 20 \angle 30^\circ = 17.32 + j10$

$I_2 = 40 \angle 60^\circ = 20 + j34.64$

∴ Current through capacitor lags voltage by 90°

∴ $I_3 = I \angle -90^\circ = -jI$

∴ $I = I_1 + I_2 + I_3 = 37.32 + j(44.64 - I)$

∴ P.f. of I is unity ∴ Its imaginary part is 0

∴ $44.64 - I = 0$ ∴ $I = 44.64 A$

∴ Current through capacitor is $I_3 = -j44.64$

Q9) Let $V' = \sqrt{V_R^2 + V_{coil}^2} = 216.33 V$

∴ $V' \neq 230 V$ ∴ Coil is impure and has internal resistor r

∴ $V_R = I \cdot R$ ∴ $120 = 6 \times R$ ∴ $R = 20 \Omega$

∴ $V_{coil} = I \cdot X_{coil}$ ∴ $X_{coil} = 180/6 = 30 \Omega$ 230V, 50Hz

$X_{coil} = \sqrt{X_L^2 + r^2}$ ∴ $30 = \sqrt{X_L^2 + r^2}$ ∴ $r^2 + X_L^2 = 900$

∴ $Z = V/I = 230/6 = 38.33 \Omega$



∴ $Z = \sqrt{(R+r)^2 + X_L^2} = \sqrt{(20+r)^2 + X_L^2} = \sqrt{400 + 40r + r^2 + X_L^2}$

From eq (I) we get, $38.33 = \sqrt{400 + 40r + 900}$

∴ $r = 4.23 \Omega$ Subs. in eq (I) ∴ $X_L = 29.7 \Omega$

$V_r = I r = 25.38 V$, $V_L = I \cdot X_L = 178.2 V$

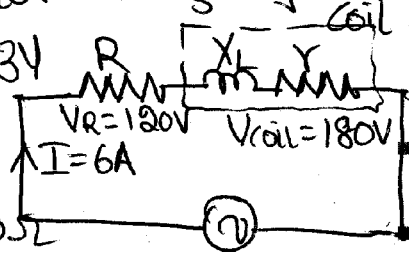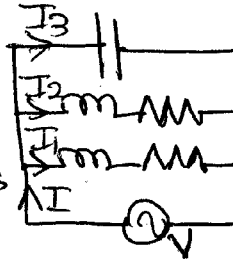
$\cos \phi_{coil} = r/Z_{coil}$ ∴ $\phi_{coil} = 81.89^\circ$, $\cos \phi = (R+r)/Z$, $\phi = 50.7^\circ$



Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

Phasor diagram is:-

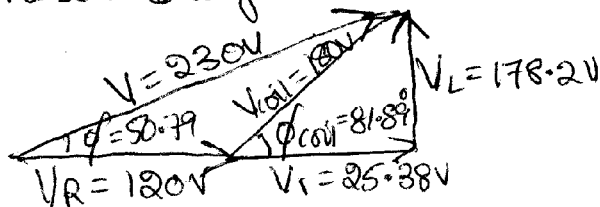

Q10) $R = 20\Omega$, $L = 0.2H$, $C = 200 \times 10^{-6}F$



$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \frac{1}{2\pi} \sqrt{\frac{1}{0.2 \times 200 \times 10^{-6}} - \frac{20^2}{0.2^2}} = 19.49 \text{ Hz}$$

$$Z_{\text{dynamic}} = L/RC = 50\Omega$$


$$I = \frac{V}{Z_{\text{dynamic}}} = \frac{230}{50} = 4.6A$$

$$I_1 = \frac{V}{Z_{\text{coil}}} = \frac{V}{R + jX_L} = \frac{V}{R + j2\pi f_0 L} = \frac{230}{20 + j7.27} = 4.6 - j5.63$$
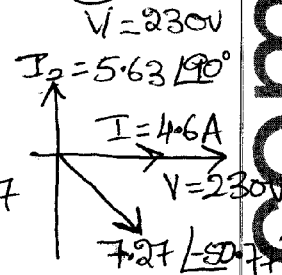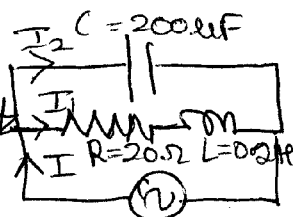
$$I_2 = \frac{V}{-jX_C} = \frac{V}{-j(1/2\pi f_0 C)} = +j5.63$$



Q11) Solved Eq. Q14 [Polyphase ckts]

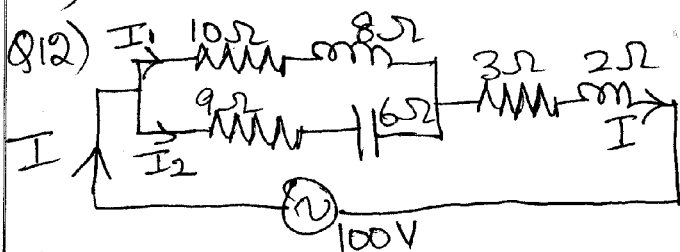

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} \therefore \frac{1}{Z_p} = \frac{1}{10 + j8} + \frac{1}{9 - j6}$$

$$Z_p = (7.25 - j0.13)\Omega$$

$$Z = Z_p + Z_3 = (10.25 - j2.13)\Omega$$

$$I = \frac{V}{Z} = \frac{100}{10.25 - j2.13} = 9.35 + j1.94$$

Navlakhī's



Tel: 23868356/23886023/9820246760 POWER

Tel: 9820246760 / 23886023 / 23868356

$$V_p = I \cdot Z_p = (9.35 + j1.94)(7.25 - j0.13)$$

$$V_p = 68.04 + j12.85 = 69.24 \angle 10.69^\circ$$

$$I_1 = \frac{V_p}{Z_1} = \frac{68.04 + j12.85}{10 + j8} = 4.78 - j2.54 = 5.41 \angle -27.97^\circ$$

$$I_2 = \frac{V_p}{Z_2} = \frac{68.04 + j12.85}{9 - j6} = 4.58 + j4.48 = 6.4 \angle 44.39^\circ$$

$$I_A = I_1 = 5.41 \angle -27.97^\circ$$

$$I_B = I_2 = 6.4 \angle 44.39^\circ$$

Q(3) $Z_1 = 50 \angle -45^\circ$ $\therefore pf = 0.707$ (lead) $\therefore \phi = -45^\circ$

$$Z_1 = 35.36 - j35.36$$

$$Z_2 = 40 \Omega$$


$$I = 3A$$

$$Z = Z_1 + Z_2 = 75.36 - j35.36$$

$$V = I \times Z = 3(75.36 - j35.36)$$

$$V = 226.08 - j106.08 = 249.73 \angle -25.14^\circ$$

$$\therefore \phi = -25.14^\circ$$

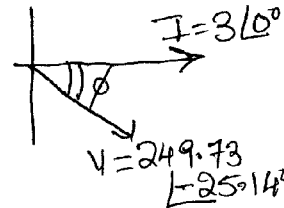

phase angle = 25.14 (lead)

Q(4) Total power = 1,500W

$pf = 0.2$ (lag)

$V_L = 440V$

$f = 50Hz$

For Star connection:-

$V_L = \sqrt{3} V_{ph}$

$\therefore V_{ph} = 254.03V$

navlakhī.com



$$\text{Total power} = \sqrt{3} V_L I_L \cos \phi$$

$$1500 = \sqrt{3} \times 440 \times I_L \times 0.2$$

$$\therefore I_L = 9.84 \text{ A}$$

$$I_L = I_{ph} = 9.84 \text{ A}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = 25.81 \Omega$$

$$\cos \phi = \frac{R}{Z_{ph}} \quad \therefore R = 25.81 \times 0.2 = 5.16 \Omega$$

$$Z_{ph} = \sqrt{R^2 + X_L^2} \quad \therefore X_L = 25.29 \Omega$$

$$X_L = 2\pi f L \quad \therefore L = 0.0805 \text{ H}$$

Q15) Solved Eqs Q5 [R-L-C ckts]

$$Q16) e_1 = 25 \sin \omega t = \frac{25}{\sqrt{2}} \angle 0^\circ = \frac{25}{\sqrt{2}} + j0 = 17.68 + j0$$


$$e_2 = 10 \sin(\omega t + \frac{\pi}{6}) = \frac{10}{\sqrt{2}} \angle 30^\circ = 6.12 + j3.54$$

$$e_3 = 30 \cos \omega t = 30 \sin(\omega t + 90^\circ) = \frac{30}{\sqrt{2}} \angle 90^\circ = j21.21$$

$$e_4 = 20 \sin(\omega t - \frac{\pi}{4}) = \frac{20}{\sqrt{2}} \angle -45^\circ = 10 - j10$$

$$e = e_1 + e_2 + e_3 + e_4 = 33.8 + j14.75 = 36.88 \angle 23.58^\circ$$
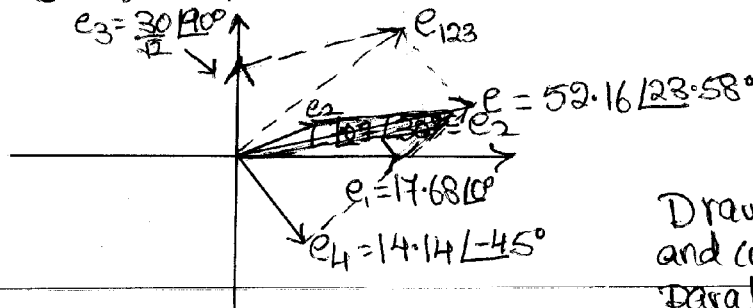
$$\therefore e = 36.88 \sqrt{2} \sin(\omega t + 23.58^\circ) = 52.16 \sin(\omega t + 23.58^\circ)$$



Draw to scale
and complete
parallelogram

Q17) Let $v = V_m \sin(\theta + \phi)$

On y-axis, $\theta = 0^\circ$ and $v = 0.866 V_m$ (given)

$$\therefore 0.866 V_m = V_m \sin(0 + \phi)$$

$$\therefore \phi = \sin^{-1}(0.866) = \pi/3$$

$$\therefore v = V_m \sin(\theta + \pi/3)$$

$$\text{Time period} = 2\pi - \frac{\pi}{3} = \frac{5\pi}{3}$$

$$\begin{aligned} V_{avg} &= \frac{1}{2\pi/3} \int_0^{2\pi/3} V_m \sin(\theta + \pi/3) d\theta \\ &= \frac{3V_m}{2\pi} \left[-\cos(\theta + \pi/3) \right]_0^{2\pi/3} \\ &= -\frac{3V_m}{2\pi} \left[\cos(\pi) - \cos(\pi/3) \right] \\ &= -\frac{3V_m}{2\pi} \left[-1 - \frac{1}{2} \right] = +\frac{9V_m}{4\pi} \end{aligned}$$



Q18) $Z \angle -\phi = R - jX_c$

$\therefore$ Imaginary part of Z is negative because of negative phase angle
 $\therefore$ Circuit is capacitive

For an capacitive circuit, imaginary part of Z is negative, since a circuit at resonance has only real part hence its imaginary part is zero therefore an inductor should be

added in series having $X_L = X_C$ hence $jX_L = -jX_C$ hence positive imaginary part of inductor cancels with negative part of the capacitor.

Phasor diagram for resonance is :-

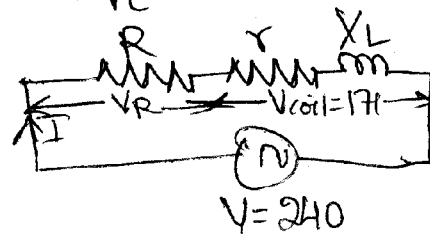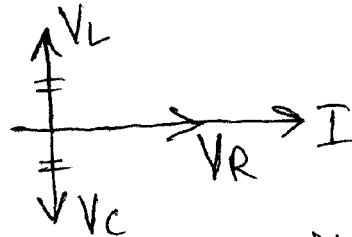

$$Q19) V = 240 \angle 0^\circ$$

$$I = 3 \angle -37^\circ$$

$$V_{coil} = 171V$$

$$Z = \frac{V}{I} = \frac{240}{3} = 80 \Omega$$

$$\cos \phi = \frac{R+r}{Z} \quad \therefore \cos(37^\circ) = \frac{R+r}{80}$$

$$\therefore R+r = 6.39 \quad \dots (I)$$

$$Z_{coil} = \frac{V_{coil}}{I} = \frac{171}{3} = 57 \Omega$$

$$\therefore Z_{coil} = \sqrt{r^2 + X_L^2}$$

$$\therefore r^2 + X_L^2 = 3249 \quad \dots (II)$$

$$Z = \sqrt{(R+r)^2 + X_L^2}$$

$$80 = \sqrt{(6.39)^2 + X_L^2} \quad \therefore X_L = 48.13 \Omega$$

$$\text{Subs. in (II)} \quad \therefore r = 30.54 \Omega$$

$$\text{Subs in (I)} \quad \therefore R = 33.36 \Omega$$

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

$$Q20) I_L = 15A$$

$$\text{Total active power} = 11,000W$$

$$\text{Total apparent power} = 15,000 VA$$

For star connection

$$I_L = I_{ph} = 15A$$

$$\text{Active power} = \sqrt{3} V_L I_L \cos \phi \quad \dots (I)$$

$$\text{Apparent power} = \sqrt{3} V_L I_L \quad \dots (II)$$

Divide by (I) by (II)

$$\therefore \cos \phi = \frac{11,000}{15,000} \quad \therefore \phi = 42.83^\circ (\text{lag})$$

From (II)

$$15,000 = \sqrt{3} V_L \times 15 \quad \therefore V_L = 577.35V$$

$$V_L = \sqrt{3} V_{ph} \quad \therefore V_{ph} = 333.33V$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = 22.22\Omega$$

$$\cos \phi = \frac{R}{Z_{ph}} \quad \therefore R = 16.3\Omega$$

$$Z_{ph} = \sqrt{R^2 + X_L^2} \quad \therefore X_L = 15.1\Omega$$

For delta connection

$$V_L = 577.35V$$

$$V_L = V_{ph} = 577.35V$$

$$Z_{ph} = 22.22\Omega$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = 25.98A$$

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

Navlakhi's




Tel: 23868356/23886023/9820246760 **POWER**

$$I_L = \sqrt{3} I_{ph} \therefore I_L = 45A$$

$$\begin{aligned} \text{Active power} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 577.35 \times 45 \times \cos 42.83 \\ &= 33 \text{ kW} \end{aligned}$$
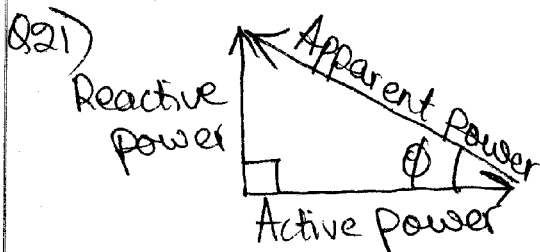
$$\begin{aligned} \text{Reactive power} &= \sqrt{3} V_L I_L \sin \phi \\ &= \sqrt{3} \times 577.35 \times 45 \times \sin 42.83 \\ &= 30.59 \text{ kVAR} \end{aligned}$$




$$\begin{aligned} \text{Active power} &= VI \cos \phi \\ \text{Units: Watts} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= VI \sin \phi \\ \text{Units: Volt-Ampere-Reactive (VAR)} \end{aligned}$$

$$\begin{aligned} \text{Apparent power} &= VI \\ \text{Units: Volt-Ampere (VA)} \end{aligned}$$

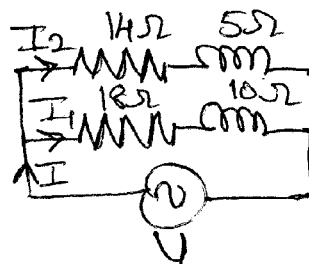Q22) Let $Z_1 = 14 + j5$
 $Z_2 = 18 + j10$
 $V = 200V$
 $f = 50 \text{ Hz}$



Tel: 9820246760 / 23886023 / 238683556

navlakhi.com

Navlakhi's



Tel: 23868356/23886023/9820246760 **POWER**

Tel: 9820246760 / 23886023 / 23868356

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \therefore Z = 7.94 + j3.47$$

$$Z = 8.66 \angle 23.59^\circ$$

$$(i) Y_1 = \frac{1}{Z_1} = 0.063 - j0.023$$

$$Y_2 = \frac{1}{Z_2} = 0.043 - j0.024$$

$$Y = \frac{1}{Z} = 0.11 - j0.046$$

$$(ii) I_1 = \frac{V}{Z_1} = \frac{200}{14 + j5} = 12.67 - j4.53 = 13.45 \angle -19.64^\circ$$

$$I_2 = \frac{V}{Z_2} = \frac{200}{18 + j10} = 8.49 - j4.72 = 9.71 \angle -29.05^\circ$$

$$I = \frac{V}{Z} = \frac{200}{7.94 + j3.47} = 21.15 - j9.24 = 23.08 \angle -23.61^\circ$$

$$(iii) Z_1 = 14 + j5 = 14.87 \angle 19.65^\circ$$

$$Z_2 = 18 + j10 = 20.59 \angle 29.05^\circ$$

$$pf_1 = \cos \phi_1 = \cos 19.65^\circ = 0.942 (\text{lag})$$

$$pf_2 = \cos \phi_2 = \cos 29.05^\circ = 0.874 (\text{lag})$$


$$P_1 = VI_1 \cos \phi_1 = 2.53 \text{ kW}$$

$$P_2 = VI_2 \cos \phi_2 = 1.7 \text{ kW}$$

$$(iv) \text{Total } pf = \cos \phi$$

$$= \cos 23.59^\circ$$

$$= 0.916 (\text{lag})$$

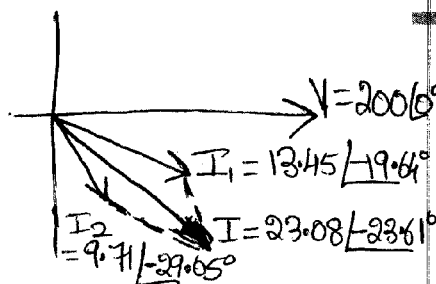

DRAW TO SCALE COMPLETE PARALL
Kunal Navlakhi ELEC RAM

Q23) $P_R = 1000W$

$P_r = 200W$

$V_R = 200V$

$V_{coil} = 300V$

(i) $P_R = V_R \times I \therefore 1000 = 200 \times I \therefore I = 5A$

$V_R = I \cdot R \therefore 200 = 5 \times R \therefore R = 40\Omega$

(ii) $I = 5A$

(iii) $P_r = I^2 \cdot r \therefore 200 = 25 \times r \therefore r = 8\Omega$

(iv) $Z_{coil} = \frac{V_{coil}}{I} = \frac{300}{5} = 60\Omega$

(v) $Z_{coil} = \sqrt{r^2 + X_L^2} \therefore 60 = \sqrt{8^2 + X_L^2} \therefore X_L = 59.46\Omega$

$Z = \sqrt{(R+r)^2 + X_L^2} = 76.42\Omega$

(vi) $V = I \cdot Z = 382.1V$

Q24) $Z_1 = 1 + j2$
 $Z_2 = R_2$

$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \therefore \frac{1}{Z} = \frac{1}{1+j2} + \frac{1}{R_2} = \frac{R_2 + 1 + j2}{R_2(1+j2)}$

$\therefore Z = \frac{R_2(1+j2)}{(1+R_2)+j2} \times \frac{(1+R_2)-j2}{(1+R_2)-j2}$

$= \frac{R_2 + j2 + R_2^2 + j2R_2 - j2R_2 + 4R_2}{(1+R_2)^2 + 4}$

$Z = \frac{R_2^2 + 5R_2 + j2}{(1+R_2)^2 + 4}$

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

$$\because pf = 0.92 \therefore \cos \phi = 0.92 \therefore \phi = 23.07^\circ$$

$$\tan \phi = \frac{2}{R_2^2 + 5R_2}$$

$$\therefore 0.426 = \frac{2}{R_2^2 + 5R_2} \therefore 0.426R_2^2 + 2.13R_2 - 2 = 0$$

$$\therefore R_2 = 0.808 \Omega$$

Q25) Total active power = 10,000 W

$$V_L = 440 \text{ V}$$

$$pf = 0.6 (\text{lead})$$

For Delta connection:-

$$V_L = V_{ph} = 440 \text{ V}$$

$$\text{Power} = \sqrt{3} V_L I_L \cos \phi$$

$$10,000 = \sqrt{3} \times 440 \times I_L \times 0.6$$

$$I_L = 21.87 \text{ A}$$

$$I_L = \sqrt{3} I_{ph} \therefore I_{ph} = 12.63 \text{ A}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = 34.84 \Omega$$

$$\cos \phi = \frac{R}{Z_{ph}} \therefore R = 20.9 \Omega$$

$$Z_{ph} = \sqrt{R^2 + X_c^2} \therefore X_c = 27.87 \Omega$$

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

Navlakhi's



Tel: 23868356/23886023/9820246760 POWER

$$\begin{aligned}\text{Reactive power} &= \sqrt{3} V_L I_L \sin \phi \\ &= 13.33 \text{ kVAR}\end{aligned}$$

$$\begin{aligned}\text{Q26) } V(t) &= 7.5t \quad 0 < t < 2 \\ &= 7.5(t-4) \quad 2 < t < 6 \\ &= 7.5(t-8) \quad 6 < t < 8\end{aligned}$$

$$\begin{aligned}V_{\text{avg}} &= \frac{1}{T} \int_0^T V(t) dt \\ &= \frac{1}{8} \left[\int_0^2 7.5t dt + \int_2^6 (-7.5)(t-4) dt \right. \\ &\quad \left. + \int_6^8 7.5(t-8) dt \right] \\ &= 0\end{aligned}$$

$$\begin{aligned}V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T V^2(t) dt} \\ &= \sqrt{\frac{1}{8} \left[\int_0^2 (7.5t)^2 dt + \int_2^6 [7.5(t-4)]^2 dt \right. \\ &\quad \left. + \int_6^8 [7.5(t-8)]^2 dt \right]} \\ &= 8.66 \text{ V}\end{aligned}$$

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

Q27) For bulbs connected in series, higher power rating of the bulb will glow brighter.
∴ 100W, 230V bulb will glow much brighter.

Q28) Reference textbook Pg 261 (Q63)

Q29) $V = 200 \sin 377t = V_m \sin \omega t$

$$i = 8 \sin(377t - \frac{\pi}{6}) = I_m \sin(\omega t + \phi)$$

$$V_m = 200V, I_m = 8A, \phi = -\pi/6, \omega = 377 \text{ rad/sec}$$

$$V = \frac{V_m}{\sqrt{2}} = 141.4V, I = \frac{I_m}{\sqrt{2}} = 5.66A, \phi = 30^\circ (\text{lag})$$

$$\text{Active power} = VI \cos \phi = 693.1W$$

$$\text{Reactive power} = VI \sin \phi = 400.16 \text{ VAR}$$

$$\text{Apparant power} = VI = 800.32 \text{ VA}$$

Q30) Solved Eq. (813) [R-L ckt.]

Q31) $P = 10,000W$

$$I_L = 80A (\text{lead})$$

$$V_L = 1100V$$

$$f = 50Hz$$

For Star Connection, $V_L = \sqrt{3} V_{ph}$

Tel: 9820246760 / 23886023 / 23868356

navlakhi.com

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 POWER

Tel: 9820246760 / 23886023 / 23868356

$$\therefore V_{ph} = \frac{1100}{\sqrt{3}} = 635.1V$$

$$I_L = I_{ph} = 80A$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = 7.94\Omega$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$10,000 = \sqrt{3} \times 1100 \times 80 \times \cos\phi$$

$$\therefore \cos\phi = 0.0656 \text{ (lead)}$$

$$\therefore \cos\phi = \frac{R}{Z_{ph}} \quad \therefore R = 0.52\Omega$$

$$Z_{ph} = \sqrt{R^2 + X_c^2} \quad \therefore X_c = 7.92\Omega$$

$$X_c = \frac{1}{2\pi f C} \quad \therefore C = 401.9\mu F$$

$$Q32) X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi f}$$

$$X_L = 2\pi f L = 8\pi f \quad \text{where } f \text{ is resonating freq.}$$

$$\text{Let } Z_1 = jX_L - jX_c = j\left(8\pi f - \frac{1}{2\pi f}\right)$$

$$\text{Let } Z_2 = -jX_c = \frac{-j}{2\pi f}$$

$$Z_p = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{16\pi^2 f^2 - 1}{2\pi f j [16\pi^2 f^2 - 2]} = \frac{-j}{2\pi f} \left[\frac{16\pi^2 f^2 - 1}{16\pi^2 f^2 - 2} \right]$$

$$Z = 10 + Z_2 = 10 - \frac{j}{2\pi f} \left[\frac{16\pi^2 f^2 - 1}{16\pi^2 f^2 - 2} \right]$$

navlakhi.com



Since circuit is at resonance
 $\therefore$ It is resistive, hence its imaginary part will be 0

$$\therefore \frac{-j}{2\pi f} \left[\frac{16\pi^2 f^2 - 1}{16\pi^2 f^2 - 2} \right] = 0$$

$$\therefore 16\pi^2 f^2 = 1 \quad \therefore f = 0.0796 \text{ Hz}$$

Q33) $Z_1 = 3 + j4$, $Z_2 = 4 - j3$, $Z_3 = 4.57 + j5.51$

i) $Y_p = Y_1 + Y_2 \quad \left(\because \frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} \right)$

$$\therefore Y_p = 0.28 - j0.04$$

$$Z_p = 3.5 + j0.5$$

$$Z = Z_p + Z_3 = 8.07 + j6.01 = 10.06 \angle 36.68^\circ$$


ii) $I = \frac{V}{Z} = 15.94 - j11.87 = 19.88 \angle -36.68^\circ$

iii) $\text{pf} = \cos \phi = \cos(36.68^\circ) = 0.82 \text{ (lag)}$

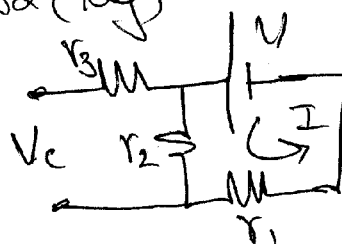Q34) $I = \frac{V}{r_2 + r_1}$

$$V_{r_2} = I \times r_2 = \frac{V r_2}{r_1 + r_2}$$

$$V_c = V_{r_2} = \frac{V \times r_2}{r_1 + r_2}$$



Q35) $V = 5 \cos \omega t = 5 \sin(\omega t + 90^\circ) = V_m \sin(\omega t + 90^\circ)$

$$i = I_m \sin \omega t$$

Navlakhi's



Tel: 23868356/23886023/9820246760 **POWER**

Tel: 9820246760 / 23886023 / 23868356

$$V = \frac{V_m}{\sqrt{2}} \angle \phi = \frac{5}{\sqrt{2}} \angle 90^\circ$$

$$I = \frac{I_m}{\sqrt{2}} \angle 0^\circ = \frac{10}{\sqrt{2}} \angle 0^\circ$$

$$\phi = 90^\circ$$

$$P = VI \cos \phi = \frac{5}{\sqrt{2}} \times \frac{10}{\sqrt{2}} \cos 90^\circ = 0 \text{ W}$$

$$Q36) V = \sqrt{V_R^2 + V_L^2} = \sqrt{(16)^2 + (12)^2} = 20 \text{ V}$$

$$Z = \frac{V}{I} = \frac{20}{5} = 4 \Omega$$

$$Q37) v = V_m \sin \theta, \quad \alpha < \theta < \pi$$

$$= 0, \text{ elsewhere}$$

$$V_{avg} = \frac{1}{T} \int_0^T v \, d\theta = \frac{1}{2\pi} \int_0^{2\pi} v \, d\theta$$

$$= \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \theta \, d\theta = \frac{V_m}{2\pi} [-\cos \theta]_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 \, d\theta} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \sin^2 \theta \, d\theta}$$

$$= \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta}$$

navlakhi.com



$$V_{rms} = \sqrt{\frac{1}{2\pi} \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right] \pi}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \left[\frac{\pi}{2} - \frac{\alpha}{2} + \frac{\sin 2\alpha}{4} \right]}$$

Q38) Solved Eq. (Q1) [Series Resonance]

Q39) Reference bk Pg 247 (Q49)

Q42) For unity pf (UPF)

$$pf = \cos \phi = 1 \quad \therefore \phi = 0^\circ$$

$$\therefore \tan \phi = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$\tan 0 = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right) \quad \therefore \omega_1 = \omega_2$$

ii) Zero pf

$$\therefore pf = \cos \phi = 0 \quad \therefore \phi = 90^\circ$$

$$\tan \phi = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$\tan 90^\circ = \infty = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$$

$$\therefore \omega_1 + \omega_2 = 0 \quad \therefore \omega_1 = -\omega_2$$

iii) pf 0.5 (lag) $\therefore \cos \phi = 0.5 \quad \therefore \phi = 60^\circ$

For lagging pf, $\tan \phi = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right) \quad \therefore \sqrt{3} = \sqrt{3} \left(\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} \right)$

$$\therefore \omega_1 - \omega_2 = \omega_1 + \omega_2 \quad \therefore \omega_2 = 0$$