

Navlakhi

9820246760 / 9769479368

$$Q44) W_1 = 2500W$$

$$W_2 = 500W$$

i) When both readings are positive

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right) = \sqrt{3} \left(\frac{2500 - 500}{2500 + 500} \right)$$

$$\therefore \phi = 49.1^\circ$$

$$Pf = \cos \phi = 0.66$$

$$ii) W_1 = 2500W$$

$$W_2 = -500W$$

When one wattmeter is reversed

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right) = \sqrt{3} \left(\frac{2500 + 500}{2500 - 500} \right)$$

$$\therefore \phi = 68.95^\circ$$

$$Pf = \cos \phi = 0.36$$

$$Q45) i = 141.4 \sin 314t$$

Comparing with $i = I_m \sin \omega t$

$$i) \text{ Peak value} = I_m = 141.4A$$

$$ii) \omega = 314$$

$$\therefore \omega = 2\pi f$$

$$\therefore 314 = 2\pi f$$

$$\therefore f = 49.98 \text{ Hz}$$

$$iii) T = \frac{1}{f} = 0.02 \text{ sec}$$

$$iv) t = 3 \times 10^{-3} \text{ sec}$$

$$i = 141.4 \sin 314(3 \times 10^{-3})$$

$$= 141.4 \times 0.016$$

$$= 2.33A$$

navlakhi.mobi

navlakhi.com

Be With the Best

Navlakhi

846) Time period is $0 < t < T$

$$v = V_m, 0 < t < T/2 \\ = 0, T/2 < t < T$$

$$V_{avg} = \frac{1}{T} \int_0^T v dt = \frac{1}{T} \int_0^{T/2} V_m dt = \frac{V_m}{T} \int_0^{T/2} dt = \frac{V_m}{T} [t]_0^{T/2}$$

$$\therefore V_{avg} = \frac{V_m}{T} \left[\frac{T}{2} \right] = \frac{V_m}{2}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (v)^2 dt} = \sqrt{\frac{1}{T} \int_0^{T/2} (V_m)^2 dt} = \sqrt{\frac{V_m^2}{T} [t]_0^{T/2}} \\ = \sqrt{\frac{V_m^2}{T} \left[\frac{T}{2} \right]} = \frac{V_m}{\sqrt{2}}$$

847) $f = 50 \text{ Hz}$

$$X_{L1} = 2\pi f L_1 = 2\pi \times 50 \times 0.0191 = 6 \Omega$$

$$X_{C2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi \times 50 \times 398 \times 10^{-6}} = 8 \Omega$$

$$X_{L3} = 2\pi f L_3 = 2\pi \times 50 \times 0.0138 = 4.34 \Omega$$

$$\text{Let } Z_1 = R_1 + jX_{L1} = 2 + j6$$

$$Z_2 = R_2 - jX_{C2} = 7 - j8$$

$$Z_3 = R_3 + jX_{L3} = 8 + j4.34$$

$$I_2 = 10 \text{ A}$$

$$V_2 = I_2 \times Z_2 = 10(7 - j8) = 70 - j80$$

$$V_2 = V_1 = 70 - j80$$

$$I_1 = \frac{V_1}{Z_1} = \frac{70 - j80}{2 + j6} = -8.5 - j14.5$$

$$I = I_1 + I_2 \text{ (only in rectangular or cartesian form)}$$

$$\therefore I = -8.5 - j14.5 + 10 = 1.5 - j14.5$$

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \therefore Z_p = 5.95 + j4.21$$

$$\text{Total } Z = Z_p + Z_3 = 13.95 + j8.55$$

9820246760 / 9769479368

navlakhi.mobi

navlakhi.com

Be With the Best

$$\begin{aligned}
 V_{AB} &= IZ \\
 &= (1.5 - j14.5)(13.95 + j8.55) \\
 &= 144.9 - j189.45 = 238.51 \angle -52.59^\circ
 \end{aligned}$$

Q48) Let $Z_1 = R = 30 \Omega$

$$V = 110V$$

$$f = 50\text{Hz}$$

$$I = 5A$$

Let $Z_2 = -jX_c$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{30} - \frac{j}{X_c} = \frac{1}{30} + \frac{j}{X_c} = \frac{X_c + j30}{30X_c}$$

$$\therefore Z = \frac{30X_c}{X_c + j30} \times \frac{(X_c - j30)}{(X_c - j30)} = \frac{30X_c^2}{X_c^2 + 900} - j\frac{900X_c}{X_c^2 + 900}$$

$$\therefore |Z| = \sqrt{\left(\frac{30X_c^2}{X_c^2 + 900}\right)^2 + \left(\frac{900X_c}{X_c^2 + 900}\right)^2}$$

$$\therefore |V| = |I| |Z|$$

$$\therefore 110 = 5 \times \sqrt{\frac{900X_c^4 + 810000X_c^2}{(X_c^2 + 900)^2}}$$

$$\therefore 484(X_c^2 + 900)^2 = 900X_c^4 + 810000X_c^2$$

$$484X_c^4 + 871200X_c^2 + 392040000 = 900X_c^4 + 810000X_c^2$$

$$\therefore 416X_c^4 - 61200X_c^2 - 392040000 = 0$$

$$\therefore X_c^2 = 1047.12 \Omega$$

$$\therefore X_c = 32.36 \Omega$$

$$X_c = \frac{1}{2\pi f C} \quad \therefore 32.36 = \frac{1}{2\pi \times 50 \times C} \quad \therefore C = 9.84 \times 10^{-5} \text{F}$$

When $I = 4A$

$$\therefore |V| = |I| |Z|$$

$$\therefore 110 = 4 \times \sqrt{\frac{900X_c^4 + 810000X_c^2}{(X_c^2 + 900)^2}}$$

$$756.25(X_c^2 + 900)^2 = 900X_c^4 + 810000X_c^2$$

$$756.25X_c^4 + 1361250X_c^2 + 612562500 = 900X_c^4 + 810000X_c^2$$

$$143.75X_c^4 - 551250X_c^2 - 612562500 = 0$$

$$\therefore X_c^2 = 4734.78 \Omega$$

$$\therefore X_c = 68.81 \Omega$$

$$X_c = \frac{1}{2\pi f_1 C}$$

$$\therefore 68.81 = \frac{1}{2\pi f_1 \times 9.84 \times 10^{-5}}$$

$$\therefore f_1 = 23.51 \text{ Hz}$$

Q49) For coil A:-

$$I_1 = 2 \text{ A}$$

$$\text{Pf}_1 = \cos \phi_1 = 0.8 \text{ (lag)}$$

$$V_1 = 10 \text{ V}$$

$$Z_1 = \frac{V_1}{I_1} = \frac{10}{2} = 5 \Omega$$

$$\cos \phi_1 = \frac{R_1}{Z_1}$$

$$\therefore 0.8 = \frac{R_1}{5} \therefore R_1 = 4 \Omega$$

$$Z_1 = \sqrt{R_1^2 + X_{L1}^2}$$

$$\therefore 5 = \sqrt{(4)^2 + X_{L1}^2}$$

$$\therefore X_{L1} = 3 \Omega$$

For coil B:-

$$I_2 = 2 \text{ A}$$

$$\text{Pf}_2 = \cos \phi_2 = 0.7 \text{ (lag)}$$

$$V_2 = 5 \text{ V}$$

$$Z_2 = \frac{V_2}{I_2} = \frac{5}{2} = 2.5 \Omega$$

$$\cos \phi_2 = \frac{R_2}{Z_2}$$

$$\therefore 0.7 = \frac{R_2}{2.5} \therefore R_2 = 1.75 \Omega$$

$$Z_2 = \sqrt{R_2^2 + X_{L2}^2}$$

$$\therefore 2.5 = \sqrt{(1.75)^2 + X_{L2}^2}$$

$$\therefore X_{L2} = 1.79 \Omega$$

(i) When coil A and B are connected in series

$$\therefore Z_1 = R_1 + jX_{L1} = 4 + j3$$

$$Z_2 = R_2 + jX_{L2} = 1.75 + j1.79$$

$$\text{Total } Z = Z_1 + Z_2 = 5.75 + j4.79$$

$$I = 2 \text{ A}$$

$$V = I \cdot Z = 11.5 + j9.58 = 14.97 \angle 39.8^\circ$$

(ii) When coil A and B are connected in parallel

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\therefore Z = 2.11 + j0.57$$

$$I = 2 \text{ A}$$

$$V = I \cdot Z = 4.22 + j1.14 = 4.36 \angle 15.17^\circ$$

$$Q50) V_L = 173.2V$$

$$W_1 = 301W$$

$$W_2 = 1327W$$

$$\begin{aligned} \text{Total power} &= W_1 + W_2 \\ &= 301 + 1327 = 1628W \end{aligned}$$

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right) = \sqrt{3} \left(\frac{301 - 1327}{301 + 1327} \right)$$

$$\therefore \phi = -47.51^\circ$$

$$\begin{aligned} \text{Total power} &= \sqrt{3} V_L I_L \cos \phi \\ \therefore 1628 &= \sqrt{3} \times 173.2 \times I_L \cos(-47.51^\circ) \end{aligned}$$

$$\therefore I_L = 8.03A$$

For star connection,

$$V_L = \sqrt{3} V_{ph}$$

$$\therefore 173.2 = \sqrt{3} V_{ph}$$

$$\therefore V_{ph} = 100V$$

$$I_L = I_{ph} = 8.03A$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{100}{8.03} = 12.45 \Omega$$

$$Q51) S = 5031 \angle 26.57^\circ VA = 4499.67 + j2250.32$$

$$V = 212.1 \angle 0^\circ = 212.1 + j0$$

Since Apparent Power = Active Power + j Reactive Power

$$\therefore \text{Active power} = 4499.67W$$

$$\text{Reactive power} = 2250.32VAR$$

$$\text{Active power} = 4499.67 = VI \cos \phi$$

$$4499.67 = 212.1 \times I \cos \phi$$

$$\therefore I \cos \phi = 21.22 \quad \text{--- (I)}$$

$$\text{Reactive power} = VI \sin \phi$$

$$2250.32 = 212.1 \times I \sin \phi$$

$$\therefore I \sin \phi = 10.61 \quad \text{--- (II)}$$

Dividing eqn (I) by eqn (II)

$$\therefore \tan \phi = 0.5$$

$$\therefore \phi = 26.57^\circ$$

Subs. in eqn (I)

$$\therefore I \cos(26.57) = 21.22$$

$$\therefore I = 23.73 \text{ A}$$

$$Z = \frac{V}{I} = \frac{212.1}{23.73} = 8.94 \Omega$$

Q52) Reactive power = 15 KVAR = 15,000 VAR

Pf = 0.8 (lag)

$$\therefore \cos \phi = 0.8 \quad \therefore \phi = 36.87^\circ \text{ (lag)}$$

Reactive power = $\sqrt{3} V_L I_L \sin \phi$

$$\therefore 15,000 = (\sqrt{3} V_L I_L) \times 0.6$$

$$\therefore \sqrt{3} V_L I_L = \frac{24,999.94}{0.6} = 41,666.57 \text{ --- (I)}$$

Total active power = $\sqrt{3} V_L I_L \cos \phi$

$$= (24,999.94) \times 0.8$$

{ Subs. from eqn (I) }

$$= 19,999.95 \text{ W}$$

$$\therefore W_1 + W_2 = 19,999.95 \text{ --- (I)}$$

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\therefore \tan 36.87 = \sqrt{3} \left(\frac{W_1 - W_2}{19,999.95} \right)$$

$$\therefore W_1 - W_2 = 8,660.27 \text{ --- (II)}$$

$$\therefore W_1 = 14,330.11 \text{ W}$$

$$W_2 = 5,669.84 \text{ W}$$

Q53) Time period is $0 < t < 2\pi$

$$\therefore 0.707 V_m = V_m \sin t$$

$$\therefore t = \pi/4, 3\pi/4$$

$$v = V_m \sin t, \quad 0 < t < \pi/4$$

$$= 0.707 V_m, \quad \pi/4 < t < 3\pi/4$$

$$= V_m \sin t, \quad 3\pi/4 < t < \pi$$

$$= 0, \quad \pi < t < 2\pi$$

$$V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} v dt = \frac{1}{2\pi} \left[\int_0^{\pi/4} V_m \sin t dt + \int_{\pi/4}^{3\pi/4} 0.707 V_m dt + \int_{3\pi/4}^{\pi} V_m \sin t dt + \int_{\pi}^{2\pi} 0 dt \right]$$

$$= \frac{1}{2\pi} \left[V_m (-\cos t)_0^{\pi/4} + 0.707 V_m (t)_{\pi/4}^{3\pi/4} + V_m (-\cos t)_{3\pi/4}^{\pi} \right]$$

$$= \frac{1}{2\pi} \left[V_m (-\cos \frac{\pi}{4} + \cos 0) + 0.707 V_m \left(\frac{\pi}{2} \right) + V_m (-\cos \pi + \cos \frac{3\pi}{4}) \right]$$

Navlakhi

$$\begin{aligned} \text{(Q54) Let } Z_1 &= 3 + j2 \\ Z_2 &= 10 + j8 \\ Z_3 &= 9 - j6 \\ V_1 &= 100V \end{aligned}$$

$$I = \frac{V_1}{Z_1} = \frac{100}{3 + j2} = 23.08 - j15.39 = 27.74 \angle -33.69^\circ$$

$$\frac{1}{Z_p} = \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\therefore Z_p = 7.25 - j0.13$$

$$\begin{aligned} V_2 = V_3 = I Z_p &= (23.08 - j15.39)(7.25 - j0.13) \\ &= 165.33 - j114.58 = 201.15 \angle -34.72^\circ \end{aligned}$$

$$I_1 = \frac{V_2}{Z_2} = \frac{165.33 - j114.58}{10 + j8} = 4.49 - j15.05 = 15.71 \angle -73.38^\circ$$

$$I_2 = \frac{V_3}{Z_3} = \frac{165.33 - j114.58}{9 - j6} = 18.59 - j0.34 = 18.6 \angle -1.03^\circ$$

$$\begin{aligned} \text{Total } Z &= Z_1 + Z_p \\ &= 3 + j2 + 7.25 - j0.13 \\ &= 10.25 + j1.87 \end{aligned}$$

$$\begin{aligned} V &= I \cdot Z \\ &= (23.08 - j15.39)(10.25 + j1.87) \\ &= 265.35 - j114.59 \\ &= 289.03 \angle -23.36^\circ \end{aligned}$$

9820246760 / 9769479368

navlakhi.mobi

navlakhi.com

Be With the Best

Q55) $R = 10 \Omega$

$L = 0.01 \text{ H}$

$C = 100 \times 10^{-6} \text{ F}$

$V(t) = 10 \sin 1000t$

$\therefore V(t) = V_m \sin \omega t$

$\therefore V_m = 10 \text{ V}, \omega = 1000 \text{ rad/sec}, V = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 \text{ V}$

i) $X_L = \omega L = 1000 \times 0.01 = 10 \Omega$

$X_C = \frac{1}{\omega C} = \frac{1}{1000 \times 100 \times 10^{-6}} = 10 \Omega$

$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(10)^2 + (10 - 10)^2} = 10 \Omega$

ii) $I = \frac{V}{Z} = \frac{7.07}{10} = 0.707$

$\text{pf} = \cos \phi = \frac{R}{Z} = \frac{10}{10} = 1$

$P = VI \cos \phi = 7.07 \times 0.707 \times 1 = 5 \text{ W}$

iii) $f_0 = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{0.01 \times 100 \times 10^{-6}}} = 159.16 \text{ Hz}$

iv) Bandwidth = R

v) Quality factor =

Q56) $i = 14.14 \sin(\omega t + \pi/6)$

Comparing with $i = I_m \sin(\omega t + \theta)$

$\therefore I_m = 14.14 \text{ A}$

$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{14.14}{\sqrt{2}} = 10 \text{ A}$

Phase angle = $\theta = \frac{\pi}{6}^\circ$

Q57) $L = 50 \times 10^{-3} \text{ H}$

$R_2 = 50 \Omega$

$C_3 = 50 \times 10^{-6} \text{ F}$

$V_L = 550 \text{ V}$

$\omega = 800 \text{ rad/sec.}$

$X_{L_1} = 2\pi f L_1 = \omega L_1 = 800 \times 50 \times 10^{-3} = 40 \Omega$

$X_{C_3} = \frac{1}{2\pi f C_3} = \frac{1}{\omega C_3} = \frac{1}{800 \times 50 \times 10^{-6}} = 25 \Omega$

Let $Z_1 = jX_{L_1} = j40 \Omega$

$Z_2 = R_2 = 50 \Omega$

$Z_3 = -jX_{C_3} = -j25 \Omega$

$\frac{1}{Z_p} = \frac{1}{Z_2} + \frac{1}{Z_3} \quad \therefore Z_p = 10 - j20$

$Z_{ph} = Z_1 + Z_p = j40 + 10 - j20 = 10 + j20 = 22.36 \angle 63.44^\circ$

Comparing with $Z_{ph} = |Z_{ph}| \angle \phi$

$\therefore \phi = 63.44^\circ \text{ (lag)}$

i) For Delta connection:-

$V_L = V_{ph} = 550 \text{ V}$

$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{550}{22.36} = 24.6 \text{ A}$

ii) $I_L = \sqrt{3} I_{ph} = 42.6 \text{ A}$

iii) $P = \sqrt{3} V_L I_L \cos \phi$
 $= \sqrt{3} \times 550 \times 42.6 \times \cos(63.44^\circ) = 10,478.45 \text{ W}$

iv) $\text{Pf} = \cos \phi = \cos 63.44^\circ = 0.4471 \text{ (lag)}$

v) Reactive power = $\sqrt{3} V_L I_L \sin \phi$
 $= \sqrt{3} \times 550 \times 42.6 \times \sin(63.44^\circ) = 20,961.51 \text{ VAR}$

Navlakhi

$$\begin{aligned} 858) \quad X_L &= 20 \Omega \\ f &= 50 \text{ Hz} \\ R &= 15 \Omega \\ V &= 200 \text{ V} \end{aligned}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(15)^2 + (20)^2} = 25 \Omega$$

$$\text{i) } \text{Pf} = \cos \phi = \frac{R}{Z} = \frac{15}{25} = 0.6 (\text{lag})$$

$$\text{ii) } I = \frac{V}{Z} = \frac{200}{25} = 8 \text{ A}$$

iii) Since current and voltage are in phase
 \therefore circuit is at resonance with capacitor in parallel with coil

$$\therefore Z_{\text{coil}} = 25 \Omega, X_L = 2\pi fL \therefore 20 = 2\pi \times 50 \times L \quad \therefore L = 0.064 \text{ H}$$

$$\therefore Z_{\text{coil}} = \sqrt{\frac{L}{C}}$$

$$\therefore 25 = \sqrt{\frac{0.064}{C}} \quad \therefore C = 1.02 \times 10^{-4} \text{ F}$$

$$\text{iv) } Z_{\text{dynamic}} = \frac{L}{RC} = \frac{0.064}{15 \times 1.02 \times 10^{-4}} = 41.83 \Omega$$

$$\frac{I}{Z_{\text{dynamic}}} = \frac{V}{Z_{\text{dynamic}}} = \frac{200}{41.83} = 4.78 \text{ A}$$

9820246760 / 9769479368

navlakhi.mobi

navlakhi.com

Be With the Best

859) $R_1 = 10 \Omega$
 $L_1 = 10 \times 10^{-3} \text{ H}$
 $R_2 = 10 \Omega$
 $C_2 = 500 \times 10^{-6} \text{ F}$
 $V = 230 \text{ V}$
 $f = 50 \text{ Hz}$

$$X_{L_1} = 2\pi f L_1 = 2\pi \times 50 \times 10 \times 10^{-3} = 3.14 \Omega$$

$$X_{C_2} = \frac{1}{2\pi f C_2} = \frac{1}{2\pi \times 50 \times 500 \times 10^{-6}} = 6.37 \Omega$$

i) $Z_1 = R_1 + jX_{L_1} = 10 + j3.14$
 $Z_2 = R_2 - jX_{C_2} = 10 - j6.37$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \therefore Z = 6.1 - j0.63 = 6.13 \angle -5.89^\circ$$

$$I = \frac{V}{Z} = \frac{230}{6.1 - j0.63} = 37.31 + j3.85 = 37.51 \angle 5.89^\circ$$

ii) $I_1 = \frac{V}{Z_1} = \frac{230}{10 + j3.14} = 20.94 - j6.57 = 21.94 \angle -17.43^\circ$

$$I_2 = \frac{V}{Z_2} = \frac{230}{10 - j6.37} = 16.36 + j10.42 = 19.4 \angle 32.5^\circ$$

iii) $\because Z_1 = 10.48 \angle 17.43^\circ \therefore \phi_1 = 17.43^\circ (\text{lag}) \therefore \text{pf}_1 = \cos \phi_1 = 0.954 (\text{lag})$

$\because Z_2 = 11.86 \angle -32.5^\circ \therefore \phi_2 = 32.5^\circ (\text{lead}) \therefore \text{pf}_2 = \cos \phi_2 = 0.844 (\text{lead})$

$\because Z = 6.13 \angle -5.89^\circ \therefore \phi = 5.89^\circ (\text{lead}) \therefore \text{pf} = \cos \phi = 0.995 (\text{lead})$

iv) $P_1 = VI_1 \cos \phi_1 = 230 \times 21.94 \times 0.954 = 4814.1 \text{ W}$


$$P_2 = VI_2 \cos \phi_2 = 230 \times 19.4 \times 0.844 = 3765.93 \text{ W}$$

Q60) Equation of semi-circle is:-

$$V^2 + t^2 = a^2$$

$$\therefore V^2 = a^2 - t^2$$
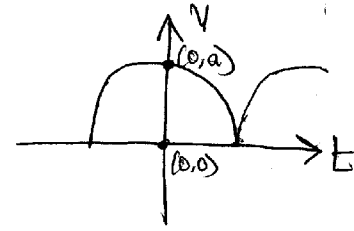
$$V = \sqrt{a^2 - t^2}, \quad -a < t < a$$



$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{2a} \int_{-a}^a V^2 dt} = \sqrt{\frac{1}{2a} \int_{-a}^a (a^2 - t^2) dt} \\ &= \frac{1}{\sqrt{2a}} \sqrt{\left[a^2 t - \frac{t^3}{3} \right]_{-a}^a} = \frac{1}{\sqrt{2a}} \sqrt{\left[a^3 - \frac{a^3}{3} + a^3 - \frac{a^3}{3} \right]} \\ &= \frac{1}{\sqrt{2a}} \left[2a^3 - \frac{2a^3}{3} \right] = \frac{1}{\sqrt{2a}} \left(\frac{4a^3}{3} \right) \end{aligned}$$

Q61) $V_R = 10V$

$V_L = 15V$

$V_C = 10V$

$$V = \sqrt{(V_R)^2 + (V_L - V_C)^2} = \sqrt{(10)^2 + (15 - 10)^2}$$

$$\therefore V = \sqrt{100 + 25} = 11.18$$

$$Pf = \cos \phi = \frac{R}{Z} = \frac{IR}{IZ} = \frac{V_R}{V} = \frac{10}{11.18} = 0.8945 (\text{lag})$$

Q62) $V_L = 400V, f = 50\text{Hz}$

$Z_{\Delta} = 8 + j6$

$Z_{\text{star}} = 4 + j3$

Converting Delta to Star

$$\therefore Z'_{\text{star}} = \frac{Z_{\Delta}}{3} = \frac{8 + j6}{3} = 2.67 + j2$$

Since Z_{star} and Z'_{star} are in parallel.

$$\frac{1}{Z_{ph}} = \frac{1}{Z_{star}} + \frac{1}{Z'_{star}} = \frac{1}{4+j3} + \frac{1}{2.67+j2}$$

$$\therefore Z_{ph} = 1.6 + j1.2 = 2 \angle 36.87^\circ$$

For star connection

$$V_L = \sqrt{3} V_{ph}$$

$$\therefore V_{ph} = \frac{400}{\sqrt{3}} = 230.94 \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{2} = 115.47 \text{ A}$$

$$I_L = I_{ph} = 115.47 \text{ A}$$

Comparing with $Z_{ph} = |Z_{ph}| \angle \phi$

$$\therefore \phi = 36.87^\circ (\text{lag})$$

$$\therefore \text{pf} = \cos \phi = \cos 36.87^\circ = 0.8 (\text{lag})$$

$$\begin{aligned} \text{Active power} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 400 \times 115.47 \times 0.8 \\ &= 63,999.97 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= \sqrt{3} V_L I_L \sin \phi \\ &= \sqrt{3} \times 400 \times 115.47 \times \sin 36.87^\circ \\ &= 48,000.09 \text{ VAR} \end{aligned}$$

$$Q63) V = 200 \angle 25^\circ = 181.26 + j84.52$$

$$I_1 = 10 \angle 45^\circ = 7.07 + j7.07$$

$$I_2 = 20 \angle -30^\circ = 17.32 - j10$$

$$Z_1 = \frac{V}{I_1} = \frac{181.26 + j84.52}{7.07 + j7.07} = 18.8 - j6.84 = 20 \angle -20^\circ$$

$$Z_2 = \frac{V}{I_2} = \frac{181.26 + j84.52}{17.32 - j10} = 5.74 + j8.19 = 10 \angle 55^\circ$$

Navlakhi

For Branch Z_1 :-

Comparing with $Z_1 = |Z_1| \angle \phi_1$

$$\therefore \phi_1 = 20^\circ \text{ (lead)}$$

Comparing with $Z_2 = |Z_2| \angle \phi_2$

$$\therefore \phi_2 = 55^\circ \text{ (lag)}$$

$$\begin{aligned} \text{Apparent power} &= VI_1 \\ &= 200 \times 10 = 2000 \text{ VA} = 2 \text{ kVA} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= VI_1 \sin \phi_1 \\ &= 200 \times 10 \times \sin 20^\circ = 684.04 \text{ VAR} = 0.684 \text{ kVAR} \end{aligned}$$

$$\begin{aligned} \text{Active power} &= VI_1 \cos \phi_1 \\ &= 200 \times 10 \times \cos 20^\circ = 1879.39 \text{ W} = 1.879 \text{ kW} \end{aligned}$$

For Branch Z_2 :-

Comparing with $Z_2 = |Z_2| \angle \phi_2$

$$\therefore \phi_2 = 55^\circ \text{ (lag)}$$

$$\begin{aligned} \text{Apparent power} &= VI_2 \\ &= 200 \times 20 = 4000 \text{ VA} = 4 \text{ kVA} \end{aligned}$$

$$\begin{aligned} \text{Reactive power} &= VI_2 \sin \phi_2 \\ &= 200 \times 20 \sin 55^\circ = 3276.61 \text{ VAR} = 3.276 \text{ kVAR} \end{aligned}$$

$$\begin{aligned} \text{Active power} &= VI_2 \cos \phi_2 \\ &= 200 \times 20 \cos 55^\circ = 2294.31 \text{ W} = 2.294 \text{ kW} \end{aligned}$$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \therefore Z = 6.92 + j4.29 = 8.14 \angle 31.83^\circ$$

$$\begin{aligned} \text{Comparing with } Z &= |Z| \angle \phi \\ \therefore \phi &= 31.83^\circ \text{ (lag)} \\ \text{pf} &= \cos \phi = 0.85 \text{ (lag)} \end{aligned}$$

9820246760 / 9769479368

navlakhi.mobi

navlakhi.com

Be With the Best

Q64) Apparent power = 10KVA = 10000 VA

$$\therefore VI = 10,000 \text{ --- (I)}$$

$$Pf = \cos \phi = 0.342$$

$$\therefore \phi = 70^\circ 6'$$

$$\begin{aligned} \text{Total power} &= VI \cos \phi \\ &= 10,000 \times \cos 70^\circ = 3420.2 \text{ W} \end{aligned}$$

$$\therefore W_1 + W_2 = 3420.2 \text{ --- (II)}$$

i) p.f. is leading

$$\tan \phi = -\sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\tan 70^\circ = -\sqrt{3} \left(\frac{W_1 - W_2}{3420.2} \right)$$

$$\therefore W_1 - W_2 = -5425.32 \text{ --- (III)}$$

Solving eqns. (II) & (III)

$$\therefore W_1 = -1,002.56 \text{ W}$$

$$W_2 = 4,422.76 \text{ W}$$

ii) p.f. is lagging

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\tan 70^\circ = \sqrt{3} \left(\frac{W_1 - W_2}{3420.2} \right)$$

$$\therefore W_1 - W_2 = 5425.32 \text{ --- (IV)}$$

Solving eqns. (II) & (IV)

$$\therefore W_1 = 4,422.76$$

$$W_2 = -1,002.56$$

Q65) $V = 125V$
 $f = 50\text{Hz}$
 $I = 2.2A$
 $P_R = 96.8W$

$$P_R = I^2 R$$

$$96.8 = 2.2^2 \times R$$

$$\therefore R = 20\Omega$$

$$Z = \frac{V}{I} = \frac{125}{2.2} = 56.82$$

$$Z = \sqrt{R^2 + X_C^2} \quad \therefore 56.82 = \sqrt{(20)^2 + X_C^2}$$

$$\therefore X_C = 53.18\Omega$$

$$X_C = \frac{1}{2\pi f C} \quad \therefore 53.18 = \frac{1}{2\pi \times 50 \times C}$$

$$\therefore C = 5.99 \times 10^{-5} F$$

Q66) $A \equiv (0, -20)$
 $B \equiv (2\pi, 140)$

$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{140 + 20}{2\pi} = \frac{80}{\pi}$$

Eqn. of line is $y - y_1 = m(x - x_1)$
 $\therefore v = \frac{80}{\pi}(t) - 20$

$$\therefore v = \frac{80t}{\pi} - 20, \quad 0 < t < 2\pi$$

$$V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} v dt = \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{80}{\pi}t - 20 \right] dt$$

$$= \frac{1}{2\pi} \left[\frac{80}{\pi} \frac{t^2}{2} - 20t \right]_0^{2\pi} = \frac{1}{2\pi} \left[\frac{80}{\pi} \times 4\pi^2 - 40\pi \right] = 60$$

$$V_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \left(\frac{80t}{\pi} - 20 \right)^2 dt} = \sqrt{\frac{1}{2\pi} \left[\frac{80t}{\pi} - 20 \right]_0^{2\pi} \times \frac{1}{3}} = \sqrt{\frac{1}{2\pi} \left[\frac{80 \times 2\pi}{\pi} - 20 \right] \times \frac{1}{3}} = \sqrt{\frac{1}{2\pi} \left[140 \right] \times \frac{1}{3}} = 75.61$$

$$\begin{aligned} \text{Q67)} \quad R &= 5\Omega \\ C &= 20 \times 10^{-6} \text{ F} \\ V &= 10\text{V} \\ \omega &= 1000 \text{ rad/sec.} \end{aligned}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \times 20 \times 10^{-6}} = 50\Omega$$

Since voltage across resistor is maximum

\therefore Circuit is at series resonance

$$\therefore V_R = V = 10\text{V}$$

$$\therefore V_R = IR$$

$$\therefore 10 = 5I \quad \therefore I = 2\text{A}$$

$$V_C = IX_C = 2 \times 50 = 100\text{V}$$

$$V_L = V_C = 100\text{V}$$

Q68)

$$Q71) V(t) = 245 \sin(1000t + 20)$$

$$R = 15 \Omega$$

$$L = 0.1 \text{ H}$$

Comparing with $V(t) = V_m \sin(\omega t + \theta_1)$

$$\therefore V_m = 245 \text{ V}, \omega = 1000 \text{ rad/sec}, \theta_1 = 20^\circ$$

Since phase angle between $V(t)$ and $i(t)$ equal to zero

\therefore Circuit is at series resonance

$$\therefore X_L = X_C$$

$$\therefore X_L = 2\pi f_0 L = \omega L = 1000 \times 0.1 = 100 \Omega$$

$$\therefore X_C = 100 \Omega$$

$$\therefore X_C = \frac{1}{2\pi f_0 C} = \frac{1}{\omega C}$$

$$\therefore 100 = \frac{1}{1000 \times C} \quad \therefore C = 10^{-5} \text{ F}$$

$$Q70) V_L = 220 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$\text{O/P power} = 11.2 \text{ kW} = 11,200 \text{ W}$$

$$\eta = 88\%$$

$$I_L = 38 \text{ A}$$

$$\eta = \frac{\text{O/P power}}{\text{I/P power}} \times 100$$

$$\therefore 88 = \frac{11,200}{\text{I/P power}} \times 100$$

$$\therefore \text{I/P power} = 12,727.27 \text{ W}$$

$$\therefore W_1 + W_2 = 12.73 \text{ — (I)}$$

$$\text{I/P power} = \sqrt{3} V_L I_L \cos \phi$$

$$12,727.27 = \sqrt{3} \times 220 \times 38 \times \cos \phi$$

$$\therefore \phi = 28.48^\circ \text{ (lag)}$$

$$\text{Pf} = \cos \phi = 0.88 \text{ (lag)}$$

$$\tan \phi = \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right)$$

{For lagging Pf}

$$\therefore \tan 28.48 = \sqrt{3} \left(\frac{W_1 - W_2}{12.73} \right)$$

$$\therefore W_1 - W_2 = 3.99 \text{ — (II)}$$

Solving eqns. (I) & (II) simultaneously

$$\therefore W_1 = 8.36 \text{ kW}$$

$$W_2 = 4.37 \text{ kW}$$

Q69) $V = 150 \text{ V}$

$$I = 32 \text{ A}$$

Let $Z_1 = 5 \Omega$, $Z_2 = j4 \Omega$

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\therefore Z_p = 1.95 + j2.44$$

$$\text{Total } Z = Z_p + R = (1.95 + R) + j2.44 \quad \therefore |Z| = \sqrt{(1.95 + R)^2 + 2.44^2}$$

$$|V| = |I||Z|$$

$$\therefore 150 = 32 \sqrt{(1.95 + R)^2 + 2.44^2}$$

$$\therefore 150 = 32 \sqrt{(1.95 + R)^2 + 2.44^2}$$

$$\left(\frac{150}{32}\right)^2 = (1.95 + R)^2 + 2.44^2$$

$$\therefore R = 2.05 \Omega$$

$$\begin{aligned} \therefore \text{Total } Z &= (1.95 + 2.05) + j2.44 \\ &= 4 + j2.44 \\ &= 4.69 / 31.38^\circ \end{aligned}$$

Comparing with $Z = |Z| \angle \phi$

$$\therefore \phi = 31.38^\circ \text{ (lag)}$$

$$\therefore \text{pf} = \cos \phi$$

$$= \cos 31.38^\circ$$

$$= 0.8537 \text{ (lag)}$$

Navlakhi

navlakhi.mobi

navlakhi.com

$$Q72) V_s = 60 \sin \omega t \quad \therefore V_m = 60V \quad \therefore V_s = \frac{V_m}{\sqrt{2}} = \frac{60}{\sqrt{2}} = 42.43V$$

$$Z_1 = 50 \Omega$$

$$Z_2 = j40 \Omega$$

$$Z_3 = -j80 \Omega$$

$$I_1 = \frac{V_s}{Z_1} = \frac{42.43}{50} = 0.85A = 0.85 \angle 0^\circ A$$

$$I_2 = \frac{V_s}{Z_2} = \frac{42.43}{j40} = -j1.06A = 1.06 \angle -90^\circ A$$

$$I_3 = \frac{V_s}{Z_3} = \frac{42.43}{-j80} = j0.53 = 0.53 \angle 90^\circ A$$

$$\text{Total } I = I_1 + I_2 + I_3 \quad (\text{Only in rectangular or cartesian form})$$

$$\therefore I = 0.85 - j1.06 + j0.53$$

$$I = 0.85 - j0.53 = 1 \angle -31.93A$$


$$\therefore Y = \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$\therefore Y = 0.02 - j0.0125$$

$$\text{Total } I = V_s \times Y$$

$$= 42.43 \times (0.02 - j0.0125)$$
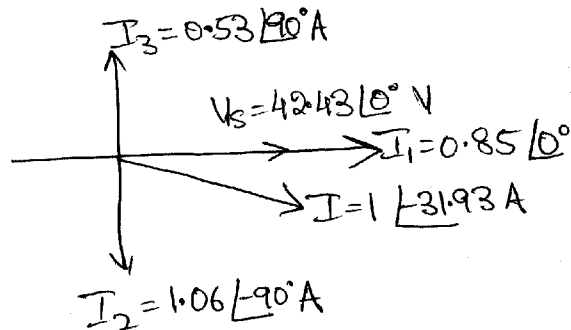
$$\therefore I = 0.85 - j0.53 = 1 \angle -31.93A$$



Be With the Best

9820246760 / 9769479368

Navlakhi

$$Q73) I_1 = 6 \sin\left(\omega t + \frac{\pi}{3}\right)$$

$$I_2 = 5 \cos\left(\omega t + \frac{\pi}{3}\right) = 5 \sin\left(\omega t + \frac{\pi}{3} + \frac{\pi}{2}\right)$$

$$= 5 \sin\left(\omega t + \frac{5\pi}{6}\right)$$

$$I_3 = 3 \cos\left(\omega t + \frac{\pi}{3}\right) = 3 \sin\left(\omega t + \frac{\pi}{3} + \frac{\pi}{2}\right)$$

$$= 3 \sin\left(\omega t + \frac{5\pi}{6}\right)$$

Comparing with $I_1 = I_{m1} \sin(\omega t + \theta_1)$

$$\therefore I_{m1} = 6A, \theta_1 = \frac{\pi}{3} = 60^\circ, I_{rms1} = \frac{I_{m1}}{\sqrt{2}} = \frac{6}{\sqrt{2}} = 4.24A$$

Comparing with $I_2 = I_{m2} \sin(\omega t + \theta_2)$

$$\therefore I_{m2} = 5A, \theta_2 = \frac{5\pi}{6} = 150^\circ, I_{rms2} = \frac{I_{m2}}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.54A$$

Comparing with $I_3 = I_{m3} \sin(\omega t + \theta_3)$

$$\therefore I_{m3} = 3A, \theta_3 = \frac{5\pi}{6} = 150^\circ, I_{rms3} = \frac{I_{m3}}{\sqrt{2}} = \frac{3}{\sqrt{2}} = 2.12A$$

$$I_1 = I_{rms1} \angle \theta_1 = 4.24 \angle 60^\circ = 2.12 + j3.67$$

$$I_2 = I_{rms2} \angle \theta_2 = 3.54 \angle 150^\circ = -3.07 + j1.77$$

$$I_3 = I_{rms3} \angle \theta_3 = 2.12 \angle 150^\circ = -1.84 + j1.06$$

$$\therefore I_1 + I_2 + I_3 + I_4 = 0$$

$$\therefore 2.12 + j3.67 - 3.07 + j1.77 - 1.84 + j1.06 + I_4 = 0$$

$$\therefore I_4 = 2.79 - j6.5 = 7.07 \angle -66.77^\circ$$

$$\therefore I_{m4} = I_{rms4} \times \sqrt{2} = 7.07 \times \sqrt{2} = 10A$$

\therefore Current in wire S is:-

$$I_4 = 10 \sin(\omega t - 66.77^\circ)$$

9820246760 / 9769479368

navlakhi.mobi

navlakhi.com

Be With the Best

Navlakhi

9820246760 / 9769479368

navlakhi.com navlakhi.mobi

Q74) $L = 0.2 \text{ H}$

$R = 20 \Omega$

$C = 200 \times 10^6 \text{ F}$

$V = 230 \text{ V}$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \frac{1}{2\pi} \sqrt{\frac{1}{0.2 \times 200 \times 10^6} - \frac{20^2}{0.2^2}}$$

$\therefore f_0 = 19.49 \text{ Hz}$

$X_L = 2\pi f_0 L = 2\pi \times 19.49 \times 0.2 = 24.49 \Omega$

$X_C = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 19.49 \times 200 \times 10^6} = 40.83 \Omega$

Let $Z_1 = R + jX_L = 20 + j24.49$

$Z_2 = -jX_C = -j40.83$

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{20 + j24.49} + \frac{1}{-j40.83}$$

$Z = 50 \Omega$

$I = \frac{V}{Z} = \frac{230}{50} = 4.6 \text{ A}$

~~$V_L = I X_L = 4.6 \times 24.49 = 112.65 \text{ V}$~~

~~$V_C = I X_C = 4.6 \times 40.83 = 187.82 \text{ V}$~~

$V_2 = V_C = V = 230 \text{ V}$

$V_1 = V_{\text{coil}} = V = 230 \text{ V}$

$I_1 = \frac{V_1}{Z_1} = \frac{230}{20 + j24.49} = 4.6 - j5.63 = 7.27 \angle -50.76^\circ$


$V_L = I_1 X_L = (4.6 - j5.63)(j24.49) = 137.88 + j112.65 = 178.05 \angle 39.25^\circ$

$V_R = I_1 R = (4.6 - j5.63)(20) = 92 - j112.6 = 145.41 \angle -50.75^\circ$

Phasor Diagrams:- $I_2 = 5.63 \angle 90^\circ$

$I_2 = \frac{V_2}{Z_2}$

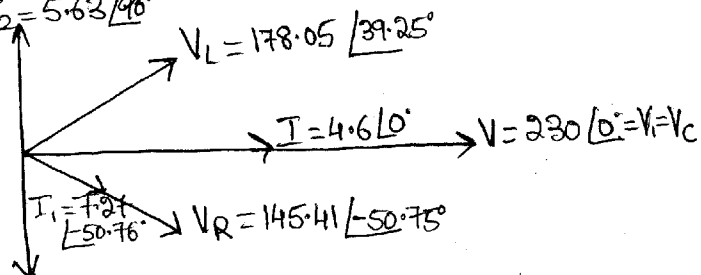$= \frac{230}{-j40.83} = +j5.63 = 5.63 \angle 90^\circ$



Be With the Best

$$Q75) p.f_{coil} = 0.6$$

$$C = 100 \times 10^{-6} \text{ F}$$

$$f = 50 \text{ Hz}$$

$$V_{coil} = V_c$$

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83 \Omega$$

$$\therefore V_{coil} = V_c$$

$$\therefore I Z_{coil} = I \cdot X_c$$

$$\therefore Z_{coil} = X_c$$

$$\therefore Z_{coil} = 31.83 \Omega$$

$$\cos \phi_{coil} = \frac{R}{Z_{coil}}$$

$$\therefore 0.6 = \frac{R}{31.83}$$

$$\therefore R = 19.1 \Omega$$

$$Z_{coil} = \sqrt{R^2 + X_L^2}$$

$$\therefore 31.83 = \sqrt{(19.1)^2 + X_L^2}$$

$$\therefore X_L = 25.46 \Omega$$

$$X_L = 2\pi f L$$

$$25.46 = 2\pi \times 50 \times L$$

$$\therefore L = 0.081 \text{ H}$$