

Q.P. Code : 25676

( 3 Hours)


[ Total Marks : 80

- N.B. :** (1) **Question No.1** is compulsory.  
 (2) Solve **any three** from remaining questions.  
 (3) Assume suitable **data** if necessary.  
 (4) **Figures** to the **right** indicate **full marks**.

1. Answer **any Five** :

20

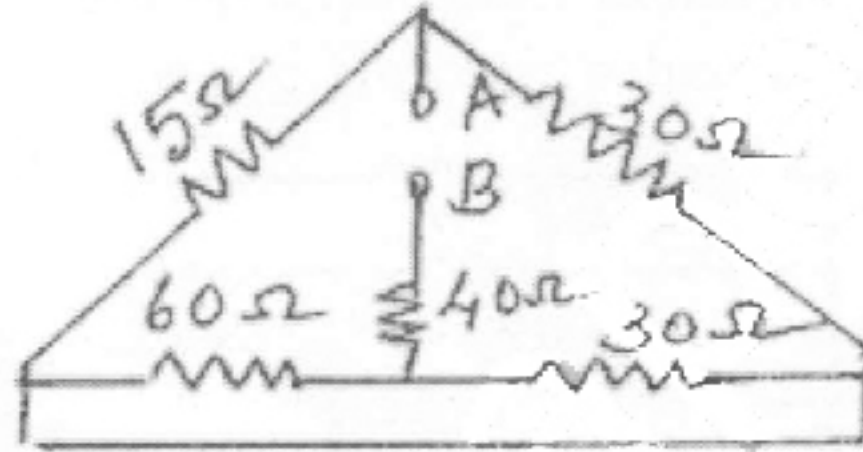
- (a) What is the difference between ideal source and actual source? Illustrate the concept using the V-I characteristics of voltage and current source.  
 (b) In a balanced three phase circuit the power factor is 0.866. What will be the ratio of two wattmeter reading if the power is measured using two wattmeters.  
 (c) Calculate  $R_{AB}$ .



- (b) Derive the equation for resonance frequency for a parallel circuit in which a capacitor is connected in parallel with a coil having resistance  $R$  and inductive reactance  $X_L$ . What is the resonance frequency if inductor is ideal?  
 (e) What are the classifications of DC motor? Specify one application for each one.  
 (f) Derive emf equation of a single phase transformer.

2. (a) Using mesh analysis find current through  $5\Omega$ .

08

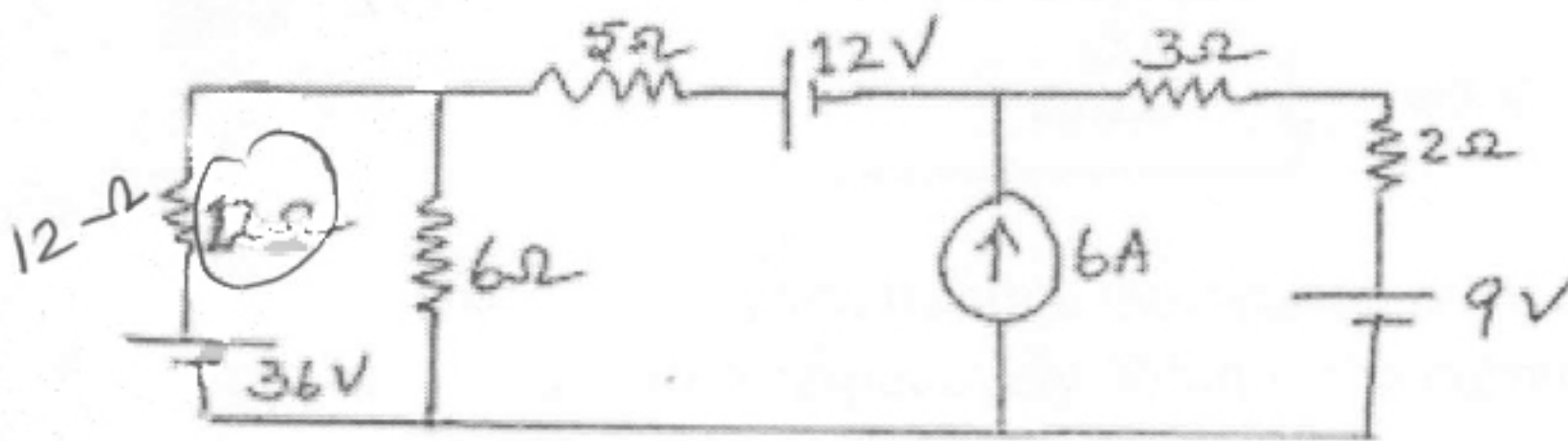


- (b) An emf of 250 V is applied to an impedance  $Z_1 = (12.5 + j20)\Omega$ . An impedance  $Z_2$  is added in series with  $Z_1$ , the current become half of the original and lead the supply voltage by  $20^\circ$ . Determine  $Z_2$ .

08

TURN OVER

- (c) Determine the potential difference  $V_{AB}$  for the given network.


04

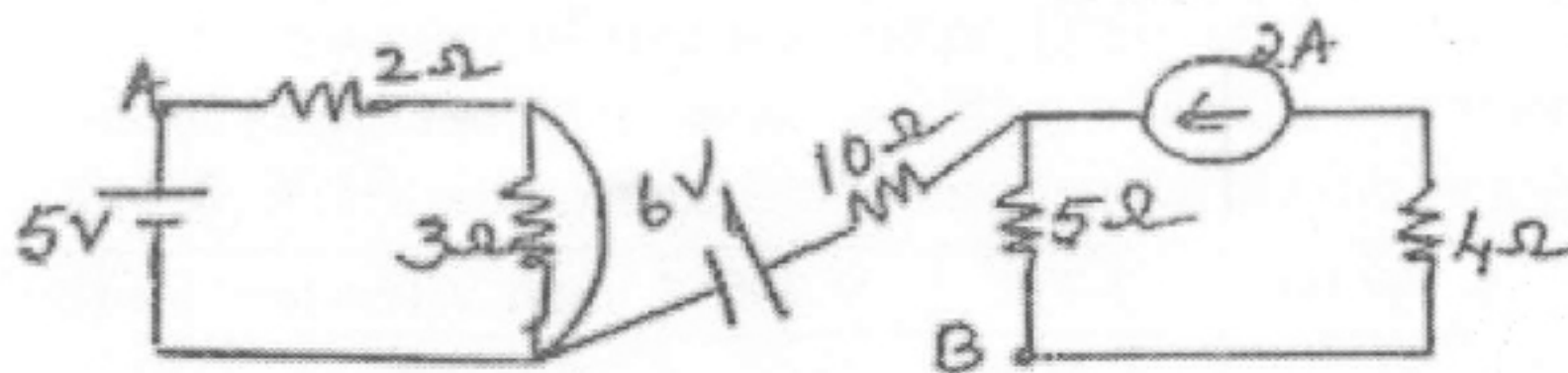

3. (a) When a voltage of 100 V, 50 Hz is applied to an impedance A current taken is 8 A lagging and power is 120 W. When it is connected to an impedance B the current is 10 A leading and power is 500 W. What current and power will be taken if it is applied to the two impedances connected in series.
- (b) Find current through 10 Ω using Thevenin's theorem.

08

08

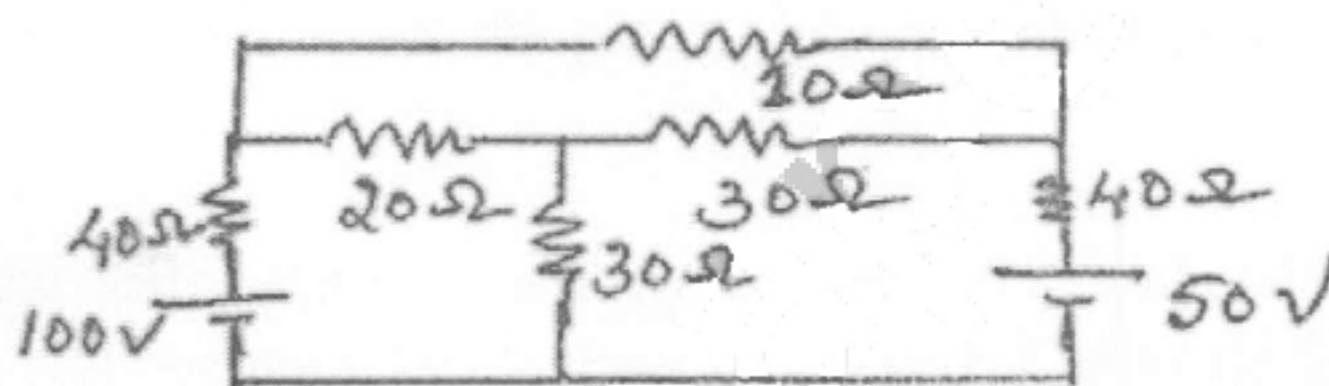


- (c) With the help of equivalent circuit of a single phase transformer show how total copper loss can be represented in primary of a transformer.

04

4. (a) Find  $V_1$  using super position theorem.

08

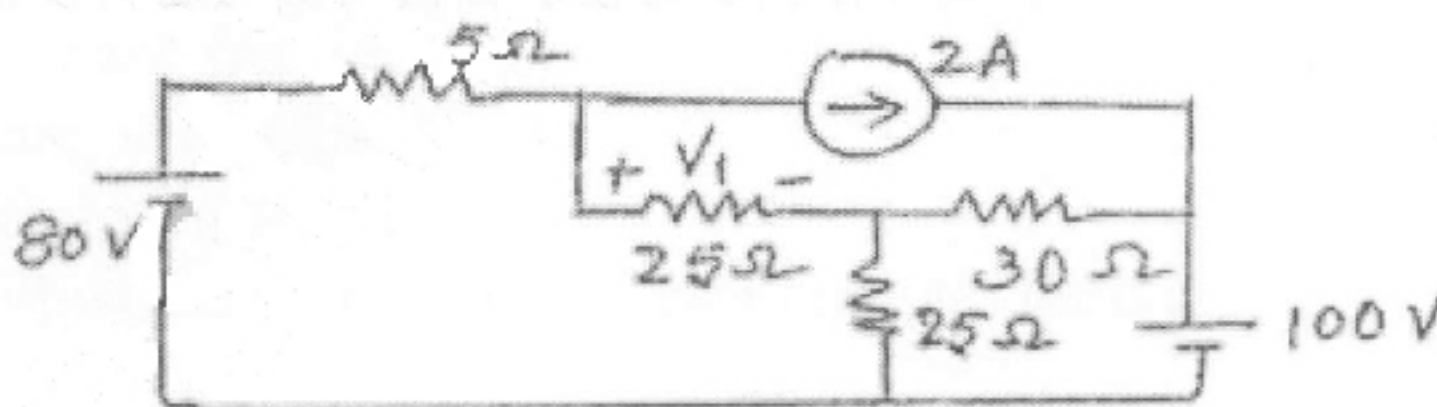

- (b) In an R-L-C parallel circuit the current through the resistor, inductor (pure) and capacitor are 20 A, 15 A and 40 A respectively. What is the current taken from the supply? Draw phasor diagram.

04

- (c) Two sinusoidal sources of emf have rms value  $E_1$  and  $E_2$ . When connected in series, with a phase displacement  $\alpha$  the resultant voltage read on an electro-dynamometer voltmeter is 41.1 V and with one source reversed 17.52 V. When the phase displacement made zero a reading of 42.5 V is observed. Calculate  $E_1$ ,  $E_2$  and  $\alpha$ .

08

TURN OVER



5. (a) Prove that the power in a balanced three phase delta connected circuit can be deduced from the readings of two wattmeter. Draw relevant connections and vector diagrams. Draw a table to show the effect of power factor on wattmeter. 08
- (b) A 5 kVA 200/400, 50 Hz single phase transformer gave the following test results. 08

OC test on LV side	200 V	0.7 A	60 W
SC test on HV side	22 V	0.16 A	120 W

- (i) Draw the equivalent circuit of the transformer and insert all parameter values.
- (ii) Efficiency at 0.9 pf lead and rated load.
- (iii) Current at which efficiency is maximum.
- (c) Prove that if the phase impedances are same, power drawn by a balanced delta connected load is three times the power drawn by the balanced star connected load. 04
6. (a) Three identical coils each having a reactance of  $20 \Omega$  and resistance of  $10 \Omega$  are connected in star across a 440 V three phase line. Calculate for each method : 08
- (i) Line current and phase current.
- (ii) Active, reactive and apparent power.
- (iii) Reading of each wattmeter connected to measure the power.
- (b) A series resonant circuit has an impedance of  $500 \Omega$  at resonant frequency. The cut off frequency observed are 10 kHz and 100 Hz. Determine : 06
- (i) Resonant frequency.
- (ii) Value of R, L and C.
- (iii) Q factor at resonance.
- (c) Draw and illustrate transformer phasor diagram for lagging power factor. 06