

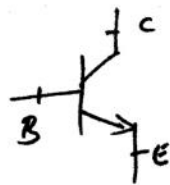


## BJT PREREQUISITES


If C-E or C-C the A.C. Model will be

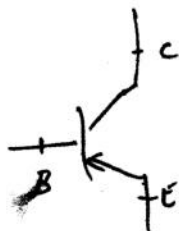


≡

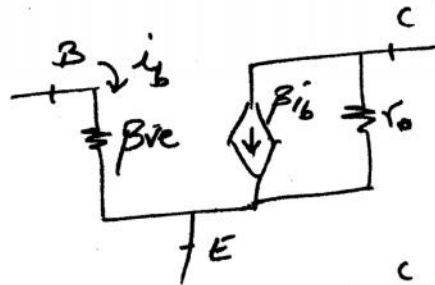


≡

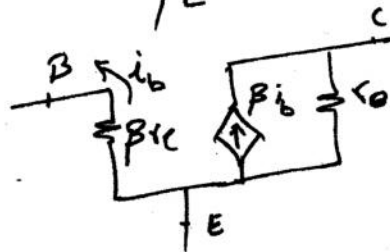


If C-B then the A.C. Model is

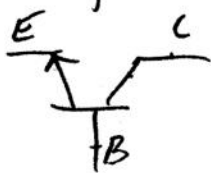

≡

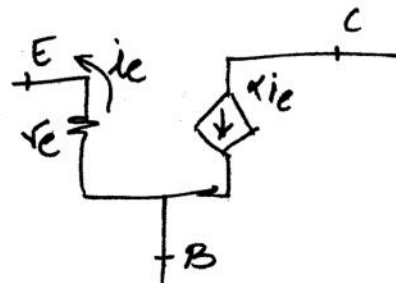


≡

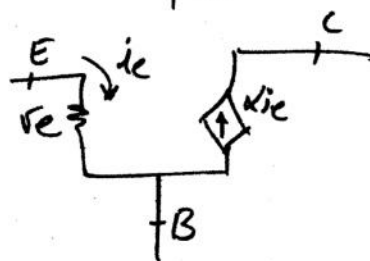

$$r_e = \frac{26mV}{I_{CQ}}$$



## (I) FIXED BIAS

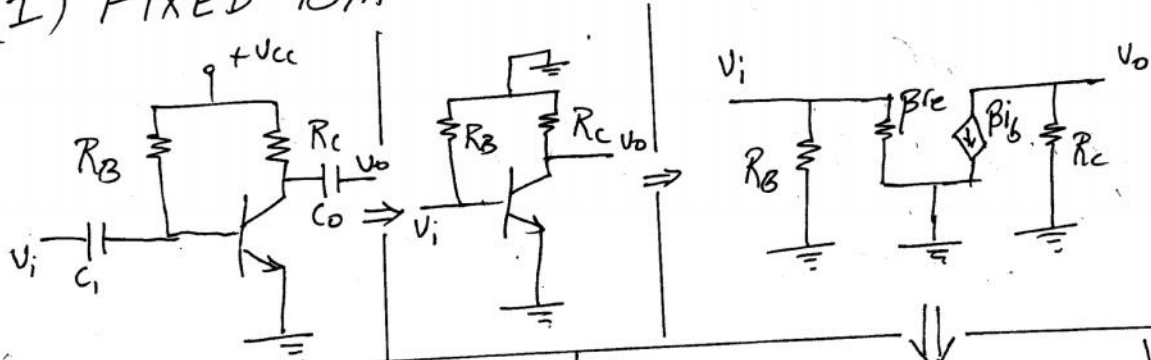


$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta i_b R_C}{i_b \beta r_e}$$

$$A_v = -\frac{R_C}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

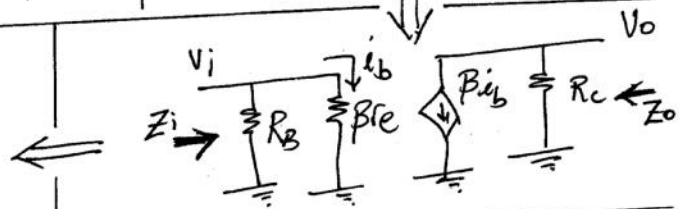


$$Z_i = R_B \parallel \beta r_e \quad Z_o = R_C \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta i_b (R_C \parallel r_o)}{i_b \beta r_e}$$

$$A_v = -\frac{R_C \parallel r_o}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

### Effect of $R_s$ & $R_L$ :

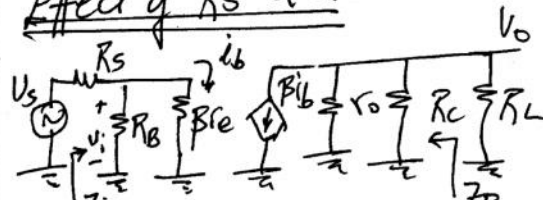

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = r_o \parallel R_C$$


$$A_v = \frac{V_o}{V_i} = -\frac{R_C \parallel r_o \parallel R_L}{r_e}$$

$$A_{v_s} = \frac{+A_v Z_i}{Z_i + R_s}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$


$$A_{i_s} = -\frac{A_{v_s} (Z_i + R_s)}{R_L}$$

### Effect of $r_o$ :

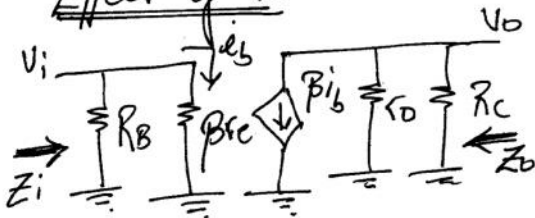



## (II) EMITTER - STABILIZED BIAS

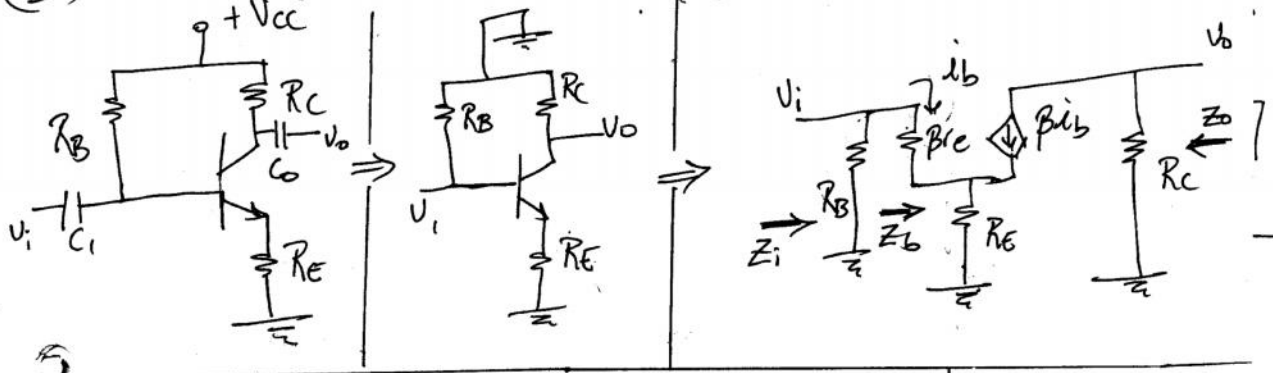

$$Z_i = R_B \parallel Z_B$$

$$Z_B = \beta r_e + (1 + \beta) R_E$$

$$\approx \beta (r_e + R_E)$$


$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b R_C}{i_b Z_B}$$

$$A_v \approx -\frac{R_C \beta}{Z_B}$$

$$A_v \approx -\frac{R_C}{r_e + R_E}$$

$$A_i = \frac{-A_v Z_i}{R_C}$$

Effect of  $r_o$ :

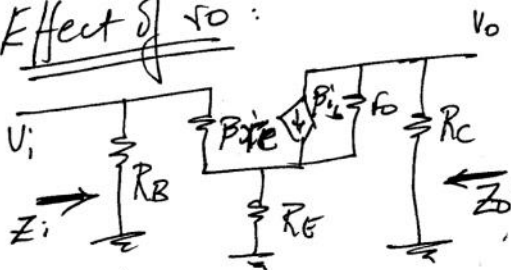

$$Z_i = R_B \parallel Z_B$$

$$Z_B = \beta r_e + (1 + \beta) R_E$$

$$\approx \beta (r_e + R_E)$$

$$A_v = \frac{V_o}{V_i} \approx \frac{-\beta i_b (R_C \parallel r_o)}{i_b Z_B}$$

$$A_v \approx -\frac{(R_C \parallel r_o)}{r_e + R_E}$$

$$A_i = \frac{-A_v Z_i}{R_C}$$

Effect of  $R_s$  &  $R_L$ :

$$Z_i = R_B \parallel Z_B$$

$$Z_B = \beta r_e + (1 + \beta) R_E$$


$$\approx \beta (r_e + R_E)$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_C \parallel r_o)}{i_b Z_B}$$

$$A_v \approx -\frac{(R_C \parallel r_o) \parallel R_L}{r_e + R_E}$$




$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_v$$
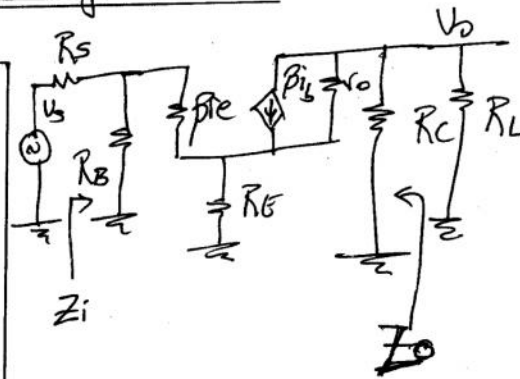
$$A_{v_s} = \frac{-A_v (Z_i + R_s)}{R_L}$$





### (III) VOLTAGE-DIVIDER BIAS :

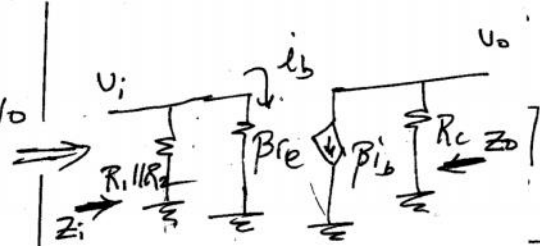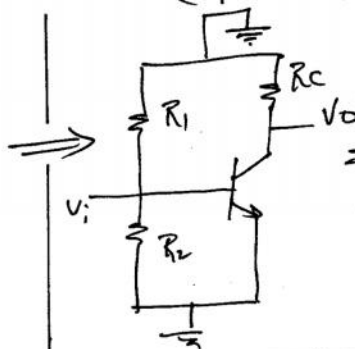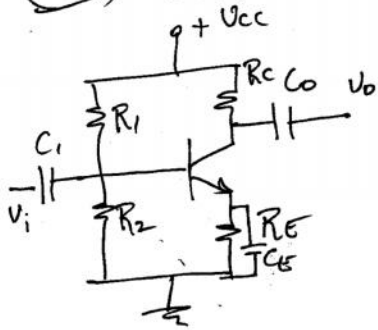

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$Z_o = R_c$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_c)}{\beta r_e i_b}$$

$$A_v = -\frac{R_c}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_c}$$

Effect of  $r_o$  :



$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$


$$Z_o = R_c \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_c \parallel r_o)}{\beta r_e i_b}$$

$$A_v = -\frac{R_c \parallel r_o}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_c}$$

Effect of  $R_s$  &  $R_L$  :

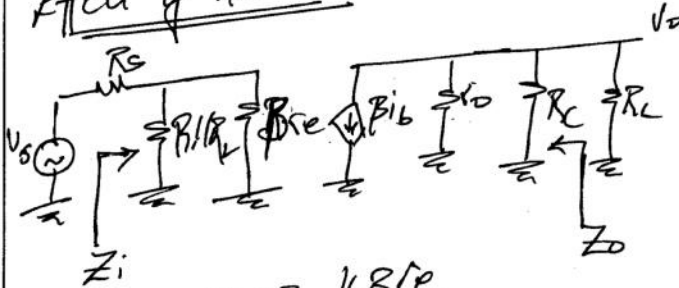

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$Z_o = R_c \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_c \parallel r_o \parallel R_L)}{\beta r_e i_b}$$


$$A_v = -\frac{R_c \parallel r_o \parallel R_L}{r_e}$$

$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_v$$

$$A_i = -\frac{A_v Z_i}{R_c}$$

$$A_{i_s} = -\frac{A_{v_s} (Z_i + R_s)}{R_c}$$
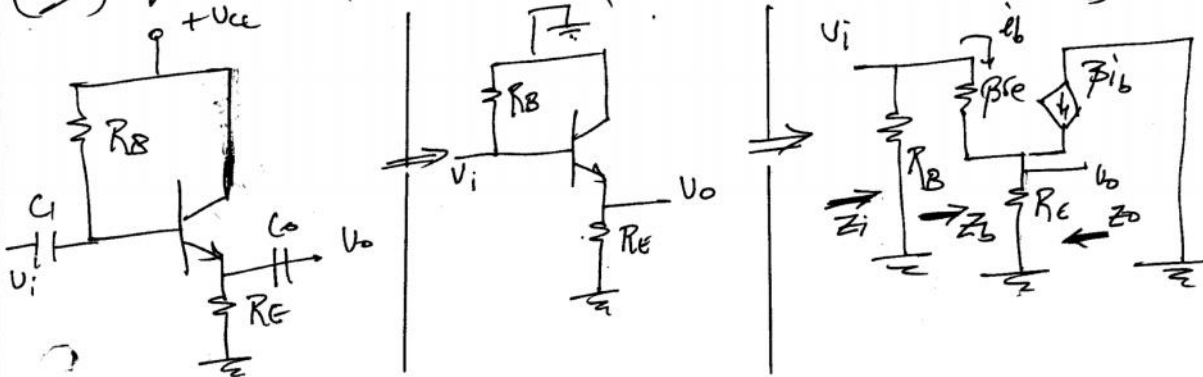
## (IV) EMITTER FOLLOWER (COMMON COLLECTOR) :



$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta) R_E$$

$$Z_o \approx \frac{\beta r_e}{1 + \beta} \parallel R_E$$


$$\approx r_e \parallel R_E$$

$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta) i_b R_E}{i_b Z_b}$$

$$A_v \approx \frac{R_E}{R_E + r_e} \approx 1$$

$$A_i = -\frac{A_v Z_i}{R_E}$$

### Effect of $r_o$ :

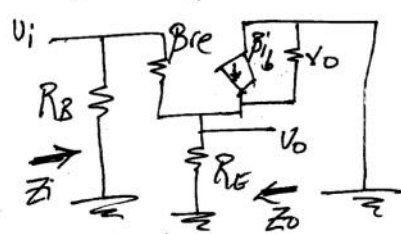

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta) R_E$$

$$\approx \beta (r_e + R_E)$$

$$Z_o = \frac{\beta r_e}{1 + \beta} \parallel R_E \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta) i_b (R_E \parallel r_o)}{i_b Z_b}$$


$$\approx \frac{R_E \parallel r_o}{R_E + r_e}$$

$$A_i = -\frac{A_v Z_i}{R_E}$$

$$A_{iS} = -\frac{A_v (Z_i + R_S)}{R_L}$$

$$A_i = -\frac{A_v Z_i}{R_L}$$

### Effect of $R_S$ & $R_L$

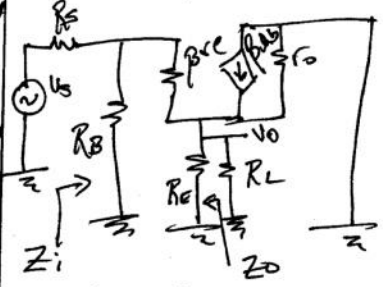

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta) (R_E \parallel R_L)$$



$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta) i_b (R_E \parallel R_L \parallel r_o)}{i_b Z_b}$$

$$A_v = \frac{R_E \parallel R_L \parallel r_o}{R_E \parallel R_L + r_e}$$

$$Z_o = \left[ \frac{R_S \parallel R_B + \beta r_e}{1 + \beta} \right] \parallel R_E \parallel r_o$$

$$A_{vS} = \frac{Z_i}{Z_i + R_S} \cdot A_v$$

(V) COMMON BASE :

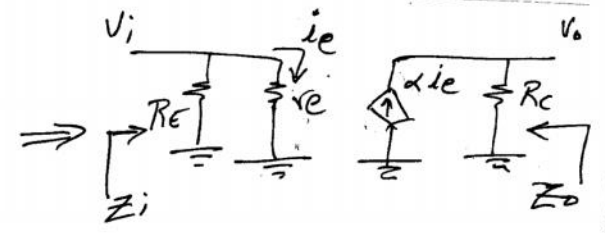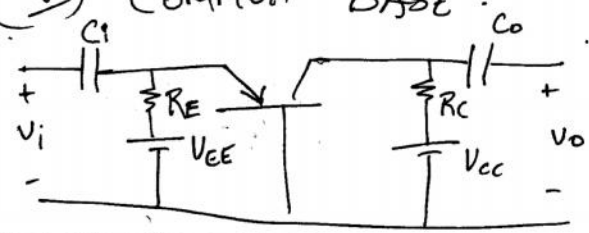


$$Z_i = R_E \parallel r_e$$

$$Z_o = R_C$$

$$A_v = \frac{\alpha i_e R_C}{i_e r_e} = \frac{\alpha R_C}{r_e}$$

$$A_i = \frac{-A_v Z_i}{R_C}$$

Effect of  $r_o$

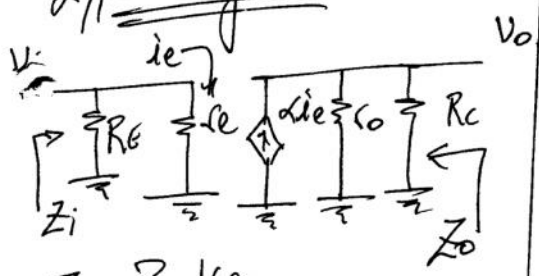

$$Z_i = R_E \parallel r_e$$


$$Z_o = R_C \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha i_e (R_C \parallel r_o)}{i_e r_e}$$

$$A_v = \frac{\alpha (R_C \parallel r_o)}{r_e}$$

$$A_i = \frac{-A_v Z_i}{R_C}$$

Effect of  $R_s$  &  $R_L$

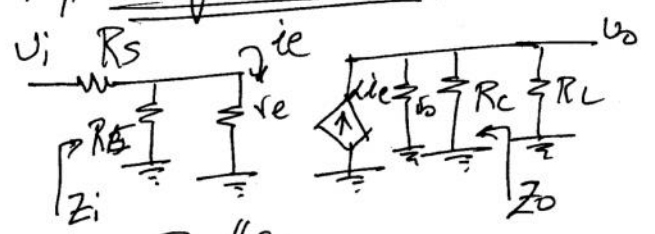

$$Z_i = R_E \parallel r_e$$

$$Z_o = R_C \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha i_e (R_C \parallel R_L \parallel r_o)}{i_e r_e}$$

$$A_v = \frac{\alpha (R_C \parallel R_L \parallel r_o)}{r_e}$$




$$A_{v_s} = \frac{Z_i}{Z_i + R_s} \cdot A_v$$

$$A_i = \frac{-A_v Z_i}{R_C}$$

$$A_{i_s} = \frac{-A_{v_s} (Z_i + R_s)}{R_L}$$



## (VI) DC FEEDBACK BIAS :

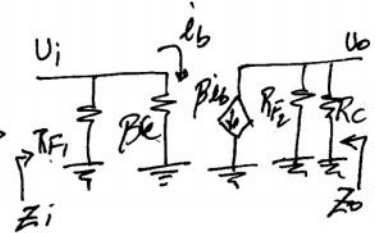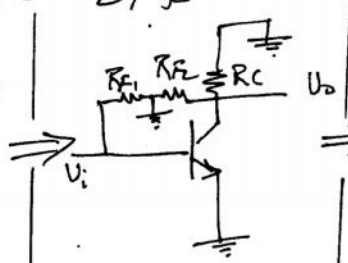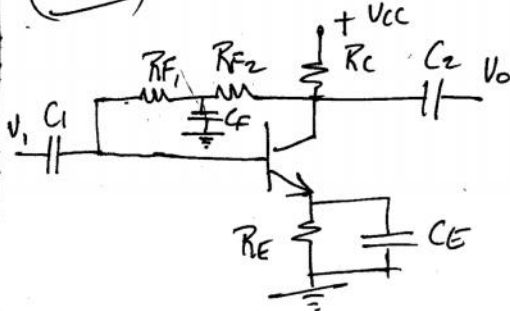

$$Z_i = R_{F1} \parallel \beta r_e$$


$$Z_o = R_C \parallel R_{F2}$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta i_b (R_C \parallel R_{F2})}{i_b (\beta r_e)}$$

$$A_v = -\frac{(R_C \parallel R_{F2})}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

### Effect of $r_o$ :

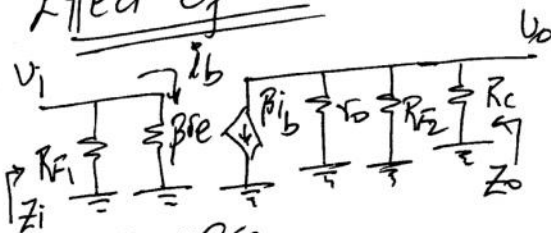


$$Z_i = R_{F1} \parallel \beta r_e$$

$$Z_o = R_C \parallel R_{F2} \parallel r_o$$

$$A_v = -\frac{V_o}{V_i} = -\frac{R_C \parallel R_{F2} \parallel r_o}{r_e}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

### Effect of $R_s$ & $R_L$

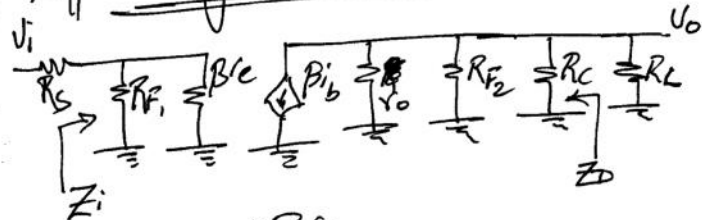

$$Z_i = R_{F1} \parallel \beta r_e$$

$$Z_o = r_o \parallel R_{F2} \parallel R_C$$



$$A_v = -\frac{V_o}{V_i} = -\frac{(R_C \parallel R_{F2} \parallel r_o) R_L}{r_e}$$

$$A_{v_s} = \frac{+A_v Z_i}{Z_i + R_s}$$

$$A_i = -\frac{A_v Z_i}{R_L}$$

$$A_{i_s} = -\frac{A_{v_s} (Z_i + R_s)}{R_L}$$

## (VII) COLLECTOR - FEEDBACK

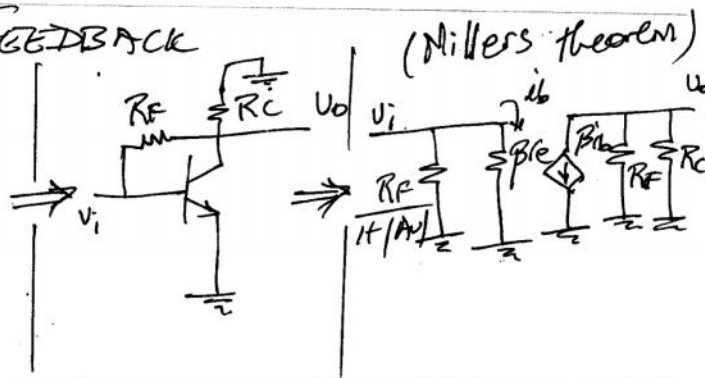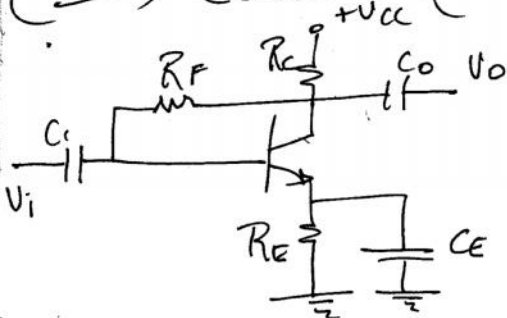

(Millers theorem)

$$A_v = \frac{+V_o}{V_i} = \frac{-\beta i_b (R_C \parallel R_E)}{i_b (\beta r_e)}$$

$$A_v = - \left( \frac{R_C \parallel R_E}{r_e} \right)$$

$$A_i = - \frac{A_v Z_i}{R_C}$$

$$Z_i = \left( \frac{R_B}{1 + |A_v|} \right) \parallel \beta r_e$$

$$Z_o = R_C \parallel R_E$$

Effect of  $r_o$




$$A_v = - \frac{R_C \parallel r_o \parallel R_E}{r_e}$$

$$A_i = - \frac{A_v Z_i}{R_C}$$

$$Z_i = \left( \frac{R_B}{1 + |A_v|} \right) \parallel \beta r_e$$

$$Z_o = R_C \parallel R_E \parallel r_o$$

Effect of  $R_s$  &  $R_L$

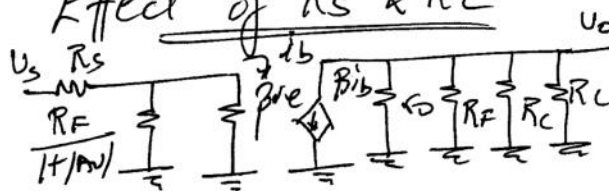

$$Z_i = \left( \frac{R_B}{1 + |A_v|} \right) \parallel \beta r_e$$

$$Z_o = R_C \parallel R_E \parallel r_o$$

$$A_v = - \frac{R_C \parallel R_E \parallel r_o \parallel R_L}{r_e}$$

$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_v$$

$$A_i = - \frac{A_v Z_i}{R_C}$$

$$A_{i_s} = - \frac{A_{v_s} (Z_i + R_s)}{R_C}$$