



Chapter 1

BJT DC

[Classwork Supplement]

Abhishek Navlakhi

www.navlakhi.com & navlakhi.mobi

Tel: 9820246760 / 9769479368 / 9820009639



Navlakhi's

Tel: 9769479368

/ 9820246760

BJT PREREQUISITES

SYMBOL :

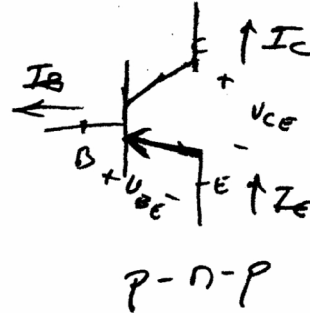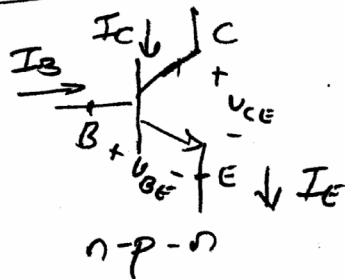

$$I_E = I_C + I_B = (1 + \beta) I_B$$

$$I_C = \beta I_B \quad I_C = \alpha I_E$$

	INPUT	OUTPUT	ϕ
COMMON EMITTER	Base	Collector	(V_{CE}, I_C)
COMMON COLLECTOR	Base	Emitter	(V_{CE}, I_C)
COMMON BASE	Emitter	Collector	(V_{CB}, I_C)

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{1 + \beta}$$

Abhishek Navlakhi

Navlakhi's


Tel: 9769479368

/ 9820246760



BJT BIASING

TYPE I : FIXED - BIAS

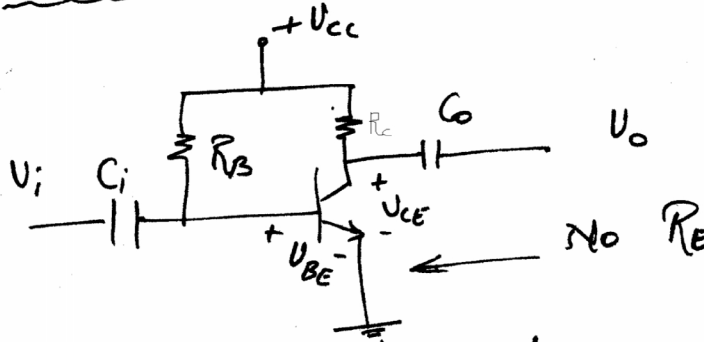

Applying KVL to B-E loop

$$V_{CC} - V_{BE} = I_B R_B$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B = \underline{\hspace{2cm}}$$

Applying KVL to CE loop

$$V_{CC} - V_{CE} = I_C R_C$$

$$\therefore V_{CE} = V_{CC} - I_C R_C$$

$$Q \equiv (V_{CE_Q}, I_{C_Q})$$

Abhishek Navlakhi


Navlakhi's

Tel: 9769479368

/ 9820246760



TYPE II : EMITTER STABILIZED BIAS

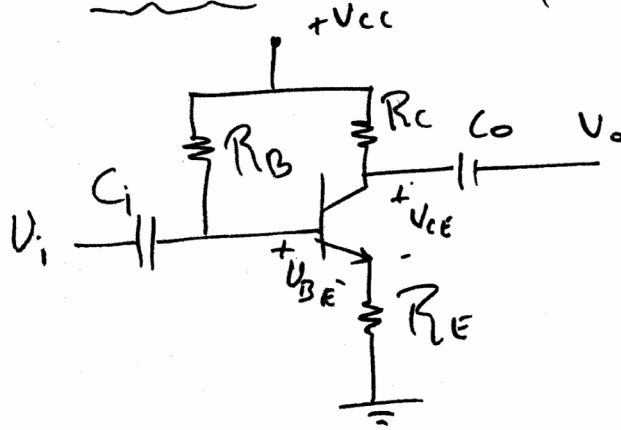

Applying KVL to BE loop

$$V_{CC} - V_{BE} = I_B R_B + I_E R_E$$

$$V_{CC} - V_{BE} = I_B R_B + (1 + \beta) I_B R_E$$

$$V_{CC} - V_{BE} = I_B [R_B + (1 + \beta) R_E]$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_C = \beta I_B = \underline{\hspace{2cm}}$$

Applying KVL to CE loop

$$V_{CC} - V_{CE} = I_C R_C + I_E R_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$Q \equiv (V_{CEQ}, I_{CQ})$$

Abhishek Navlakhi


Navlakhi's

Tel: 9769479368

/ 9820246760



TYPE III : Voltage Divider B.J.Ts.

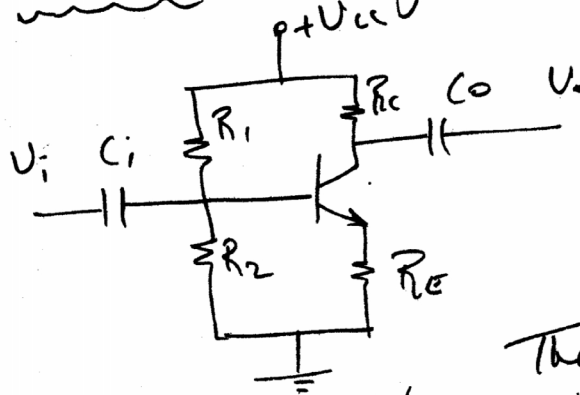

Applying KVL to B-E loop

$$V_{th} - V_{BE} = I_B R_{th} + I_E R_E$$

$$V_{th} - V_{BE} = I_B [R_{th} + (1 + \beta) R_E]$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

$$I_C = \beta I_B = \underline{\hspace{2cm}}$$


Applying KVL to C-E loop

$$V_{cc} - V_{CE} = I_C R_C + I_E R_E$$

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

$$Q \equiv (V_{CEQ}, I_{CQ})$$

Thevenising the ckt we get

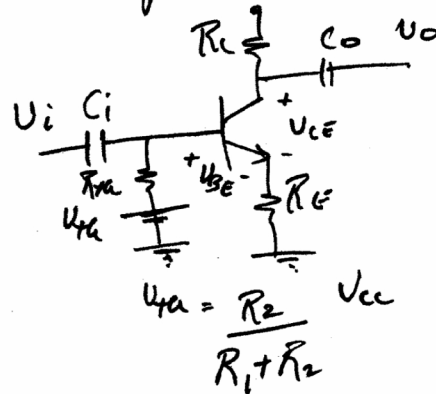

Abhishek Navlakhi


Navlakhi's

Tel: 9769479368

/ 9820246760



TYPE IV : DC BIAS WITH VOLTAGE FEEDBACK

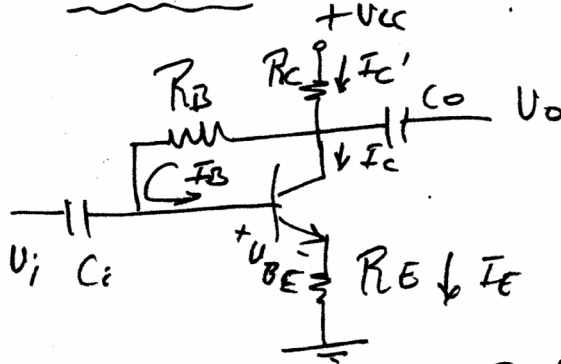

$$I_{C'} = I_C + I_B$$

Applying KVL to B-E loop

$$V_{CC} - V_{BE} = I_{C'} R_C + I_B R_B + I_E R_E$$

$$V_{CC} - V_{BE} = (1 + \beta) I_B R_C + I_B R_B + (1 + \beta) I_B R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_C + R_E)}$$

$$I_C = \beta I_B = \frac{\beta(V_{CC} - V_{BE})}{R_B + (1 + \beta)(R_C + R_E)}$$

Applying KVL to CE loop

$$V_{CC} - V_{CE} = I_C R_C + I_E R_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$


$$Q \equiv (V_{CE}, I_C)$$

Abhishek Navlakhi

Navlakhi's

Tel: 9769479368

/ 9820246760

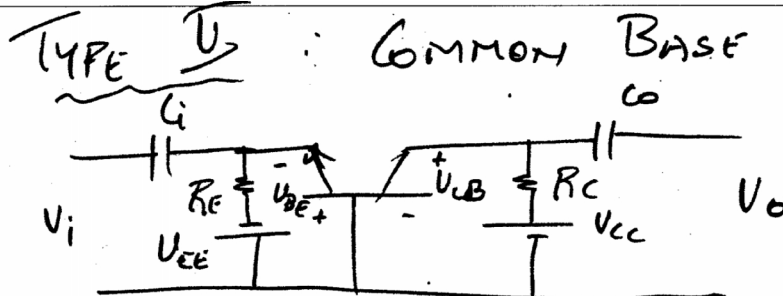

Applying KVL to E-B loop

$$V_{EE} - V_{BE} = I_E R_E$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$


$$I_C = \alpha I_E = \text{---}$$

Applying KVL to C-B loop

$$V_{CC} - V_{CB} = I_C R_C$$

$$V_{CB} = V_{CC} - I_C R_C$$

$$Q \equiv (V_{CB_Q}, I_{C_Q})$$

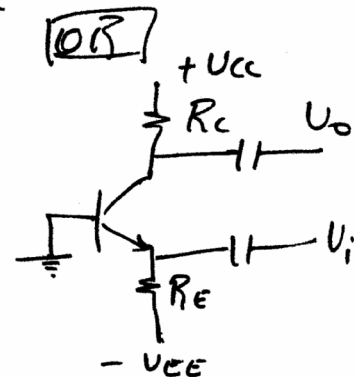

Abhishek Navlakhi