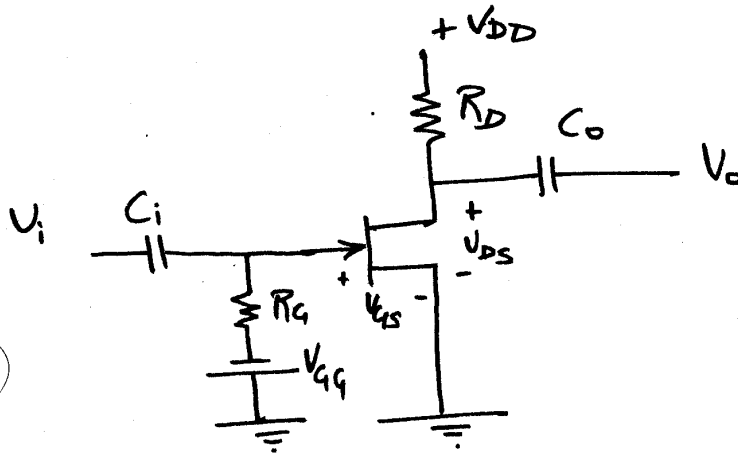




JFET BIASING

TYPE I: FIXED BIAS



Applying KVL to GS loop:

$$-V_{GG} - I_G R_G - V_{GS} = 0$$

$$\boxed{V_{GS} = -V_{GG}} \quad [\because I_G = 0]$$

By Shockley's equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Applying KVL to D-S loop


$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$=$$



TYPE II: SELF BIAS

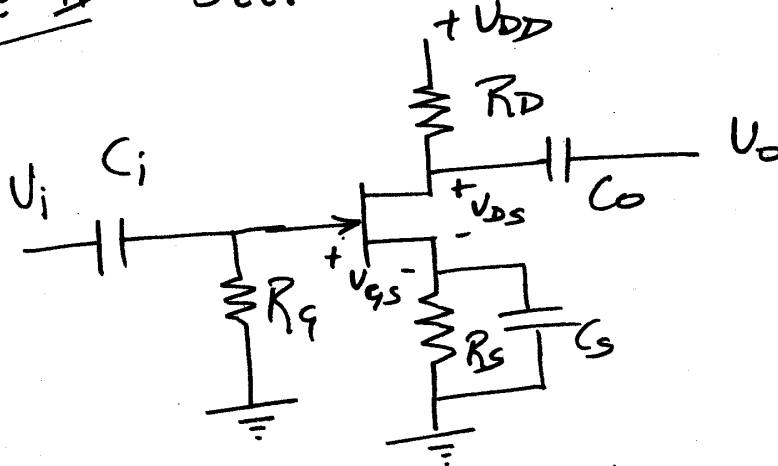

Applying KVL to G-S loop

$$-V_{GS} - I_D R_S = 0$$

$$V_{GS} = -I_D R_S \quad \text{--- (i)}$$

By Shockley's equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \text{--- (ii)}$$

Solving (i) & (ii) we get I_D & V_{GS} .

Applying KVL to D-S loop



$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$$= \underline{\hspace{2cm}}$$



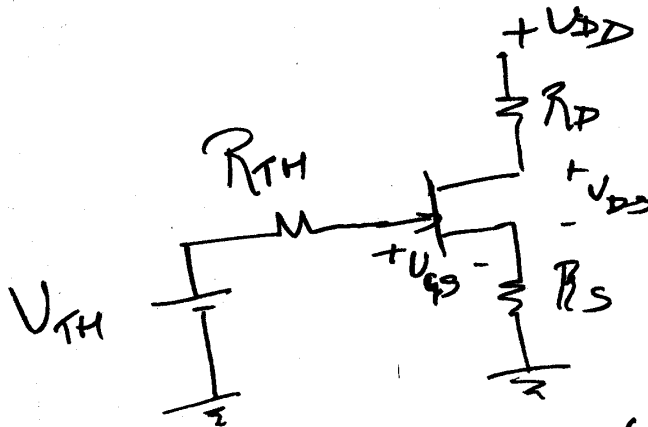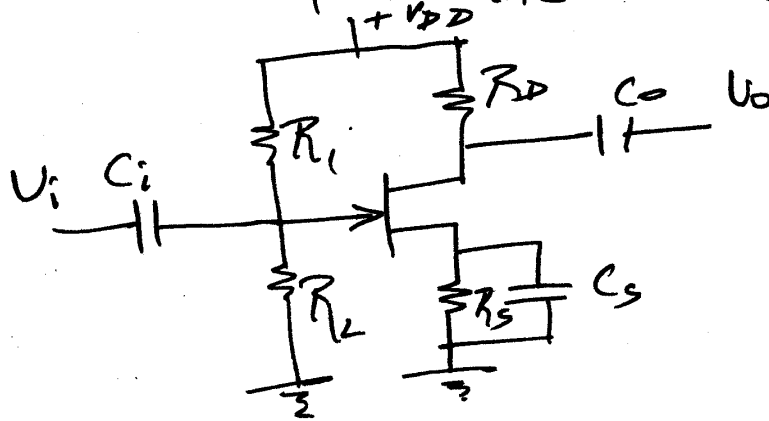TYPE III: VOLTAGE DIVIDER BIAS / POTENTIAL DIVIDER BIAS



$$R_{TH} = R_1 || R_2$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{DD}$$

Applying KVL to G-S loop

$$V_{TH} - V_{GS} - I_D R_S = 0 \quad (i)$$

By Shockley's equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad (ii)$$

Solve (i) & (ii) & get I_D & V_{GS}



KVL to D-S loop $V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$

$$V_{DS} = \underline{\hspace{2cm}}$$



JFET A.C. ANALYSIS

TYPE I: FIXED BIAS

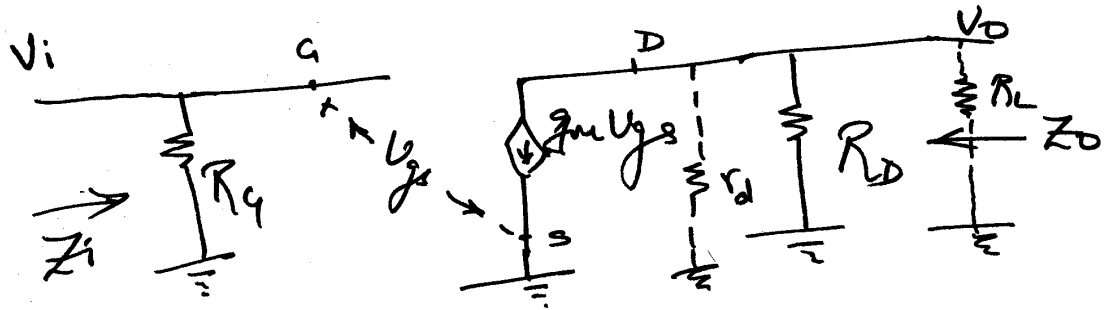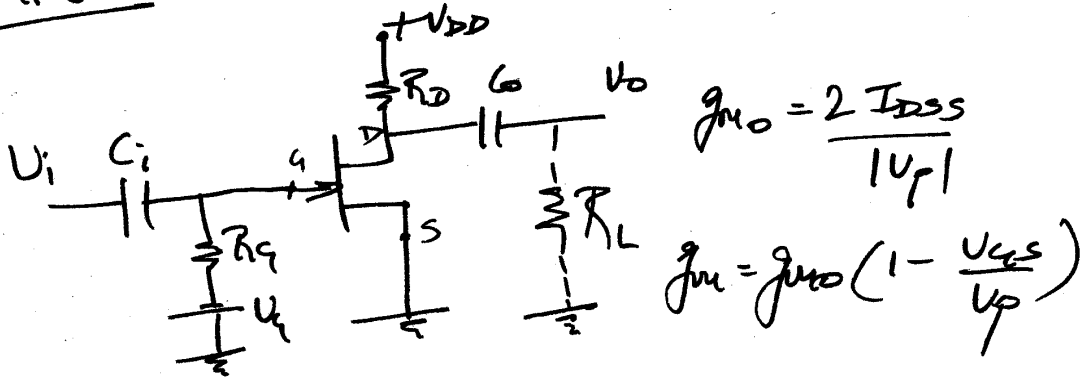

$$Z_i = R_G$$



$$Z_o = r_d \parallel R_D$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} (r_d \parallel R_D \parallel R_L)}{V_{gs}}$$

$$= -g_m (r_d \parallel R_D \parallel R_L)$$



TYPE II: (A) SELF BIAS

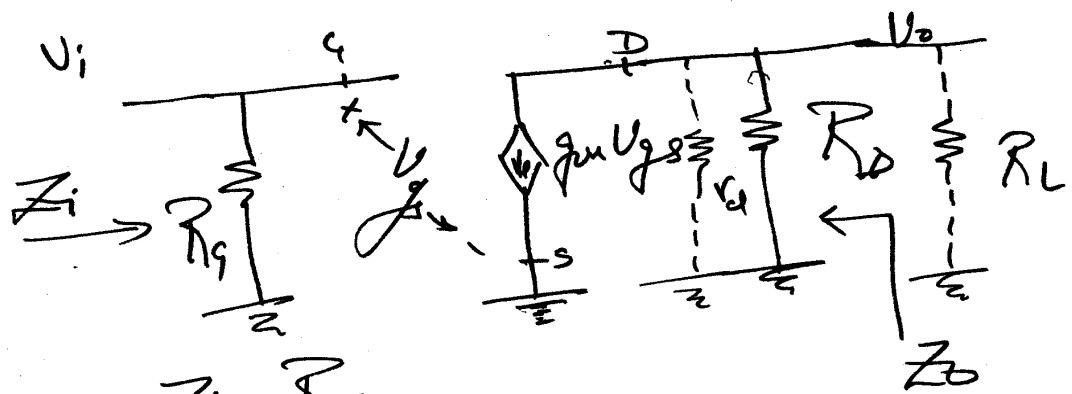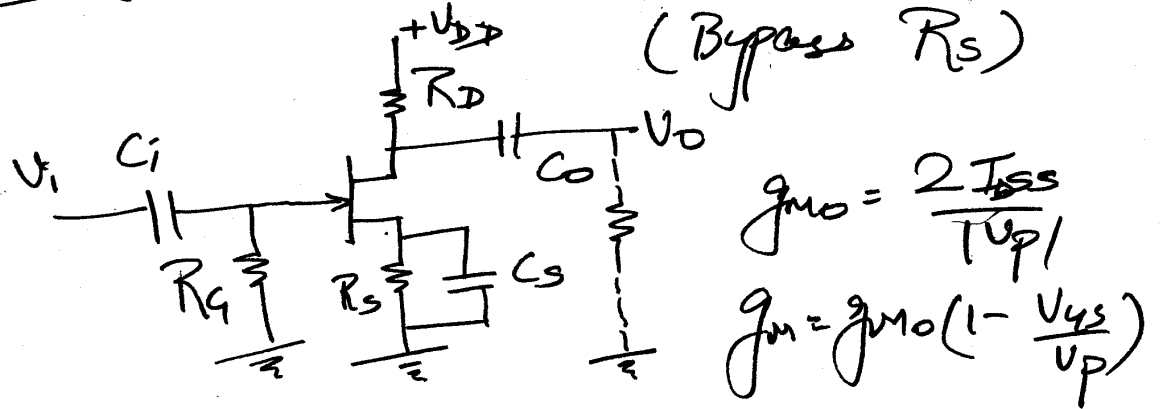

$$Z_i = R_g$$



$$Z_o = R_D \parallel r_d$$

$$A_v = \frac{-g_m V_{GS} (r_d \parallel R_D \parallel R_L)}{V_{GS}}$$

$$= -g_m (r_d \parallel R_D \parallel R_L)$$



TYPE II: (B) SELF BIAS (UNBYPASSED R_S)

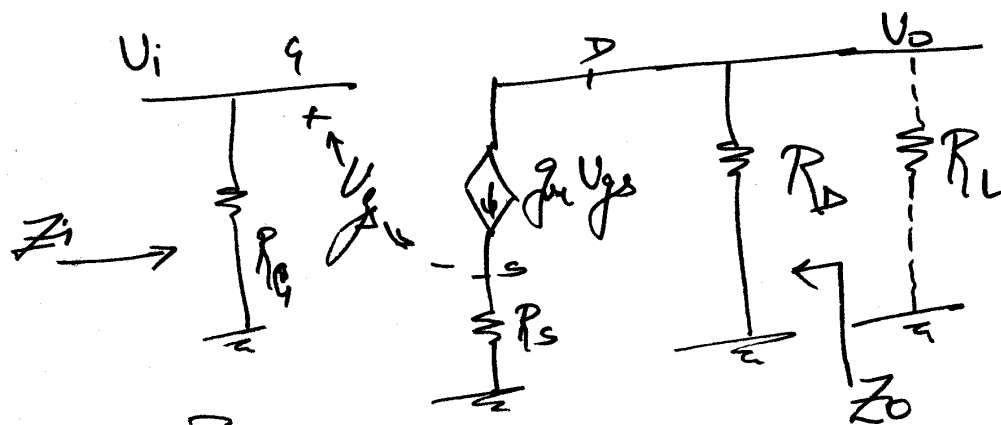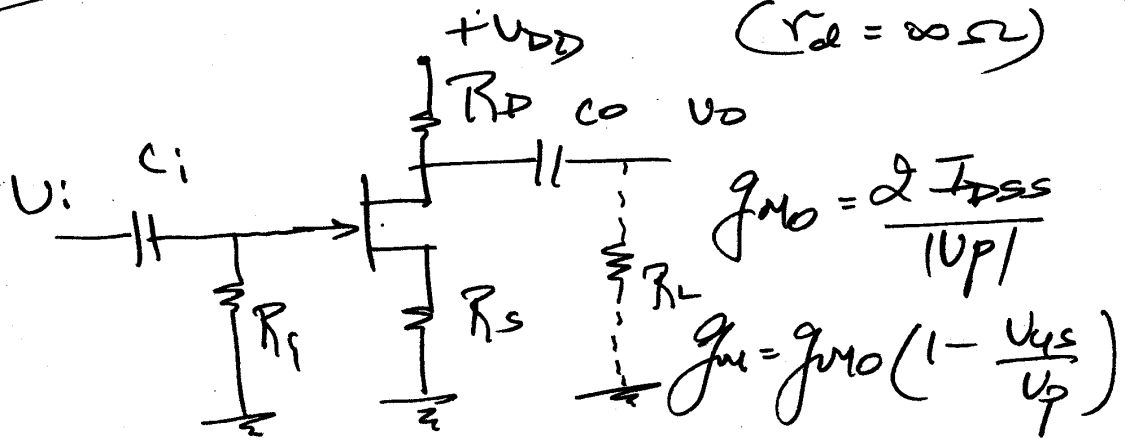


$$Z_i = R_g \quad Z_o = R_D$$

$$A_v = \frac{-g_m V_{gs} (R_D \parallel R_L)}{V_{gs} + g_m V_{gs} R_S}$$

$$= \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_S}$$




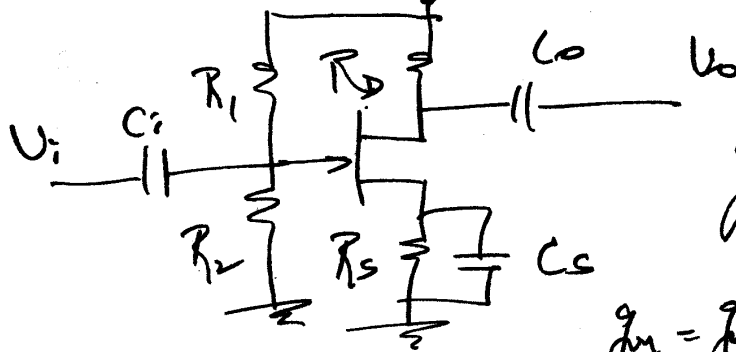TYPE III: VOLTAGE DIVIDER / POTENTIAL DIVIDER BIAS



$$g_{m0} = \frac{2I_{DSS}}{|V_p|}$$
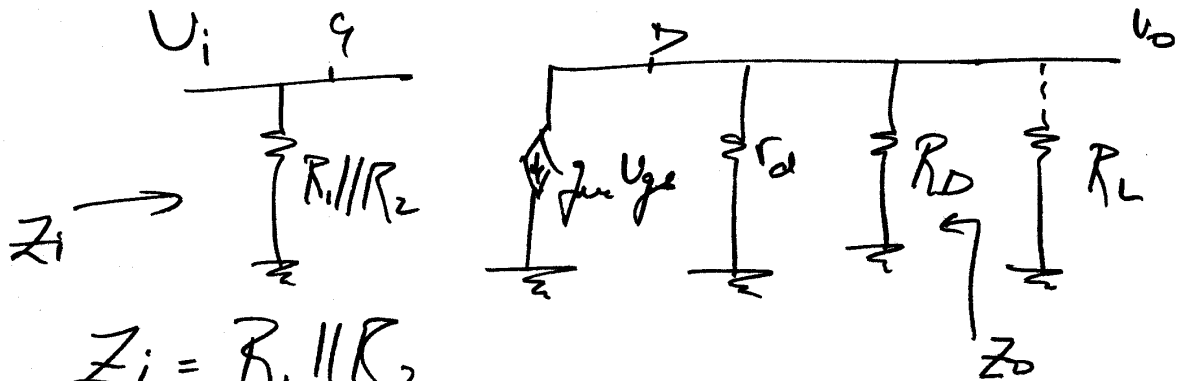
$$g_m = g_{m0} \left(1 - \frac{V_{CE}}{V_p}\right)$$



$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_e \parallel R_C$$

$$A_v = \frac{-g_m U_{be} (r_e \parallel R_C \parallel R_L)}{-U_{be}}$$


$$= -g_m (r_e \parallel R_C \parallel R_L)$$

Navlaksi's




Tel: 23868356 / 23886023 / 9820246760 **POWER**

TYPE IV: COMMON GATE

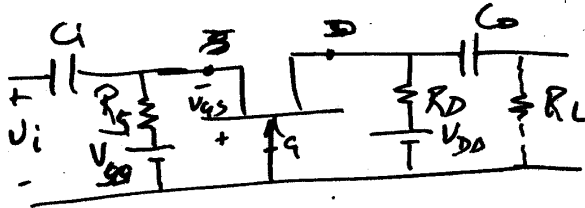

$$g_{m0} = \frac{2 I_{DSS}}{|V_p|}$$

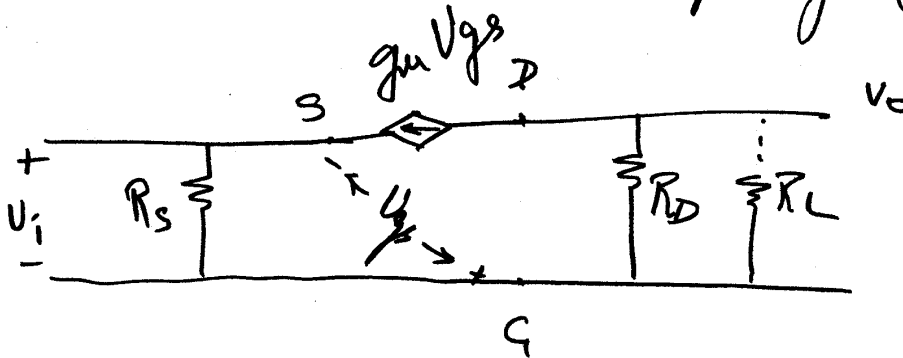
$$g_m = g_{m0} \left(1 - \frac{V_{gs}}{V_p}\right)$$



$$Z_i = R_s \parallel \frac{1}{g_m} \quad Z_o = R_D$$

$$A_v = \frac{+g_m V_{gs} (R_D \parallel R_L)}{+V_{gs}}$$


$$= g_m (R_D \parallel R_L)$$

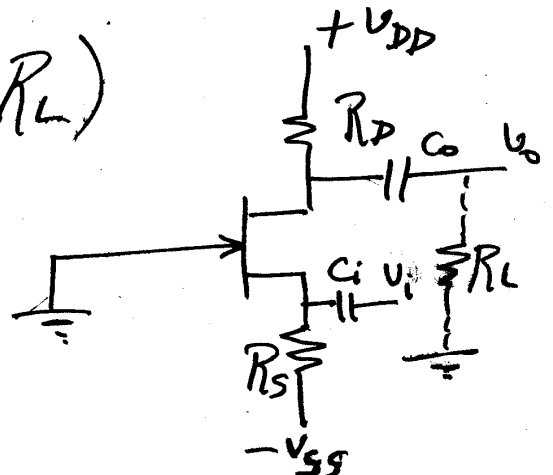

Abhishek Navlaksi





TYPE V: COMMON DRAIN

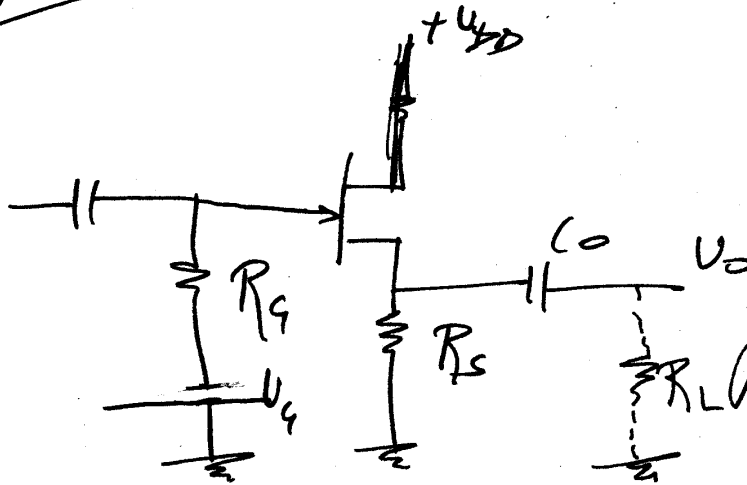

$$g_{m0} = \frac{2I_{DSS}}{|V_{p}|}$$
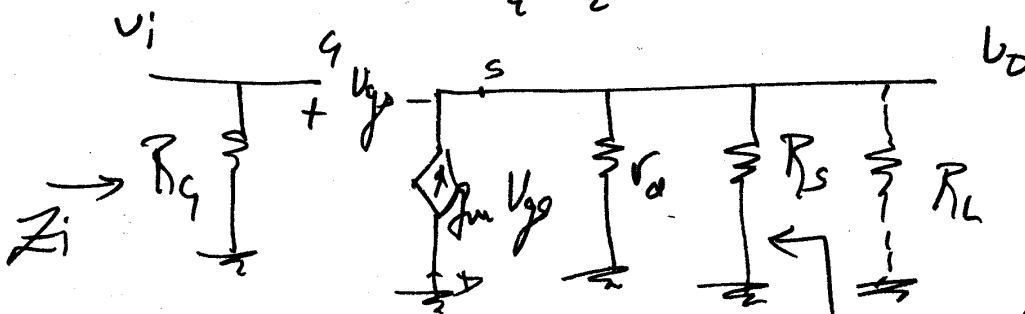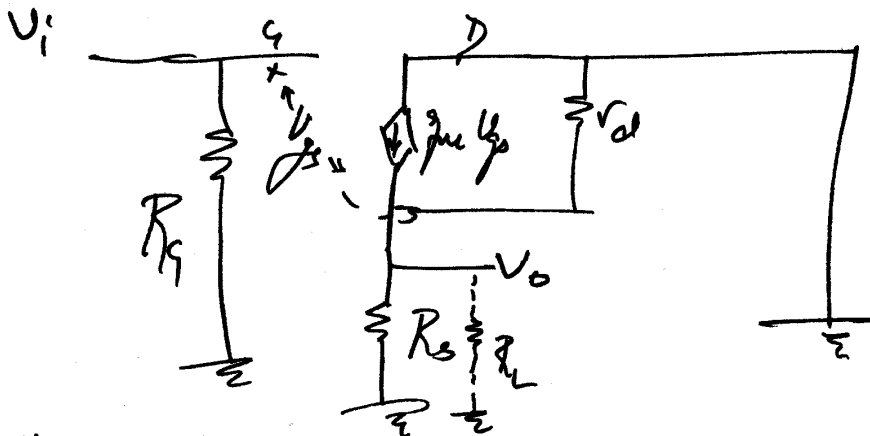
$$g_m = g_{m0} \left(1 - \frac{V_{gs}}{V_p}\right)$$



$$Z_i = R_g$$

$$Z_o = C_{ds} \parallel R_s \parallel \frac{1}{g_m}$$

$$A_v = \frac{g_m V_{gs} (r_{ds} \parallel R_s \parallel R_L)}{V_{gs} + g_m V_{gs} (r_{ds} \parallel R_s \parallel R_L)}$$

$$A_v = \frac{g_m (r_{ds} \parallel R_s \parallel R_L)}{1 + g_m (r_{ds} \parallel R_s \parallel R_L)}$$