



STABILITY

Stability of a system is a measure of the sensitivity of a network to variation in its parameters.

Collector current depends on:

β : increases with increase in temperature
 V_{BE} : decreases by about $7.5 \text{ mV}/^\circ\text{C}$ increase in temperature

I_{CO} : doubles in value for every 10°C increase in temperature.

Stability Factors:

Stability factor, S , is defined for each of the parameters affecting bias stability, as listed below:

$$S_{(I_{CO})} = \frac{\Delta I_C}{\Delta I_{CO}}$$

$$S_{(V_{BE})} = \frac{\Delta I_C}{\Delta V_{BE}}$$

$$S_{(\beta)} = \frac{\Delta I_C}{\Delta \beta}$$



Tel: 23868356 / 23886023 / 9820246760 **POWER**


Networks that are quite stable & relatively insensitive to temperature variations have low stability factors.

Thus stability is nothing but sensitivity. Higher the stability factor, the more sensitive the network to variations in the parameters.



S(Ico)

(I) FIXED-BIAS

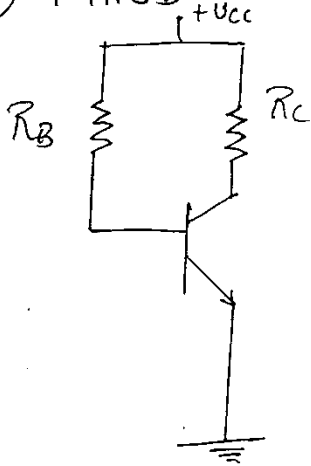

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

Diff w.r.t. I_C we get

$$1 = \beta \frac{dI_B}{dI_C} + (1 + \beta) \frac{dI_{CO}}{dI_C}$$

$$1 = \beta \frac{dI_B}{dI_C} + \frac{(1 + \beta)}{S(I_{CO})} \quad \text{--- (1)}$$

Applying KVL to B-E loop

$$V_{CC} - I_B R_B - V_{BE} = 0$$


Diff. w.r.t I_C we get

$$\frac{dI_B}{dI_C} = 0 \quad \text{--- (2)}$$

Substituting (2) in (1) we get

$$1 = 0 + \frac{(1 + \beta)}{S(I_{CO})}$$

$$\therefore S(I_{CO}) = (1 + \beta)$$

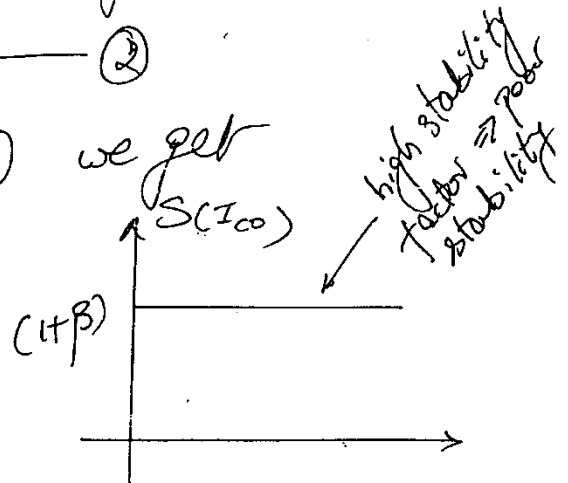


In the next derivation we will see that the worst case of emitter-bias matches with that of fixed-bias.



$S_{(I_{CO})}$

(II) Emitter - Stabilized Bias

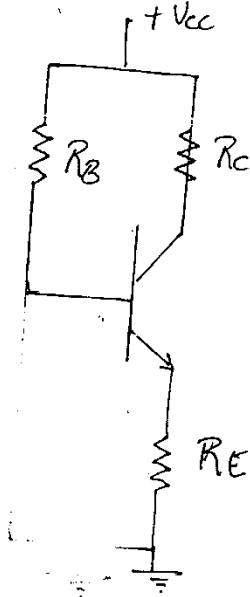

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

Diff. w.r.t. I_C we get

$$1 = \beta \frac{dI_B}{dI_C} + (1 + \beta) \frac{dI_{CO}}{dI_C}$$

$$1 = \beta \frac{dI_B}{dI_C} + \frac{1 + \beta}{S} \quad \text{--- (1)}$$

Applying KVL to the base-emitter loop

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (I_C + I_B) R_E = 0$$

$$V_{CC} - I_B [R_B + R_E] - I_C R_E - V_{BE} = 0$$

Diff w.r.t. I_C we get

$$\frac{dI_B}{dI_C} = \frac{-R_E}{R_E + R_B} \quad \text{--- (2)}$$

Substituting (2) in (1) we get

$$1 = \beta \left[\frac{-R_E}{R_E + R_B} \right] + \frac{1 + \beta}{S_{(I_{CO})}}$$



$$\frac{1+\beta}{S(I_{co})} = 1 + \frac{\beta R_E}{R_E + R_B}$$

$$\frac{1+\beta}{S(I_{co})} = \frac{R_E(1+\beta) + R_B}{R_E + R_B}$$

$$S(I_{co}) = (1+\beta) \frac{R_E + R_B}{(1+\beta)R_E + R_B}$$


$$S(I_{co}) = (1+\beta) \frac{1 + R_B/R_E}{(1+\beta) + R_B/R_E}$$

If $R_B/R_E \gg (1+\beta)$ then $S(I_{co}) \approx \beta + 1$

If $R_B/R_E \ll 1$ then $S(I_{co}) \approx 1$



Thus stability factor approaches its lowest (best case) level as R_E

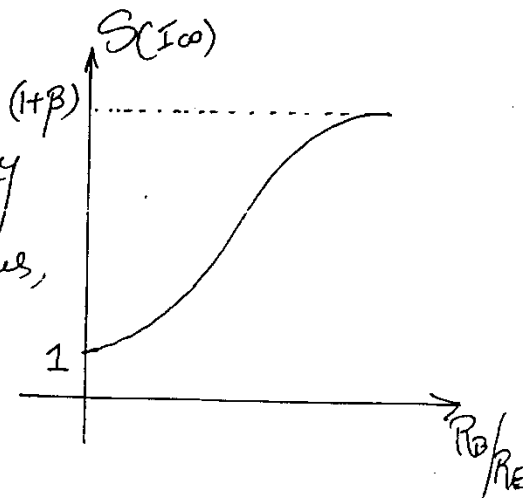becomes sufficiently large. But for good stability control we need $R_B > R_E$. Thus, a trade-off must be achieved between best stability & good design.





S(Ico):
 (III) VOLTAGE DIVIDER BIAS:

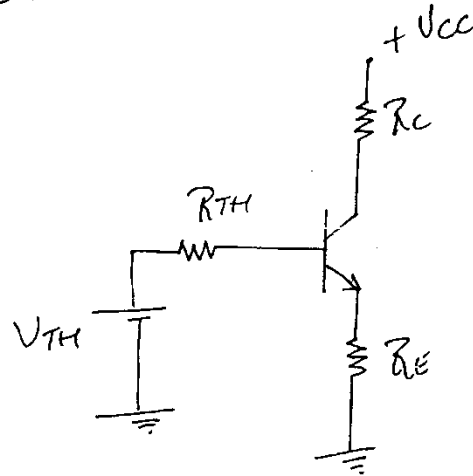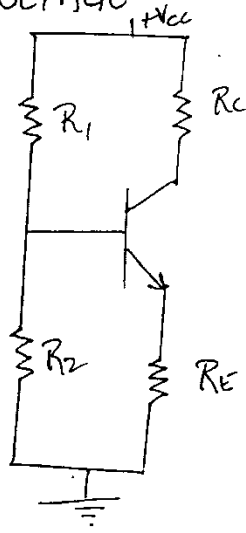

where $R_{TH} = R_1 || R_2$
 $V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

Diff. w.r.t. I_C we get

$$1 = \beta \frac{dI_B}{dI_C} + (1 + \beta) \frac{dI_{CO}}{dI_C}$$

$$1 = \beta \frac{dI_B}{I_C} + \frac{(1 + \beta)}{S(I_{CO})} \quad \text{--- (1)}$$

Applying KVL to B-E loop we get

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_{TH} - V_{BE} - (I_B + I_C) R_E = 0$$

Navlakhi

Navlakhi's



Tel: 23868356 / 23886023 / 9820246760 **POWER**

$$V_{TH} - I_B(R_{TH} + R_E) - V_{BE} - I_C R_E = 0$$

Diff w.r.t. I_C

$$\frac{dI_B}{dI_C} = \frac{-R_E}{R_E + R_{TH}} \quad \text{--- (2)}$$

Substituting (2) in (1) we get


$$1 = \beta \left[\frac{-R_E}{R_E + R_{TH}} \right] + \frac{(1+\beta)}{S(I_C)}$$

$$\frac{1+\beta}{S(I_C)} = 1 + \frac{\beta R_E}{R_E + R_{TH}}$$

$$\frac{1+\beta}{S(I_C)} = \frac{R_E(1+\beta) + R_{TH}}{R_E + R_{TH}}$$

$$\frac{S(I_C)}{1+\beta} = \frac{R_E + R_{TH}}{(1+\beta)R_E + R_{TH}}$$
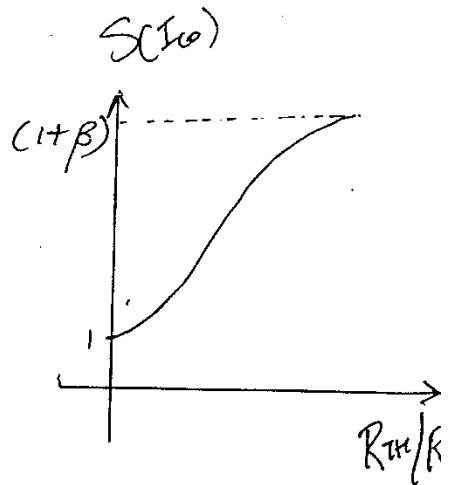
$$S(I_C) = (1+\beta) \frac{R_E + R_{TH}}{(1+\beta)R_E + R_{TH}}$$



$$S(I_C) = (1+\beta) \frac{1 + R_{TH}/R_E}{(1+\beta) + R_{TH}/R_E}$$

If $R_{TH}/R_E \gg (1+\beta)$ then $S(I_C) \approx 1+\beta$

If $R_{TH}/R_E \ll 1$ then $S(I_C) \approx 1$

Abhishek Navlakhi

9820246760 / 9769479368


navlakhi.com | navlakhi.mobi

Be With The Best



S(Ico)

(iv) COLLECTOR FEEDBACK BIAS:

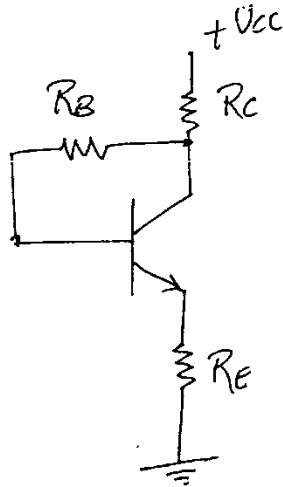

$$I_c = \beta I_B + (1 + \beta) I_{CO}$$

Diff. w.r.t. I_c

$$1 = \beta \frac{dI_B}{dI_c} + (1 + \beta) \frac{dI_{CO}}{dI_c}$$

$$1 = \beta \frac{dI_B}{dI_c} + \frac{(1 + \beta)}{S(I_{CO})} \quad \text{--- (1)}$$

Applying KVL to B-E loop

$$V_{CC} - I_c R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - (I_c + I_B) R_C - I_B R_B - V_{BE} - (I_c + I_B) R_E = 0$$

$$V_{CC} - I_B (R_C + R_B + R_E) - I_c (R_C + R_E) - V_{BE} = 0$$

Diff. w.r.t. I_c

$$\frac{dI_B}{dI_c} = - \frac{R_C + R_E}{R_C + R_E + R_B} \quad \text{--- (2)}$$

Substituting (2) in (1) we get

$$1 = \beta \left[\frac{-(R_C + R_E)}{R_C + R_E + R_B} \right] + \frac{1 + \beta}{S(I_{CO})}$$



$$\frac{1+\beta}{S(I_{co})} = \frac{1 + \beta(R_c + R_e)}{R_c + R_e + R_B}$$


$$\frac{1+\beta}{S(I_{co})} = \frac{(1+\beta)(R_c + R_e) + R_B}{(R_c + R_e) + R_B}$$

$$S(I_{co}) = (1+\beta) \frac{R_c + R_e + R_B}{(1+\beta)(R_c + R_e) + R_B}$$

$$S(I_{co}) = (1+\beta) \frac{1 + R_B/(R_c + R_e)}{(1+\beta) + R_B/(R_c + R_e)}$$

If $R_B/(R_c + R_e) \gg (1+\beta)$ then $S(I_{co}) \approx 1+\beta$

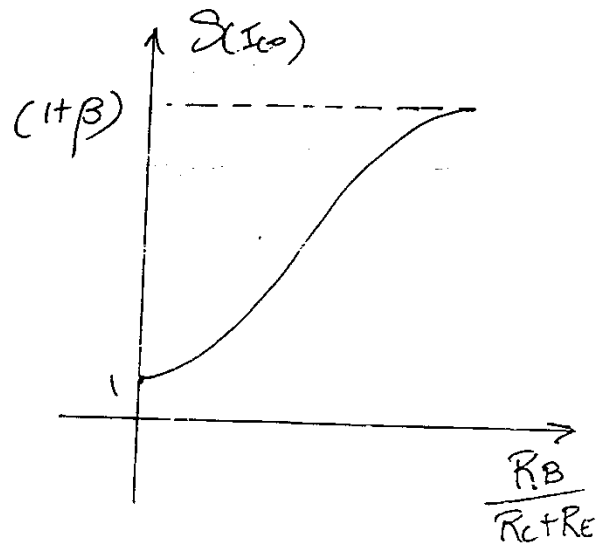If $R_B/(R_c + R_e) \ll 1$ then $S(I_{co}) \approx 1$.




Abhishek Navlakhhi



Tel: 23868356 / 23886023 / 9820246760 **POWER**

S(V_{BE})

(I) Fixed-Bias

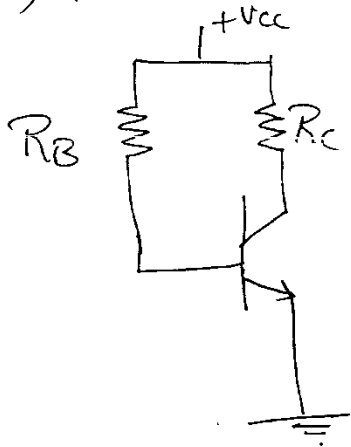

Applying KVL to B-E loop

$$V_{cc} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{I_C}{\beta}$$

$$\therefore V_{cc} - \frac{I_C R_B}{\beta} - V_{BE} = 0$$

Dif w.r.t to I_C

$$0 - \frac{R_B}{\beta} \frac{dI_C}{dI_C} - \frac{dV_{BE}}{dI_C} = 0$$


$$\therefore \frac{dI_C}{dV_{BE}} = \frac{-\beta}{R_B}$$

$$\boxed{S(V_{BE}) = \frac{-\beta}{R_B}}$$



$S_{(V_{BE})}$:

(II) EMITTER STABILIZED BIAS:

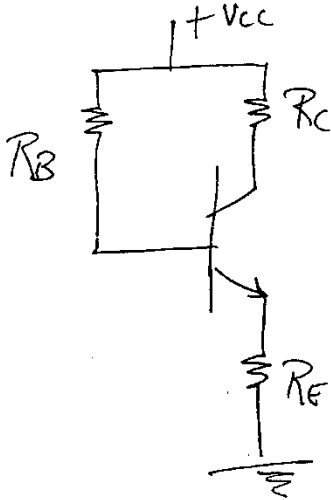

Applying KVL to B-E loop

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (I_C + I_B) R_E = 0$$

$$V_{CC} - \frac{I_C}{\beta} R_B - V_{BE} - I_C R_E - \frac{I_C R_E}{\beta} = 0$$

Diff w.r.t I_C .

$$0 - \frac{R_B}{\beta} - \frac{dV_{BE}}{dI_C} - R_E - \frac{R_E}{\beta} = 0$$

$$\frac{dV_{BE}}{dI_C} = - \frac{R_E + R_B + \beta R_E}{\beta}$$


$$\frac{dI_C}{dV_{BE}} = - \frac{\beta}{R_B + (1 + \beta) R_E}$$

$$S_{(V_{BE})} = \frac{-\beta}{R_B + (1 + \beta) R_E}$$



SC_{VBE}:

(III) VOLTAGE DIVIDER BIAS:

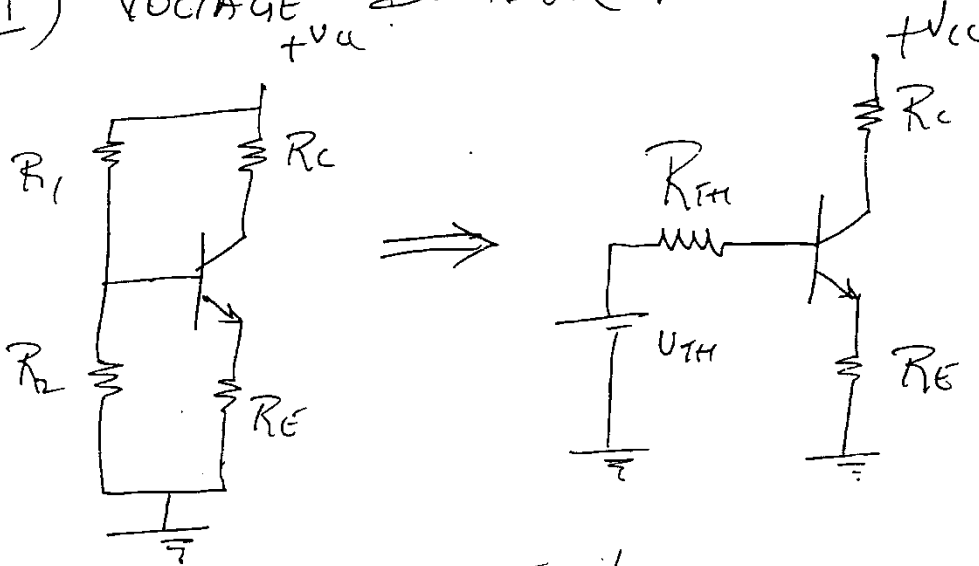

Applying KVL to B-E loop

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_{TH} - V_{BE} - (I_C + I_B) R_E = 0$$

$$V_{TH} - \frac{I_C R_{TH}}{\beta} - V_{BE} - I_C R_E - \frac{I_C R_E}{\beta} = 0$$

Dif. w.r.t I_C

$$0 - \frac{R_{TH}}{\beta} \frac{dV_{BE}}{dI_C} - R_E - \frac{R_E}{\beta} = 0$$

$$S_{C_{V_{BE}}} = \frac{-\beta}{(1+\beta)R_E + R_{TH}}$$


Abhishek Navlakhi



Tel: 23868356 / 23886023 / 9820246760 **POWER**

$S_{(V_{BE})}$:

(IV) Collector-feedback bias:

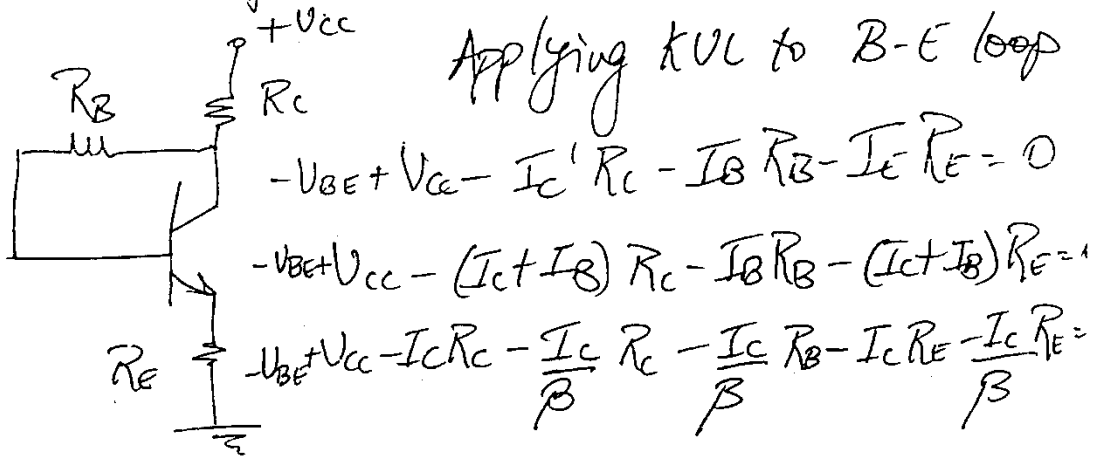

Diff w.r.t I_C

$$0 - R_C - \frac{R_C}{\beta} - \frac{R_B}{\beta} - R_E - \frac{R_E}{\beta} - \frac{dV_{BE}}{dI_C} = 0$$

$$\frac{dV_{BE}}{dI_C} = - \left[\frac{(1+\beta)(R_C + R_E) + R_B}{\beta} \right]$$

$$S_{(V_{BE})} = \frac{-\beta}{(1+\beta)(R_C + R_E) + R_B}$$