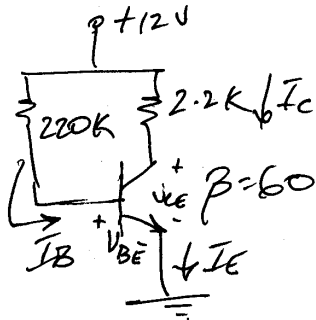




3868356 / 23886023 / 9820246760 **POWER**

①



Applying KVL to B-E loop

$$V_{CC} - I_B(220k) - V_{BE} = 0$$

$$12 - (220k)I_B - 0.7 = 0$$

$$I_B = \underline{51.36 \mu A}$$

$$I_C = \beta I_B = \underline{3.082 mA}$$


Applying KVL to C-E loop

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$12 - (3.082 mA)(2.2k) - V_{CE} = 0$$

$$V_{CE} = \underline{5.22 V}$$

$$Q \text{ point} = (5.22 V, 3.082 mA)$$

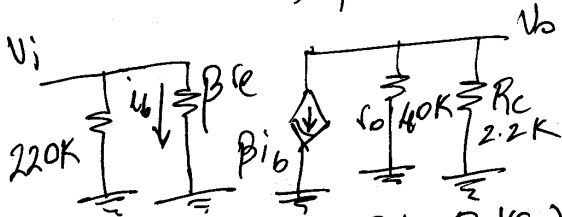

$$r_e = \frac{26mV}{I_C} = 8.44 \Omega$$

$$Z_i = 220k \parallel (60)(8.44)$$

$$= \underline{0.505 k \Omega}$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_C \parallel r_o)}{\beta i_b r_e}$$

$$= - \frac{(2.2k \parallel 40k)}{8.44 \Omega}$$

$$Z_o = R_C \parallel r_o$$

$$= 2.2k \parallel 40k$$


$$= \underline{2.09 k \Omega}$$

$$A_i = - \frac{A_v Z_i}{R_C} = \frac{+247.63(0.505k)}{2.2k}$$

$$= \underline{56.84}$$

Abhishek Navlakhia

② $A_V = -200$

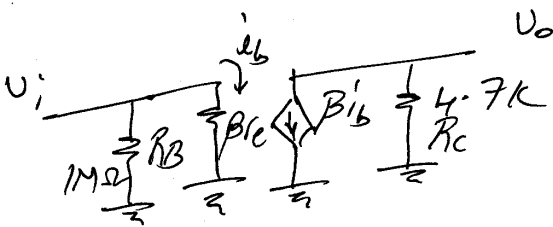

$$A_V = \frac{V_o}{V_i} = \frac{-\beta i_b R_C}{\beta i_b R_E}$$

$$A_V = -\frac{4.7k}{r_e}$$


$$-200 = -\frac{4.7k}{r_e}$$

$$r_e = 23.5 \Omega$$

$$\frac{26mV}{I_C} = 23.5$$

$$I_C = 1.11 mA$$
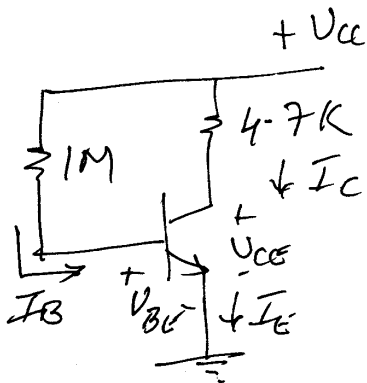
$$I_B = \frac{I_C}{\beta} = 12.29 \mu A$$




Applying KVL to B-E loop

$$V_{CC} - I_B(1M) - V_{BE} = 0$$

$$V_{CC} - (12.29 \mu A)(10^6) - 0.7 = 0$$

$$\underline{\underline{V_{CC} = 13V}}$$

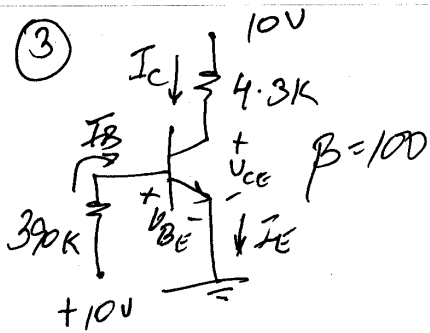

Applying KVL to B-E loop

$$10 - I_B(390k) - 0.7 = 0$$

$$I_B = 23.85 \mu A$$

$$I_C = \beta I_B = 2.385 mA$$


Applying KVL to C-E loop.

$$10 - (4.3k)I_C - V_{CE} = 0$$

$$V_{CE} = -0.256 V$$

$$Q = (-0.256, 2.385 mA)$$

$$r_e = \frac{26mV}{I_C} = 10.9 \Omega$$

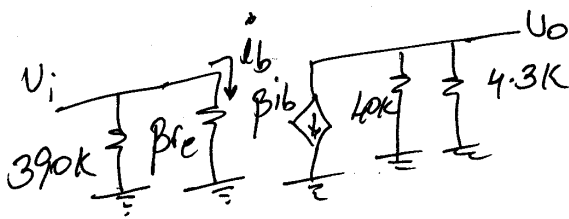

$$Z_i = 390k // \beta r_e$$

$$= 0.087k \Omega$$

$$Z_o = 40k // 4.3k = 3.88k \Omega$$


$$A_v = \frac{V_o}{V_i} = \frac{-\beta (40k // 4.3k)}{\beta r_e}$$

$$A_v = -356.2$$

$$A_i = -\frac{A_v Z_i}{4.3k} = 23.779004$$



(4)

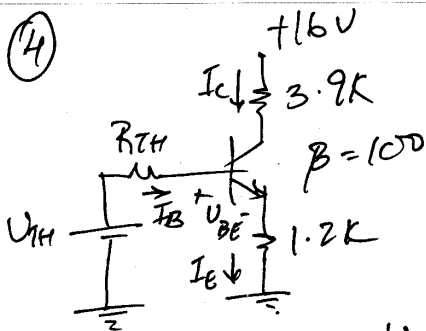

$$V_{TH} = \left(\frac{4.7}{4.7+39} \right) \cdot 16 = 1.72V$$

$$R_{TH} = 39k \parallel 4.7k = 4.195k\Omega$$

Applying KVL to B-E loop.

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$1.72 - I_B (4.195k) - 0.7 - (1+100)I_B (1.2k) = 0$$

$$I_B = 8.134 \mu A$$

$$I_C = \beta I_B = 0.813 mA$$

Applying KVL to C-E loop.


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$16 - (0.813 mA)(3.9k) - V_{CE} - (101)(8.134 \mu A)(1.2k) = 0$$

$$V_{CE} = 11.84V$$

$$Q = (11.84V, 0.813 mA)$$

$$r_e = \frac{26mV}{I_C} = 32\Omega$$

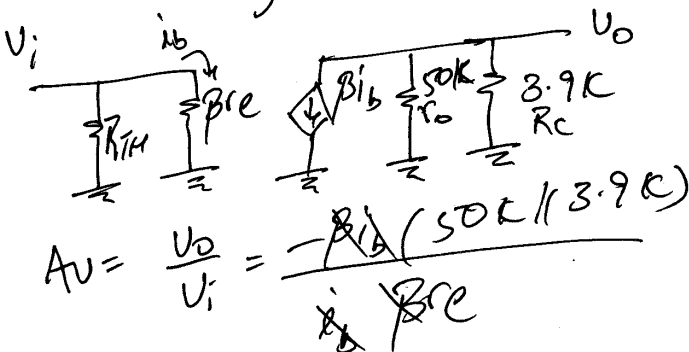

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (50k \parallel 3.9k)}{i_b r_e}$$

$$A_v = -113.06$$


$$A_i = -\frac{A_v Z_i}{R_c} = 52.62$$

$$Z_i = R_{TH} \parallel \beta r_e = 1.815k\Omega$$

$$Z_o = 50k \parallel 3.9k = 3.618k\Omega$$



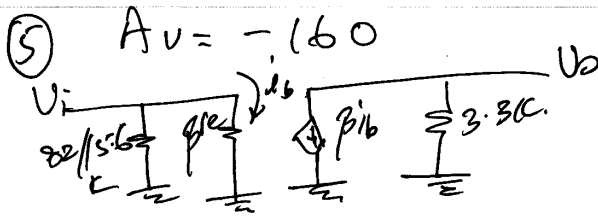Tel: 23868356 / 23886023 / 9820246760 **POWER**



$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_c (3.3k)}{\beta R_{e1}}$$


$$-160 = -\frac{3.3k}{r_e}$$

$$r_e = 20.625 \Omega$$

$$\frac{26mV}{I_e} = 20.625 \Omega$$

$$I_c = 1.26mA$$

$$I_b = \frac{I_c}{\beta} = 12.6 \mu A$$

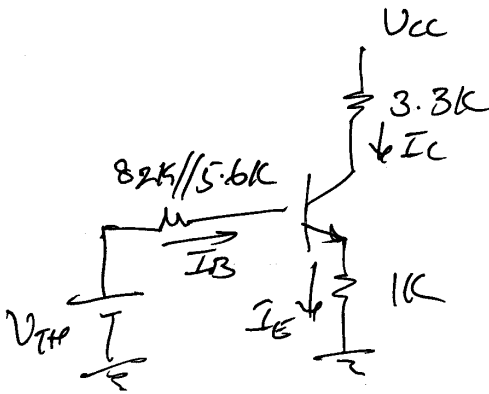

$$V_{TH} = \left(\frac{5.6}{5.6 + 82} \right) V_{CC}$$

Applying KVL to B-E loop
 $V_{TH} - I_b R_{TH} - V_{BE} - I_e R_e = 0$

$$\left(\frac{5.6}{5.6 + 82} \right) V_{CC} - (12.6 \mu A)(82k // 5.6k) - 0.7 - (101)(12.6 \mu A)(1k) = 0$$


$$0.064 V_{CC} - 0.066 - 0.7 - 1.2726 = 0$$

$$V_{CC} = \underline{\underline{31.85 V}}$$

Abhishek Navlakhki



⑥

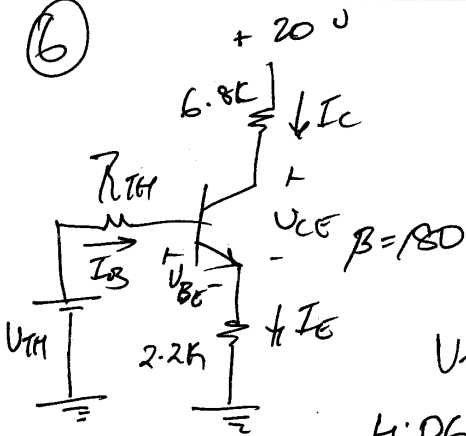

$$R_{TH} = 220k // 56k = 44.64k\Omega$$

$$V_{TH} = \left(\frac{56}{56+220} \right) 20 = 0.203 \times 20 = 4.06V$$

Applying KVL to B-E loop.

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$4.06 - I_B (44.64k) - 0.7 - (181) I_B (2.2k) = 0$$

$$I_B = 7.59 \mu A$$

$$I_C = \beta I_B = 1.366 mA$$

Applying KVL to C-E loop.


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$20 - (1.366 mA)(6.8k) - V_{CE} - (181)(7.56 \mu A)(2.2k) = 0$$

$$V_{CE} = 7.7V$$

$$Q = (7.7V, 1.366 mA)$$
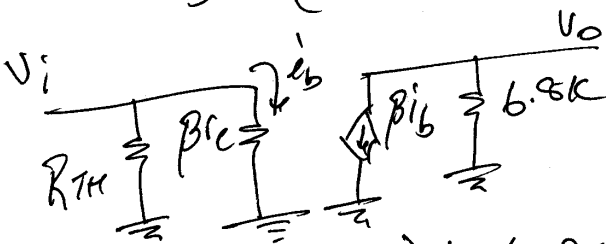
$$r_e = \frac{26mV}{I_C} = 19.03 \Omega$$



$$Z_i = R_{TH} // (\beta r_e) = 3.18 k\Omega$$

$$Z_o = 6.8 k\Omega$$


$$A_v = \frac{V_o}{V_i} = - \frac{\beta (6.8k)}{\beta r_e} = -357.33$$

$$A_i = - \frac{A_v Z_i}{6.8k} = 167.157$$



Tel: 23868356 / 23886023 / 9820246760 **POWER**

⑦

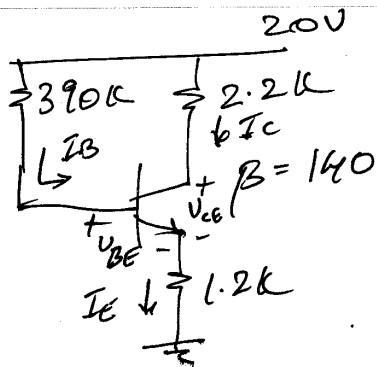

Applying KVL to BE loop

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$20 - (390k) I_B - 0.7 - (1.2k)(140 I_B) = 0$$

$$I_B = 34.51 \mu A$$

$$I_C = \beta I_B = 4.832 mA$$

Applying KVL to C-E loop.


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$20 - (4.832 mA)(2.2k) - V_{CE} - (141)(34.51 \mu A)(1.2k) = 0$$

$$V_{CE} = 3.53V$$

$$Q = (3.53V, 4.832 mA)$$

$$r_e = \frac{26mV}{I_C} = 5.38 \Omega$$

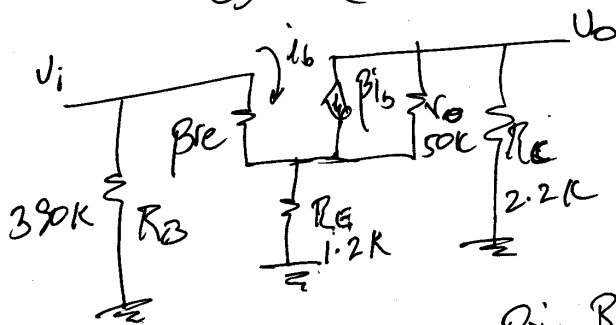

$$Z_b = \beta r_e + (1 + \beta) R_E$$

$$= \frac{170}{\beta} + (1 + \beta) R_E$$

$$Z_i = R_B \parallel Z_b = 118.37k$$

$$Z_o = R_C = 2.2k \Omega$$

$$A_v = \frac{V_o}{V_i} \approx \frac{-\beta i_b R_C}{\beta r_e i_b + (1 + \beta) R_E i_b} = -1.81$$

$$A_i = -\frac{A_v Z_i}{2.2k} = 97.5$$

NOTE: The reduced A_v gain is because of unbypassed R_E .

Abhishek Navlakhki


Tel: 9820246760 / 9769479368

navlakhki.com navlakhki.com navlakhki.com

Best One Can Get



⑧ $A_v = -10$ $r_e = 3.8 \Omega$

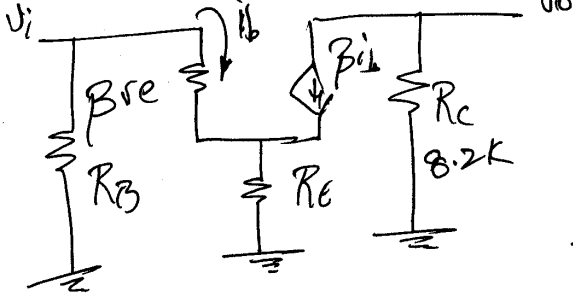

$$A_v = \frac{v_o}{v_i} = \frac{-\beta i_b R_C}{i_b \beta (r_e + R_E)}$$


$$-10 = -\frac{8.2k}{3.8\Omega + R_E}$$

$$R_E = 0.816 k\Omega$$

$$r_e = \frac{26mV}{I_E}$$

$$I_C = 6.842mA$$

$$I_B = \frac{I_C}{\beta} = 57.02\mu A$$

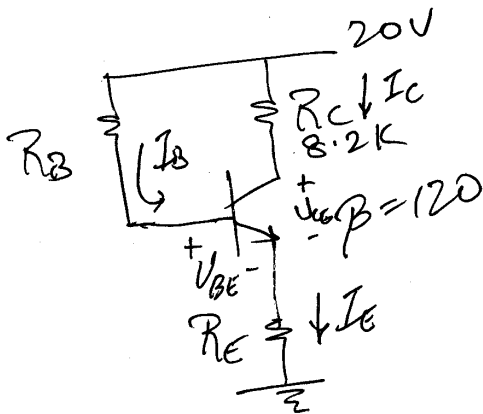


Applying KVL to B-E loop

$$20 - I_B R_B - V_{BE} - I_E R_E = 0$$

$$20 - (57.02\mu A) R_B - 0.7 - (120) I_B (0.816k) = 0$$

$$R_B = 239.74 k\Omega$$

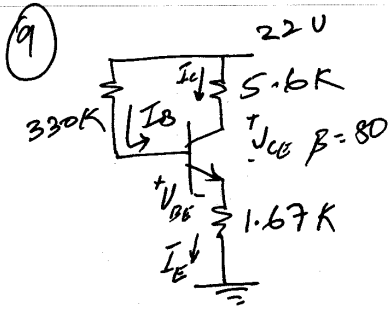

Applying KVL to B-E loop.

$$22 - (330k)I_B - 0.7 - (1.67k)I_E = 0$$

$$22 - (330k)I_B - 0.7 - (1.67k)(81)I_B = 0$$

$$I_B = 45.78 \mu A$$

$$I_C = \beta I_B = 3.66 \text{ mA}$$


Applying KVL to C-E loop.

$$22 - I_C(5.6k) - V_{CE} - (1.67k)I_E = 0$$

$$V_{CE} = -4.69 \text{ V}$$

$$Q \equiv (-4.69 \text{ V}, 3.66 \text{ mA})$$
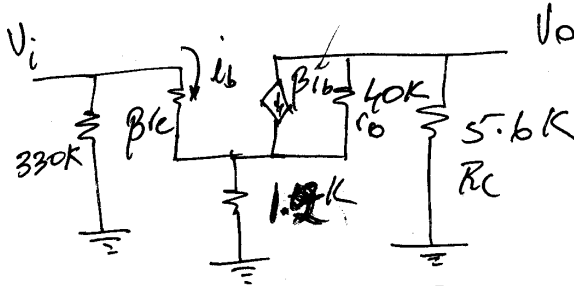
$$r_e = \frac{26 \text{ mV}}{I_C} = 7.1 \Omega$$



$$Z_i = 330k \parallel Z_B$$

$$Z_B = \beta r_e + (1 + \beta)(1.67k)$$

$$= 97.77k \Omega$$

$$Z_i = \underline{75.42 \text{ k}\Omega}$$

$$Z_o \approx R_C = \underline{5.6 \text{ k}\Omega}$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b R_C}{i_b Z_B}$$

$$A_v = \underline{-4.58}$$


$$A_i = \frac{-A_v Z_i}{R_C} = \underline{61.71}$$

Navlakhis

Navlakhis



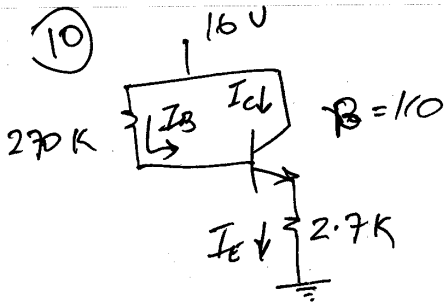Tel: 23868356 / 23886023 / 9820246760 **POWER**



Applying KVL to B-E loop

$$16 - (270K)I_B - V_{BE} - (2.7K)I_E = 0$$

$$I_B = \frac{16 - V_{BE}}{270K + 2.7K(110)} = 16.86 \mu A$$

$$I_C = \beta I_B = 110 \times 16.86 \mu A = 1.855 mA$$

Applying KVL to C-E loop.

$$16 - V_{CE} - I_E(2.7K) = 0$$

$$V_{CE} = 16 - 7.95 \times 2.7 = 7.95 V$$

$$r_e = \frac{26mV}{I_C} = \frac{26mV}{1.855mA} = 14.01 \Omega$$

$$Q = (7.95V, 1.855mA)$$


$$Z_i = 270K \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta)(R_E \parallel r_o)$$

$$= 110 \times 14.01 + (1 + 110)(2.7K \parallel 40K)$$

$$= 137.86 K\Omega$$

$$Z_i = 137.86 K\Omega$$

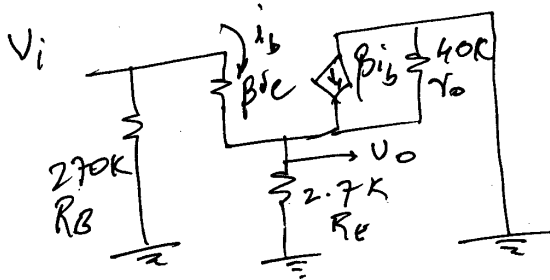

$$A_v = \frac{V_o}{V_i} = \frac{+i_b (1 + \beta)(R_E \parallel r_o)}{i_b Z_b}$$

$$= 0.997$$

$$Z_o = \frac{\beta r_e}{1 + \beta} \parallel R_E \parallel r_o$$

$$= \frac{110 \times 14.01}{1 + 110} \parallel 2.7K \parallel 40K$$

$$= 8.7 \Omega$$

$$A_i = -\frac{A_v Z_i}{R_E} = -\frac{0.997 \times 137.86K}{2.7K} = -50.88$$

Abhishek Navlakhis


navlakhis.com navlakhis.com navlakhis.com

Tel: 9820246760 / 9769479368

Best One Can Get



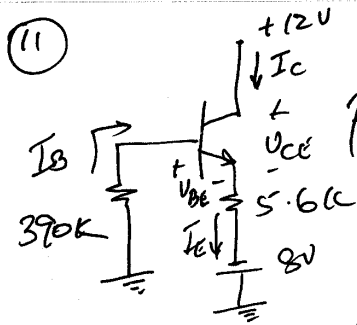Tel: 23868356 / 23886023 / 9820246760 **POWER**



Applying KVL to B-E loop

$$\beta = 120 \quad (390k) I_B - V_{BE} - (5.6k) I_E + 8V = 0$$

$$I_B = 6.84 \mu A$$

$$I_C = \beta I_B = 0.821 mA$$


Applying KVL to C-E loop

$$12 - V_{CE} - I_E (5.6k) + 8 = 0$$

$$V_{CE} = 15.365 V$$

$$Q = (15.37 V, 0.821 mA)$$
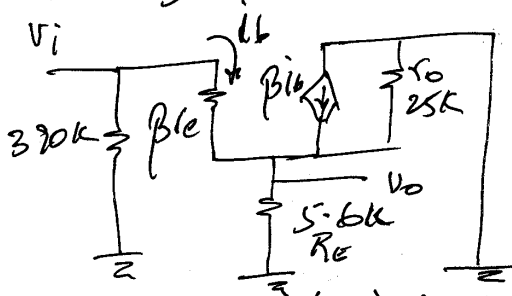
$$r_e = \frac{26mV}{I_E} = 31.67 \Omega$$



$$Z_i = 390k \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta)(R_E \parallel R_L)$$

$$= 557.4k \Omega$$

$$Z_i = 229.45k \Omega$$

$$Z_o = \frac{\beta r_e}{1 + \beta} \parallel R_E \parallel R_L$$

$$= 31.2 \Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{(\beta + 1) i_b (R_E \parallel R_L)}{i_b Z_b}$$

$$A_v = 0.993$$


$$A_i = -\frac{A_v Z_i}{R_E} = -40.69$$

$$A_v = \frac{V_o}{V_i}$$

$$0.993 = \frac{V_o}{1mV}$$

$$\therefore V_o = 0.993 mV$$

Abhishek Navlakhki

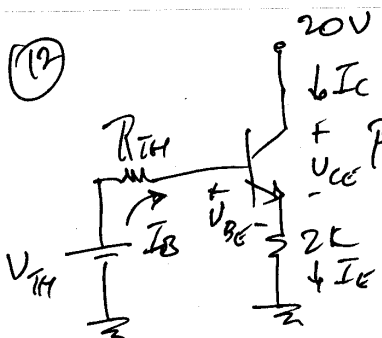

$$V_{TH} = \left(\frac{8.2}{8.2 + 56} \right) 20 = 2.55V$$

$$R_{TH} = 56k // 8.2k = 7.15k\Omega$$

Applying KVL to B-E loop

$$V_{TH} - I_B R_{TH} - V_{BE} - (1 + \beta) I_B (2k) = 0$$

$$I_B = 4.52 \mu A \quad I_C = \beta I_B = 0.90 mA$$


Applying KVL to C-E loop.

$$20 - V_{CE} - I_E (2k) = 0$$

$$V_{CE} = 18.18V$$

Q = (18.18V, 0.90mA)

$$r_c = \frac{26mV}{I_C} = 28.89\Omega$$

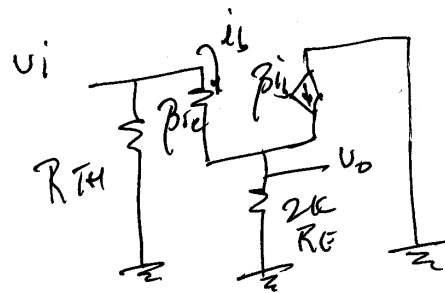

$$Z_i = R_{TH} // Z_b$$

$$Z_b = \beta r_{be} + (1 + \beta) R_E$$

$$= 407.78k\Omega$$

$$Z_i = 7.03k\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta) i_b R_E}{i_b Z_b}$$


$$Z_o = \frac{\beta r_{be}}{1 + \beta} // R_E = 28.34\Omega$$

$$A_v = 0.986$$

$$A_i = -\frac{A_v Z_i}{R_E} = -3.465$$



(13)

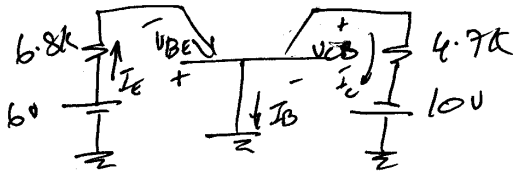

Applying KVL to B-E loop

$$6V - 6.8k(I_E) + V_{BE} = 0$$

$$6 - (6.8k) I_E - 0.7 = 0$$

$$I_E = 0.779mA$$

$$I_C = \beta I_E = 0.778mA$$

Applying KVL to C-B loop


$$-10 + (4.7k) I_C - V_{CB} = 0$$

$$V_{CB} = -6.34V$$

$$Q \equiv (-6.34V, 0.778mA)$$

$$r_e = \frac{26mV}{I_C}$$

$$= 33.42\Omega$$

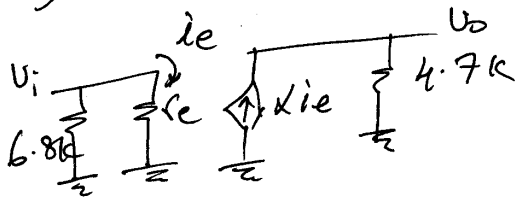

$$Z_i = 6.8k \parallel r_e$$

$$= 33.26\Omega$$

$$Z_o = 4.7k\Omega$$


$$A_v = \frac{v_o}{v_i} = \frac{\beta i_e (4.7k)}{\beta i_e r_e}$$

$$= \underline{140.35}$$

$$A_i = -\frac{A_v Z_i}{R_c} = \underline{-0.993}$$



(14)

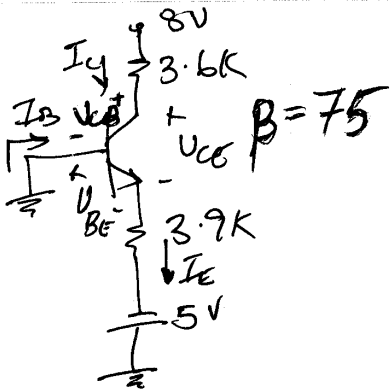

Applying KVL to B-E loop

$$-V_{BE} - I_E(3.9k) + 5 = 0$$

$$-0.7 - (1+\beta)(3.9k) I_B + 5 = 0$$

$$I_B = \frac{5 - 0.7}{(76)(3.9k)} = 14.51 \mu A$$


$$I_C = \beta I_B = 1.09 mA$$

Applying KVL to C-B loop

$$0 - I_C(3.6k) - V_{CB} = 0$$

$$V_{CB} = 4.076 V$$

$$Q \equiv (4.076 V, 1.09 mA)$$

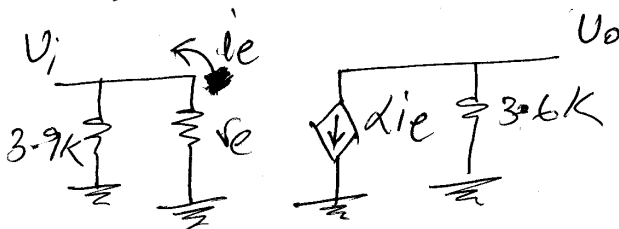

$$A_v = \frac{V_o}{V_i} = \frac{-\alpha i_e (3.6k)}{-i_e r_e} = 148.95$$

$$A_v^* = \frac{-A_v Z_i}{R_c} = 0.981$$

$$r_c = \frac{26mV}{I_C} = 23.85 \Omega$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\alpha = \frac{\beta}{1+\beta} = 0.9868$$

$$Z_i = 3.9k // r_e = 23.71 \Omega$$

$$Z_o = 3.6k$$


Navlakhis

Navlakhis



Tel: 23868356 / 23886023 / 9820246760 **POWER**

15

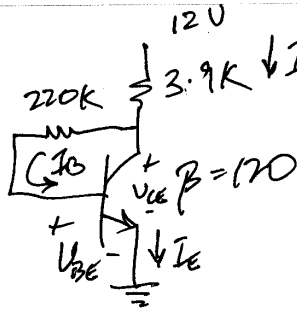

Applying KVL to B-E loop

$$12 - 3.9k(Ic) - (220k)Ib - V_{BE} = 0$$

$$12 - (3.9k)(120)Ib - (220k)Ib - 0.7 = 0$$

$$Ib = 16.33 \mu A$$


$$Ic = \beta Ib = 1.96 mA$$

Applying KVL to C-E loop

$$12 - (3.9k)Ic - V_{CE} = 0$$

$$V_{CE} = 4.29 V$$

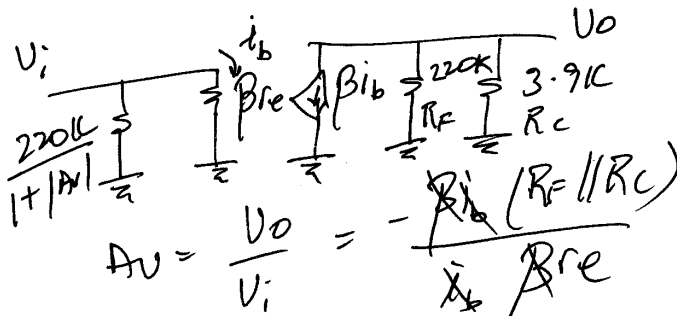$Q = (4.29 V, 1.96 mA)$ $r_e = \frac{26mV}{Ic} = 13.27 \Omega$



$$A_v = \frac{V_o}{V_i} = - \frac{\beta i_b (R_c || R_F)}{i_b \beta r_e}$$

$$A_v = -288.78$$

$$A_i = - \frac{A_v Z_i}{R_c}$$

$$= 38.07$$

$$Z_i = \frac{220k}{1 + \beta} || \beta r_e$$

$$= 514.1 \Omega$$

$$Z_o = R_c || R_F$$


$$= 3.83 k\Omega$$

Abhishek Navlakhis

Tel: 9820246760 / 9769479368

navlakhis.com navlakhis.com navlakhis.com

Best One Can Get

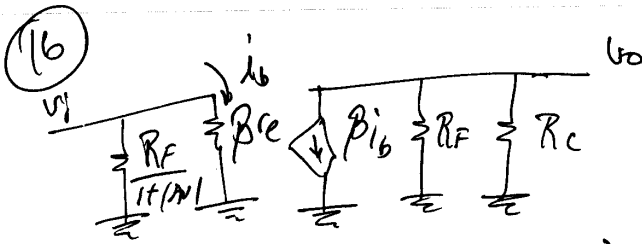

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_F \parallel R_C)}{i_b R_E}$$

$$A_i = -\frac{A_v Z_i}{R_C}$$

$$19 = \frac{160 (2000 \parallel \frac{R_F}{161})}{R_C}$$

$$\frac{1}{(160 \times 10)} = \left(\frac{1}{R_F} + \frac{1}{R_C} \right)$$

$$\frac{1}{R_C} = \frac{19}{160 (2000 \parallel \frac{R_F}{161})} \quad \text{--- (2)}$$

$$\frac{1}{R_C} = \frac{1}{1600} - \frac{1}{R_F} \quad \text{--- (1)}$$

From (1) & (2)

~~$$\frac{1}{1600} - \frac{1}{R_F} = \frac{19 (2000 R_F)}{160 (R_F + 2000 \times 161)}$$~~

~~$$\frac{R_F - 1600}{1600 R_F} = \frac{38000 R_F}{(R_F + 322000) 160}$$~~

~~$$R_F^2 + 320400 R_F - 5152 \times 10^5 = 38000 R_F^2$$~~

~~$$37999 R_F^2 - 320400 R_F + 5152 \times 10^5 = 0$$~~

~~$$R_F^2 - 8.432 R_F + 13558.25 = 0$$~~

~~$$\frac{1}{1600} - \frac{1}{R_F} = \frac{19 (R_F + 2000 \times 161)}{160 (2000 R_F)}$$~~

~~$$\frac{R_F - 1600}{1600 R_F} = \frac{19 (R_F + 322000)}{160 (2000 R_F)}$$~~




$$200 R_F - 320000 = 19 R_F + 6118000$$

$$R_F = \underline{35.57 K\Omega}$$

sub in ①

$$\frac{1}{R_C} = \frac{1}{1600} - \frac{1}{35.57 K}$$
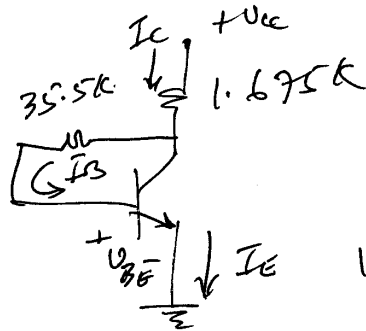
$$\therefore R_C = \underline{1.675 K\Omega}$$




Applying KVL to B-E loop

$$V_{CC} - I_C (1.675 K) - I_B (35.57 K) - V_{BE} = 0$$

$$V_{CC} - \frac{26 mV}{r_e} (1.675 K) - \frac{26 mV}{\beta r_e} (35.57 K) - 0.7 = 0$$

$$V_{CC} = \underline{5.52 V}$$

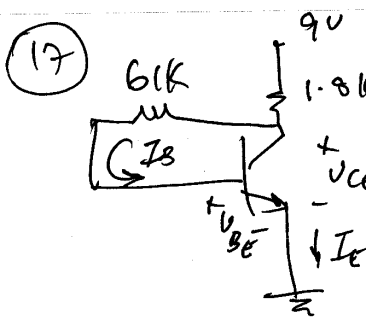

Applying KVL to B-E loop

$$9 - (1.8k) I_C - (6k) I_B - V_{BE} = 0$$

$$9 - (1.8k) (\beta) I_B - (6k) I_B - 0.7 = 0$$

$$I_B = 40.14 \mu A$$

$$I_C = \beta I_B = 3.21 mA$$


Applying KVL to C-E loop.

$$9 - (1.8k) I_C - V_{CE} = 0$$

$$V_{CE} = 3.148 V$$

$Q = (3.148 V, 3.21 mA)$

$$r_e = \frac{26mV}{I_C} = 8.1 \Omega$$

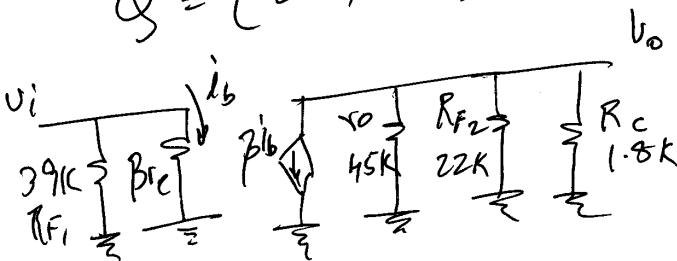

$$Z_i = R_{F1} \parallel \beta r_e$$

$$= 637.4 \Omega$$


$$Z_o = 45k \parallel 22k \parallel 1.8k$$

$$= 1.60 k\Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{-\beta i_b (R_{F2} \parallel R_C)}{\beta r_e}$$

$$= -198.1$$

$$A_i = \frac{-A_v Z_i}{R_C} = 70.15$$

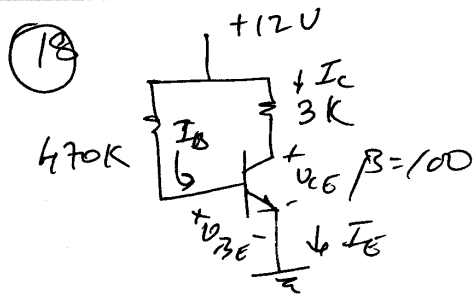

Applying KVL to B-E loop

$$12 - (470k)I_B - V_{BE} = 0$$

$$I_B = 24.04 \mu A$$

$$I_C = \beta I_B = 2.404 mA$$


Applying KVL to C-E loop.

$$12 - (3k)I_C - V_{CE} = 0$$

$$V_{CE} = 4.788 V$$

$$Q = (4.788 V, 2.404 mA)$$
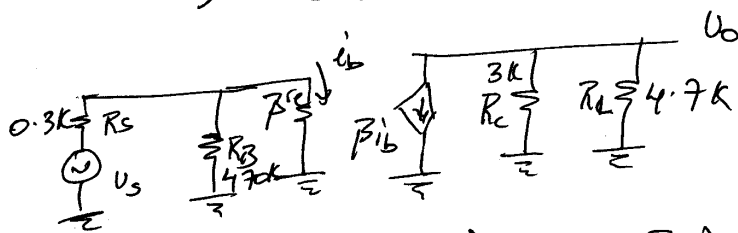
$$r_e = \frac{26mV}{I_C} = 10.82 \Omega$$



$$Z_i = R_B \parallel \beta r_e = 1.08 k\Omega$$

$$Z_o = R_C = 3k$$

$$A_v = \frac{V_o}{V_i} = - \frac{\beta (R_C \parallel R_L)}{r_e}$$

$$A_v = -169.24$$


$$A_i = \frac{-A_v Z_i}{R_L} = 38.89$$

$$A_{v_s} = \frac{Z_i}{Z_i + R_s} \cdot A_v = -132.45$$

$$A_{i_s} = \frac{-A_{v_s} (Z_i + R_s)}{R_L} = 38.89$$



(19)

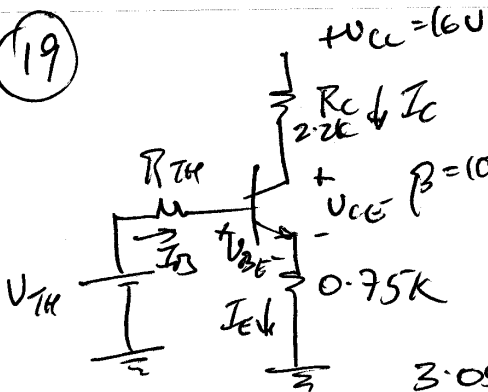

$$R_{TH} = 68k // 16k = 12.95k\Omega$$

$$V_{TH} = \left(\frac{16}{16+68} \right) 16 = 3.05V$$

Applying KVL to B-E loop

$$V_{TH} - I_B R_{TH} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$3.05 - I_B (12.95k) - 0.7 - (101)(0.75k) I_B = 0$$

$$I_B = 26.5 \mu A$$

$$I_C = \beta I_B = 2.65 mA$$

Applying KVL to C-E loop


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$16 - (2.65mA)(2.2k) - V_{CE} - (101)(26.5 \mu A)(0.75k) = 0$$

$$V_{CE} = 8.16 V$$

$$Q = (8.16 V, 2.65 mA)$$

$$r_e = \frac{26mV}{I_C} = 9.81 \Omega$$

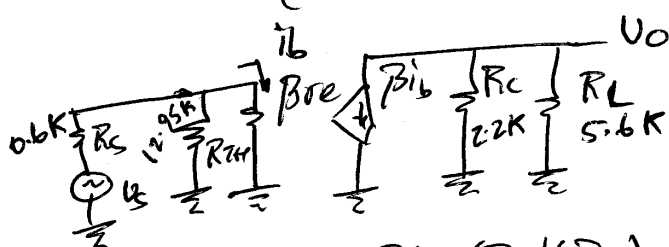

$$Z_i = 12.95k // \beta r_e$$

$$= 911.92 \Omega$$

$$Z_o = R_C = 2.2k \Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_C // R_L)}{i_b \beta r_e}$$

$$A_v = -161$$

$$A_i = -\frac{A_v Z_i}{R_L} = 26.22$$

$$A_{v_s} = \frac{Z_i}{Z_i + R_s} \cdot A_v$$

$$= -97.11$$

$$A_{v_s} = -\frac{A_{v_s} (Z_i + R_s)}{R_C}$$

$$= 26.22$$

Abhishek Navlakhii


Tel: 9820246760 / 9769479368

navlakhii.com navlakhii.com navlakhii.com

Best One Can Get



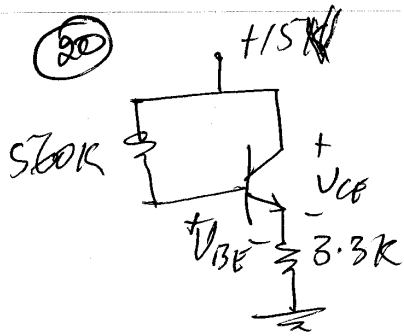Tel: 23868356 / 23886023 / 9820246760 **POWER**



Applying KVL to B-E loop
 $15 - 560k I_B - V_{BE} - 3.3k I_E = 0$
 $15 - 560k I_B - 0.7 - 3.3k(1+\beta)I_B = 0$

$$I_B = \frac{15 - 0.7}{560k + (66)(3.3k)}$$


$$I_B = 18.39 \mu A$$

$$I_C = \beta I_B = 1.195 mA$$

Applying KVL to CE loop
 $15 - V_{CE} - I_E(3.3k) = 0$
 $V_{CE} = 11V$

$$Q = (11V, 1.195mA)$$
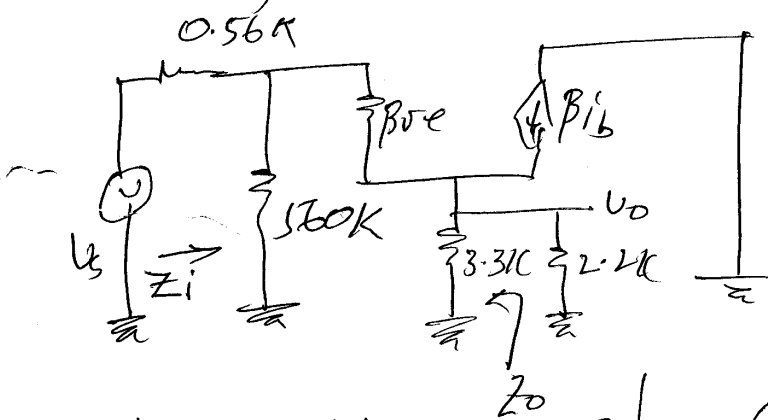
$$r_e = \frac{26mV}{I_C} = 21.76 \Omega$$



$$Z_i = 560k \parallel [\beta r_e + (1+\beta)(3.3k/2.2k)]$$

$$Z_i = 76.45 k\Omega$$

$$A_v = \frac{V_o}{V_i} = \frac{(1+\beta) i_b [3.3k/2.2k]}{i_b [\beta r_e + (1+\beta)(3.3k/2.2k)]}$$


$$A_v = 0.984$$

$$A_i = -\frac{A_v Z_i}{2.2k} = -34.19$$

$$Z_o = 29.56 \Omega$$

Abhishek Navlakhia

(21)

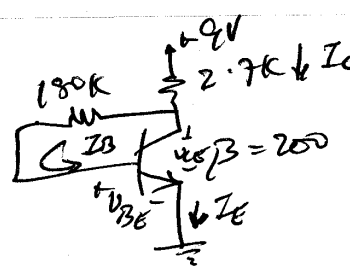


Applying KVL to B-E loop
 $9 - (2.7k) I_C - (180k) I_B - V_{BE} = 0$
 $I_B = 11.48 \mu A$
 $I_C = \beta I_B = 2.3 mA$

Applying KVL to C-E loop:

$9 - (2.7k) I_C - V_{CE} = 0$
 $V_{CE} = 2.77 V$
 $Q = (2.77 V, 2.3 mA)$

$r_e = \frac{26mV}{I_C} = 11.3 \Omega$

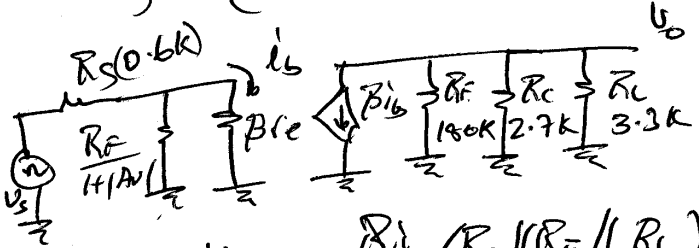

$Z_o = R_C \parallel R_L = \underline{\underline{2.66 k\Omega}}$

$A_v = \frac{V_o}{V_i} = \frac{-\beta i_b (R_C \parallel R_L)}{\beta i_b r_e}$

$A_v = \underline{\underline{-130.34}}$

$Z_i = \frac{R_F}{131.34} \parallel \beta r_e$

$Z_i = 853.14 \Omega$


$A_i = \frac{-A_v Z_i}{R_L} = \underline{\underline{33.7}}$

$A_{v_s} = \frac{Z_i}{Z_i + R_s} \cdot A_v = \underline{\underline{-76.52}}$

$A_{i_s} = \frac{-A_{v_s} (Z_i + R_s)}{R_L} = \underline{\underline{33.7}}$



(22)

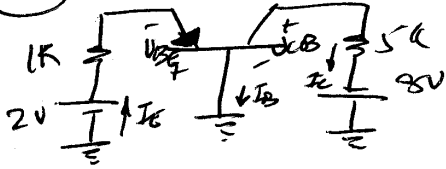

Applying KVL to B-E loop

$$2 - I_E(1k) + V_{BE} = 0$$

$$2 - (1k) I_E - 0.7 = 0$$

$$I_E = 1.3 \text{ mA}$$

$$I_C = \alpha I_E = 1.3 \text{ mA}$$

Applying KVL to C-B loop.


$$-8 + I_C(5k) - V_{CB} = 0$$

$$V_{CB} = -1.5 \text{ V}$$

$$Q \equiv (-1.5 \text{ V}, 1.3 \text{ mA})$$

$$r_e = \frac{26 \text{ mV}}{I_C}$$

$$= 20 \Omega$$

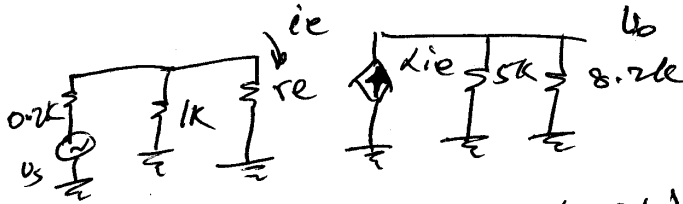

$$Z_i = 1k \parallel r_e$$

$$= 19.6 \Omega$$

$$Z_o = R_C = 5k \Omega$$


$$A_v = \frac{U_o}{U_i} = \alpha \frac{i_e (5k \parallel 8.2k)}{i_e r_e}$$

$$A_v = \underline{\underline{155.3}}$$

$$A_i = - \frac{A_v Z_i}{8.2k} = - \underline{\underline{0.37}}$$

$$A_{v_s} = \frac{Z_i}{Z_i + R_s} A_v = \underline{\underline{13.86}}$$
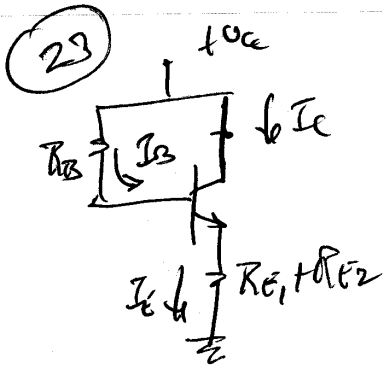
$$A_{i_s} = - \frac{A_{v_s} (Z_i + R_s)}{8.2k} = - \underline{\underline{0.37}}$$




Applying KVL to B-E loop
 $V_{CC} - I_B R_B - V_{BE} - (I_B)(R_{E1} + R_{E2}) = 0$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)(R_{E1} + R_{E2})}$$

$$I_{CQ} = \beta I_B$$

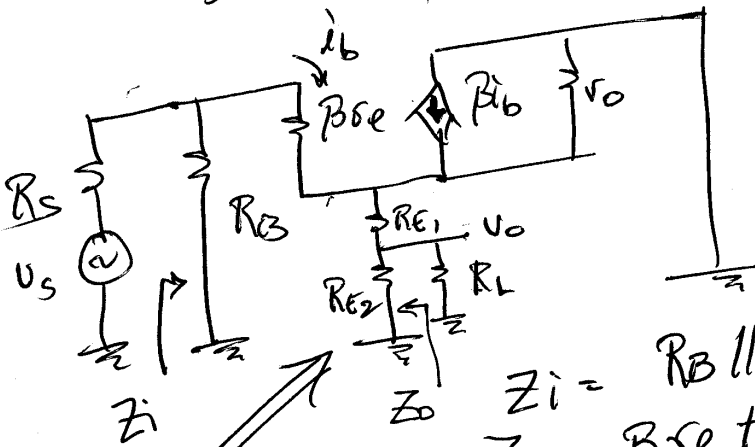Applying KVL to C-E loop
 $V_{CC} - V_{CEQ} - I_{CQ}(R_C) - I_{EQ}(R_{E1} + R_{E2}) = 0$
 $V_{CEQ} = V_{CC} - (1 + \beta)I_B(R_{E1} + R_{E2}) - I_{CQ}R_C$
 $Q = (V_{CEQ}, I_{CQ})$
 $r_{ce} = \frac{26mV}{I_{CQ}}$



$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (1 + \beta) \left[(R_{E2} \parallel R_L) + R_{E1} \parallel r_o \right]$$

$$Z_o = \left[\frac{(R_S \parallel R_B) + \beta r_e}{1 + \beta} \parallel r_o \right] + R_{E1} \parallel R_{E2}$$






$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta) i_b \left[(R_L \parallel R_{E2}) \right]}{i_b Z_b}$$

$$A_i = -\frac{A_v Z_i}{R_L}$$

$$A_{vS} = \frac{Z_i}{Z_i + R_S} A_v$$

$$A_{iS} = -\frac{A_{vS} (Z_i + R_S)}{R_L}$$

Abhishek Navlakhia

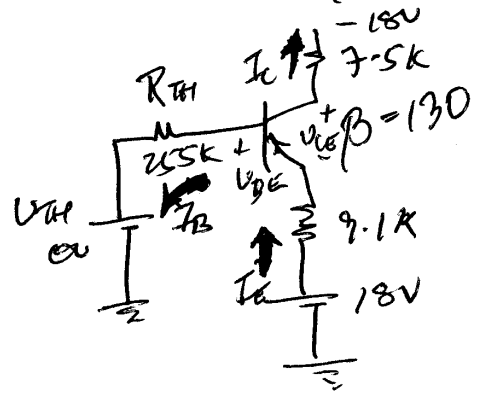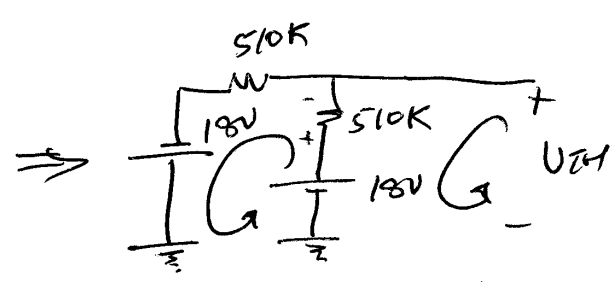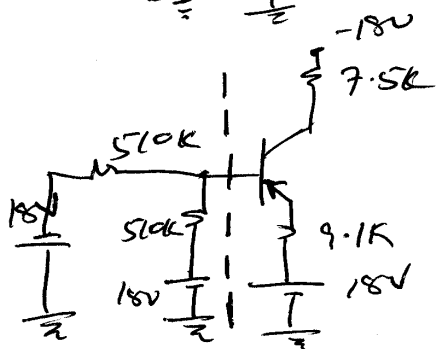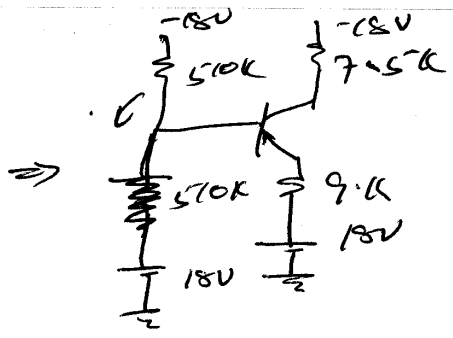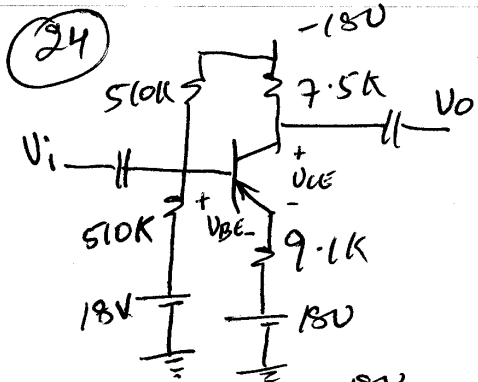

$$18 - (510K)I - (510K)I + 18 = 0$$

$$I = 0.035A$$

$$V_{th} + (510K)I - 18 = 0$$

$$V_{th} = 0V$$

$$R_{th} = 255K$$

Applying KVL to B-E loop

$$18 - I_E(9.1K) + V_{BE} - I_B(255K) = 0$$

$$18 - (131)I_B(9.1K) - 0.7 - (255K)I_B = 0$$

$$I_B = 11.95 \mu A$$

$$I_C = \beta I_B = 1.55 mA$$

Applying KVL to C-E loop

$$-18 + I_C(7.5K) - V_{CE} + I_E(9.1K) - 18 = 0$$

$$V_{CE} = -10.13V$$

$$Q = (-10.13V, 1.55 mA)$$


Abhishek Navlakhhi

Tel: 9820246760 / 9769479368

navlakhhi.com navlakhhi.com navlakhhi.com

Best One Can Get
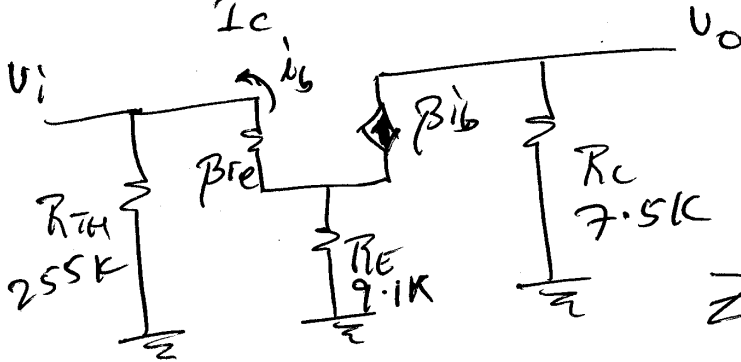
$$r_e = \frac{26mV}{I_c} = 16.77 \Omega \quad \beta_{ac} = 150$$



$$Z_o = 7.5K$$

$$Z_i = R_{TH} \parallel Z_b$$

$$Z_b = \beta_{ac} r_e + (1 + \beta_{ac}) R_E = 1.38 M\Omega$$

$$Z_i = 215.15 K\Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{\beta_{ac} R_C}{-r_b Z_b}$$

$$A_v = -0.815$$

$$A_i = -\frac{A_v Z_i}{R_C} = 23.39$$