

4.7.1 Diode Compensation for V_{BE} :

The voltage divider bias circuit with diode compensation is as shown in Fig. 4.7.1. The additional power supply V_{DD} is connected in order to forward bias the diode D . The diode is of same material and type as the transistor. The voltage V_F across the diode has the same temperature coefficient ($-2.5 \text{ mV}/^\circ\text{C}$) as that of the base to emitter voltage V_{BE} .

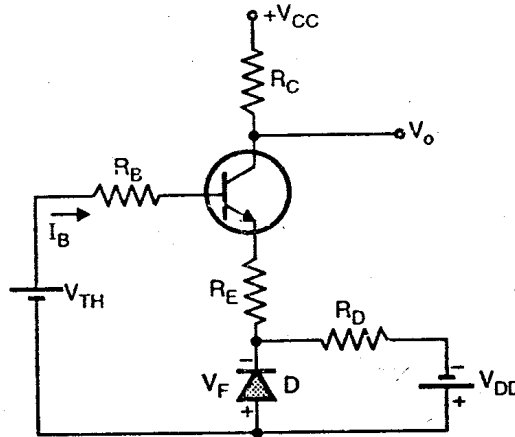


Fig. 4.7.1 : Diode compensation for V_{BE}

How does the compensation take place ?

From Fig. 4.7.1 the KVL for the base circuit gives :

$$V_{TH} = I_B R_B + V_{BE} + (I_B + I_C) R_E - V_F \quad \dots(4.7.1)$$

$$\text{But, } I_C = \beta_{dc} I_B + (1 + \beta_{dc}) I_{CBO} \quad \dots(4.7.2)$$

$$\therefore V_{TH} = I_B (R_B + R_E) + V_{BE} + I_C R_E - V_F \quad \dots(4.7.3)$$

$$\text{From Equation (4.7.2) } I_B = \frac{I_C}{\beta_{dc}} - \frac{(1 + \beta_{dc}) I_{CBO}}{\beta_{dc}}$$

Substituting this value in Equation (4.7.3) we get,

$$V_{TH} = \frac{I_C}{\beta_{dc}} (R_B + R_E) - \frac{(1 + \beta_{dc})(R_B + R_E)}{\beta_{dc}} I_{CBO} + V_{BE} + I_C R_E - V_F$$

$$\therefore V_{TH} = V_{BE} - V_F + \frac{R_B + R_E (1 + \beta_{dc})}{\beta_{dc}} I_C - \frac{(R_B + R_E)}{\beta_{dc}} (1 + \beta_{dc}) I_{CBO} \quad \dots(4.7.4)$$

As the diode is made of same material as that of the transistor and has the same temperature coefficient, the change in voltage across the diode (V_F) will be equal to change in V_{BE} due to temperature. In Equation (4.7.4) these terms have opposite sign. Hence the change in V_{TH} is compensated by change in V_F and I_C will become insensitive to variations in V_{BE} .

4.7.2 Diode Compensation for I_{CO} :

For the germanium transistors, changes in I_{CO} due to change in temperature is more important than changes in V_{BE} due to temperature. The diode compensation circuit shown in Fig. 4.7.2 offers the stabilization against variation in I_{CO} .

How is the compensation provided ?

- (i) The diode and the transistor are of same type and material. Therefore the reverse saturation current of the diode i.e. I_O will increase with temperature at the same rate as the current I_{CO} .

- (ii) Referring to Fig. 4.7.2. We can write that,

$$I = \frac{V_{CC} - V_{BE}}{R_1} \approx \frac{V_{CC}}{R_1} = \text{constant}$$

- (iii) The base current $I_B = I - I_O$. Now substitute this value of I_B in the following equation :

$$\begin{aligned} I_C &= \beta_{dc} I_B + (1 + \beta_{dc}) I_{CO} \\ &= \beta_{dc} (I - I_O) + (1 + \beta_{dc}) I_{CO} \end{aligned}$$

$$\therefore I_C = \beta_{dc} I - \beta_{dc} I_O + (1 + \beta_{dc}) I_{CO} \quad \dots(4.7.5)$$

- (iv) Looking at the last two terms of Equation (4.7.5), we conclude that if $\beta \gg 1$ and if I_O of D and I_{CO} of the transistor track each other over the desired temperature range then I_C will remain constant. Thus compensation is provided.

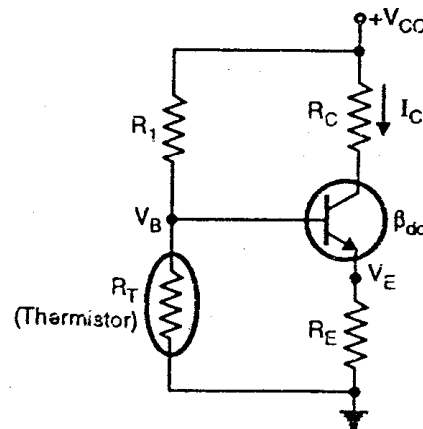
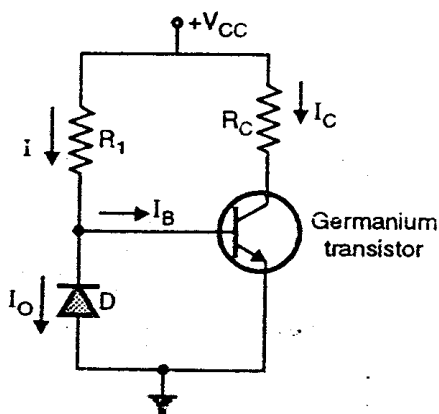


Fig. 4.7.2 : Diode compensation for I_{CO} Fig. 4.7.3 : Bias compensation using a thermistor

4.7.3 Bias Compensation using Thermistor :

In the two previous circuits we have seen how to use a diode for compensation. Now let us see how a thermistor can be used for compensation. Thermistor is a resistor the resistance of which is temperature dependent. Its resistance decreases exponentially with increase in temperature. Hence it has a negative temperature coefficient of resistivity.

The use of thermistor for bias compensation is demonstrated in Fig. 4.7.3.

Operation of the circuit :

As we have seen earlier with increase in temperature, the collector current I_C tends to increase. Now let us see how this increased I_C is reduced.

- (i) As the temperature increases, resistance R_T of the thermistor decreases.
- (ii) Due to decrease in R_T voltage drop across R_T also decreases.
- (iii) This reduces V_B and therefore V_{BE} of the transistor.
- (iv) Due to reduction in V_{BE} , the base current I_B decreases which in turn will reduce the increased collector current I_C . Thus the compensation is achieved.

4.7.4 Bias Compensation using Sensistor :

The bias compensation circuit using a sensistor is shown in Fig. 4.7.4. Sensistor is a temperature dependent resistance, the resistance of which increases with increase in temperature. Thus it has a positive temperature coefficient of resistivity.

Operation of the circuit :

- (i) As the temperature increases, R_T increases.
- (ii) As R_T increases, voltage drop across R_2 i.e. V_B will decrease.
- (iii) As V_B decreases, V_{BE} also will decrease. Due to reduction in V_{BE} , base current I_B will decrease.
- (iv) This will reduce the increased I_C due to increase in I_{CBO} with temperature. Thus the compensation is achieved.

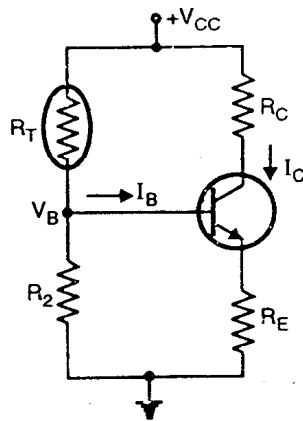


Fig. 4.7.4 : Bias compensation using a sensistor