

NAVLAKHI'S

Navlakhi's



Chapter 1

AC – DC Networks

[Classwork Supplement]

Kunal Navlakhi

BE Electronics/Entrepreneurship management, Welingkar

Tel: 9820246760 / 9769479368

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Best One Can Get

NAVLAKHI'S

KNOW YOUR INSTRUCTORS

NAME:	<i>Kunal Navlakhi</i>
QUALIFICATION:	<i>B.E. Electronics and Entrepreneurship Management, Welingkar</i>
INDUSTRY EXPERIENCE:	<i>2 years in Educational Technology Unit at NCST</i>
SOME ACADEMIC ACHIEVEMENTS:	<ul style="list-style-type: none">• <i>First class each year in engineering</i>• <i>88/100 in Maths2</i>• <i>Distinction in sem8</i>

OTHER INSTRUCTOR AT NAVLAKHI'S

NAME:	<i>Abhishek Navlakhi</i>
QUALIFICATION:	<i>B.E. Computers</i>
INDUSTRY EXPERIENCE:	<i>2 years as system analyst/programmer at CMC Ltd.</i>
SOME ACADEMIC ACHIEVEMENTS:	<ul style="list-style-type: none">• <i>First class each year in engineering</i><ul style="list-style-type: none">• <i>80/100 in ED</i>• <i>92 percentile in Data Structures at all India NCST G level examination</i><ul style="list-style-type: none">• <i>100/100 in physics at hsc</i>• <i>89.5% aggregate In hsc</i>• <i>192/200 in electronics at hsc</i>

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Page 2

Best One Can Get

NAVLAKHI'S

• PROBLEMS •

Mesh analysis :

1. Find currents I_x and I_y .

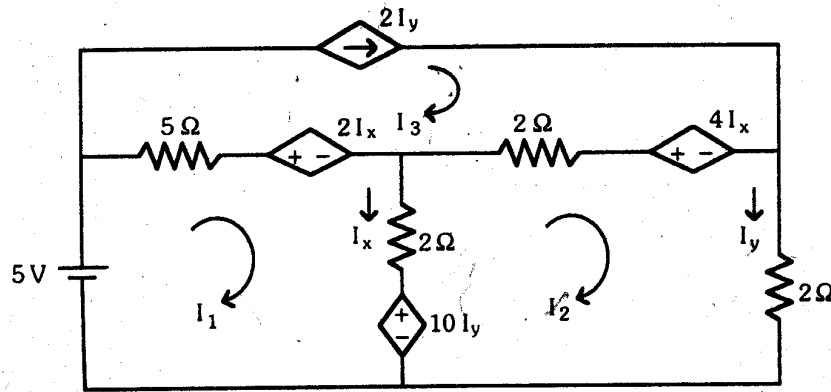


Fig.

(0.5 A, 0.1 A)

2. Use mesh analysis to find V_3 if element A is

- Short circuit
- a 5Ω resistor
- 20 V independent voltage source, positive reference on the right.
- a dependent voltage source of $1.5 i_1$ with positive reference on the right.
- a dependent current source $5 i_1$ arrow directed to the right.

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Page 3

Best One Can Get

NAVLAKHI'S

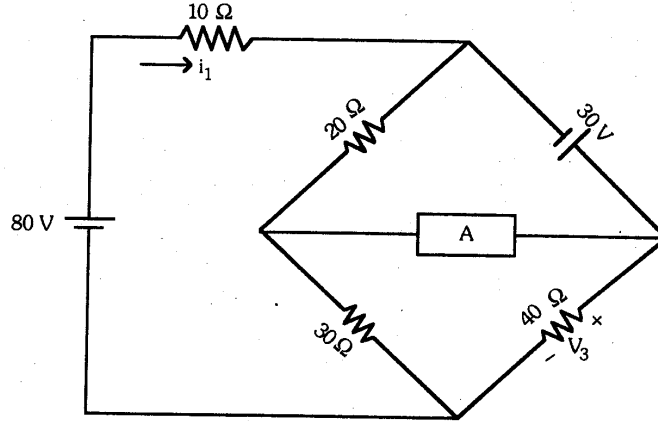


Fig.

(69.4 V, 72.38 V, 73.68 V, 70.71 V, 97.39 V)

3. Find I_1 if the dependent voltage is labelled (i) $2 V_2$ (ii) $1.5 V_3$.

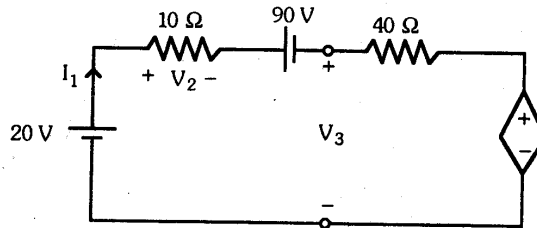


Fig.

(-1 A, 1 A)

4. Find currents I_1 , I_2 and I_3 .

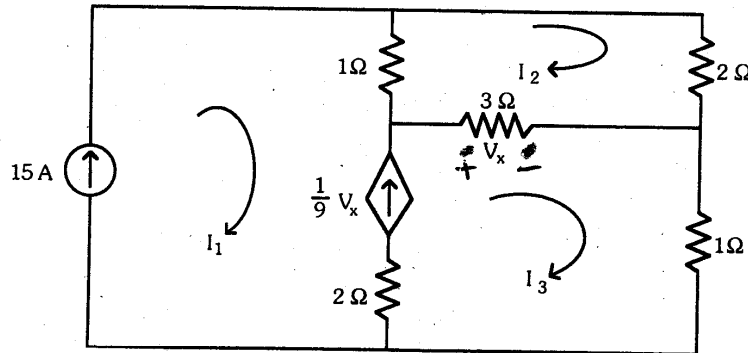


Fig.

(15 A, 11 A, 17 A)

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

5. Find current I_x .

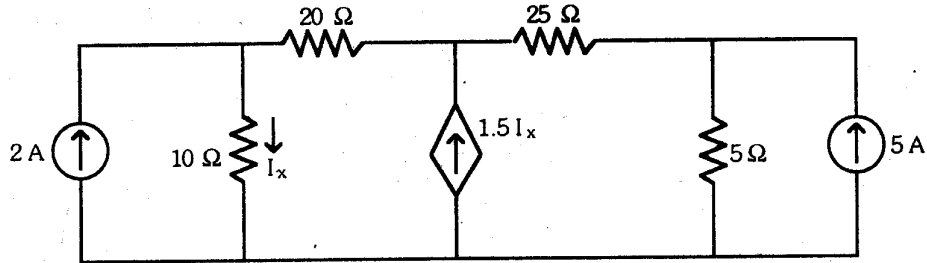


Fig.

(8.33 A)

6. Find current I_1 .

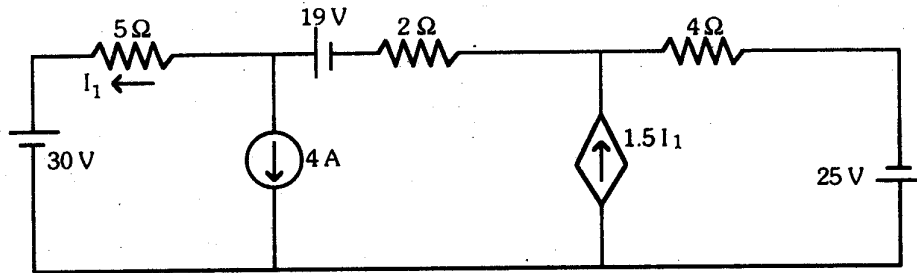


Fig.

(-12 A)

7. Find the current through $3 + j4 \Omega$ impedance.

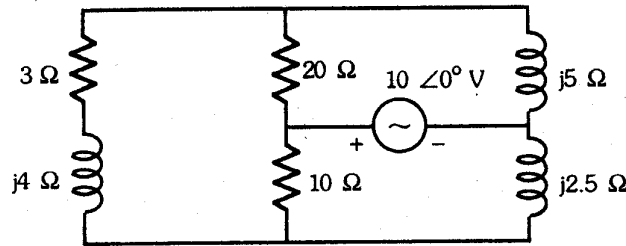


Fig.

[0]

8. In the network of Fig. find V_0 .

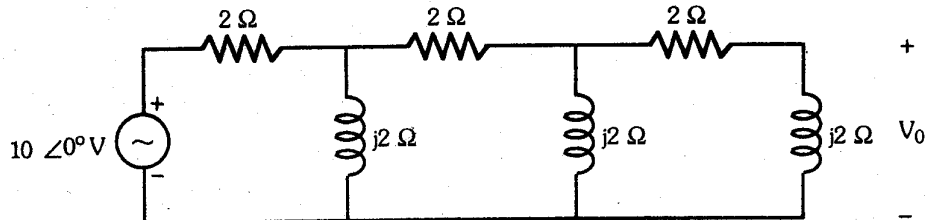


Fig.

[1.56 \angle 128.7° V]

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

9. Find the current I_3 in the network of Fig.

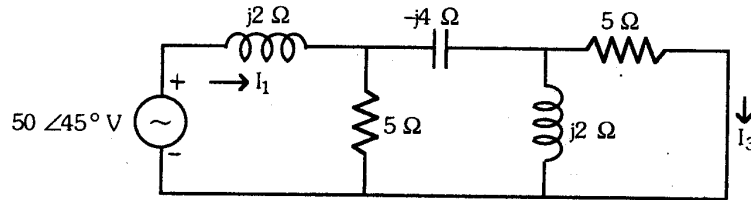


Fig.

[11.6 $\angle 113.2^\circ$ A]

10. In the network of Fig. find V_2 which results in zero current through 4 Ω resistor.

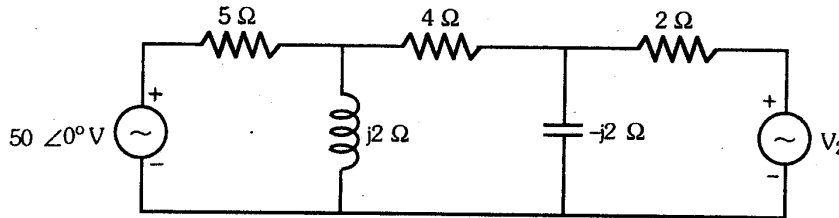


Fig.

[26.3 $\angle 113.2^\circ$ V]

Nodal analysis :

11. Find voltage V_x .

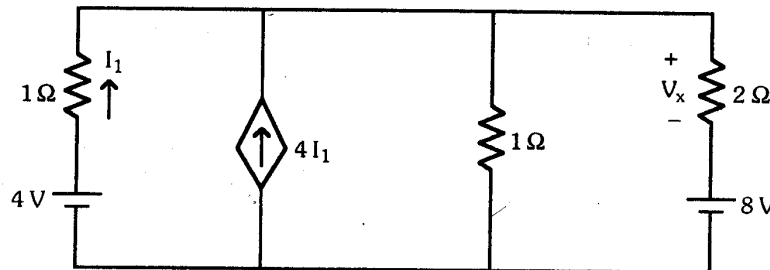


Fig.

(-4.31 V)

12. Find voltage V_x .

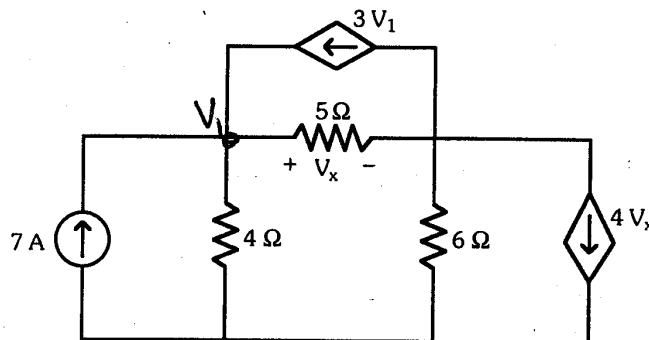


Fig.

(2.09 V)

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

13. Find voltage V_x .

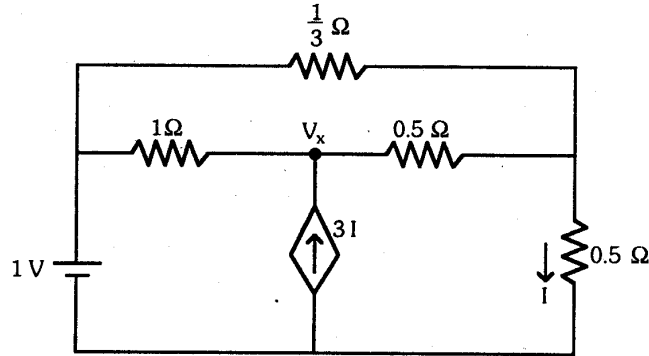


Fig.

(6.2 V)

14. Determine V_1 .

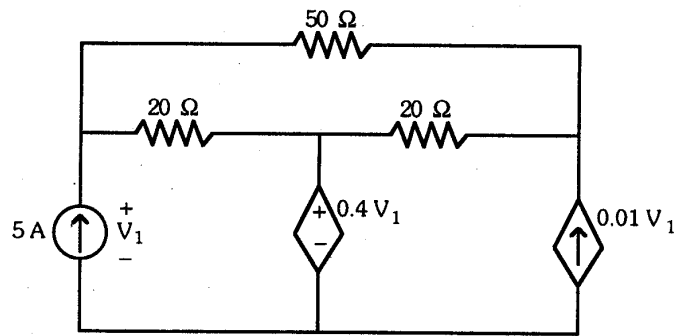


Fig.

(140 V)

15. Find voltage V_y .

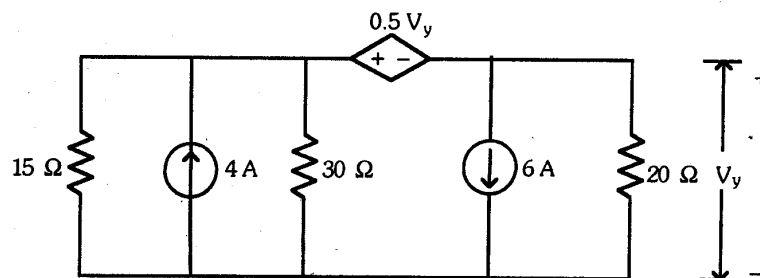


Fig.

(-10 V)

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

NAVLAKHI'S

16. Find voltage V_2 .

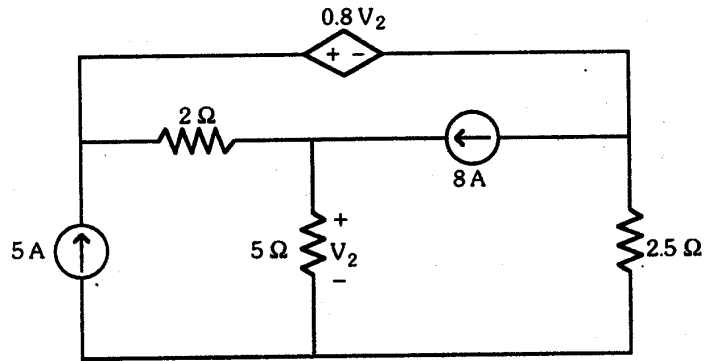


Fig.

(25.9 V)

17. For the network shown in Fig., find the voltage V_{AB} .

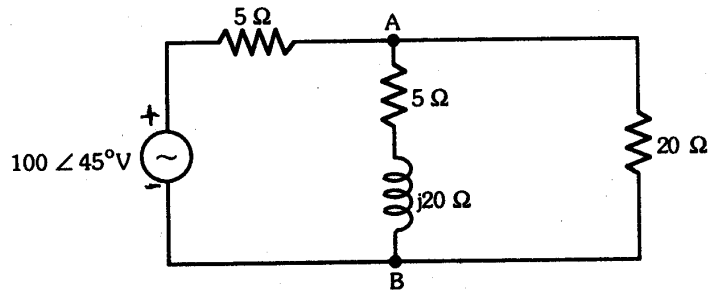


Fig.

[75.4 ∠55.2° V]

18. Find the voltages at nodes 1 and 2 in the network of Fig.

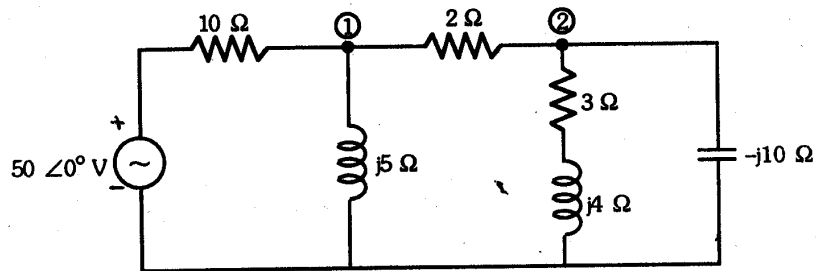


Fig.

[15.95 ∠49.94° V, 12.9 ∠55.5° V]

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

✓ 19. In the network of Fig. find current in the $10 \angle 30^\circ$ V source.

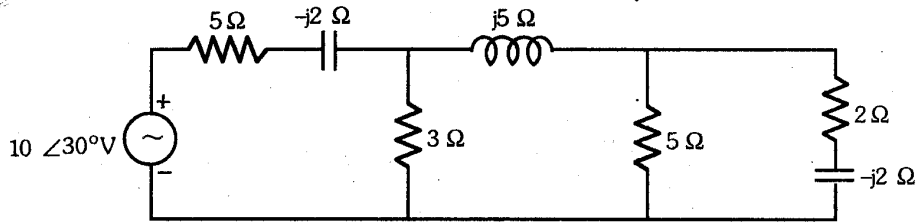


Fig.

[1.44 $\angle 38.8^\circ$ A]

Superposition theorem :

20. Find voltage V_x .

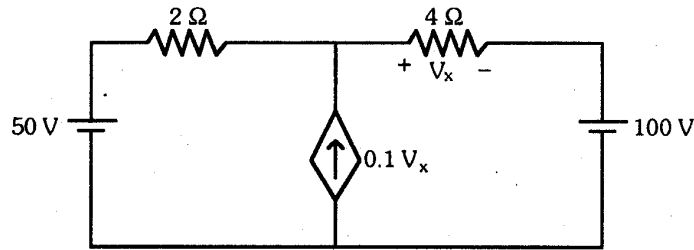


Fig.

(-38.5 V)

21. Determine voltages V_1 and V_2 .

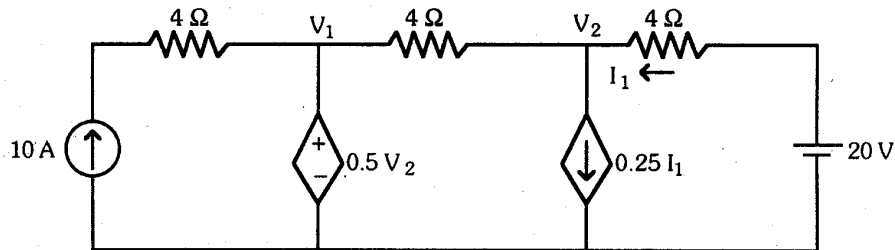


Fig.

(6 V, 12 V)

22. Find voltage V_x .

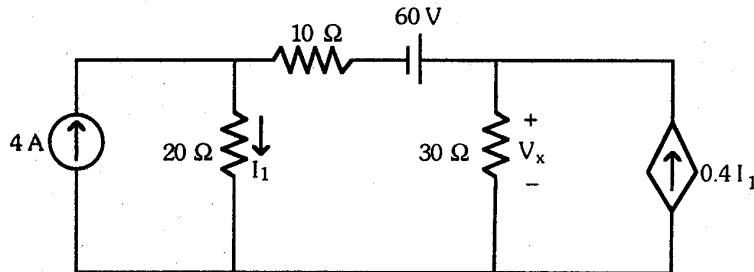


Fig.

(82.5 V)

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

Tel: 9820246760 / 9769479368

23. For the network shown, find the current 10Ω resistor.

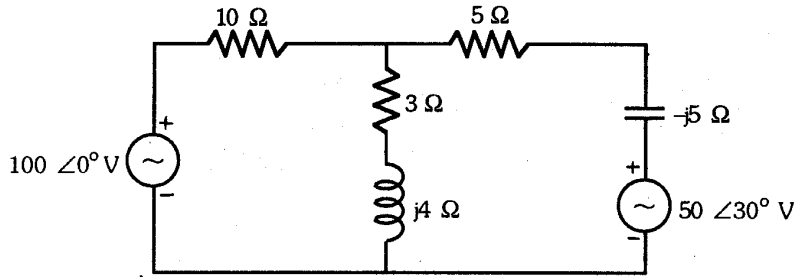


Fig.

24. In the network of Fig. find current through capacitance.

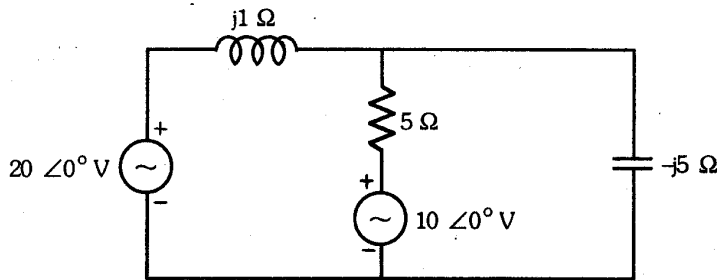


Fig.

[73 A ∠-21.84° A]

Thevenin's and Norton's theorem :

25. Determine Thevenin's equivalent network for the Fig. shown.

(a)

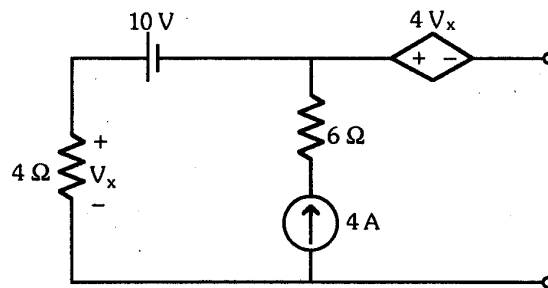


Fig.

(58 V, 12 Ω)

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

NAVLAKHI'S

Tel: 9820246760 / 9769479368

(b)

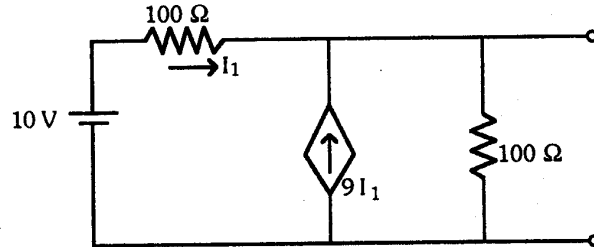


Fig.

(9.09 V, 9.09 Ω)

(c)

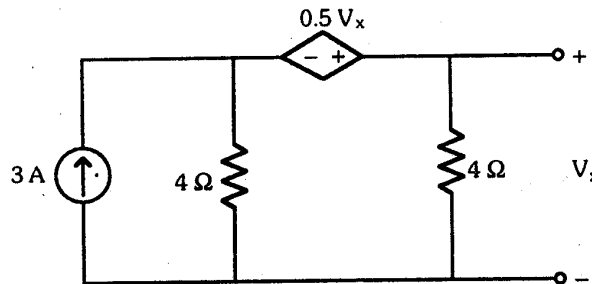


Fig.

(8 V, 2.66 Ω)

(d)

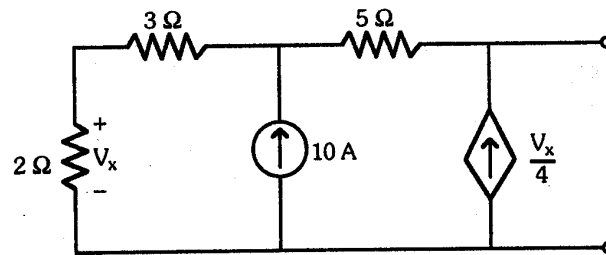


Fig.

(150 V, 20 Ω)

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

NAVLAKHI'S

Tel: 9820246760 / 9769479368

(e)

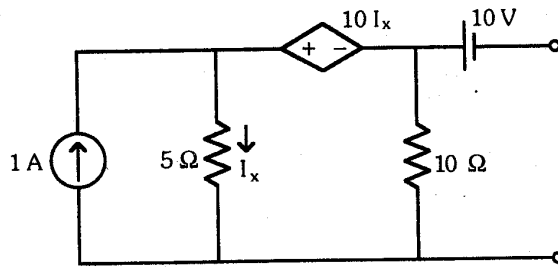


Fig.

(-20 V, -10 Ω)

(f)

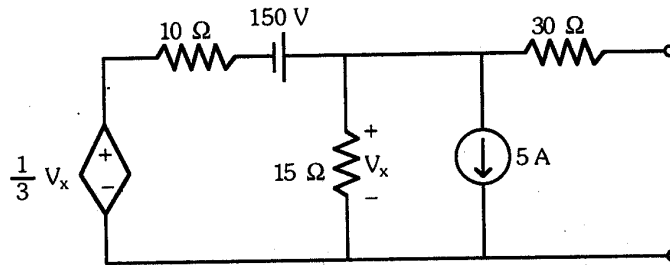


Fig.

(75 V, 37.5 Ω)

(g) Find V_{Th} and R_{Th} between the point A and B in Fig.

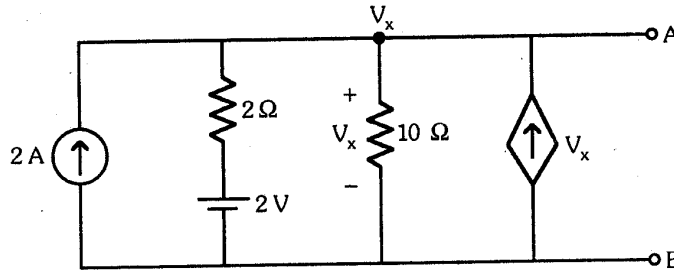


Fig.

26. Find Norton's equivalent network and hence find current in 10 Ω resistor.

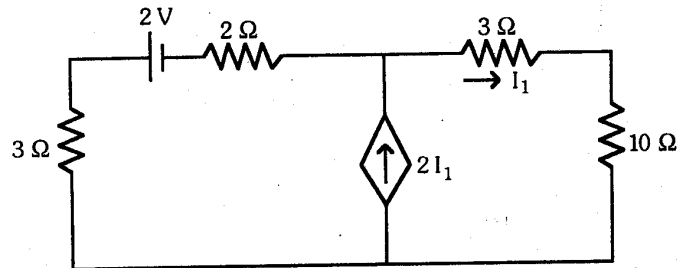


Fig.

(0.25 A)

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

NAVLAKHI'S

27. Find current I_x .

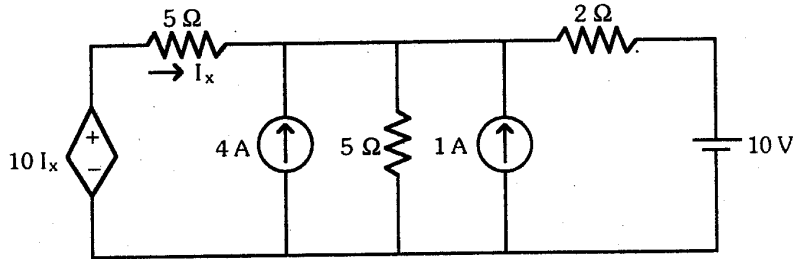


Fig.

(4 A)

28. Find power delivered to 10Ω resistor.

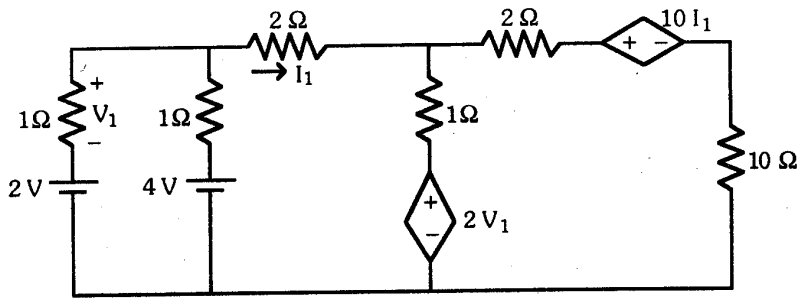


Fig.

(0.138 W)

29. Find current in 24Ω resistor.

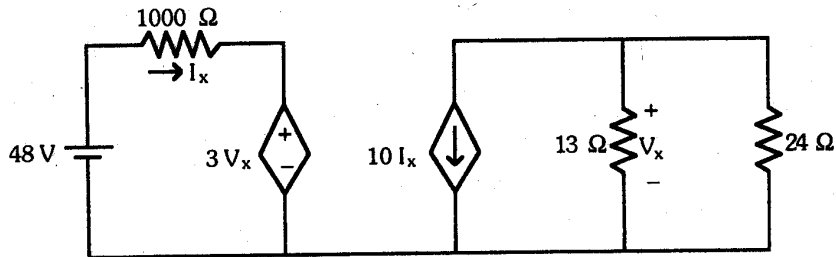


Fig.

(0.225 A)

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

NAVLAKHI'S

30. Find Norton's equivalent network.

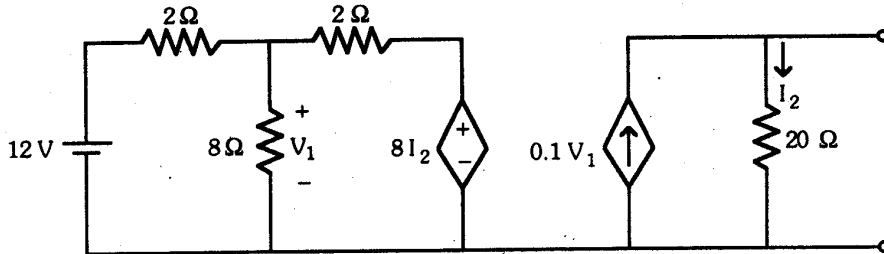


Fig.

(0.533 A, 31 Ω)

31. Obtain Thevenin's equivalent network.

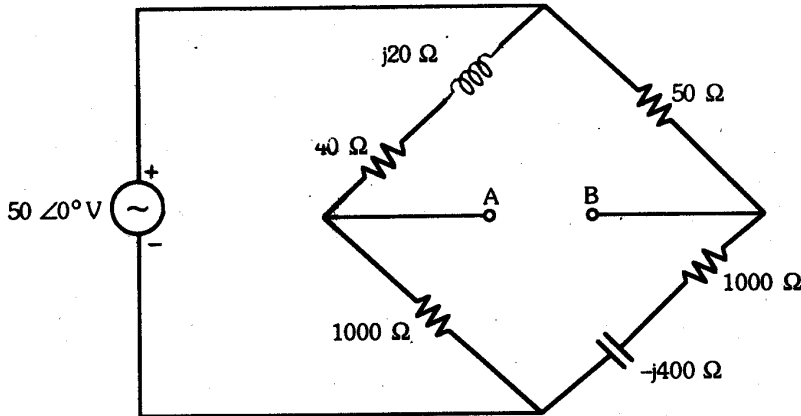


Fig.

[0.192 ∠-43.4° V, 88.7 ∠11.55° Ω]

32. Obtain Thevenin's equivalent network for the Fig. shown.

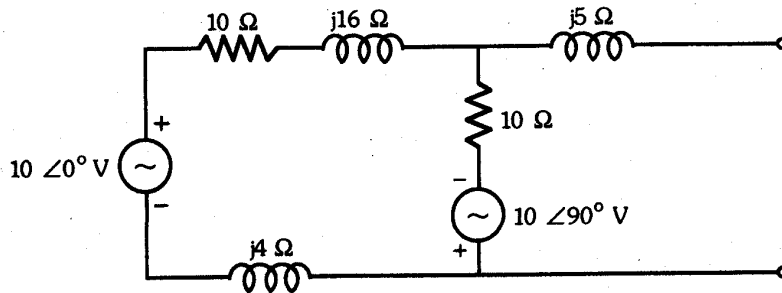


Fig.

[11.17 ∠-63.4° V, 10.6 ∠45° Ω]

Tel: 9820246760 / 9769479368


navlakh.com navlakh.com navlakh.com

Navlakh's

Best One Can Get

NAVLAKHI'S

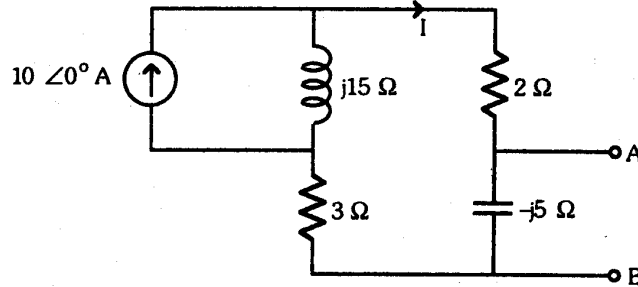33. Obtain Thevenin's equivalent network for the Fig. shown.



34. Obtain Thevenin's equivalent network for the Fig. shown.

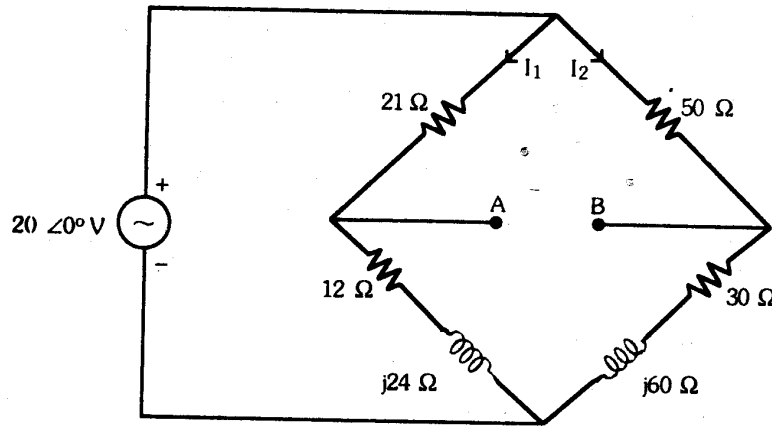


Fig.

35. Determine the maximum power delivered to the load in the network shown in Fig.

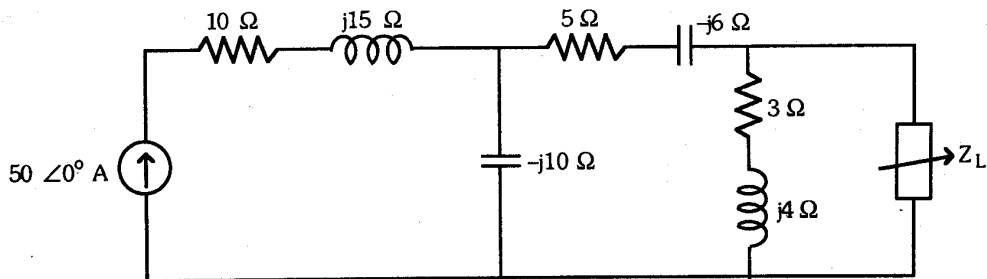


Fig.

[1032.35 W]

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

36. For the network shown, find the value of Z_L that will receive the maximum power. Determine also this power.

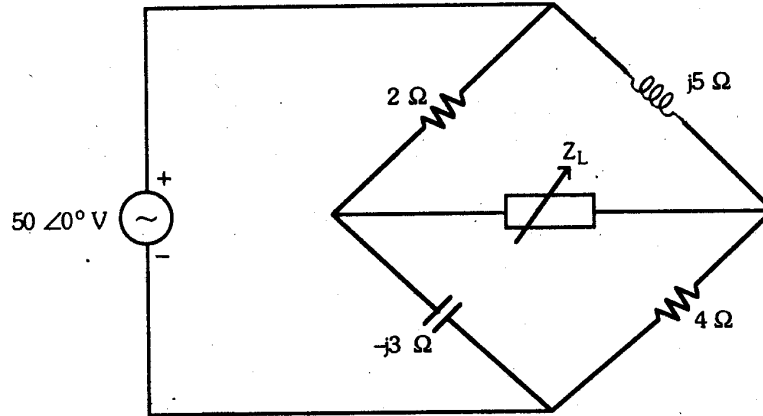


Fig.

$\{-3.82 - j1.03 \Omega, 54.5 \text{ W}\}$

37. Calculate the power dissipated across 10Ω resistor by using source transformation technique.

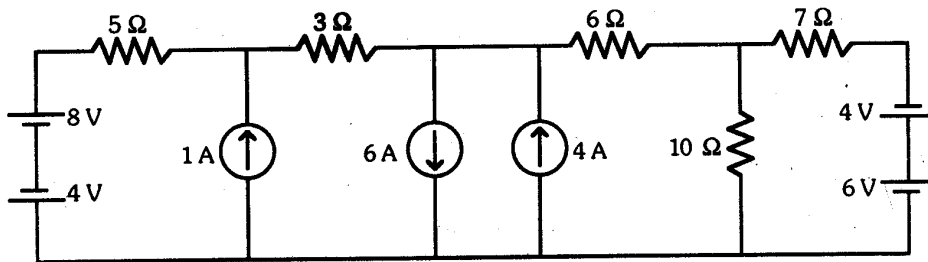


Fig.

(0.046 W)

38. Determine voltage V_x by source shifting technique.

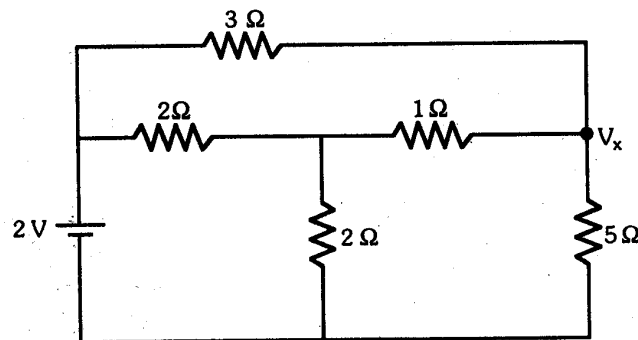


Fig.

$\left(\frac{35}{31} \text{ V}\right)$

Tel: 9820246760 / 9769479368

navlakhi.com navlakhi.com navlakhi.com

Navlakhi's

Best One Can Get

NAVLAKHI'S

39. Use source transformation to simplify the network until two elements remain to the left of terminals a and b.

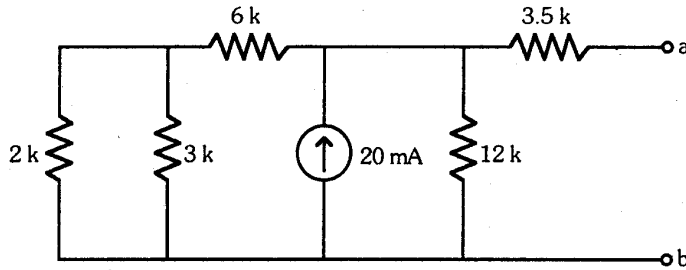


Fig.

(90 V, 8 K Ω)

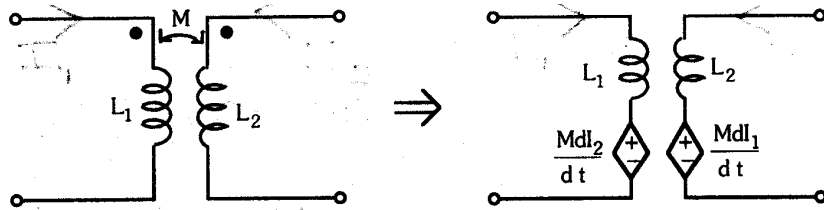


Fig.

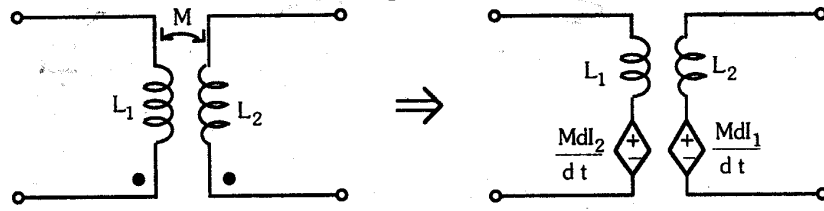


Fig.


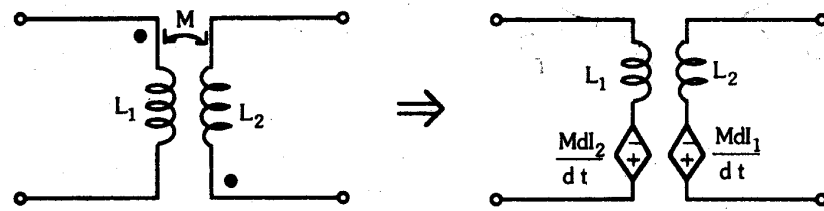


Fig.

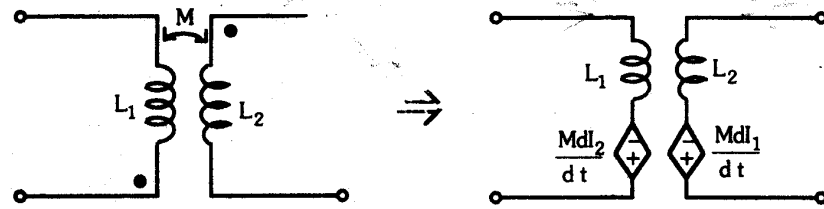

Tel: 9820246760 / 9769479368


navlakh.com navlakh.com navlakh.com

Navlakh's


Best One Can Get

NAVLAKHI'S

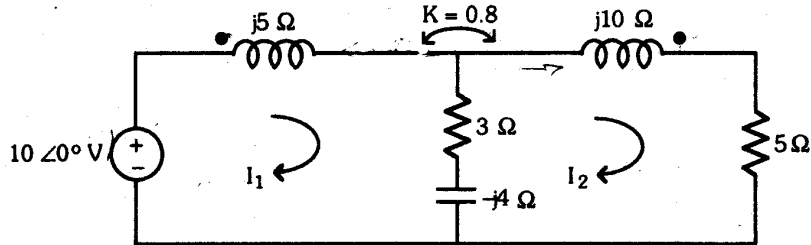
40. Find voltage across 5Ω resistor using mesh analysis.



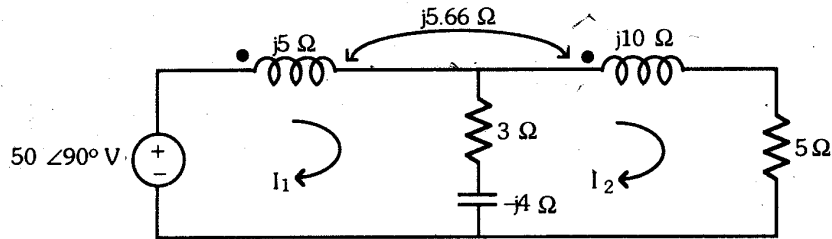41. Find voltage across 5Ω resistor using mesh analysis.



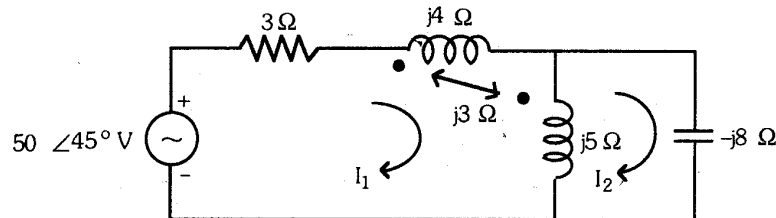42. Find current I_2 using mesh analysis.



Tel: 9820246760 / 9769479368

navlakh.com navlakh.com navlakh.com

Navlakh's

Page
18

Best One Can Get