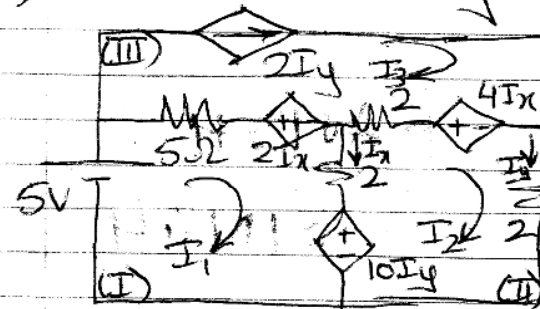


TYPE I: MESH ANALYSIS
Q1) Find I_x and I_y



$$\frac{I_2}{I_x} = I_y \quad \text{--- (I)}$$

$$I_x = I_1 - I_2 \quad \text{--- (II)}$$

By KVL to loop (I):-

$$5 - 2I_x - 10I_y = 7I_1 - 2I_2 - 5I_3$$

From (I) & (II)

$$5 - 2(I_1 - I_2) - 10I_2 = 7I_1 - 2I_2 - 5I_3$$

$$\therefore 9I_1 + 6I_2 = 5 - 5I_3 \quad \text{--- (III)}$$

By KVL to loop (II)

$$10I_y - 4I_x = -2I_1 + 6I_2 - 2I_3$$

From (I) & (II)

$$10I_2 - 4(I_1 - I_2) = -2I_1 + 6I_2 - 2I_3$$

$$\therefore 2I_1 + 8I_2 - 2I_3 = 0 \quad \text{--- (IV)}$$

From loop (III)
KVL cannot be applied to current source

$$I_3 = 2I_y$$

From (I)

$$I_3 = 2I_2$$

$$\therefore 0I_1 + 2I_2 - I_3 = 0 \quad \text{--- (V)}$$

$$\therefore \begin{bmatrix} 9 & +6 & -5 \\ 2 & -8 & -2 \\ 0 & 2 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$I_1 = \frac{\Delta I_1}{\Delta} = \begin{vmatrix} 5 & +6 & -5 \\ 0 & -8 & -2 \\ 0 & 2 & -1 \end{vmatrix}$$

$$\therefore I_1 = \cancel{0.455} 0.6$$

$$I_2 = \frac{\Delta I_2}{\Delta} = \begin{vmatrix} 9 & 5 & -5 \\ 2 & 0 & -2 \\ 0 & 0 & -1 \end{vmatrix}$$


$$\therefore I_2 = \cancel{-0.057} 0.1$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \begin{vmatrix} 9 & +6 & 5 \\ 2 & -8 & 0 \\ 0 & 2 & 0 \end{vmatrix}$$

$$\therefore I_3 = \cancel{-0.114} 0.2$$

$$I_x = I_1 - I_2 = \cancel{0.512} 0.5$$

$$I_y = I_2 = \cancel{-0.057} 0.1$$

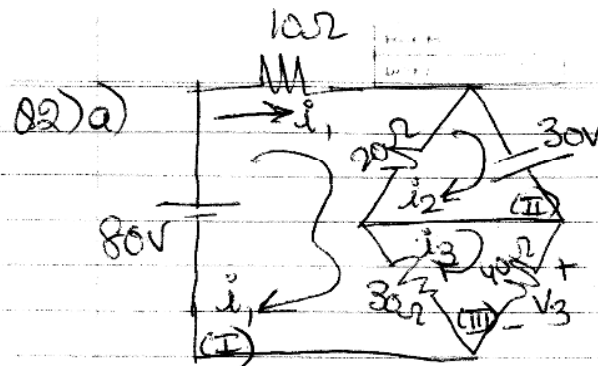

By KVL to loop I:-


$$80 = 60i_1 - 20i_2 - 30i_3 \quad \text{--- (I)}$$

By KVL to loop II:-

$$30 = -20i_1 + 20i_2 + 0i_3 \quad \text{--- (II)}$$

By KVL to loop III:-
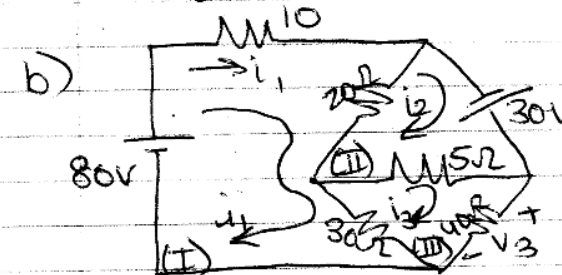
$$0 = -30i_1 + 0i_2 + 70i_3 \quad \text{--- (III)}$$



By KVL to loop I:-

$$80 = 60i_1 - 20i_2 - 30i_3 \quad \text{--- (I)}$$

$$\begin{aligned} i_1 &= 0.405 \\ i_2 &= 5.553 \\ i_3 &= 1.737 \end{aligned}$$

$$\begin{aligned} V_3 &= 40i_3 \\ &= 69.48 \text{ V} \end{aligned}$$

By KVL to loop II:-

$$30 = -20i_1 + 25i_2 - 5i_3 \quad \text{--- (II)}$$

By KVL to loop III:-


$$0 = -30i_1 - 5i_2 + 75i_3 \quad \text{--- (III)}$$

$$\therefore i_1 = 3.7619$$

$$i_2 = 4.5714$$

$$i_3 = 1.8095$$

$$V_3 = 40i_3 \\ = 72.38V$$

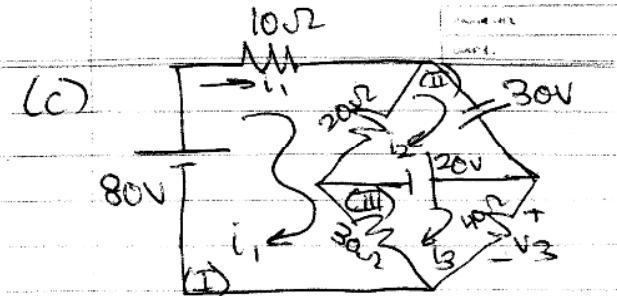

By KVL to loop I:-

$$80 = 60i_1 - 20i_2 - 30i_3 \quad \text{--- (I)}$$

By KVL to loop II:-


$$10 = -20i_1 + 20i_2 + 0i_3 \quad \text{--- (II)}$$

By KVL to loop III:-

$$20 = -30i_1 + 0i_2 + 70i_3 \quad \text{--- (III)}$$

$$\begin{aligned} \therefore i_1 &= 3.632 \\ i_2 &= 4.132 \\ i_3 &= 1.842 \end{aligned}$$
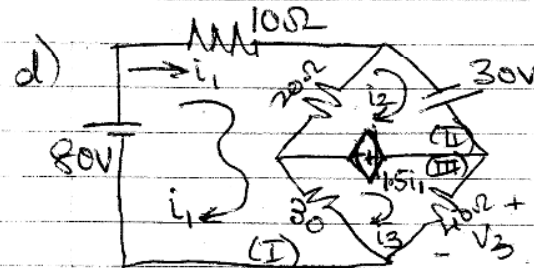
$$\begin{aligned} V_3 &= 40i_3 \\ &= 73.68 \end{aligned}$$



By KVL to loop I:-

$$80 = 60i_1 - 20i_2 - 30i_3 \quad \text{--- (I)}$$

By KVL to loop II:-

$$30 - 1.5i_1 = -20i_1 + 20i_2 + 0i_3$$

$$\therefore 30 = -18.5i_1 + 20i_2 + 0i_3 \quad \text{--- (II)}$$


By KVL to loop III:-

$$1.5i_1 = -30i_1 + 0i_2 + 70i_3$$

$$\therefore -31.5i_1 + 0i_2 + 70i_3 = 0 \quad \text{--- (III)}$$

$$\begin{aligned} \therefore i_1 &= 3.929 \\ i_2 &= 5.134 \\ i_3 &= 1.768 \end{aligned}$$

$$V_3 = 40i_3 = 70.72V$$

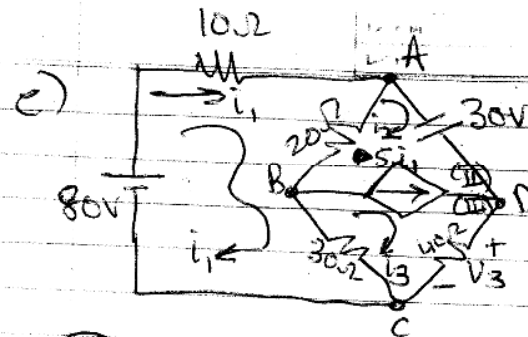

By KVL to loop I:-

$$80 = 60i_1 - 20i_2 - 30i_3 \quad \text{--- (I)}$$

Loops II and (III) form
Supermesh

*1 { Since a current source is
between the two loop?
Equation of supermesh is

$$i_3 - i_2 = 5i_1$$

$$\therefore 5i_1 + i_2 - i_3 = 0 \quad \text{--- (II)}$$

By KVL to outer loop
A-B-C-D-A:-

$$30 = -50i_1 + 20i_2 + 70i_3 \quad \text{--- (III)}$$


$$\underline{i_1 = 1.261}$$

$$i_2 = -3.87$$

$$i_3 = 2.435$$

$$V_3 = 40i_3$$

$$= 97.4V$$

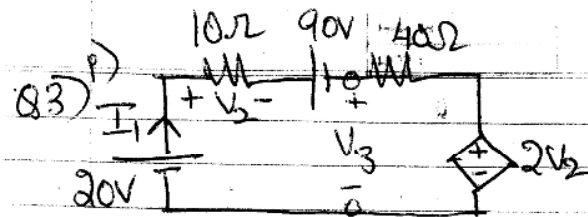

$$V_2 = 10I_1 \quad \text{--- (I)}$$

By KVL


$$20 - 90 - 2V_2 = 50I_1$$

$$-70 = 2V_2 + 50I_1$$

From (I)

$$-70 = 20I_1 + 50I_1$$

$$I_1 = -1A$$

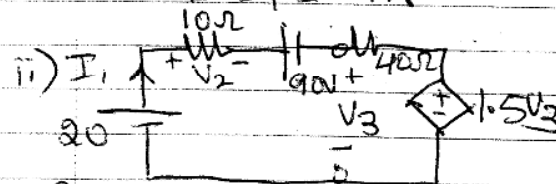

{KVL to right of V_3 }

$$V_3 - 1.5V_3 = 40I_1$$

$$-0.5V_3 = 40I_1$$

$$\therefore V_3 = -80I_1 \quad \text{--- (I)}$$

By KVL,


$$20 - 90 - 1.5V_3 = 50I_1$$

$$-70 = 1.5V_3 + 50I_1$$

From (I)

$$-70 = 1.5(-80I_1) + 50I_1$$

$$\therefore I_1 = 1A$$

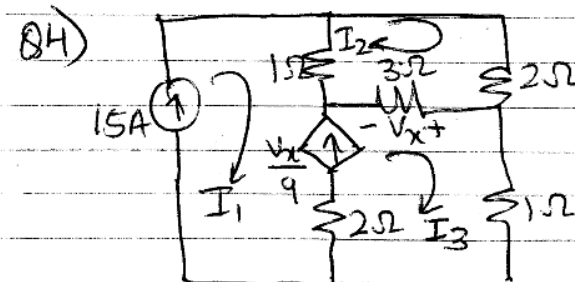

$$I_1 = 15A \quad \text{--- (I)}$$

By KVL to loop II:-

$$-I_1 + 6I_2 - 3I_3 = 0$$

From (I)

$$-15 + 6I_2 - 3I_3 = 0$$

$$0V_x + 6I_2 - 3I_3 = 15 \quad \text{--- (II)}$$

Eq. of supermesh is,

$$I_3 - I_1 = \frac{V_x}{9}$$

$$\therefore I_3 - 15 = \frac{V_x}{9} \quad \text{From (I)}$$

$$V_x - 9I_3 = -135$$

$$V_x + 0I_2 - 9I_3 = -135 \quad \text{--- (III)}$$

$$\text{Also, } V_x = 3(-I_2 + I_3)$$


$$\therefore V_x + 3I_2 - 3I_3 = 0 \quad \text{--- (IV)}$$

From (II), (III), (IV)

$$V_x = 18$$

$$I_2 = 1$$

$$I_3 = 17$$

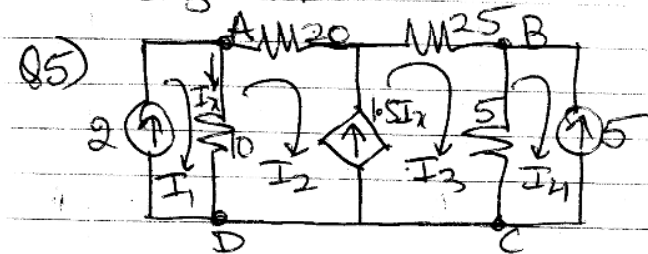

$$I_1 = 2 \quad \text{--- (I)}; I_x = I_1 - I_2$$

$$I_4 = -5 \quad \text{--- (II)} \quad \text{--- (III)}$$

Eq. of supermesh is

$$I_3 - I_2 = 1.5I_x$$

From (III)

$$I_3 - I_2 = 1.5(I_1 - I_2)$$

from (I)

$$I_3 - I_2 = 1.5(2 - I_2)$$

$$0.5I_2 + I_3 = 3 \quad \text{--- (IV)}$$

By KVL to A-B-C-D-A:-

$$-10I_1 + 30I_2 + 30I_3 - 5I_4 = 0$$

from (I) & (II)

$$-20 + 30I_2 + 30I_3 + 25 = 0$$


$$\therefore 30I_2 + 30I_3 = -5 \quad \text{--- (V)}$$

from (IV) & (V)

$$I_2 = -6.333$$

$$I_3 = +6.167$$
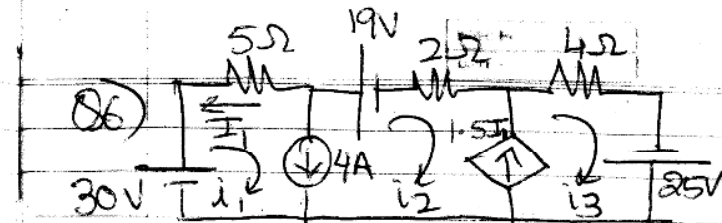
$$\text{from (I)} \quad I_1 = 2 + 6.333 = 8.333 \text{ A}$$



$$i_1 = -I_1 \quad \text{--- (I)}$$

Eq. of supermesh-1

$$i_1 - i_2 = 4$$

$$i_1 - i_2 + 0i_3 = 4 \quad \text{--- (II)}$$

Eq. of supermesh-2

$$i_3 - i_2 = 1.5I_1$$

from (I)

$$i_3 - i_2 = -1.5i_1$$


$$\therefore 1.5i_1 - i_2 + i_3 = 0 \quad \text{--- (III)}$$

By KVL to outer loop:-

$$30 - 19 + 25 = 5i_1 + 2i_2 + 4i_3$$

$$\therefore 5i_1 + 2i_2 + 4i_3 = 36 \quad \text{--- (IV)}$$
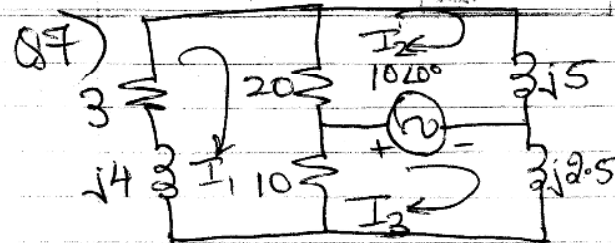
$$\therefore i_1 = 12; i_2 = 8; i_3 = -10 \quad \therefore I_1 = -1$$



By KVL to loop I:-
 $(3+j4)I_1 - 20I_2 - 10I_3 = 0$ — (I)


By KVL to loop II:-
 $-20I_1 + (20+j5)I_2 = 10$
 $\therefore I_2 = \frac{20I_1}{20+j5}$ — (II)

By KVL to loop III:-
 $-10I_1 + (10+j2.5)I_3 = -10$
 $\therefore I_3 = \frac{10I_1}{10+j2.5}$ — (III)

Subs. (II) & (III) in (I)

$$I_1 \left[(3+j4) \left(1 - \frac{20(20)}{(20+j5)} - \frac{10(10)}{10+j2.5} \right) \right] = 0$$

$$\therefore I_1 = 0 \text{ A}$$

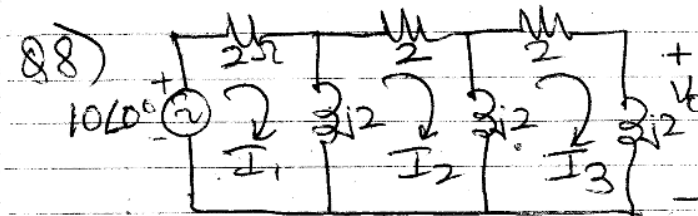

By KVL to loop I:-
 $(2+j2)I_1 - j2I_2 = 10$
 $\therefore I_1 = \frac{10+j2I_2}{2+j2}$ — (I)

By KVL to loop II:-
 $-j2I_1 + (2+j4)I_2 - j2I_3 = 0$ — (II)

By KVL to loop III:-

$$-j2I_2 + (2+j4)I_3 = 0$$

$$\therefore I_2 = \left(\frac{2+j4}{j2} \right) I_3 \quad \text{--- (III)}$$

Subs. in (I)

$$\therefore I_1 = 10 + (j2) \left(\frac{2+j4}{j2} \right) I_3$$

$$I_1 = 10 + (2+j2)I_3 \quad \text{--- (IV)}$$

Subs. (III) & (IV) in (II)

$$\therefore -j2 \left[10 + (2+j2)I_3 \right] + (2+j4)I_3 = 0$$


$$\therefore I_3 \left[\frac{-j2(2+j4)}{2+j4} + \frac{(2+j4)^2}{j2} - j2 \right] = j20$$

$$I_3 = 0.7353 + j0.4412$$

$$I_3 = 0.6098 + j0.4878$$

$$V_0 = j2(I_3) = -0.9756 + j1.2195$$

$$V_0 = 1.5617 \angle 128.66^\circ$$

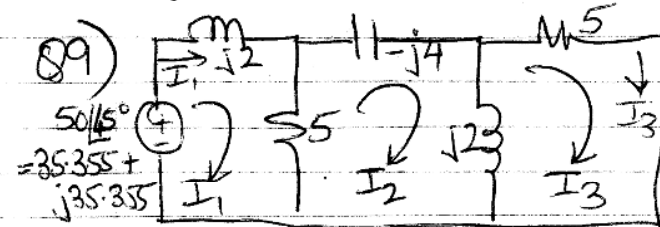

By KVL to loop I:-

$$(5+j2)I_1 - 5I_2 = 35.355 + j35.355$$

$$I_1 = \frac{(35.355 + j35.355) + 5I_2}{5+j2} \quad \text{--- (I)}$$

By KVL to loop II:-

$$-5I_1 + (5-j2)I_2 - j2I_3 = 0 \quad \text{--- (II)}$$

By KVL to loop III:-

$$(-j2)I_2 + (5+j2)I_3 = 0$$

$$I_2 = \frac{(5+j2)}{j2} I_3 \quad \text{--- (III)}$$

Subs. (III) in (I)

$$\therefore I_1 = (35.355 + j35.355) + 5 \frac{(5+j2)}{j2} I_3$$

$$= \frac{35.355 + j35.355}{5+j2} + \left(\frac{5}{j2}\right) I_3 \quad \text{--- (IV)}$$


Subs. (III) & (IV) in (I)

$$-5 \left[\frac{35.355 + j35.355}{5+j2} + \frac{5}{j2} I_3 \right] + (5-j2) \frac{(5+j2)}{j2} I_3 = 0$$

$$I_3 \left[\frac{-25}{j2} + \frac{29-j2}{j2} \right] = \frac{5(35.355 + j35.355)}{5+j2}$$

$$I_3 \left[-j4 \right] = I_3 = -4.572 + j10.667j$$

$$= 11.61 \angle 113.2^\circ$$

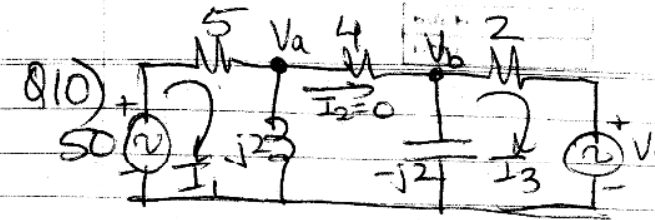

By KVL to loop I:-

$$(5+j2)I_1 = 50$$

$$\therefore I_1 = \frac{50}{5+j2} = 8.621 - j3.448$$

$$V_a = j2(I_1) = 6.897 + j17.24j$$

By KVL to loop II:-

$$(2-j2)I_3 = -V_2$$

$$I_3 = \frac{-V_2}{(2-j2)}$$


$$V_b = (-j2)I_3 = \left(\frac{-j2}{2-j2}\right)V_2$$

$$\therefore I_2 = 0 \therefore V_a = V_b$$

$$\therefore 6.897 + j17.24 = \frac{-j2 V_2}{(2-j2)}$$

$$\therefore V_2 = -10.345 + j24.138$$
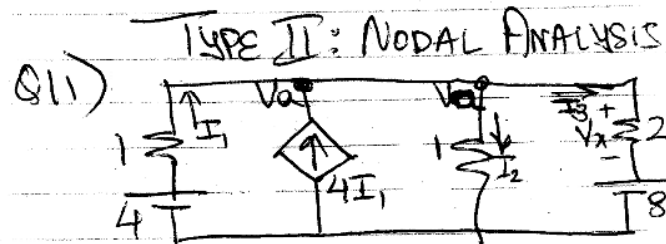
$$V_2 = 26.26 \angle 113.2^\circ \text{ V}$$



By KCL,

$$I_1 + 4I_1 = I_2 + I_3$$

$$5I_1 = I_2 + I_3$$

$$5 \left(\frac{4 - V_a}{1} \right) = \frac{V_a}{1} + \frac{V_a - 8}{2}$$


$$20 - 5V_a = V_a + 0.5V_a - 4$$

$$6.5 V_a = 24$$

$$\therefore V_a = 3.692$$

$$I_3 = \frac{V_a - 8}{2} = -2.154$$

$$V_n = 2I_3 = -4.308 \text{ V}$$

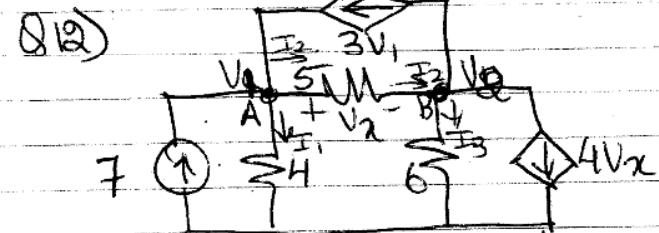

By KCL at node A:-

$$7 + 3V_1 = I_1 + I_2$$

$$7 + 3V_1 = \frac{V_1}{4} + \left(\frac{V_1 - V_2}{5} \right)$$

$$\left(\frac{1}{4} + \frac{1}{5} - 3 \right) V_1 - \frac{1}{5} V_2 = 7 \quad \text{--- (1)}$$

$$V_1 - V_x - V_2 = 0$$

$$\therefore V_x = V_1 - V_2$$

By KVL at node B:-

$$I_2 = I_3 + 4V_x + 3V_1$$

$$\left(\frac{V_1 - V_2}{5}\right) = \frac{V_2}{6} + 4(V_1 - V_2) + 3V_1$$

$$\left(4 + 3 - \frac{1}{5}\right)V_1 = \left(4 - \frac{1}{5} - \frac{1}{6}\right)V_2$$

$$\frac{34}{5}V_1 = \left(\frac{109}{30}\right)V_2$$

$$V_2 = \frac{187V}{109} \text{ (I)}$$

Subs. (I) in (I),

$$-2.55V_1 - \frac{V_2}{5} = 7$$

$$-5V_1 - \frac{1}{5}V_2 = 35$$

$$V_1 = \frac{1}{5} \times 35 = 7$$


$$-2.55V_1 - \frac{1.87V_1}{5} = 7$$

$$V_1 = -2.394V$$

$$V_2 = -4.477V \text{ } \left\{ \text{from (I)} \right\}$$

$$V_x = V_1 - V_2$$

$$= 2.083V$$

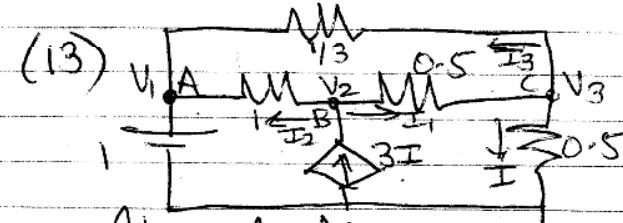

At node A:-

$$V_1 = 1V \text{ (I)}$$

By KCL at node B:-

$$3I = I_1 + I_2$$

$$3I = \frac{V_2 - V_3}{0.5} + \frac{V_2 - V_1}{1}$$

$$\text{Subs. } I = \frac{V_3}{0.5}$$

$$\therefore \frac{3V_3}{0.5} = \frac{V_2 - V_3}{0.5} + V_2 - 1$$

$$V_2 \left(\frac{1}{0.5} + 1 \right) + \left(-\frac{1}{0.5} - \frac{3}{0.5} \right) V_3 = 1$$

$$3V_2 - 8V_3 = 1 \quad \text{--- (II)}$$

By KCL at node C:-

$$I_1 = I + I_3$$

$$\frac{V_2 - V_3}{0.5} = \frac{V_3}{0.5} + \left(\frac{V_3 - V_1}{1/3} \right)$$


From from (I)

$$2V_2 - 2V_3 = 2V_3 + 3V_3 - 3V_1 \quad \text{--- (I)}$$

$$2V_2 - 7V_3 = -3 \quad \text{--- (II)}$$

from (II) & (III)

$$\therefore V_2 = 6.2V, V_3 = 2.2V$$

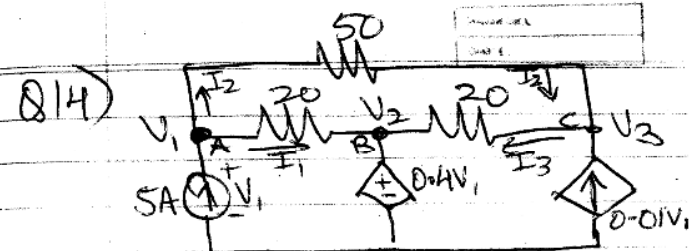

KCL At node A:-

$$5 = I_1 + I_2$$

$$5 = \left(\frac{V_1 - V_2}{20} \right) + \left(\frac{V_1 - V_3}{50} \right)$$

$$\left(\frac{1}{20} + \frac{1}{50} \right) V_1 - \frac{1}{20} V_2 - \frac{1}{50} V_3 = 5$$

$$0.07V_1 - 0.05V_2 - 0.02V_3 = 5$$

$$7V_1 - 5V_2 - 2V_3 = 500 \quad \text{--- (I)}$$

At node B:-

$$V_2 = 0.4V_1$$

$$\therefore 0.4V_1 - V_2 + 0V_3 = 0 \quad \text{--- (II)}$$

By KCL at node C:-

$$I_2 + 0.01V_1 = I_3$$

$$\frac{V_1 - V_3}{50} + 0.01V_1 = \frac{V_3 - V_2}{20}$$

$$\left(0.01 + \frac{1}{50}\right)V_1 + \frac{1}{20}V_2 + \left(\frac{-1}{50} - \frac{1}{20}\right)V_3 = 0$$

$$0.03V_1 + 0.05V_2 - 0.07V_3 = 0$$


$$\therefore 3V_1 + 5V_2 - 7V_3 = 0 \quad \text{--- (III)}$$

From (I), (II) & (III)

$$V_1 = 140 \text{ V}$$

$$V_2 = 58 \text{ V}$$

$$V_3 = 100 \text{ V}$$

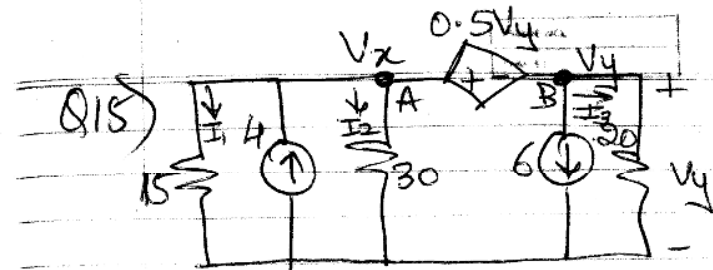

Nodes A & B are supernodes as there is a volt. source bet. them without any resist.

Eqn. of supernode is

$$V_x - 0.5V_y - V_y = 0$$

$$V_x = 1.5V_y \quad \text{--- (I)}$$

KCL at nodes A & B:-


$$I_1 + I_2 + 6 + I_3 = 4$$

$$\frac{V_x}{15} + \frac{V_x}{30} + 2 + \frac{V_y}{20} = 0$$

From (I)

$$\frac{1.5V_y}{15} + \frac{1.5V_y}{30} + \frac{V_y}{20} = -2$$

$$\therefore V_y = -10V$$

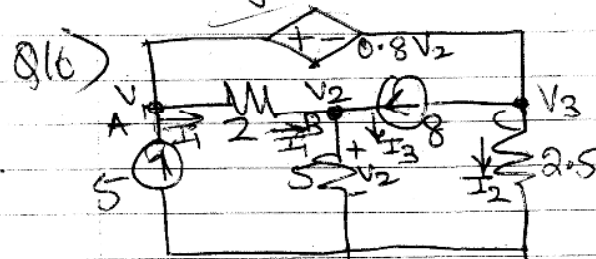

Nodes A & C are supernodes.

Eq. of supernode is

$$V_1 - 0.8V_2 - V_3 = 0 \quad \text{--- (I)}$$

KCL at A & C:-

$$5 = I_1 + 8 + I_2$$

$$5 = \left(\frac{V_1 - V_2}{2}\right) + 8 + \left(\frac{V_3}{2.5}\right)$$

$$\frac{1}{2}V_1 - \frac{1}{2}V_2 + \frac{1}{2.5}V_3 = -3$$

$$0.5V_1 - 0.5V_2 + 0.4V_3 = -3 \quad \text{--- (II)}$$

KCL at node B:-

$$I_1 + 8 = I_3$$

$$\left(\frac{V_1 - V_2}{2}\right) + 8 = \frac{V_2}{5}$$


$$\frac{1}{2}V_1 + \left(-\frac{1}{2} - \frac{1}{5}\right)V_2 = -8$$

$$0.5V_1 - 0.7V_2 = -8 \quad \text{--- (III)}$$

$$V_1 = 20.27 V$$

$$V_2 = 25.91 V$$

$$V_3 = -0.455 V$$

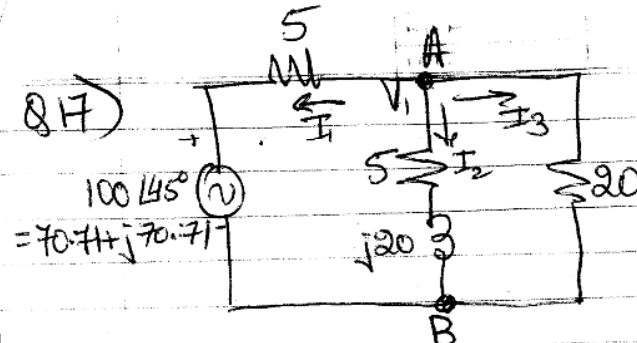


By KCL at node A:-
 $I_1 + I_2 + I_3 = 0$

$$\frac{V_1 - 70.71 - j70.71}{5} + \frac{V_1}{5 + j20} + \frac{V_1}{20} = 0$$

$$V_1 \left(\frac{1}{5} + \frac{1}{5 + j20} + \frac{1}{20} \right) = \frac{70.71 + j70.71}{5}$$

$$V = 42.93 + j61.74$$

$$= 75.2 \angle 55.19^\circ$$

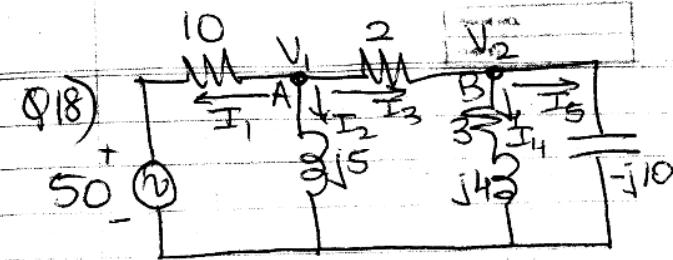

By KCL at node A:-

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - 50}{10} + \frac{V_1}{j5} + \frac{V_1 - V_2}{2} = 0$$

$$V_1 \left(\frac{1}{10} + \frac{1}{j5} + \frac{1}{2} \right) - \frac{V_2}{2} = 5 \quad \text{--- (I)}$$

By KCL at node B:-

$$I_3 = I_4 + I_5$$

$$\frac{V_1 - V_2}{2} = \frac{V_2}{3 + j4} + \frac{V_2}{-j10}$$

$$V_1 \left(\frac{1}{2} \right) = V_2 \left(\frac{1}{2} + \frac{1}{3 + j4} - \frac{1}{j10} \right)$$

$$V_1 = (1.24 - j0.12)V_2 \quad \text{--- (I)}$$

Subs. in (I)


$$V_2 [(1.24 - j0.12)(0.6 - 0.2j) - 0.5] = 5$$

$$V_2 = 7.29 + j10.61$$

$$= 12.88 \angle 55.49^\circ$$

From (I) $V_1 = 10.32 + j12.28$

$$= 16.04 \angle 49.96^\circ$$

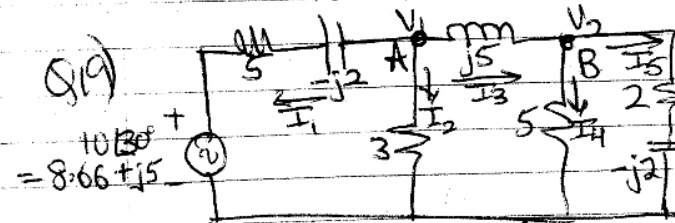

By KCL at node A:-

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - 8.66 - j5}{5 - j2} + \frac{V_1}{3} + \frac{V_1 - V_2}{j5} = 0$$

$$V_1 \left(\frac{1}{5 - j2} + \frac{1}{3} + \frac{1}{j5} \right) - \frac{V_2}{j5} = \frac{8.66 - j5}{5 - j2}$$

$$V_1 (0.506 - 0.131j) + 0.2jV_2 = 1.48 + j1.46 \quad \text{--- (I)}$$

By KCL at node B

$$I_3 = I_4 + I_5$$

$$\frac{V_1 - V_2}{j5} = \frac{V_2}{5} + \frac{V_2}{2 - j2}$$

$$V_1 \left(\frac{1}{j5} \right) = V_2 \left(\frac{1}{j5} + \frac{1}{5} + \frac{1}{2 - j2} \right)$$

$$V_1 = (-0.25 + j2.25)V_2 \quad \text{--- (II)}$$

Subs. in (I)


$$V_2 = -1.15 - j0.7$$

$$V_1 = -1.29 + j2.76$$

$$I_1 = \frac{V_1 - 8.66 - j5}{5 - j2} = -1.12 - j0.9$$

$$\therefore \text{Current from } 10\angle 30^\circ = -I_1 = 1.44 \angle 38.8^\circ$$

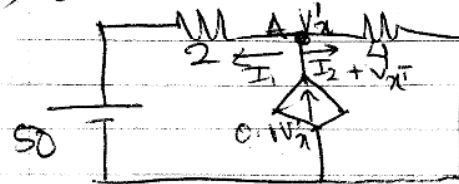TYPE III: SUPERPOSITION THE.
Q20) Consider 50V & short 100V



By KCL at node A:-


$$I_1 + I_2 = 0.1V_x'$$

$$\frac{V_x' - 50}{2} + \frac{V_x'}{4} = 0.1V_x'$$

$$V_x' \left(\frac{1}{2} + \frac{1}{4} - 0.1 \right) = 25$$

$$V_x' = 38.46 \text{ V}$$

Consider 100V & short 50V

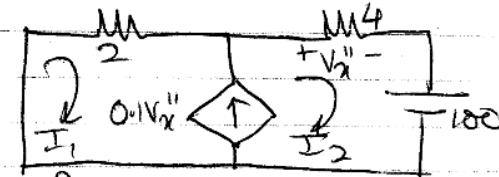

Eq. of supermesh:-

$$I_2 - I_1 = 0.1V_x''$$

$$-I_1 + I_2 - 0.1V_x'' = 0 \quad \text{--- (i)}$$

Also,

$$V_x'' = 4I_2$$

$$0I_1 + 4I_2 - V_x'' = 0 \quad \text{--- (ii)}$$

By KVL to outer loop-


$$-100 = 2I_1 + 4I_2$$

$$2I_1 + 4I_2 + 0V_x'' = 100 \quad \text{--- (iii)}$$

$$V_x'' = -76.93$$

$$V_x = V_x' + V_x''$$

$$= -38.46 \text{ V}$$

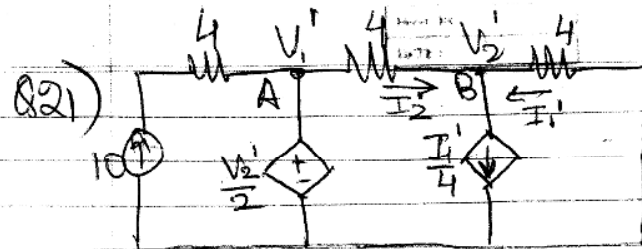

Consider 10A & short 20V

At node A:-

$$V_1' = \frac{V_2'}{2} \therefore V_2' = 2V_1' \quad \text{--- (I)}$$

KCL at node B:-

$$I_2' + I_1' = \frac{I_1'}{4}$$


$$\frac{V_1' - V_2'}{4} = -\frac{3}{4} \left(-\frac{V_2'}{4} \right)$$

$$\frac{V_1'}{4} - \frac{V_2'}{4} = \frac{3V_2'}{16}$$

$$V_1' = 1.75 V_2' \quad \text{--- (II)}$$

From (I) & (II) $V_1' = 0; V_2' = 0$

When 10A is open & cons. 20V

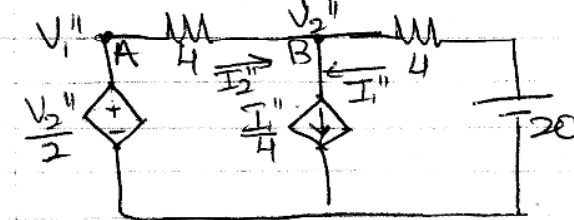

At node A:-

$$V_1'' = \frac{V_2''}{2} \therefore V_2'' = 2V_1'' \quad \text{--- (I)}$$


KCL at node B

$$I_2'' + I_1'' = \frac{I_1''}{4}$$

$$\frac{V_1'' - V_2''}{4} = -\frac{3}{4} \left(\frac{20 - V_2''}{4} \right)$$

$$\frac{V_1''}{4} = -\frac{15}{4} + \left(\frac{1}{4} + \frac{3}{16} \right) V_2''$$
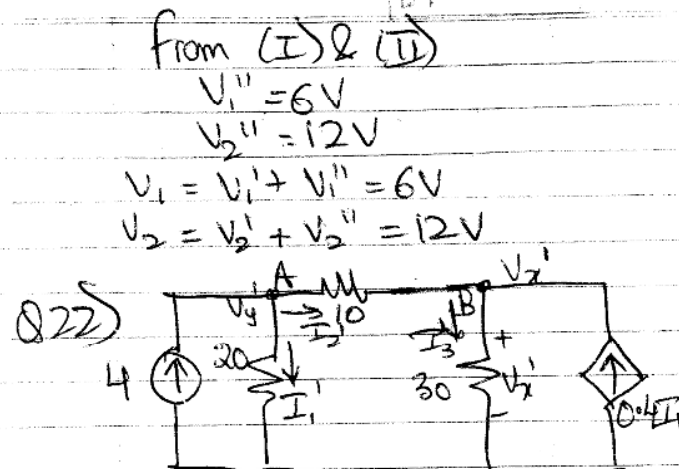
$$V_1'' = -15 + 1.75 V_2'' \quad \text{--- (II)}$$



Consider 4A & short 60V

KCL at node A

$$4 = I_1' + I_2'$$

$$4 = \frac{V_y'}{20} + \frac{V_y' - V_x'}{10}$$

$$V_x' = V_y' \left(\frac{1}{2} + 1 \right) - 40$$

$$V_x' = 1.5V_y' - 40 \quad \text{--- (I)}$$

KCL at node B:-

$$I_2' + 0.4I_1' = I_3'$$

$$\frac{V_y' - V_x'}{10} + 0.4 \left(\frac{V_y'}{20} \right) = \frac{V_x'}{30}$$

$$V_y' \left(\frac{1}{10} + \frac{1}{50} \right) = V_x' \left(\frac{1}{30} + \frac{1}{10} \right)$$


$$0.12V_y' = 0.133V_x'$$

$$V_y' = 1.11V_x' \quad \text{--- (II)}$$

from (I) & (II)

$$V_x' = 60V$$

Consider 60V Battery & open 4A

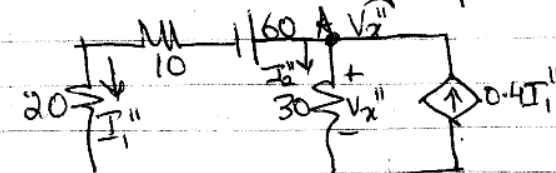

KCL at node A:-


$$0.4I_1'' = I_1'' + I_2''$$

$$-0.6 \left(\frac{V_x'' - 60}{30} \right) = \frac{V_x''}{30}$$

$$\frac{0.6 \times 60}{30} = V_x'' \left(\frac{1}{30} + \frac{0.6}{30} \right)$$

$$V_x'' = 22.5 \text{ V}$$

$$V_x = V_x' + V_x'' = 82.5 \text{ V}$$

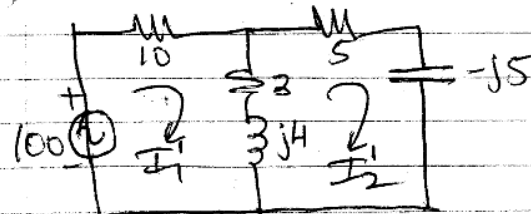Q23) Consider 100 V short $50 \angle 30^\circ \text{ V}$ 

KVL to loop I:-

$$100 = (10 + 3 + j4)I_1 - (3 + j4)I_2$$

$$100 = (13 + j4)I_1 - (3 + j4)I_2 \quad \text{--- (I)}$$


By KVL to loop II:-

$$-(3 + j4)I_1 + (8 - j)I_2 = 0$$

$$I_2 = (+0.308 + 0.54j)I_1 \quad \text{--- (II)}$$

from (I) & (II)

$$I_1 = 6.981 - j0.566$$

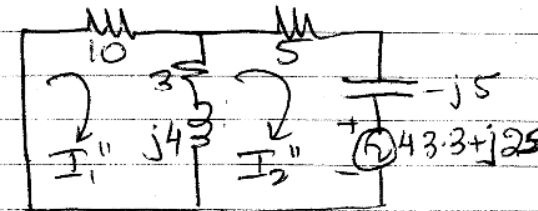Consider $50 \angle 30^\circ$ & short 100V

By KVL to loop I:-

$$(13 + j4)I_1 - (3 + j4)I_2 = 0$$


$$I_2'' = (2.2 - j1.6) I_1'' \quad \text{--- (I)}$$

By KVL to loop II:-
 $-(3+j4)I_1'' + (8-j)I_2'' = 43.3 + j25$
 --- (II)

From (I) & (II)

$$\begin{aligned} I_1'' &= -0.166 - j2.166 \\ I_1 &= I_1' + I_1'' \\ &= 6.815 - j2.732 \\ &= 7.34 \angle -21.845^\circ \end{aligned}$$

Q24) Consider 20V & Short 10V

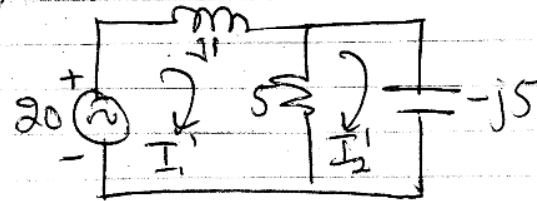


KVL to loop I:-
 $(5+j)I_1' - 5I_2' = 20$ --- (I)

KVL to loop II
 $-5I_1' + (5-j5)I_2' = 0$
 $I_1' = (1-j)I_2'$ --- (II)

Subs. (II) in (I)
 $(5+j)(1-j)I_2' - 5I_2' = 20$
 $I_2 = 1.176 + j4.706$

Consider 10V & Short 20V

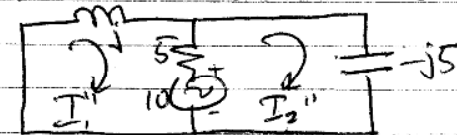

KVL to loop I:-
 $(5+j)I_1'' - 5I_2'' = -10$
 --- (I)

KVL to loop II:-
 $-5I_1'' + (5-j5)I_2'' = 10$ — (C)

$$\Delta = \begin{vmatrix} 5+j & -5 \\ -5 & 5-j5 \end{vmatrix} = 5-j20$$


~~$$\Delta_2 = \begin{vmatrix} 5+j & -10 \\ -5 & 5-j5 \end{vmatrix}$$~~

$$\Delta_2 = \begin{vmatrix} 5+j & -10 \\ -5 & 10 \end{vmatrix} = 10j$$

$$I_2'' = \frac{\Delta_2}{\Delta} = -0.471 + j0.118$$

$$\begin{aligned} I_2 &= I_2' + I_2'' \\ &= 0.705 + j4.824 \\ &= 4.875 \angle 81.69^\circ \end{aligned}$$

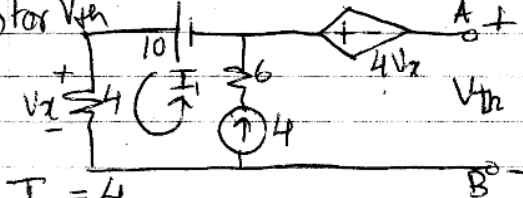TYPE IV: THEVENIN'S & NORTON'S THE
 Q25a) For V_{th}



$$I_1 = 4$$

$$V_x = 4I_1 = 4(4) = 16 \text{ V}$$

By KVL to outer loop:-


$$V_{th} + 4V_x + 10 = 4I_1$$

$$V_{th} + 4(16) + 10 = 4(4)$$

$$V_{th} + 64 + 10 = 16$$

$$V_{th} = -58 \text{ V}$$

For I_{sc}

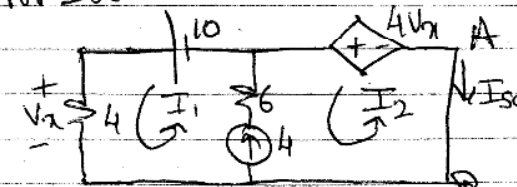

$$I_{sc} = -I_2 ; V_x = 4I_1$$

$$I_1 = I_2 = 4 \text{ — (I)}$$

By KVL to outer loop:-

$$4V_x + 10 = 4I_1$$

$$4(4I_1) + 10 = 4I_1$$

$$I_1 = -0.833 \text{ A}$$



Subst. in (I)

$$\therefore I_2 = -4.833 \text{ A}$$

$$I_{sc} = 4.833 \text{ A}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = 12 \Omega$$

Thevenin Eq. ckt. is

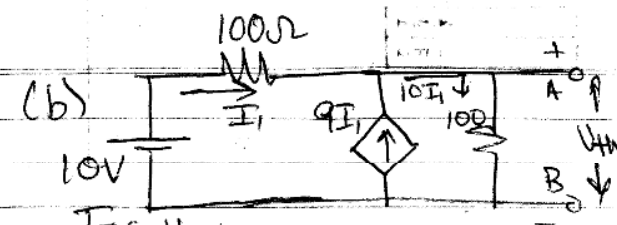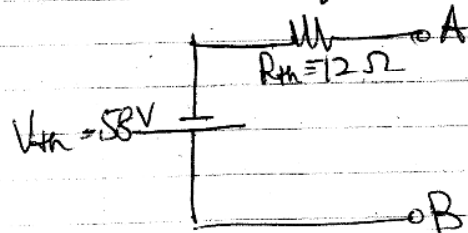

For V_{th} :-

$$V_{th} = (10I_1)(100) = 1000I_1$$


By KVL to outer loop:-

$$100I_1 + 1000I_1 = 10$$


$$\therefore I_1 = 0.00909 \text{ A}$$

$$V_{th} = 9.09 \text{ V}$$

For I_{sc} :-

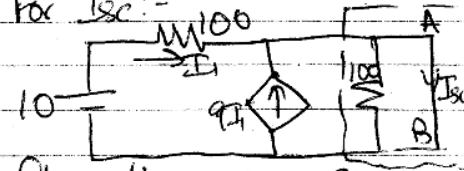

Short // resist. $\approx$ Short

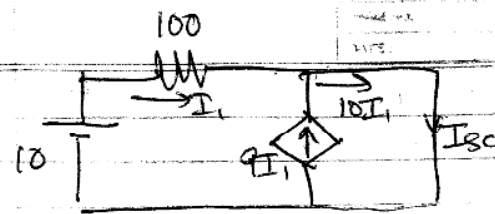

$$I_{sc} = 10I_1$$

By KVL to outer loop:-



$$100I_1 = 10$$

$$\therefore I_1 = 0.1A$$

$$\therefore I_{sc} = 1A$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = 9.09\Omega$$

Thevenin's Eq. ckt. is

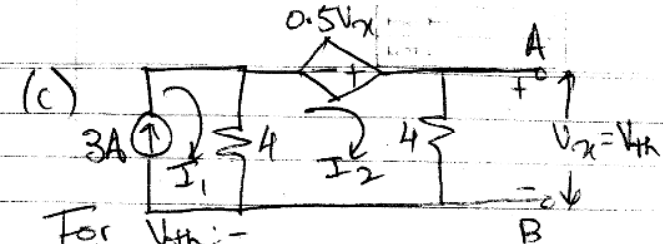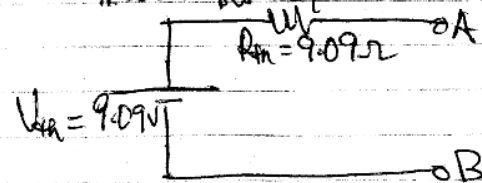

For V_{th} :-

$$V_{th} = V_x$$

$$V_x = 4I_2 \quad \text{--- (I)}$$

$$I_1 = 3A \quad \text{--- (II)}$$

By KVL to loop II:-

$$-4I_1 + 8I_2 = 0.5V_x$$

$$-4(3) + 8I_2 = 0.5(4I_2)$$


$$\therefore I_2 = 2A$$




from (I)

$$V_x = 4I_2 = 8V$$

$$V_{th} = V_x = 8V$$



For I_{sc}

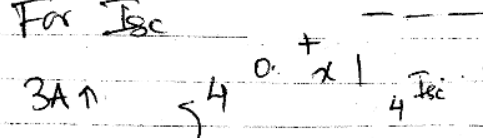

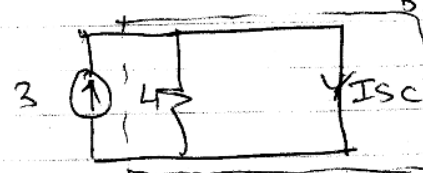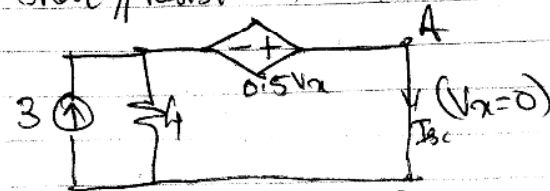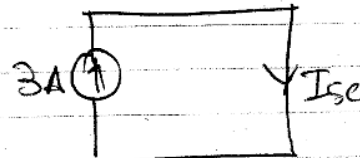Short // Resist. $\rightarrow$ ShortShort // Resist. $\rightarrow$ Short

$$I_{sc} = 3A$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{3} = 2.667\Omega$$

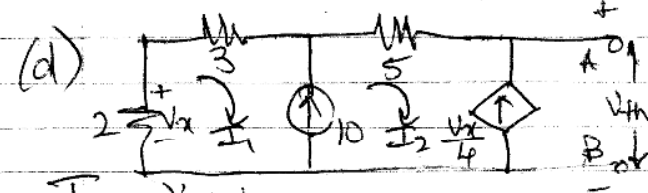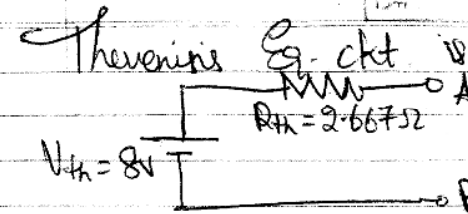For V_{th} :-

$$I_2 = -\frac{V_x}{4} \quad \text{--- (I)}$$

$$V_x = -2I_1 \quad \text{--- (II)}$$

From (I) & (II)

$$I_1 = 2I_2 \quad \text{--- (III)}$$

Eq. of supermesh is:-

$$I_2 - I_1 = 10 \quad \text{--- (IV)}$$

From (III) & (IV)

$$I_1 = -20A$$

$$I_2 = -10A$$


By KVL to outer loop

$$5I_1 + 5I_2 = -V_{th}$$

$$\therefore 5(-20) + 5(-10) = -V_{th}$$

$$V_{th} = 150V$$

For I_{sc} :-

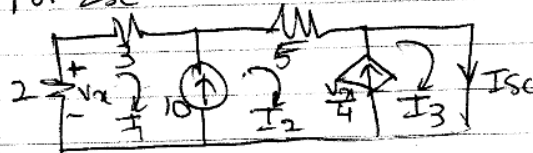

$$I_{sc} = I_3$$

$$V_x = -2I_1 \quad \text{--- (I)}$$

Eqs. of supermesh are :-

$$I_2 - I_1 = 10 \quad \text{--- (II)}$$

$$I_3 - I_2 = \frac{V_x}{4}$$

from (I),

$$I_3 - I_2 = -\frac{I_1}{2}$$

$$0.5I_1 - I_2 + I_3 = 0 \quad \text{--- (III)}$$

By KVL to outer loop :-

$$5I_1 + 5I_2 = 0$$

$$I_1 + I_2 + 0I_3 = 0 \quad \text{--- (IV)}$$

from (II), (III) & (IV)


$$I_1 = -5A$$

$$I_2 = 5A$$

$$I_{sc} = I_3 = 7.5A$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{150}{7.5} = 20\Omega$$

~ Thevenin Eq.ckt is

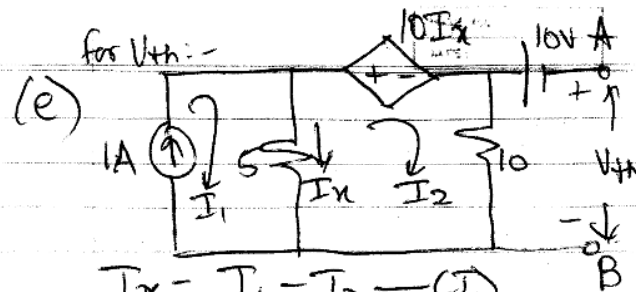

$$I_x = I_1 - I_2 - (1)$$

$$I_1 = 1A$$

$$\therefore I_x = 1 - I_2 - (I)$$

By KVL to loop II:-

$$-5I_1 + 15I_2 = -10I_x$$

$$-5I_1 + 15I_2 = -10(1 - I_2) \quad \text{from (I)}$$

$$\therefore -5I_1 + 5I_2 = -10$$

$$5I_1 - 5I_2 = 10$$

$$5(1) - 5I_2 = 10$$


$$I_2 = -1A$$

By KVL to loop III:-

$$V_{th} + 10 = 10I_2$$

$$\therefore V_{th} = -20V$$

for I_{sc} :-

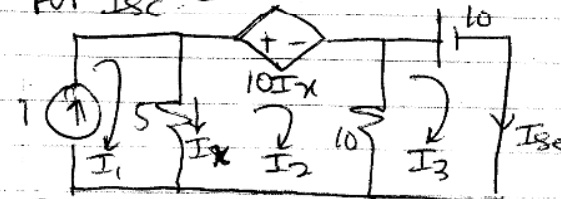

$$I_{sc} = I_3$$

$$I_1 = 1$$

$$I_x = I_1 - I_2 = (1 - I_2)$$

By KVL to loop II:-

$$-10I_3 - 5I_1 + 15I_2 = -10I_x$$

$$-10I_3 - 5(1) + 15I_2 = -10(1 - I_2)$$

$$-10I_3 - 5 + 15I_2 = -10 + 10I_2$$

$$-10I_3 + 5I_2 = -5 \quad \text{--- (I)}$$


$$\therefore I_2 = -1A$$

By KVL to loop III:-

$$-10I_2 + 10I_3 = -10$$

$$\begin{aligned}
 I_2 &= 3A \\
 I_3 &= 2A \\
 I_{sc} &= I_3 = 2A \\
 R_{th} &= \frac{V_{th}}{I_{sc}} = \frac{-20}{2} = -10\Omega
 \end{aligned}$$

Thevenin Eq. ch. 10

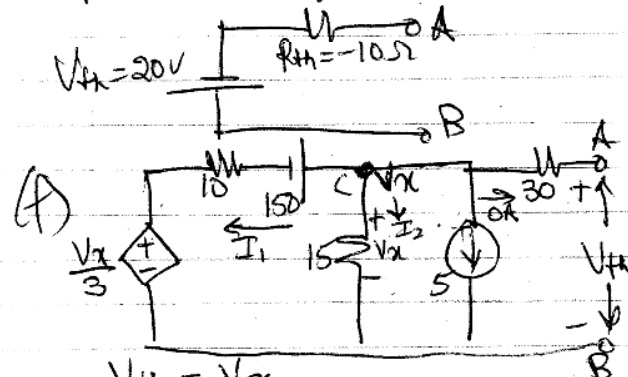


$$\begin{aligned}
 V_{th} &= V_x \\
 \text{By KCL at node C} \\
 I_1 + I_2 + 5 &= 0
 \end{aligned}$$

$$\frac{V_x - 150 - V_x/3}{10} + \frac{V_x}{15} + 5 = 0$$

$$V_x \left(\frac{1}{10} - \frac{1}{30} + \frac{1}{15} \right) = 15 - 5$$

$$\therefore V_x = V_{th} = 75V$$

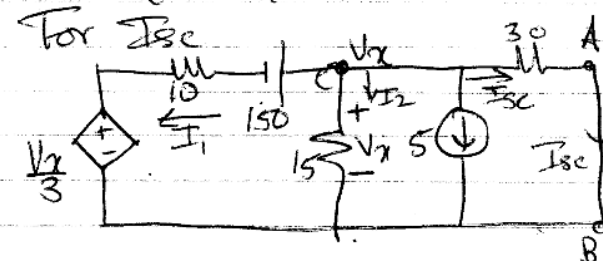

By KCL at node C

$$I_1 + I_2 + 5 + I_{sc} = 0$$

$$\left(\frac{V_x - 150 - V_x/3}{10} \right) + \frac{V_x}{15} + 5 + \frac{V_x}{30} = 0$$

$$V_x \left(\frac{1}{10} - \frac{1}{30} + \frac{1}{15} + \frac{1}{30} \right) = 15 - 5$$

$$I_3 = I_x = I_{sc}$$

Eq. of supermesh,

$$I_3 - I_2 = 3I_x$$
$$I_3 - I_2 = 3I_3$$
$$0I_1 + I_2 + 2I_3 = 0 \quad \text{--- (I)}$$


By KVL to loop II:-

$$-1(7) + 6I_1 - 3I_2 = -2I_x$$
$$6I_1 - 3I_2 + 2I_3 = 7 \quad \text{--- (II)}$$

By KVL to A-B-C-D-A:-


$$-3I_1 + 3I_2 + 2I_3 = 0 \quad \text{--- (III)}$$

$$I_1 =$$
$$I_2 =$$
$$I_3 =$$


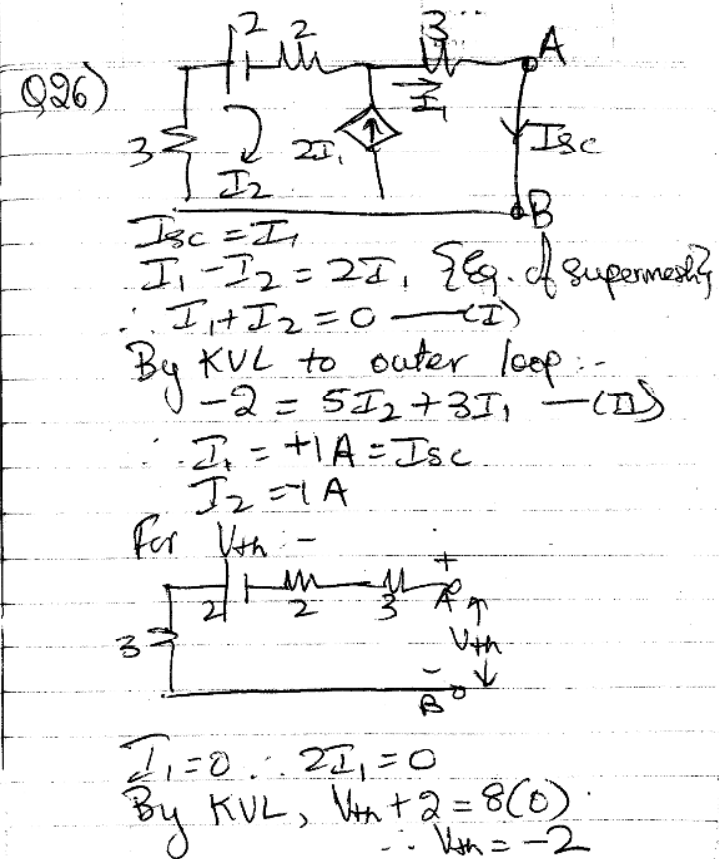


$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{-2}{+1} = 2$$

Norton's eq. obt. is

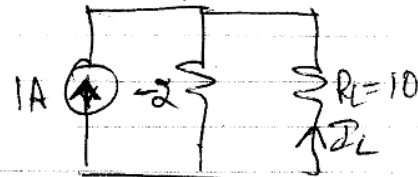
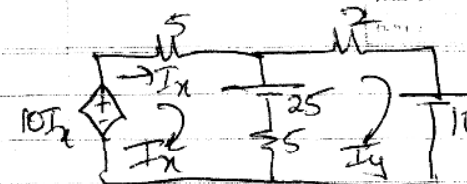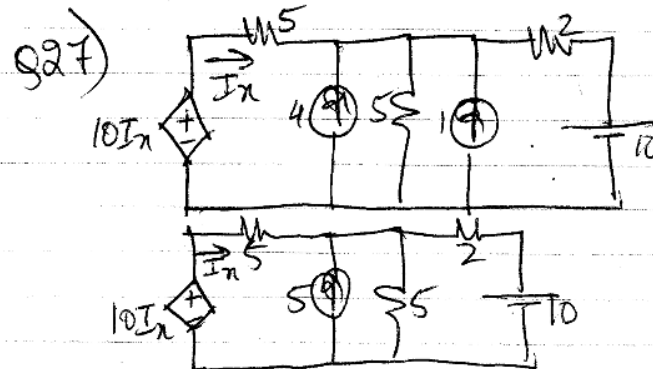
$$I_L = 1 \left(\frac{-2}{10} \right) = -\frac{1}{5} = -0.2 \text{ A}$$



By KVL to loop I:-

$$10I_x - 5I_y = 10I_x - 25$$


$$\therefore I_y = 5 \text{ A}$$

By KVL to loop II:-

$$-5I_x + 7I_y = 15$$

$$\therefore I_y = 5$$

$$\therefore I_x = 4 \text{ A}$$

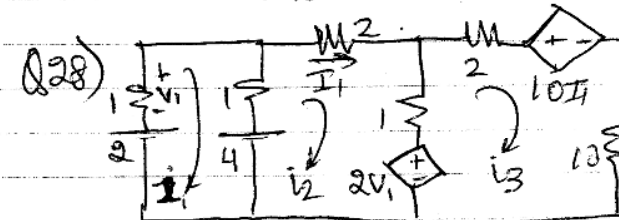

$$i_2 = I_1$$

$$V_1 = -i_1 \text{ — (I)}$$

By KVL to loop I:-

$$2i_1 - i_2 + 0i_3 = -2 \quad \text{---(II)}$$

By KVL to loop II:-

$$\begin{aligned} -i_1 + 4i_2 - i_3 &= 4 - 2V_1 \\ -3i_1 + 4i_2 - i_3 &= 4 \quad \text{from (I)} \end{aligned} \quad \text{---(III)}$$

By KVL to loop III:-

$$\begin{aligned} -i_2 + 13i_3 &= 2V_1 - 10i_2 \\ +2i_1 + 9i_2 + 13i_3 &= 0 \end{aligned} \quad \text{---(IV)}$$


$$i_1 = -0.824 \text{ A}$$

$$i_2 = 0.353 \text{ A}$$

$$i_3 = -0.118 \text{ A}$$

$$\begin{aligned} P_{\text{loss}} &= i_3^2 (R) \\ &= 0.139 \text{ W} \end{aligned}$$

Q29)

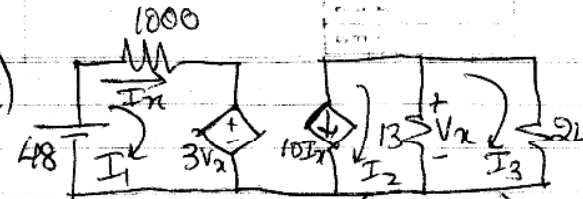

$$I_1 = I_x ; V_x = (I_2 - I_3) \cdot 3$$

By KVL to loop I:-

$$1000I_1 = 48 - 3V_x$$

$$1000I_1 = 48 - 3(I_2 - I_3) \cdot 3$$

$$1000I_1 + 9I_2 - 9I_3 = 48 \quad \text{---(I)}$$

$$I_2 = -10I_1$$

$$I_2 = -10I_1$$



$$10I_1 + I_2 + 0I_3 = 0 \quad \text{---(II)}$$

By KVL to loop III:-

$$0I_1 - 13I_2 + 37I_3 = 0 \quad \text{---(III)}$$

$$I_1 = 0.0643 ; I_2 = -0.643$$

$$I_3 = -0.226 \text{ A}$$

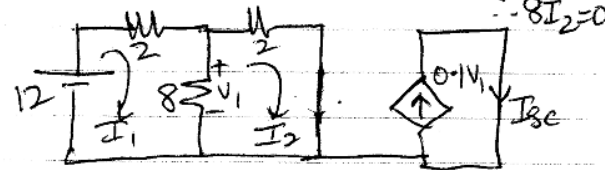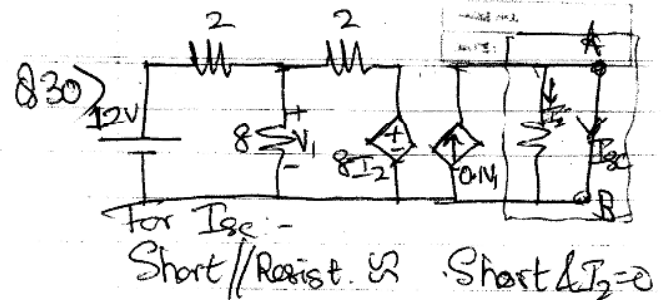

$$I_{sc} = 0.1 V_1$$

By KVL to loop I:-
 $10I_1 - 8I_2 = 12 \quad \text{--- (I)}$


By KVL to loop II:-
 $-8I_1 + 10I_2 = 0$

$$I_1 = 3.333 \text{ A}$$

$$I_2 = 2.667 \text{ A}$$

$$V_1 = 8(I_1 - I_2) = 5.328 \text{ V}$$

$$\therefore I_{sc} = 0.1 V_1 = 0.5328$$

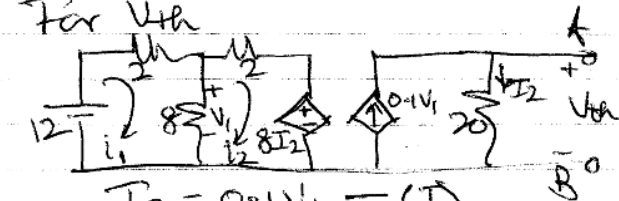

$$I_2 = 0.1 V_1 \quad \text{--- (I)}$$

$$V_{th} = 20I_2 = 2V_1$$

By KVL to loop I:-

$$10I_1 - 8I_2 = 12 \quad \text{--- (II)}$$

KVL to loop II:-
 $-8I_1 + 10I_2 = -8I_2$

$$-8I_1 + 10I_2 = -0.8V_1 \quad \text{[from (I)]}$$

$$-8I_1 + 10I_2 + 0.8V_1 = 0 \quad \text{--- (III)}$$

Also, $V_1 = 8(I_1 - I_2)$

$$\therefore +8I_1 - 8I_2 - V_1 = 0 \quad \text{--- (IV)}$$

$$I_1 = 1.862$$


$$I_2 = 0.828$$

$$V_1 = 8.276$$


$$V_{th} = 16.558V$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{16.558}{0.5328} = 31.067\Omega$$

Norton's Eq ckt. is

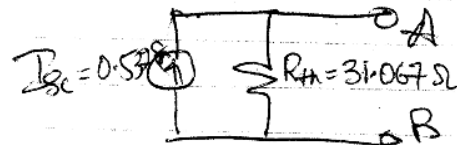

Q31)

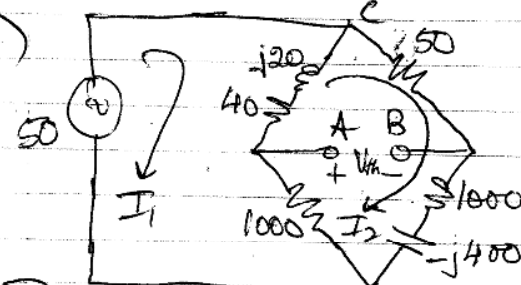

By KVL to loop I :-

$$(40 + j20 + 1000)I_1 - (40 + j20 + 1000)I_2 = 50$$

$$\therefore (1040 + j20)I_1 - (1040 + j20)I_2 = 50 \quad \text{--- (I)}$$

By KVL to loop II :-

$$-(1040 + j20)I_1 + (1040 + j20 + 1050 - j400)I_2 = 0$$

$$-(1040 + j20)I_1 + (2090 - j380)I_2 = 0$$

$$I_1 = \frac{(2090 - j380)}{(1040 + j20)}I_2 \quad \text{--- (II)}$$

Subs. (II) in (I)

$$I_2 [(2090 - j380) - (1040 + j20)] = 50$$


$$I_2 = \frac{50}{1050 - j400} = 0.0416 + j0.0158$$

$$I_1 = 0.0897 + j0.0148$$

By KVL to A-B-C-A :-

$$-(40 + j20)I_1 + (90 + j20)I_2 = V_{th}$$

$$V_{th} = 0.138 - j0.132 = 0.191 \angle -43.7^\circ$$

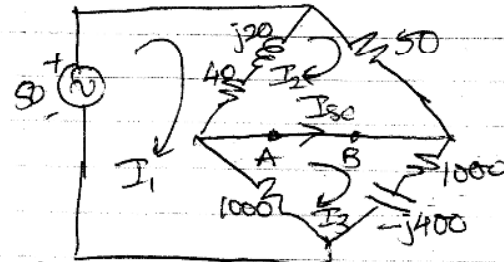For I_{sc} :-

By KVL to loop I:-
 $(1040 + j20)I_1 - (40 + j20)I_2 - 1000I_3 = 0$ — (I)

By KVL to loop II:-
 $-(40 + j20)I_1 + (90 + j20)I_2 = 0$
 $\therefore I_1 = \frac{(90 + j20)}{(40 + j20)}I_2$ — (II)


By KVL to loop III:-
 $-1000I_1 + (2000 - j400)I_3 = 0$
 $\therefore I_1 = \frac{(2000 - j400)}{1000}I_3$ — (III)


[Use more sign. places]

from (II) & (III)
 $\frac{(90 + j20)}{(40 + j20)}I_2 = \frac{(2000 - j400)}{1000}I_3$
 $I_2 = (0.988 + j0.0471)I_3$ — (IV)

Subs. (II) & (IV) in (I):-
 $I_3(1049.42 - j397.64) = 50$
 $I_3 = 0.04167 + j0.0158$
 $\therefore I_2 = 0.0404 + j0.0176$
 $I_{sc} = I_3 - I_2 = 0.00127 - j0.0018$
 $R_{th} = \frac{V_{th}}{I_{sc}} = \frac{88.58 + j17.92}{0.00127 - j0.0018}$
 $I_{sc} = 88.36 \angle 11.48^\circ$

Therefore Eq. ckt. is

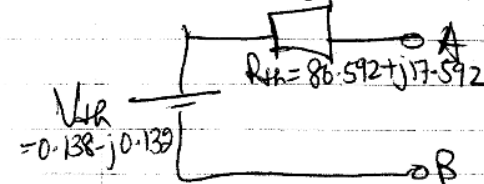

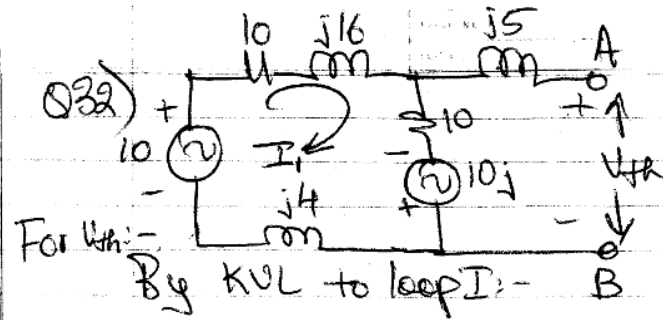

$$(20 + j20)I_1 = 10 + j10$$


$$I_1 = 0.5 + j0$$

By KVL to loop II:-

$$V_{th} + 10j = 10I_1$$

$$\therefore V_{th} = 5 - j10 = 11.18 \angle -63.44^\circ$$

For I_{sc} :-

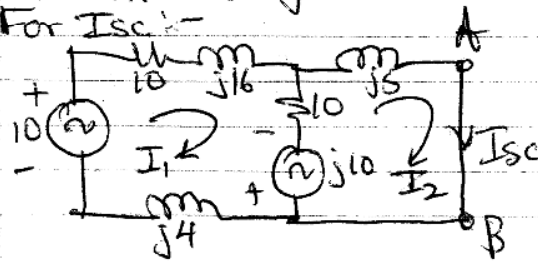

By KVL to loop I:-

$$(20 + j20)I_1 - 10I_2 = 10 + j10 \quad \text{--- (I)}$$

By KVL to loop II:-

$$-10I_1 + (10 + j5)I_2 = -j10 \quad \text{--- (II)}$$

$$A = \begin{vmatrix} 20 + j20 & -10 \\ -10 & 10 + j5 \end{vmatrix}$$

$$= j300$$

$$A_2 = \begin{vmatrix} 20 + j20 & 10 + j10 \\ -10 & -j10 \end{vmatrix}$$

$$= 300 - j100$$


$$I_2 = \frac{A_2}{A} = -0.333 - j$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{5 - j10}{-0.333 - j} = 7.5 + j7.5$$

Thevenin's Impedance

$$R_{th} = 7.5 + j7.5$$

$$V_{th} = 5 - j10$$

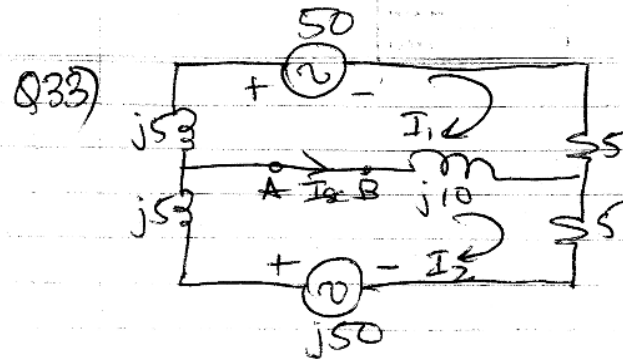

By KVL to loop I:-
 $(5 + j15)I_1 - (j10)I_2 = -50$
 — (I)

By KVL to loop II:-
 $-(j10)I_1 + (5 + j15)I_2 = j50$
 — (II)

$$A = \begin{vmatrix} 5 + j15 & -j10 \\ -j10 & 5 + j15 \end{vmatrix}$$

$$= -100 + j150$$



$$\Delta_1 = \begin{vmatrix} -50 & -j10 \\ j50 & 5 + j15 \end{vmatrix} = -750 - 250j$$

$$I_1 = \frac{\Delta_1}{A} = 1.154 + j4.231$$

$$\Delta_2 = \begin{vmatrix} 5 + j15 & -50 \\ -j10 & j50 \end{vmatrix}$$

$$= -750 - j250$$

$$I_{sc} = I_2 - I_1 =$$

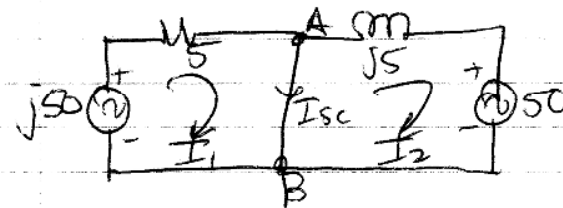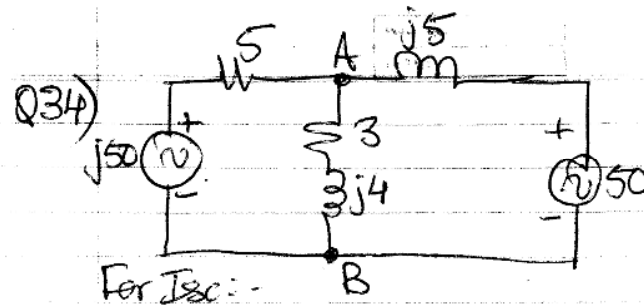

By KVL to loop I:-

$$5I_1 = j50$$


$$\therefore I_1 = j10$$

By KVL to loop II:-

$$(j5)I_2 = -50$$

$$\therefore I_2 = j10$$

$$I_{sc} = I_1 - I_2 =$$

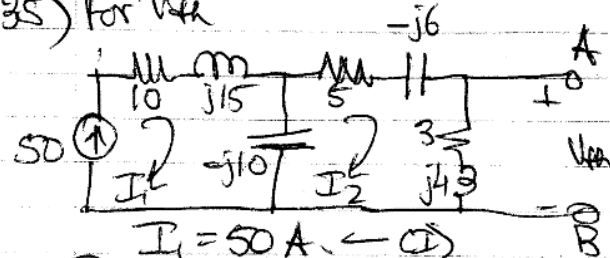Q35) For V_{th} 

$$I_1 = 50 \text{ A} \leftarrow (I)$$

By KVL to loop II:-

$$(j10)I_1 + (8-j6)I_2 = 0$$


$$(j10)I_1 + (8-j12)I_2 = 0$$

from (I)

$$I_2 = \frac{-50(j10)}{(8-j12)} = 28.85 \angle 19.23^\circ$$

$$V_{th} = (3+j4)I_2$$

$$= 163.47 + j57.71$$

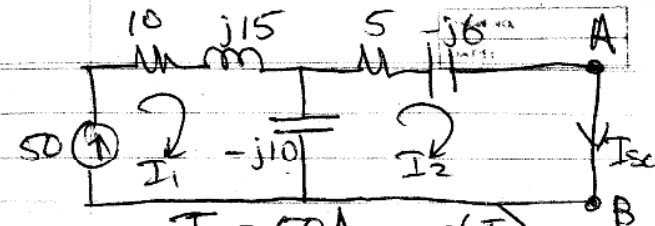For I_{sc} , short A-B3+j4 // short $\approx$ short

$$I_1 = 50 \text{ A} \leftarrow (I)$$

By KVL to loop II:-

$$(j10)I_1 + (5-j16)I_2 = 0$$

$$\therefore I_2 = \frac{-500j}{5-j16} = 28.47 - j8.897$$


$$I_{sc} = I_2 = 28.47 - j8.897$$

For R_{th}

$$R_{th} = \frac{V_{th}}{I_{sc}} = 4.654 + j3.481$$


$$R_L = R_{th} = 4.654 - j3.481$$

Thevenin Eq. ckt. is

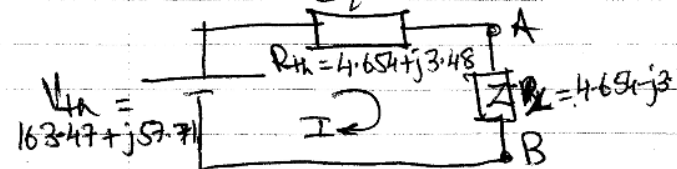

$$\begin{aligned}
 \text{Max. Power} &= I^2 R_L \\
 &= \left(\frac{V_{th}}{Z_L + Z_{th}} \right)^2 \cdot R_L \\
 &= \frac{(163.47 + j57.71)^2}{(9.308)^2} \times (4.654) \\
 &= 1256.55 \text{ W} \\
 I_L &= \frac{V_{th}}{Z_L + Z_{th}} = 17.56 + j6.2 \\
 |I_L| &= 18.625 \\
 P &= |I_L|^2 \cdot R_L \\
 &= (18.625)^2 \times (4.654) \\
 &= 1,614.36 \text{ W}
 \end{aligned}$$

836) For V_{th} :-

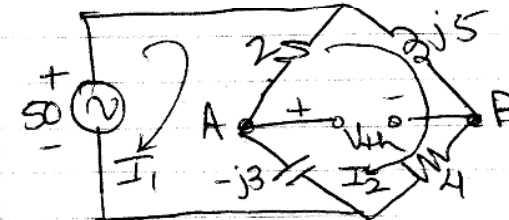

By KVL to loop I :-

$$(2 - j3)I_1 + (2 - j3)I_2 = 50 \quad \text{--- (I)}$$

By KVL to loop II :-

$$-(2 - j3)I_1 + (6 + j2)I_2 = 0$$

$$I_1 = \frac{(6 + j2)}{(2 - j3)} I_2 \quad \text{--- (II)}$$

Subs. (II) in (I)

$$[(6 + j2) + (2 - j3)] I_2 = 50$$

$$I_2 = \frac{50}{8 - j} = 6.154 + j0$$



$$I_1 = 1.539 + j10.77$$

By KVL

$$V_{th} = -2I_1 + (2 + j5)I_2$$

$$V_{th} = 5.386 + j10.77$$


For Z_{th}

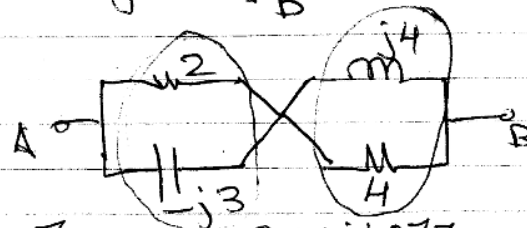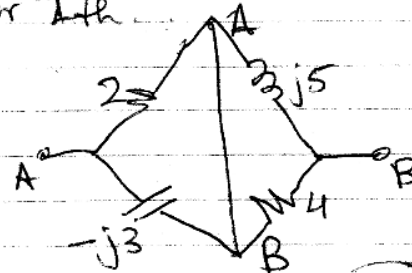

$$Z_{th} = 3.385 + j1.077$$

$$Z_L = Z_{th} = 3.385 - j1.077$$

Thevenin Eq. ckt.

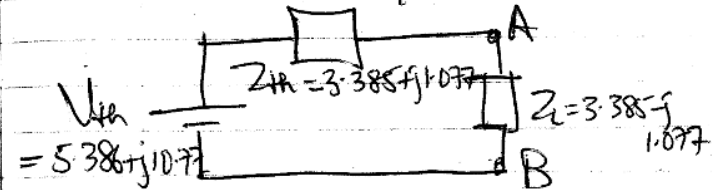

$$P = I^2 R_L$$

$$= \left(\frac{V_{th}}{Z_L + Z_{th}} \right)^2 (R_L)$$

$$= \left(\frac{5.386 + j10.77}{6.77} \right)^2 \times (3.385)$$










$$I_L = \frac{V_{th}}{Z_L + Z_{th}} = 0.796 + j1.591$$



$$|I_L| = 1.779$$


$$P = I_L^2 R_L$$

$$= (1.779)^2 (3.385)$$

$$= 10.71 \text{ W}$$

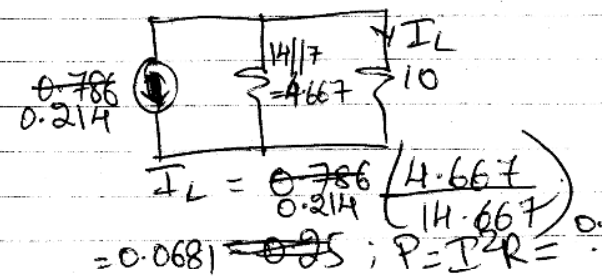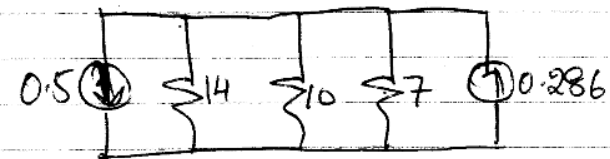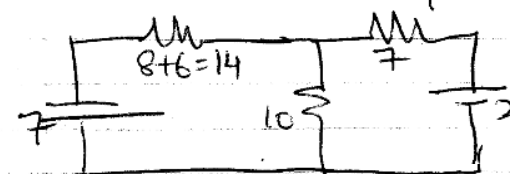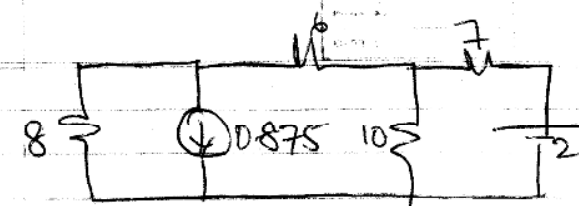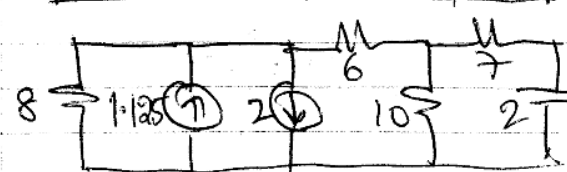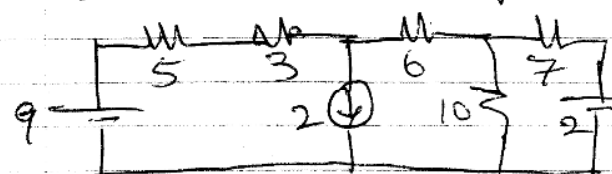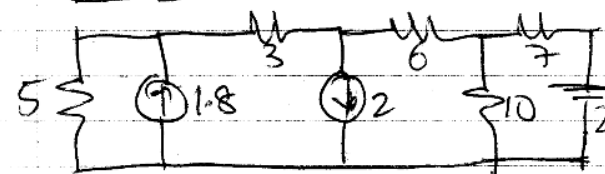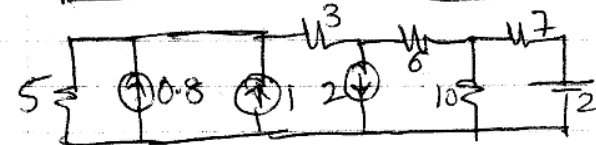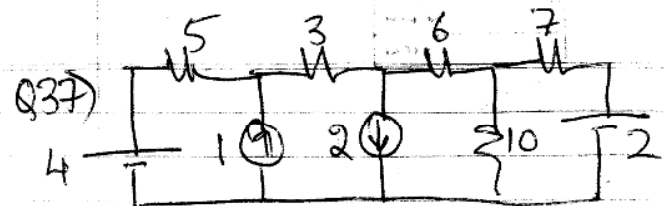

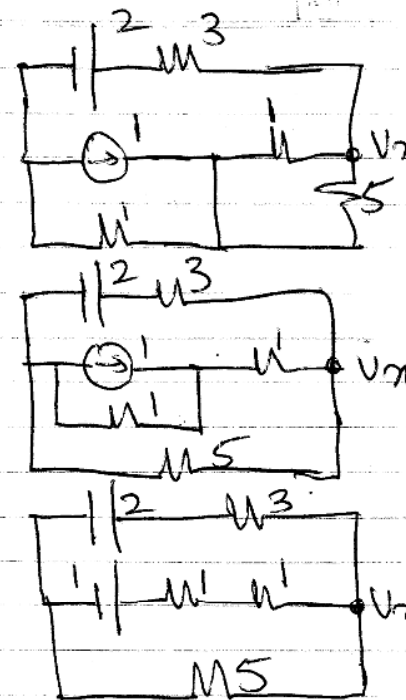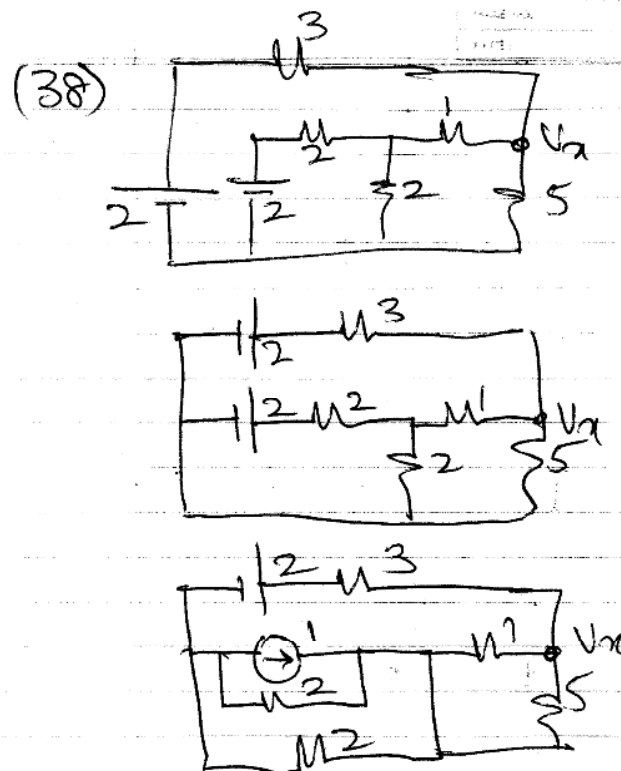

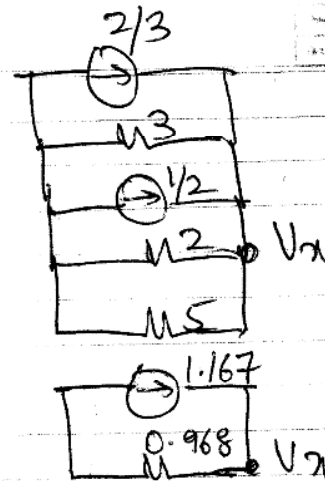

$$V_x = (1.167)(0.968) \\ = 1.129 \text{ V}$$

