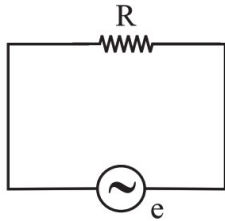



## RESISTIVE CIRCUIT




$$e = e_o \sin(\omega t)$$

$$i = \frac{e}{R} = \frac{e_o}{R} \sin(\omega t) = i_o \sin(\omega t)$$

Waveform:

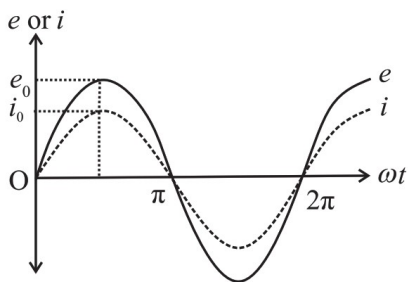


Phasor Diagram:

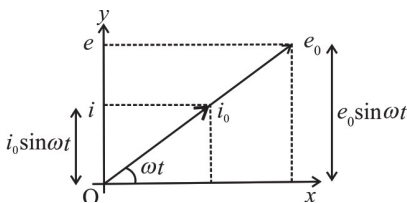

$$\begin{aligned} \text{Power } P &= e_{rms} \times i_{rms} \cos \phi \\ &= \frac{e_o i_o}{2} \cos 0^\circ = \frac{e_o i_o}{2} \end{aligned}$$

## INDUCTIVE CIRCUIT

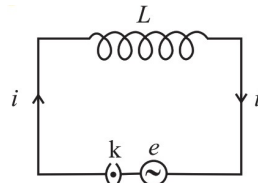

$$\text{Induced emf } e_b = -L \frac{di}{dt}$$

Applied emf  $e$  should be equal and opposite  $e = -e_b = L \frac{di}{dt}$

$$di = \frac{e}{L} dt. \text{ Integrating,}$$

$$\int di = \int \frac{e}{L} dt$$

$$i = \frac{1}{L} \int e_o \sin(\omega t) dt$$

$$\begin{aligned} &= \frac{e_o}{L} \left[ \frac{-\cos(\omega t)}{\omega} \right] \\ &= -\frac{e_o}{\omega L} \cos(\omega t) = -\frac{e_o}{X_L} \cos(\omega t) \end{aligned}$$

$$i = -\frac{e_o}{X_L} \sin\left(\frac{\pi}{2} - \omega t\right)$$


$$i = \frac{e_o}{X_L} \sin\left(\omega t - \frac{\pi}{2}\right)$$

Thus, current lags voltage by  $\frac{\pi}{2}$


where  $X_L = \omega L = 2\pi fL$

is the reactance of the inductor  
S.I. Unit  $\Omega$

Waveform:

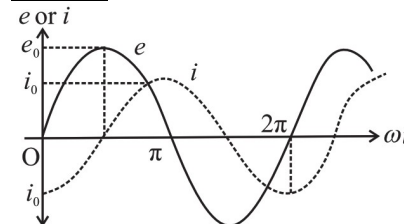


Phasor:

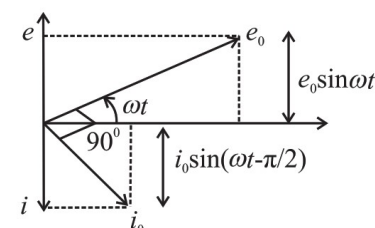

$$P = e_{rms} \times i_{rms} \cos \frac{\pi}{2} = 0$$

## CAPACITIVE CIRCUIT

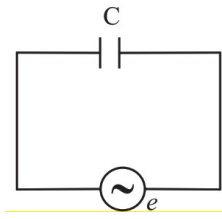

$$i = \frac{dq}{dt} = \frac{d(C \cdot e)}{dt}$$

$$i = \frac{d}{dt} (C \cdot e_o \sin(\omega t))$$

$$i = C e_o \frac{d}{dt} \sin(\omega t)$$

$$i = C e_o \cos(\omega t) \cdot \omega$$

$$i = \frac{e_o}{\frac{1}{\omega C}} \cos(\omega t) = \frac{e_o}{X_C} \cos(\omega t)$$

$$i = \frac{e_o}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right)$$


Thus, current leads voltage by  $\frac{\pi}{2}$

where  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$


is the reactance of capacitor

S.I. Unit  $\Omega$

Waveform:

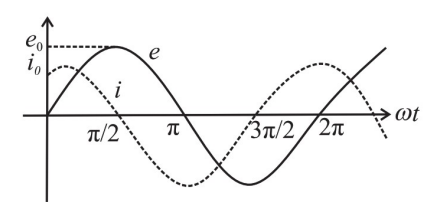

Phasor:

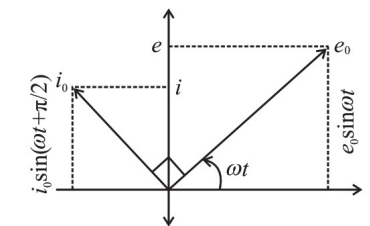

$$P = e_{rms} \times i_{rms} \cos \frac{\pi}{2} = 0$$

**NOTE:**


for DC,  $f = 0$ ,

thus  $X_L = 0$  and  $X_C = \infty$


Thus, coil or inductor act as short circuit for DC and capacitor blocks DC

As  $f$  increases,  $X_L$  increases  
and  $X_C$  decreases

### SERIES LCR CIRCUIT

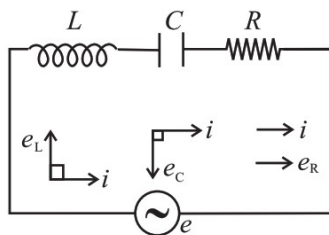

Phasor:

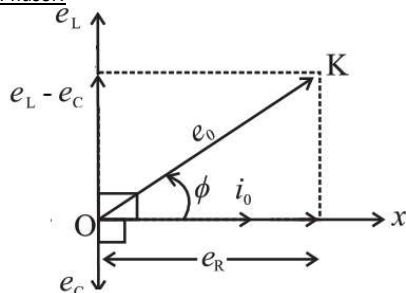


$$e = \sqrt{e_R^2 + (e_L - e_C)^2}$$

$$iZ = \sqrt{(iR)^2 + (iX_L - iX_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance triangle

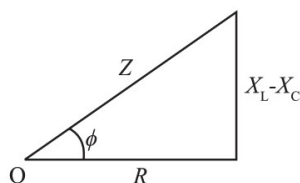

NOTE:

$$\tan \phi = \frac{X_L - X_C}{R}$$

(i) If  $X_L > X_C$ ,  
 $\tan \phi$  is positive and

circuit will be inductive,  
 voltage will lead current by  $\phi$

(ii) If  $X_L < X_C$ ,  
 $\tan \phi$  is negative and

circuit will be capacitive,  
 voltage will lag current by  $\phi$

(iii) If  $X_L = X_C$ ,  
 $\tan \phi = 0$ , circuit is resistive

$Z_{min} = R$  and

current is maximum  $i_0 = \frac{e_0}{R}$

### SERIES RESONANCE (Acceptor Circuit)

If  $X_L = X_C$ ,

$$\omega L = \frac{1}{\omega C}, \quad \omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

thus, Resonant frequency

$$f = \frac{1}{2\pi\sqrt{LC}}$$

At resonance,

$\tan \phi = 0$ , circuit is resistive


$Z_{min} = R$  and

current is maximum  $i_0 = \frac{e_0}{R}$

$$P = e_{rms} \cdot i_{rms} \cdot \cos \phi$$

$$P = \frac{e_0}{\sqrt{2}} \cdot \frac{i_0}{\sqrt{2}} \cdot \cos 0 = \frac{e_0 \cdot i_0}{2}$$
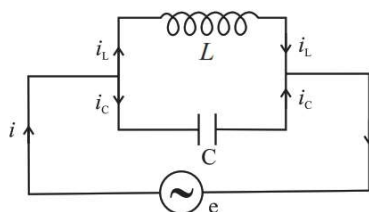
### PARALLEL RESONANCE (Rejector Circuit)



If  $X_L = X_C$ ,

$$\omega L = \frac{1}{\omega C}, \quad \omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

thus, Resonant frequency


$$f = \frac{1}{2\pi\sqrt{LC}}$$

At resonance,  $i$  is minimum

$Z$  is maximum
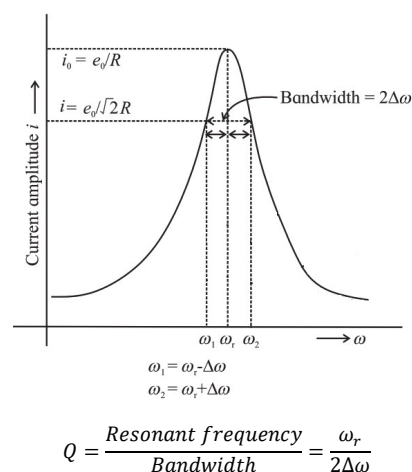
### Q- FACTOR/QUALITY FACTOR

Q factor of a series resonant circuit is defined as the ratio of resonant frequency to the difference in two frequencies taken on both sides of resonant frequency such that at each of these frequencies the current amplitude is  $1/\sqrt{2}$  times the value at resonant frequency.



**Definition:**

**Peak value:** Peak value of an alternating current (or emf) is the maximum value of the current (or emf) in either direction.

**Average / Mean value:**

Average value or mean value of one HALF cycle can be found as follows:

Average or mean value of current

$$= \frac{\int_0^\pi i_0 \sin \theta \, d\theta}{\int_0^\pi d\theta} = \frac{i_0 \int_0^\pi \sin \theta \, d\theta}{[\theta]_0^\pi}$$

$$= \frac{i_0 [-\cos \theta]_0^\pi}{\pi - 0} = \frac{i_0 [-\cos \pi - (-\cos 0)]}{\pi}$$

$$= \frac{2i_0}{\pi} = 0.637i_0$$

Similarly, mean or avg value of voltage

$$\text{over one half cycle} = \frac{2e_0}{\pi} = 0.637e_0$$

**NOTE:** Average value over a full cycle of sin or cos wave is zero.

**Effective value / Virtual Value / RMS value:**

Consider an AC current of peak value  $i_0$  passing through a resistor  $R$  and producing heat  $H$  in time  $t$ . Then, the steady value of current, which produces the same heat in a resistor ( $R$ ) in same time  $t$  is called as effective/virtual/RMS value of current.

RMS value can be found as follows:

$$\text{RMS Value of current} = \sqrt{\frac{\int_0^{2\pi} i_0^2 \sin^2 \theta \, d\theta}{2\pi}}$$

$$= \sqrt{\frac{i_0^2 \int_0^{2\pi} \sin^2 \theta \, d\theta}{2\pi}}$$

$$= \sqrt{\frac{i_0^2}{2\pi} \int_0^{2\pi} \left( \frac{1 - \cos 2\theta}{2} \right) d\theta}$$

$$= \sqrt{\frac{i_0^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}}$$

$$= \sqrt{\frac{i_0^2}{4\pi} \cdot 2\pi} = \frac{i_0}{\sqrt{2}} = 0.707 i_0$$

Similarly,

$$\text{RMS voltage} = \frac{e_0}{\sqrt{2}} = 0.707 e_0$$